

Midterm II

1) You are implementing an 4:1 Multiplexer that has the following specifications:

Inputs: I_0 - I_3

Output: Z

Control Inputs: C_2 - C_0 (C_2 is MSB)

The input is selected based on a Johnson counter scheme (000- \rightarrow I_0 , 100- \rightarrow I_1 , 110- \rightarrow I_2 , 111- \rightarrow I_3).

All other states select I_0 .

a) Write out the functional form of the truth table for this multiplexor.

C_2 C_1 C_0 Z I_m

0 0 0 I_0 1

0 0 1 I_0 0

0 1 0 I_0 1

0 1 1 I_0 0


1 0 0 I_1 0

1 0 1 I_0 0


1 1 0 I_2 1

u
|
Z

 d) Implement $F(A,B,C) = \Sigma(4, 7)$ using the above multiplexer. Indicate the connections in the diagram below. Simplify as appropriate.



 e) Implement $G(A,B,C) = \Sigma(0, 2, 6, 7)$ using the above multiplexer. Indicate the connections in the diagram below. Simplify as appropriate.




| | |
 A B C


f) Implement the multiplexer using NAND gates and Tri-State Inverters. Draw the circuit below.

Use inverters

active high
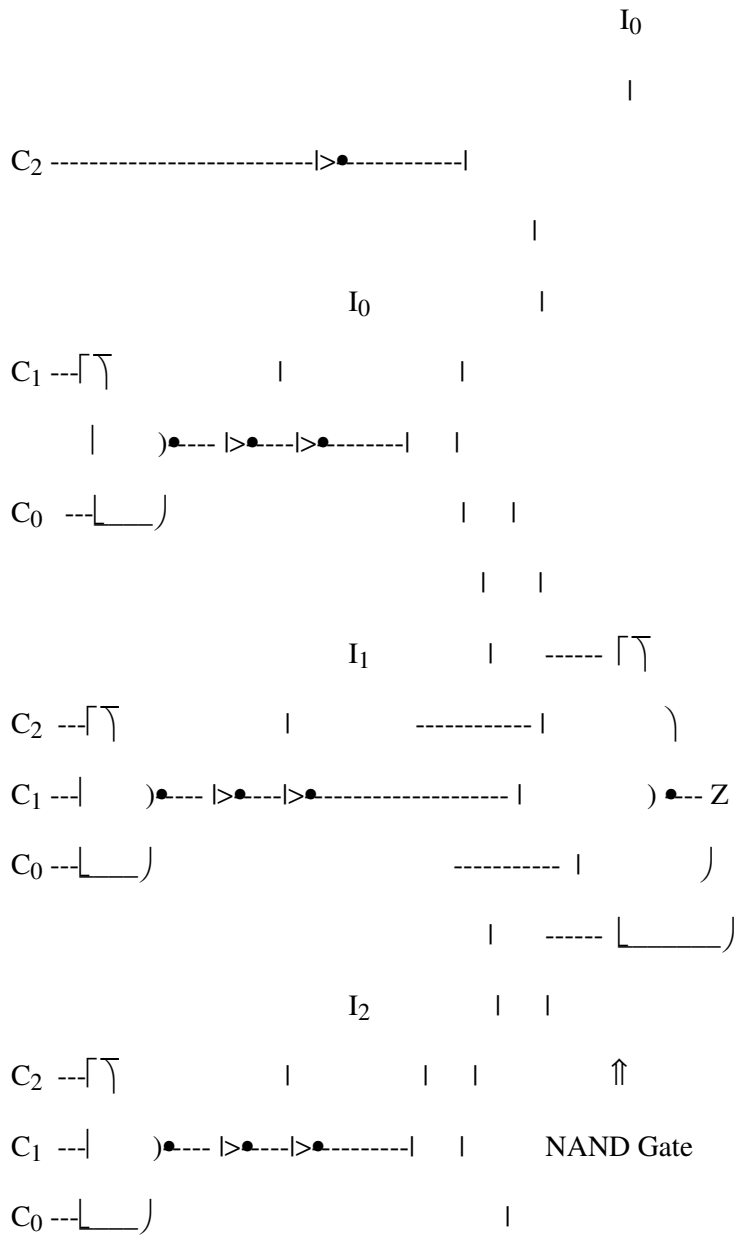
$$Z = C_2I_0 + C_1C_0I_0 + C_2C_1C_0I_1 + C_2C_1C_0I_2 + C_2C_1C_0I_3$$



 

g) Assume the Tri-State Inverters require 4 transistors. How many transistors are required to implement the multiplexer:

i) Using Tri-State Inverters / NAND gates:

ii) Using NAND / NAND gates:

2) Back in the days of mainframe computing, there were two standard for textual information interchange ASCII and EBCDIC. You are implementing a counter that counts in hexadecimal. The output of the counter is either in ASCII (0-9 = 48-57, A-F = 65-70) or EBCDIC (0-9 = 240-249, A-F = 193-198) depending on the value of a control switch (C = 0 -> ASCII, C = 1 -> EBCDIC). You are provided with the following parts:

A 4-bit binary counter (Pins: CLK, RESET, C3-C0 outputs)


A 4:16 DEMUX (Pins: G enable, S3-S0 select lines, Z output)

A 32x8 bit ROM (Pins: A4-A0 address lines, D7-D0 data lines)

As many NAND gates as you need

You may use some or all of the parts above. You may choose to program the ROM with whatever values you need.

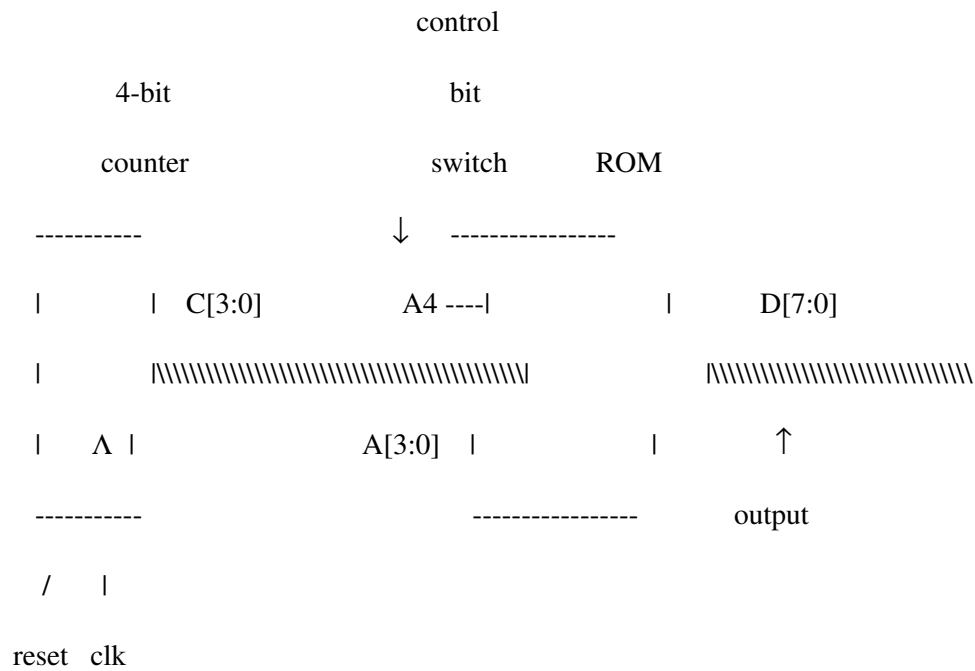a) Design the ASCII/EBCDIC counter. Use block diagrams for the individual parts and label pinouts.



$$C = A4$$

b) Fill out the following table with the values that you chose to store in the ROM. You should write the data in decimal for convenience (and ease of grading).

Address	Data	Address	Data	Address	Data	Address	Data

00000	48	01000	56	10000	240	11000	248

00001	49	01001	57	10001	241	11001	249

00010	50	01010	65	10010	242	11010	193

| 00011 | 51 | 01011 | 66 | 10011 | 243 | 11011 | 194 |

| 00100 | 52 | 01100 | 67 | 10100 | 244 | 11100 | 195 |

| 00101 | 53 | 01101 | 68 | 10101 | 245 | 11101 | 196 |

| 00110 | 54 | 01110 | 69 | 10110 | 246 | 11110 | 197 |

| 00111 | 55 | 01111 | 70 | 10111 | 247 | 11111 | 198 |

3) Consider the following truth table:

| Inputs | | | Output |

| A | B | C | Z |

| 0 | 0 | 0 | 0 |

| 0 | 0 | 1 | 1 |

| 0 | 1 | 0 | 0 |

| 0 | 1 | 1 | 0 |

| 1 | 1 0 | 1 0 | 0 | 1 |

| 1 | 1 0 | 1 1 | 1 | 1 |

| 1 | 1 1 | 1 0 | 1 | 1 |

| 1 | 1 1 | 1 1 | 1 | 1 |

a) Minimize the truth table using a K-Map. Identify the prime implicants and essential prime implicants on the map.

A\BC 00 01 11 10

0 | 1 0 | 1 0 | 1 1 | 0 1 |

1 | 1 1 | 1 0 | 1 1 | 1 1 |

B = 1, C = 1, A = anything: essential prime implicants

A = 1, B = 1, C = anything: prime implicants





A = 1, C = 0, B = anything: essential prime implicants

b) Write a minimal SoP function (Z1) that describes the above truth table, and an SoP function (Z2) that has product terms covering all the prime (essential and non-essential) implicants.

$$Z1(A,B,C) = AB + BC$$

$$Z2(A,B,C) = AB + BC + AC$$

    c) You are not provided with the complemented inputs, so you will need to use inverters as necessary. Draw circuits that implements Z1 and Z2 using AND gates, OR gates, and Inverters.



d) Complete the timing diagram below, that shows the transition from ABC = 111 to ABC = 101 for both Z1 and Z2. Assume the propagation delay is 5ns, independent of gate type.

| E | F | F | 0 | 0 |

| F | A | F | X | 1 |

a) Minimize the number of states using the implication chart below:

B | B-B |

D-F

C | \ / | \ / |
| / \ | / \ |

D | \ / | \ / | A-B |
| / \ | / \ | F-F |

E | B-F | B-F | \ / | \ / |
| D-F | F-F | / \ | / \ |

F | \ / | \ / | A-B | A-A | \ / |
| / \ | / \ | F-F | F-F | / \ |

A B C D E

List the equivalencies:

$$A = B, C = F, D = F, C = D$$

b) Now, suppose state F is changed such that the output is 0 when IN=1. Repeat your simplification under these new conditions.

Present State	Next State	Output
	IN=0 IN=1	IN=0 IN=1
A	B D	0 0
B	B F	0 0
C	B F	X 1
D	A F	1 X
E	F F	0 0
F	A F	X 0

B | B-B |

| D-F |

C | \ / | \ / |

| / \ | / \ |

D | \ / | \ / | A-B |

| / \ | / \ | F-F |

E | B-F | B-F | \ / | \ / |

| D-F | F-F | / \ | / \ |

F | A-B | A-B | \ / | A-A | A-F |

| D-F | F-F | / \ | F-F | F-F |

A B C D E

List the equivalencies:

A = B, C = D, A = E, A = F, B = E, B = F, D = F, F = E

c) Is your simplification in part B unique? Are there other possible equivalencies? If so, list them. If not, give reasons for your answer.

Part A: A = B, C = F, D = F, C = D

Part B: $A = B, C = D, A = E, A = F, B = E, B = F, D = F, F = E$

No, since weve simplified as much as possible using the diagram.