
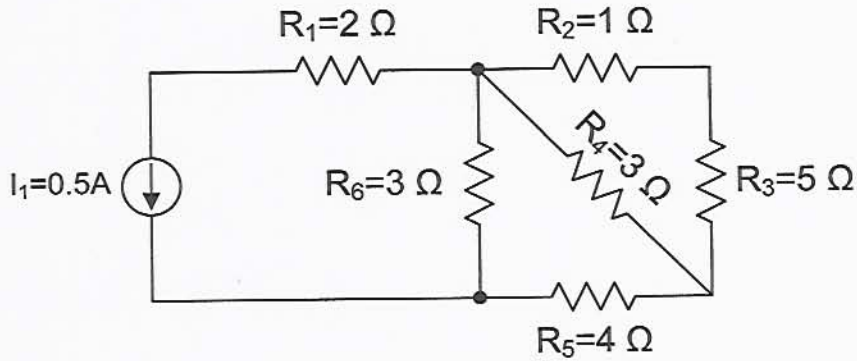


Problem 1 [20 points]

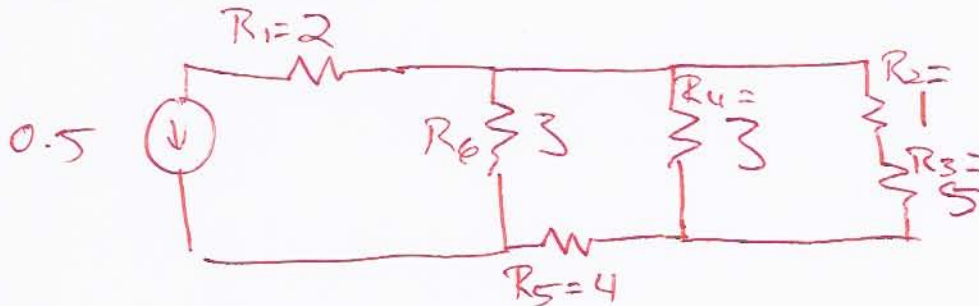

Calculate the numerical value of the power delivered to the circuit by the source I_1 . Write down intermediate results and do not forget the unit.

$$P = 1W$$



$$R_A = R_2 + R_3 = 6\Omega$$

$$R_B = R_A \parallel R_4 = 2\Omega$$

$$R_C = R_B + R_5 = 6\Omega$$


$$R_D = R_6 \parallel R_C = 2\Omega$$

$$R_E = R_1 + R_D = 4\Omega$$

$$P = I^2 R = 0.5^2 \cdot 4 = 1W$$

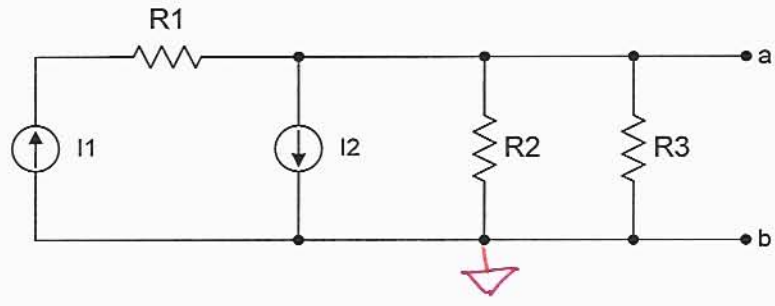Problem 2 [20 points]

Find algebraic expressions for the voltage and resistance of a Thevenin equivalent of the circuit below (looking into terminals a-b).



$$V_T = \frac{R_2 R_3}{R_2 + R_3} (I_1 - I_2)$$

$$R_T = \frac{R_2 R_3}{R_2 + R_3}$$

OPEN CIRCUIT VOLTAGE

@ a $I_2 + \frac{V_a}{R_2} + \frac{V_a}{R_3} - I_1 = 0$

$V_a = V_{oc} = V_{TH}$

$$(I_1 - I_2) \frac{R_2 R_3}{R_2 + R_3} = V_a$$


SHORT CIRCUIT CURRENT

$I_{sc} = I_1 - I_2$

$$R_{TH} = \frac{V_{oc}}{I_{sc}} = \frac{R_2 R_3}{R_2 + R_3}$$

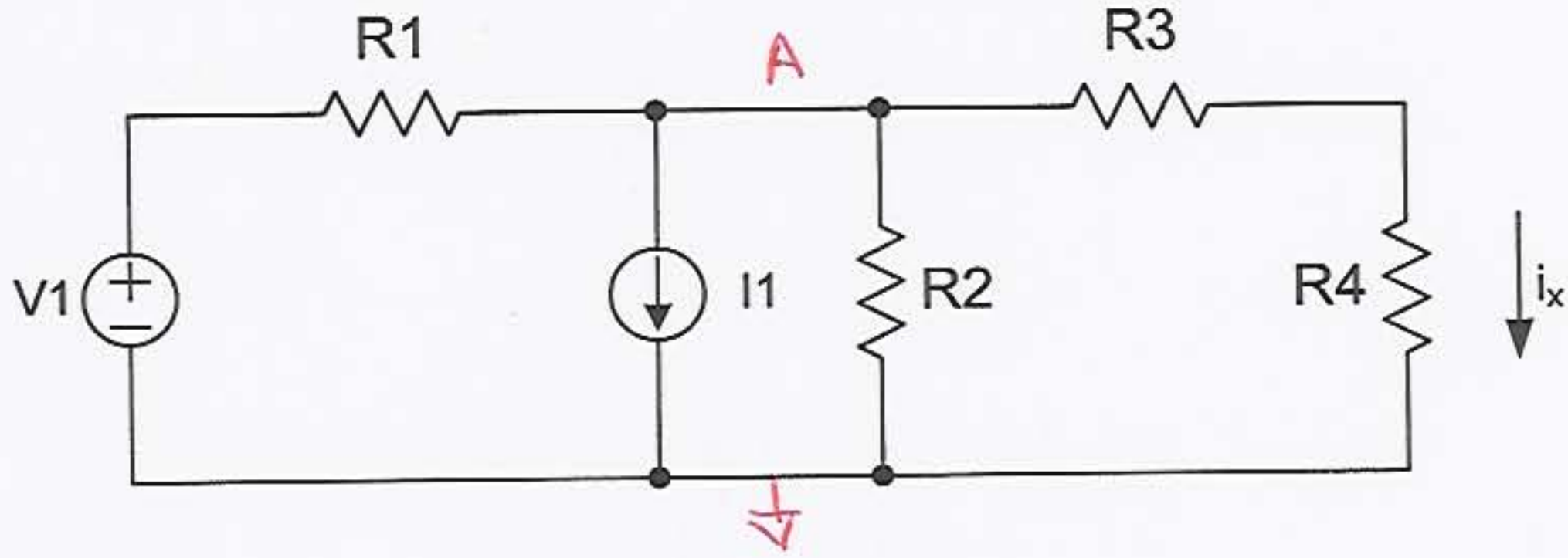Problem 3 [20 points]

Find an algebraic expression for the current i_x . Simplify as much as possible.



$$i_x = \left(\frac{V_1}{R_1} - I_1 \right) \frac{R_1 R_2}{(R_1 + R_2)(R_3 + R_4) + R_1 R_2}$$

$$\textcircled{A} \quad I_1 + \frac{V_A}{R_2} + \frac{V_A - V_1}{R_1} + \frac{V_A}{R_3 + R_4} = 0$$


$$I_1 - \frac{V_1}{R_1} + V_A \left(\frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3 + R_4} \right) = 0$$

$$V_A = \left(\frac{V_1}{R_1} - I_1 \right) \frac{R_1 R_2 (R_3 + R_4)}{R_2 (R_3 + R_4) + R_1 (R_3 + R_4) + R_1 R_2}$$

$$i_x = \frac{V_A}{R_3 + R_4} = \left(\frac{V_1}{R_1} - I_1 \right) \frac{R_1 R_2}{(R_2 + R_1)(R_3 + R_4) + R_1 R_2}$$

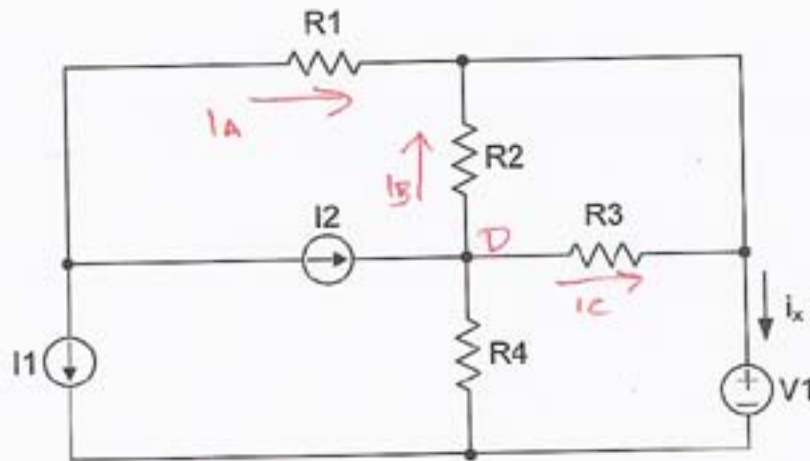Problem 4 [20 points]

Find an algebraic expression for the current i_x . Simplify your result to the extent possible.



$$i_x = I_A + I_B + I_C$$

$$i_x = -I_1 - I_2 + \left(I_2 + \frac{V_1 (R_2 + R_3)}{R_2 R_3} \right) \frac{(R_2 + R_3) R_4}{R_2 R_3 + R_2 R_4 + R_3 R_4} - \frac{V_1 (R_2 + R_3)}{R_2 R_3}$$

$$I_A = -I_1 - I_2$$

$$\text{@D: } \frac{V_D}{R_4} + \frac{(V_D - V_1)(R_2 + R_3)}{R_2 R_3} - I_2 = 0$$

$$V_D \frac{R_2 R_3 + (R_2 + R_3) R_4}{R_2 R_3 R_4} = I_2 + \frac{V_1 (R_2 + R_3)}{R_2 R_3}$$


$$V_D = \left(I_2 + \frac{V_1 (R_2 + R_3)}{R_2 R_3} \right) \frac{R_2 R_3 R_4}{R_2 R_3 + R_2 R_4 + R_3 R_4}$$

$$I_B + I_C = \frac{V_D - V_1}{R_2 R_3} = \left(I_2 + \frac{V_1 (R_2 + R_3)}{R_2 R_3} \right) \frac{R_2 R_3 R_4}{R_2 R_3 + R_2 R_4 + R_3 R_4} \frac{(R_2 + R_3)}{R_2 R_3} - \frac{V_1 (R_2 + R_3)}{R_2 R_3}$$

$$= \left(I_2 + \frac{V_1 (R_2 + R_3)}{R_2 R_3} \right) \frac{(R_3 + R_2) R_4}{R_2 R_3 + R_2 R_4 + R_3 R_4} - \frac{V_1 (R_2 + R_3)}{R_2 R_3}$$

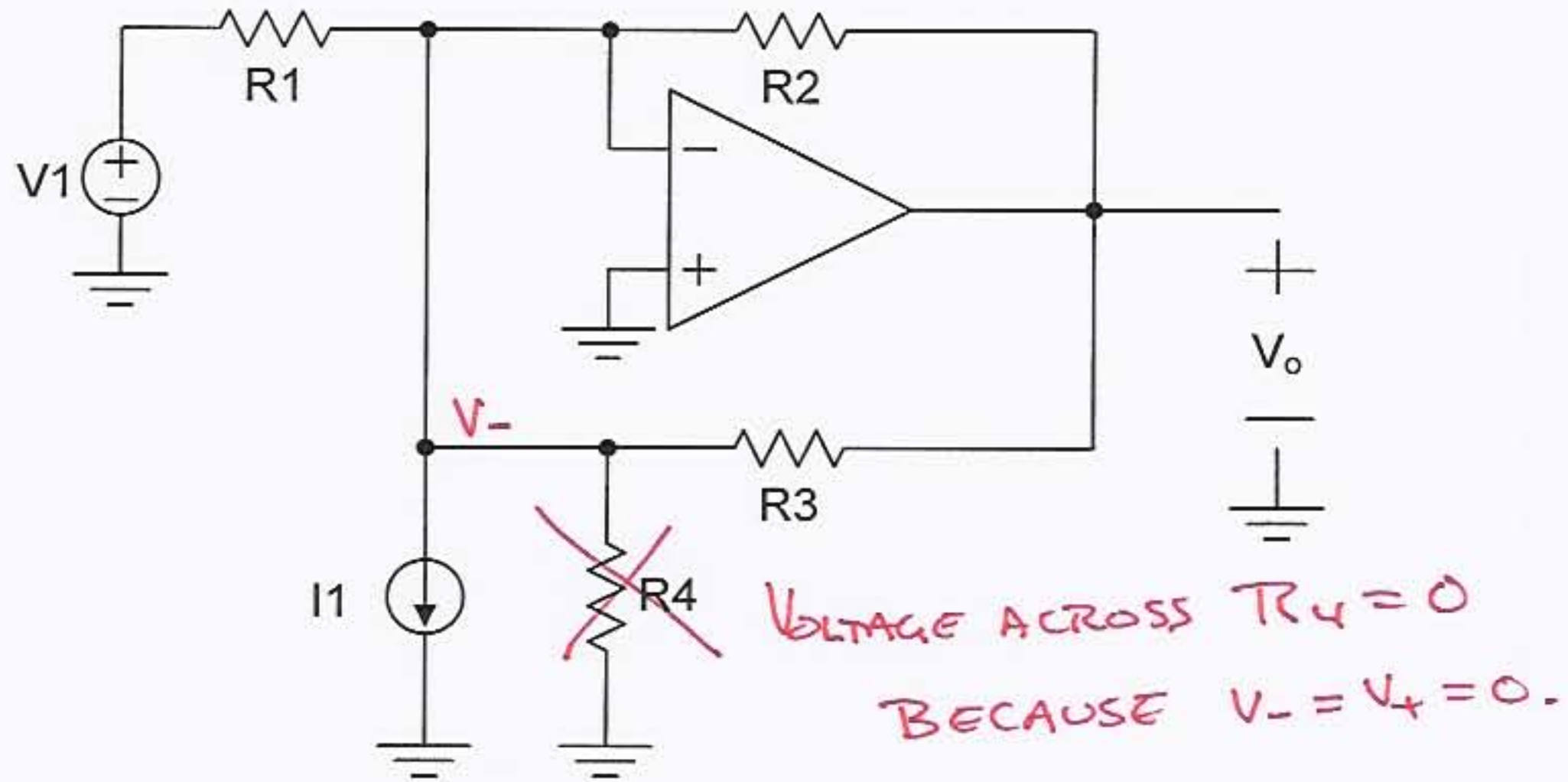Problem 5 [20 points]

Find an algebraic expression for V_o as a function of I_1 , V_1 , and resistor values. Assume that the operational amplifier is ideal.



$$V_o = \frac{R_2 R_3}{R_2 + R_3} \left(I_1 - \frac{V_1}{R_1} \right)$$

$$\textcircled{a} V_-: I_1 + \frac{V_- - V_o}{R_3 // R_2} + \frac{V_- - V_1}{R_1} = 0$$

$$I_1 + \frac{-V_o (R_2 + R_3)}{R_2 R_3} + \frac{-V_1}{R_1} = 0$$

$$\frac{V_o (R_2 + R_3)}{R_2 R_3} = I_1 - \frac{V_1}{R_1}$$

$$V_o = \frac{R_2 R_3}{R_2 + R_3} \left(I_1 - \frac{V_1}{R_1} \right)$$