

NAME:

ID #:

# 1	# 2	# 3	# 4	# 5	# 6	TOTAL
12	18	15	15	15	15	90

Instructions:

- 1 Write your name and student ID number.
- 2 Read the questions carefully.
- 3 Write your solution clearly.
- 4 This exam has 6 questions worth 90 points, so you should proceed at approximately 1 point per minute.

Problem # 1 (2 + 2 + 2 + 2 + 1 + 3 = 12 points)

Convert the following sinusoids to phasors.

(a) $3 \cos(\omega t) + 4 \sin(\omega t)$

(b) $\sqrt{2} \sin(\omega t - 45^\circ)$

Convert the following phasors to sinusoids. Assume the frequency is ω .

(d) $3 + 4j$

(e) $5 \exp(j\pi/2)$

Number conversions.

(c) Write the binary number 1111 in decimal.

(d) Write the decimal number 1111 in binary.

Problem # 2 ($3 + 3 + 3 + 3 + 3 + 3 = 18$ points)

- (a) List three features of digital electronics that make its use attractive.

- (b) An inexpensive low pass filter can be built using an inductor or using a capacitor. Which is preferable? Why?

- (c) The (Kanji) Chinese alphabet has 3000 characters. How many 8-bit bytes are needed to represent one Chinese character?

- (d) English text is to be transmitted by modem on a serial binary line. Each character is encoded in ASCII using 1 eight bit byte. The maximum transmission rate is 56 Kilo baud. How many seconds does it take to transmit one page consisting of 700 English characters?


- (e) You want to build a digital speedometer capable of measuring speeds in the range from -30 mph to 150 mph. Your digital speedometer can have a quantization error of ± 0.25 mph. How many binary lines are needed in the output data bus of the digital speedometer?

- (f) What are the units of capacitance in MKS (meter-kilogram-second-coulomb) units?

Problem # 3 (7+7+1 = 15 points)

(a) Build a **NOR** gate using at most 4 **NAND** gates.

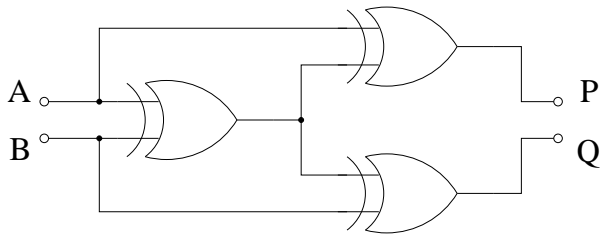
(b) For the logic circuit shown below, fill out the truth-table.
What does this circuit do ?




A	B	P	Q
0	0		
0	1		
1	0		
1	1		

Problem # 4 (4+8+1+2 = 15 points)

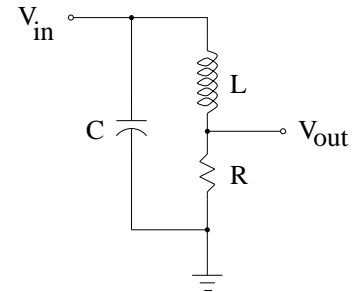- (a) Consider the circuit shown across. Let V_{in} and V_{out} be the phasors of the input voltage V_{in} and the output voltage V_{out} respectively. Find V_{out} in terms of R, L, C, ω and V_{in} .



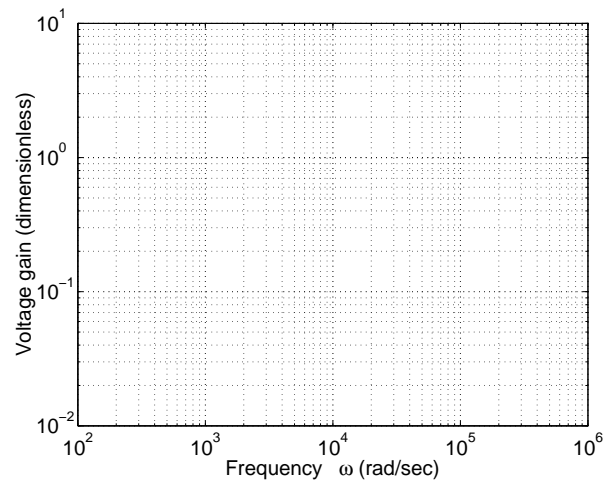- (b) With $R = 1 \text{ K}\Omega, L = 100 \text{ mH}, C = 3 \mu\text{F}$, sketch the frequency response of the voltage magnitude gain from V_{in} to V_{out} . Use the log-log scale graph-paper supplied below.





- (c) Is this a low-pass, band-pass, or high-pass filter ?

- (d) Find the $3db$ bandwidth of the filter.

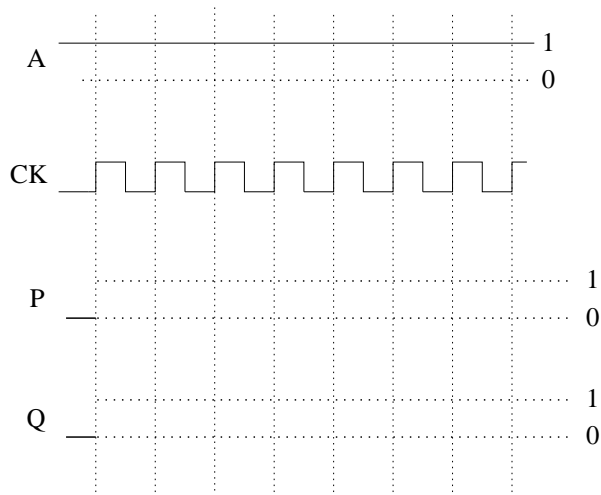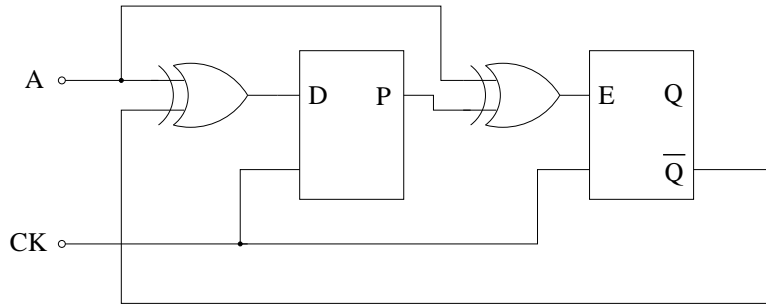Problem # 5 (15 points)

Draw the timing diagram for the circuit shown below. Here, both flip-flops are D-type and trigger on the rising edge of the clock. Note that (as discussed in class) because of propagation delays, when a flip-flop triggers, the data signal *immediately* before triggering is transferred to the flip-flop output.

Hint: Note that $A = 1$ always. Now, figure out what D and E are in terms of P and Q .



Problem # 6 (15 points)

In this problem, you are asked to design a digital circuit. There is serial binary data arriving at **A**. You have to build a circuit that detects the presence of *three consecutive zeros* on this serial line. Anytime you get three consecutive zeros at **A**, the output of your circuit **F** equals **1**, and is held until the next bit arrives at **A**.

A sample timing diagram of how this circuit should behave is shown below.

You can use three D-type flip-flops and logic gates. There is also available a clock **CK** that is synchronized with the bit arrivals on the serial line **A**.

