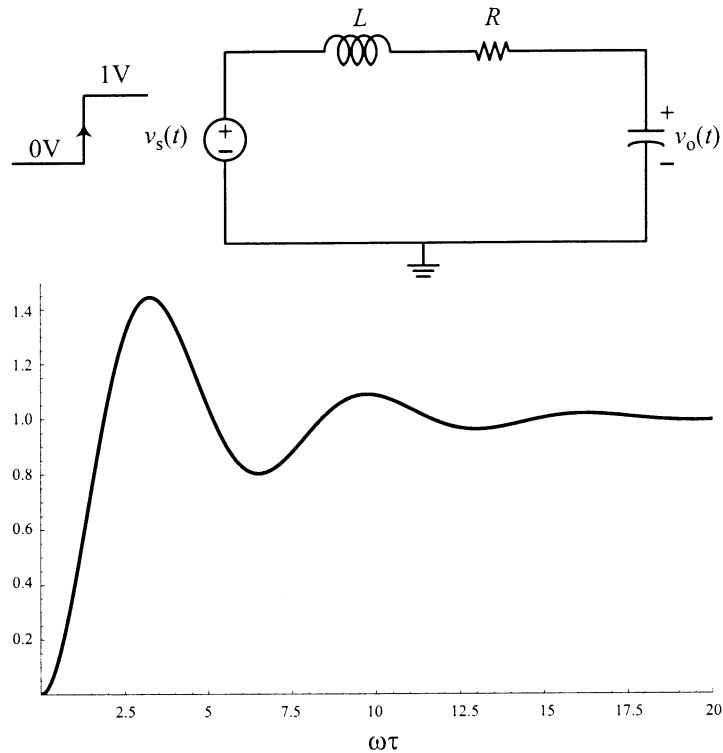


Midterm Exam (closed book)
Thursday, September 25, 2003

Helpful hints appear at the end of the exam.

1. (20 points) The step response of the series LCR circuit is shown below.



- (a) Is the damping factor ζ greater than or less than unity?

$$\zeta < 1 \quad (\text{OVERSHOOT, RINGING})$$

- (b) Qualitatively, describe the effect of decreasing the capacitance of the circuit.

$$Q = \frac{1}{\omega_0 RC} \quad \omega_0 = \sqrt{\frac{1}{LC}}$$

$$Q = \frac{\sqrt{LC}}{RC} = \frac{\sqrt{LC}}{R}$$

$$C \downarrow \Rightarrow Q \uparrow \quad \text{MORE RINGING}$$

(c) If it is desired to obtain a critically damped response, find the value of the series resistance R if $\sqrt{L/C} = 50\Omega$.

$$\zeta = 1 = \frac{1}{2Q} \quad Q = \frac{1}{2} = \frac{\sqrt{L/C}}{R}$$

$$R = 100\Omega$$

(d) If the circuit is now driven with a sinusoidal voltage source of frequency $\omega \neq \omega_0$, find an expression for the power dissipation in the resistor R ?

$$Z = R + j\omega L + \frac{1}{j\omega C}$$


$$P = \frac{1}{2} \operatorname{Re}(VI^*) = \frac{1}{2} \operatorname{Re}\left(\frac{VV^*}{Z^*}\right)$$

$$= \frac{1}{2} |V|^2 \operatorname{Re}\left(\frac{Z}{ZZ^*}\right) = \frac{1}{2} |V|^2 \frac{\operatorname{Re}(Z)}{|Z|^2}$$

$$\operatorname{Re}(Z) = R$$

$$|Z|^2 = R^2 + (\omega L - \frac{1}{\omega C})^2$$

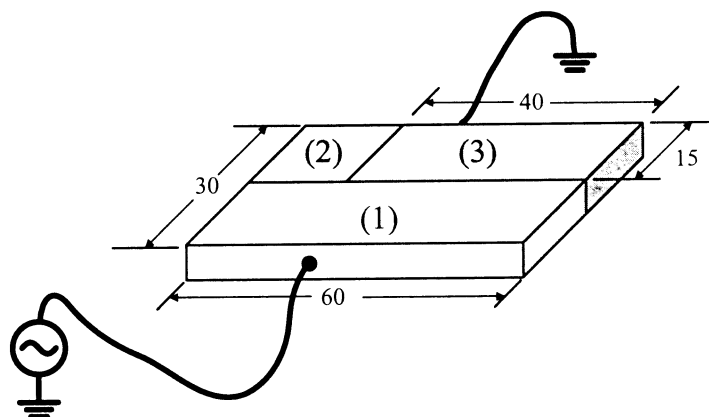2. (20 points) For the resistor shown below



The sheet resistances of the region are $R_{\square}^1 = 10\text{k}\Omega/\text{sq}$, $R_{\square}^2 = 50\text{k}\Omega/\text{sq}$, $R_{\square}^3 = 30\text{k}\Omega/\text{sq}$.

(a) Calculate the resistance of the structure

$$R_{eq} = R_1 + R_2 || R_3 = 2.5k + 8.65k = 11.15k$$

$$R_1 = \frac{15}{60} 10k = 2.5k$$

$$R_2 = \frac{15}{20} 50k = 37.5k$$

$$R_2 || R_3 = 8.65k$$

$$R_3 = \frac{15}{40} 30k = 11.25k$$

$$R_{eq} = 11.15k$$

(b) At what voltage level does Ohm's law begin to fail, assuming that the carriers saturate when the electric field approaches 10^4 V/cm?

$$E = \frac{V_x}{L}$$

$$V_x = I R_x$$

$$I = V / R_{eq}$$

V ACROSS REGION 2/3 IS HIGHEST

$$V_x = R_x \cdot E = 10^4 \frac{V}{cm} 15\mu = 15V$$

$$I = \frac{15}{R_2 || R_3}$$

$$V = I \cdot R_{eq} \approx 19.3V$$

3. (20 points) A diffusion resistor is fabricated by doping Si with a group three element. The doping has a uniform concentration of 10^{18}cm^{-3} . The thickness of the diffusion region is unknown but the measured resistance of a long rectangular resistor with $L = 100\mu$ and $W = 5\mu$ is $3k\Omega$. (a) Estimate the free carrier electron and hole densities.

$$N_A = 10^{18} \text{cm}^{-3} \Rightarrow p = 10^{18} \text{cm}^{-3} \quad n = \frac{10^{20}}{10^{18}} = 10^2 \text{cm}^{-3}$$

- (b) Calculate the thickness of the diffusion region (be careful with units of cm!).

$$R = \left(\frac{L}{W}\right) \frac{1}{\sigma t}$$

$$\sigma t = \left(\frac{L}{W}\right) \frac{1}{R} = \left(\frac{100}{5}\right) \frac{1}{3k} = \frac{20}{3} \text{ mS}$$

$$\sigma \approx p \mu q = 10^{18} \text{ cm}^{-3} \times 160 \times \frac{\text{cm}^2}{\text{V}\cdot\text{s}} \times 1.6 \times 10^{-19} \text{ C}$$

$$= 25.6 \text{ S/cm}$$

$$t = 2.6 \times 10^{-4} \text{ cm} = 2.6 \mu$$

(c) The same sample is now heated to extend the diffusion region. It is known that the diffusion region grows uniformly by 5μ , so the device now has a length of $L = 110\mu$, a width $W = 15\mu$, and a thickness that increases by 5μ . Calculate the resistance of the diffusion resistor.

$$V_1 = 100\mu \times 5\mu \times 2.6\mu = 1300 \mu^3$$

$$V_2 = 110\mu \times 15\mu \times 7.6\mu = 12540 \mu^3$$


$$\frac{V_2}{V_1} \approx 10$$

$$N_A' = 10^{17} \text{ cm}^{-3} \Rightarrow \mu_p = 330$$

$$\sigma = p \mu q = 5.28 \text{ S/cm}$$

$$R = \left(\frac{L}{W}\right) \frac{1}{\sigma t} = 1.8 \text{ k}\Omega$$

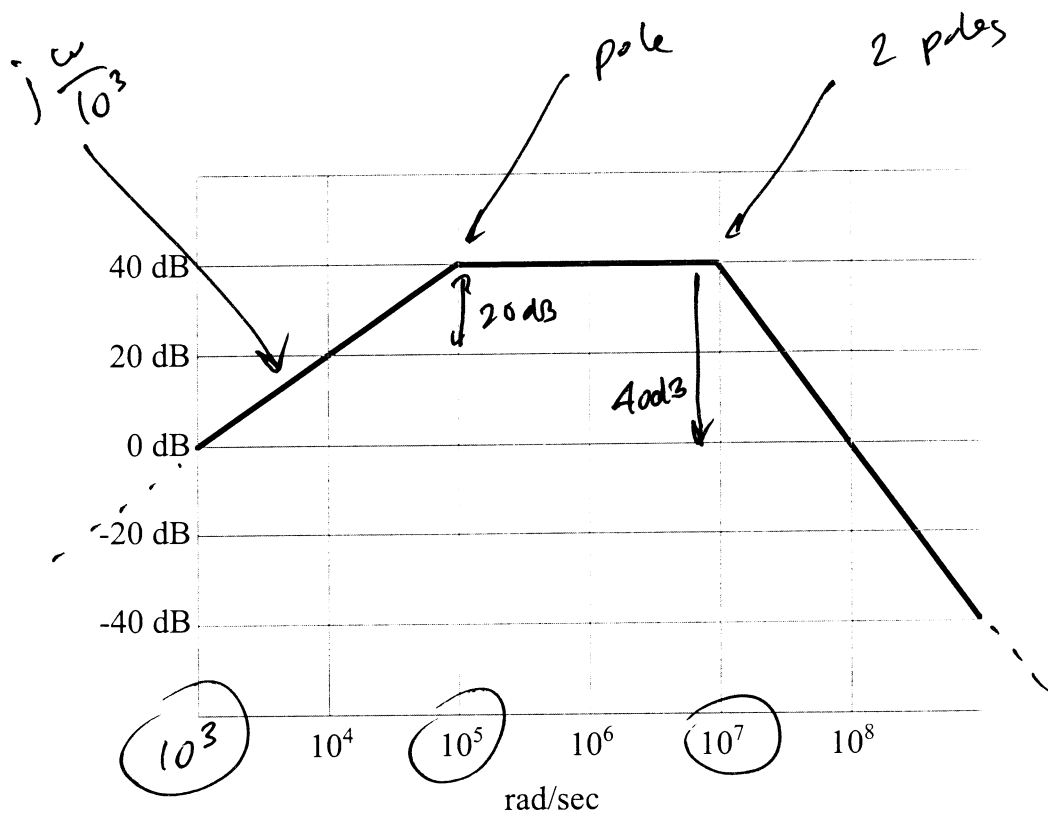
4. (20 points) Given the Bode plot shown below




(a) write the transfer function.

$$H(j\omega) = \frac{\frac{j\omega}{10^3}}{\left(1 + \frac{j\omega}{10^5}\right) \left(1 + \frac{j\omega}{10^7}\right)^2}$$

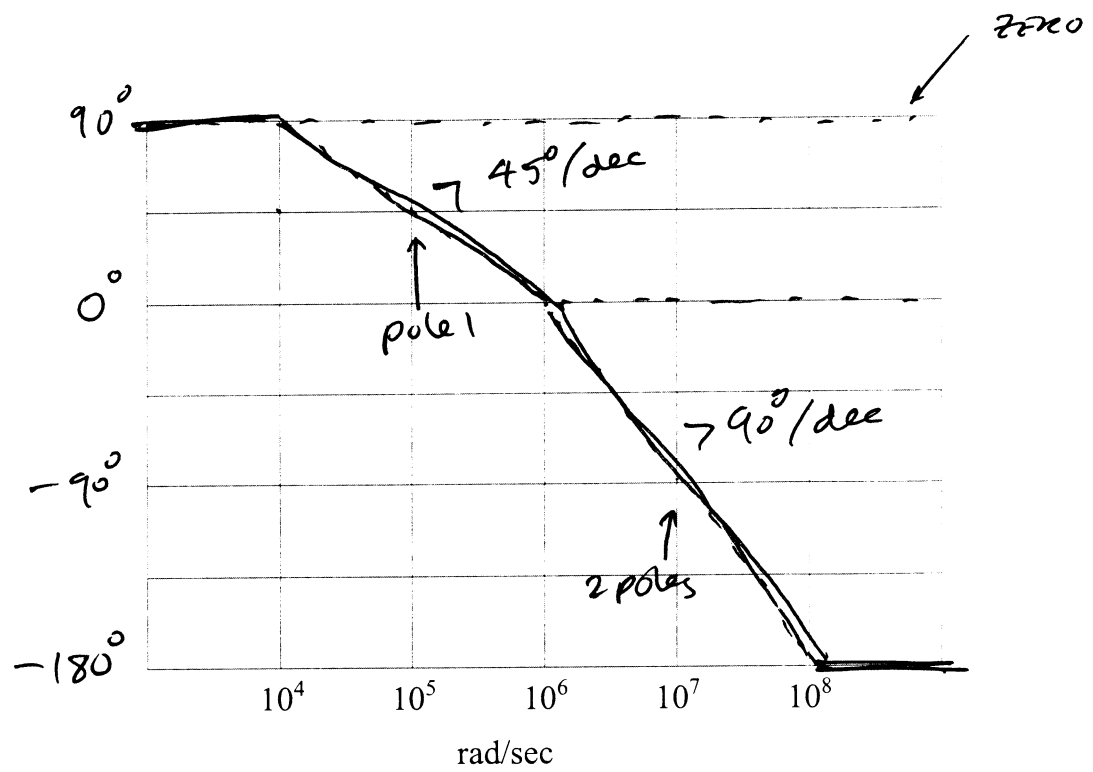(b) Draw the phase response assuming all poles and zero occur in the left half plane (in the provided graph).



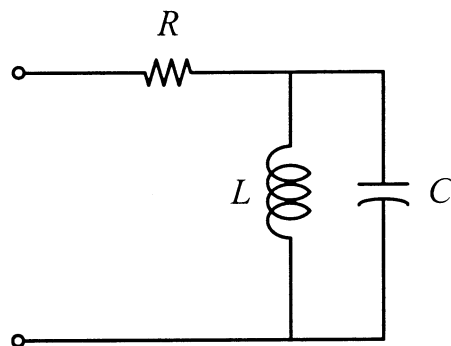5. (20 points) Given the circuit shown below



(a) Calculate the impedance transfer function. Identify the poles and zeros assuming that $\omega_0 L/R = 10$.

$$\begin{aligned}
 Z &= R + j\omega L \parallel \frac{1}{j\omega C} \\
 &= R + \frac{j\omega L \cdot \frac{1}{j\omega C}}{j\omega L + \frac{1}{j\omega C}} = R + \frac{j\omega L}{1 + (j\omega)^2 LC} \\
 &= \frac{R(1 + (j\omega)^2 LC) + j\omega L}{1 + (j\omega)^2 LC} \quad \leftarrow \text{poles: } \pm j\omega_0 \\
 \omega_0 &\equiv \sqrt{\frac{1}{LC}} \quad \text{Q-factor: } = R \frac{1 + \frac{j\omega L}{R} + (j\omega)^2 LC}{1 + (j\omega)^2 LC}
 \end{aligned}$$

(b) The denominator for the transfer function is a second order function. What is the Q of the denominator of the transfer function?

$$\begin{aligned}
 Z(j\omega) &= R \frac{1 + j \frac{\omega}{\omega_0} \left(\frac{\omega_0 L}{R}\right) + \left(j \frac{\omega}{\omega_0}\right)^2}{1 + \left(j \frac{\omega}{\omega_0}\right)^2} \\
 2\zeta &= \frac{\omega_0 L}{R} = 10 \quad \zeta = 5 > 1 \\
 &\text{TWO DISTINCT ZEROS ON REAL AXIS}
 \end{aligned}$$

(b) $Q = \infty$

(c) What happens at frequency $\omega = \sqrt{LC}$? Explain qualitatively the operation of the circuit at this frequency.

L & C RESONATE AND PRODUCE AN OPEN

$$Z = R + Z_{L||C} = R + \text{OPEN} = \infty$$

