

Problem 1 [20 points]: Semiconductor Basics

Consider a Si pn junction diode, maintained at $T = 300\text{K}$, with a structure and potential distribution as shown.


a) Estimate the resistivity of the more lightly doped side. [5 pts]

$$n = N_D = 10^{16} \text{ cm}^{-3}$$

$$\mu_n = 1200 \text{ cm}^2/\text{V}\cdot\text{s}$$

$$q\mu_n n = 1.6 \times 10^{-19} \cdot 1200 \cdot 10^{16} \approx 2$$
 
$$\rho = \frac{1}{q\mu_n n} = \frac{1}{2} \Omega\text{-cm}$$



b) Calculate the built-in potential, V_0 . [4 pts]

$$V_0 = \frac{kT}{q} \ln \frac{N_A N_D}{n_i^2} = 0.026 \ln \frac{10^{19} \cdot 10^{16}}{10^{20}} = 0.026 \ln 10^{15}$$

$$= 15 (0.026 \ln 10) = 15 \cdot 60 \text{ mV} = \underline{\underline{0.9 \text{ V}}}$$

c) What is the bias voltage, V_D ? [3 pts]

$$\text{Total potential drop across junction} = V_0 - V_D = 2 \text{ V}$$

$$\Rightarrow V_D = V_0 - 2 \text{ V} = \underline{\underline{-1.1 \text{ V}}}$$

d) Calculate the areal junction (depletion) capacitance. [3 pts]

$$C_J = \frac{\epsilon_{Si}}{W_{\text{dep}}} = \frac{10^{-12} \text{ F/cm}}{0.5 \times 10^{-4} \text{ cm}} = \underline{\underline{2 \times 10^{-8} \text{ F/cm}^2}}$$

e) Show qualitatively (by sketching a curve on the plot above) the potential distribution $V(x)$ for $V_D = 0\text{V}$. [2 pts]

f) Why does a reverse-biased pn junction have an associated (voltage-dependent) small-signal capacitance? [3 pts]

The depletion charge changes with the bias voltage, i.e. a change in V_D requires a change in $|Q_{\text{depl}}|$ on either side of the junction. $C_J \equiv \frac{\partial V_0}{\partial Q_{\text{depl}}}$

Problem 2 [20 points]: Bipolar Junction Transistor



a) What is the base-width modulation effect, and why is it undesirable? [4 pts]

An increase in $|I_C|$ with increasing $|V_{CE}|$ due to decreasing quasi-neutral base width (W) with increasing reverse bias on the collector junction. This results in a finite output resistance ($r_o < \infty$) which degrades the intrinsic gain of the BJT.

b) How should the base region of a BJT be designed to maximize current gain, and what is the trade-off? [4 pts]

- The base should be more lightly doped than the emitter ($N_B \ll N_E$)
- The quasi-neutral base width should be short ($W \ll L_B$)
- Trade-off is large base-width modulation effect (low V_A and r_o)

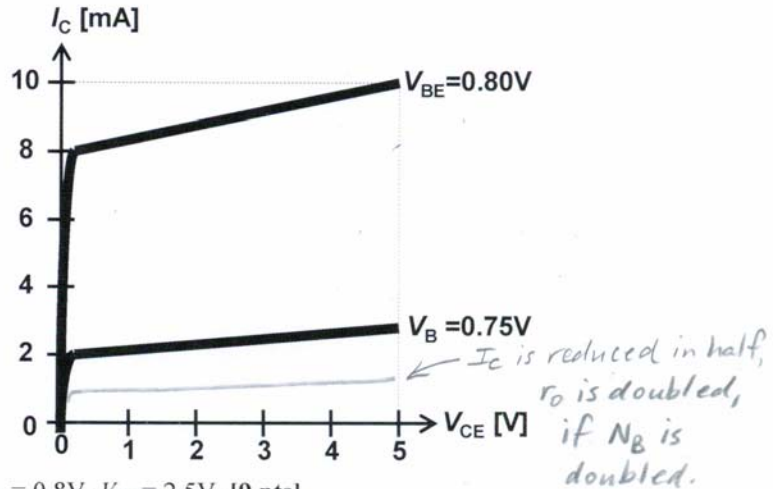 c) Consider a BJT with the I - V characteristics as shown below.



i) Draw the small-signal model for the DC bias condition $V_{BE} = 0.8V$, $V_{CE} = 2.5V$. [9 pts]
(Indicate numerical values and units for the small-signal parameters, and label the transistor terminals.)


$$I_C = 9 \text{ mA} \Rightarrow g_m = \frac{I_C}{V_T} = \frac{9 \text{ mA}}{26 \text{ mV}} = \underline{\underline{0.355}}$$

$$I_B = 80 \mu\text{A} \Rightarrow \beta = \frac{9 \text{ mA}}{80 \mu\text{A}} = 112.5$$

$$r_{\pi} = \frac{\beta}{g_m} = \frac{112.5}{0.355} = \underline{\underline{320 \Omega}}$$

$$r_o = \frac{\partial V_{CE}}{\partial I_C} = \frac{5V}{2 \text{ mA}} = \underline{\underline{2.5 \text{ k}\Omega}}$$

Small-signal model:

 


ii) Indicate by sketching a curve on each of the plots above, for $V_{BE} = 0.75V$, how the I - V characteristics would change if the base dopant concentration were to be increased by a factor of 2. [3 pts]

Problem 3 [20 points]: BJT Amplifiers

Consider the amplifier stage as shown. Assume $V_A = \infty$ and active mode operation for the BJT.

 
a) What are the purposes of C_1 and C_B ? [4 pts]

- C_1 allows the input signal to be coupled to the BJT, without disturbing its DC bias point
- C_B provides an AC ground for the BJT, to increase the voltage gain.



b) Write expressions for the small-signal voltage gain (A_v), input resistance (R_{in}), and output resistance (R_{out}). [8 pts]

circuit for AC analysis:

 


(R_1 and R_C are in parallel between output node and AC ground.)

This is a common-base amplifier, with

- " R_C " = $R_C \parallel R_1$
- " R_B " = 0
- " R_E " = $R_s \parallel R_E$

Thevenin equivalent circuit

 

$$A_v = \frac{R_C \parallel R_1}{\frac{1}{g_{m1}} + R_s \parallel R_E} \cdot \frac{R_E}{R_s + R_E}$$

$$R_{in} = R_E \parallel \frac{1}{g_{m1}}$$

$$R_{out} = R_C \parallel R_1$$

c) Describe the trade-off between headroom and voltage gain, in selecting the value for R_C . How can this tradeoff be alleviated? [6 pts]

- For large headroom, R_C should be small (so that the BJT collector is biased at a voltage $\gg V_B$).
- For large voltage gain, R_C should be large.
- This trade-off can be alleviated by increasing V_{CC} .

d) What is the main disadvantage (weakness) of this voltage amplifier design? [2 pts]

Small R_{in} (approximately $\frac{1}{g_{m1}}$), undesirable in most cases except when R_s is very small.

Problem 4 [20 points]: MOSFETs

a) Explain why the current (I_D) in a long-channel MOSFET saturates with increasing drain-to-source voltage (V_{DS}). [3 pts]

As the drain voltage increases to become greater than $V_{GS} - V_{TH}$, the inversion layer in the channel becomes pinched off at the drain end.

As V_D is increased beyond $V_{GS} - V_{TH}$, the voltage dropped across the pinch-off region increases, while the voltage across the inversion layer remains the same.

Since the lateral E-field doesn't increase with V_D , I_D doesn't increase with V_D .

b) How can the channel length modulation effect be minimized, and what is the trade-off? [3 pts]

The channel length modulation effect can be reduced by


- increasing L , and/or

- increasing N_B (which increases V_{TH})

to reduce the size of the pinch-off region relative to L .

The trade-off is lower g_m , hence lower gain.

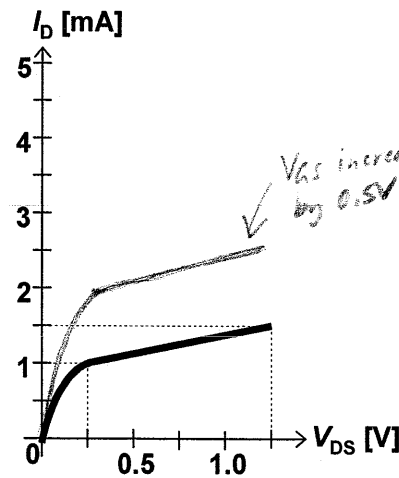c) Consider a MOSFET with threshold voltage $V_{TH} = 0.5V$, biased such that $V_{GS} = 1.0V$, with the $I-V$ characteristic shown.



i) Is this a long-channel or short-channel MOSFET? Justify your answer. [2 pts]

$V_{DSAT} = 0.25V$, which is less than $V_{GS} - V_{TH} = 0.5V$

ii) Indicate by sketching a curve on the plot how the $I-V$ characteristic would change if V_{GS} were to be increased by 0.5 V. [3 pts]

$V_{GS} - V_{TH}$ is doubled.
 $\Rightarrow I_D$ is doubled.

iii) What is the output resistance (r_o) of this MOSFET? [3 pts]

$$r_o = \frac{\partial V_{DS}}{\partial I_D} = \frac{1V}{0.5mA} = 2k\Omega$$

e) Indicate in the table below how the parameters of a short-channel MOSFET would change, if the carrier mobility were to be enhanced (e.g. by 2x). Provide qualitative reasoning for your answers. [6 pts]

MOSFET Parameter	Parameter will			Brief Justification (No equations or formulas!)
	increase	decrease	not change	
Transconductance, g_m	✓			higher $\mu \rightarrow$ higher velocity of carriers injected into the channel. \Rightarrow an incremental change in # of carriers (due to ΔV_{GS}) \rightarrow larger incremental change in I_D
Output resistance, r_o		✓		DIBL causes V_{TH} to be reduced as V_{DS} increases. If μ is increased, then the magnitude of the increase in current (I_D) with decreasing V_{TH} is increased.


Problem 5 [20 points]: MOSFET Amplifiers

a) For a given bias current, why is the transconductance for a MOSFET generally smaller than that for a BJT? [4 pts]

For a BJT, $g_m = \frac{I_C}{V_T}$. For a MOSFET, $g_m = \frac{2I_D}{V_{GS} - V_{TH}}$.

Typically, a MOSFET requires a bias $V_{GS} - V_{TH} \gg 2V_T$ (usually $\approx 0.5V$) to achieve comparable current. $\Rightarrow g_m$ is larger for a BJT.

 b) Consider the amplifier circuit below. M_1 and M_2 are long-channel MOSFETs with $\mu_n C_{ox} = 200 \mu A/V^2$, $V_{TH} = 0.4V$, and $\lambda = 0$, and are biased such that $I_{D1} = I_{D2} = 0.1mA$. $V_{DD} = 1.8V$. $(W/L)_1 = 16$ and $(W/L)_2 = 1$.



i) What is the DC bias voltage at the input (V_{G1})? [4 pts]

$$I_{D1} = \frac{1}{2} \left(\frac{W}{L} \right)_1 \mu_n C_{ox} (V_{GS1} - V_{TH})^2$$

$$(V_{GS1} - V_{TH})^2 = \frac{2I_{D1}}{\left(\frac{W}{L} \right)_1 \mu_n C_{ox}} = \frac{2 \times 10^{-4}}{16 \cdot 200 \times 10^{-6}} = \frac{1}{16}$$

$$V_{GS1} - V_{TH} = \frac{1}{4} V = 0.25V$$

$$V_{GS1} = 0.25V + 0.4V = \underline{\underline{0.65V}}$$

ii) What is the voltage gain? (A numerical answer is required.) [5 pts]

This is a common source amplifier with " R_D " = $\frac{1}{g_{m2}}$

$$\Rightarrow A_v = -g_{m1} \left(\frac{1}{g_{m2}} \right)$$

$$g_m = \sqrt{2I_D \mu_n C_{ox} \left(\frac{W}{L} \right)}$$

$$= - \sqrt{\frac{(W/L)_1}{(W/L)_2}}$$

$$= - \sqrt{\frac{16}{1}} = \underline{\underline{-4}}$$

iii) Calculate the headroom, i.e. the maximum amplitude of the small-signal output voltage for which M_1 operates in saturation. [7 pts]

$$\text{Headroom} = (V_{DD} - V_{GS2}) - (V_{GS1} - V_{TH})$$

$$I_{D2} = \frac{1}{2} \left(\frac{W}{L} \right)_2 \mu_n C_{ox} (V_{GS2} - V_{TH})^2$$


$$(V_{GS2} - V_{TH})^2 = \frac{2I_{D2}}{\left(\frac{W}{L} \right)_2 \mu_n C_{ox}} = \frac{2 \times 10^{-4}}{200 \times 10^{-6}} = 1$$

$$V_{GS2} - V_{TH} = 1$$

$$V_{GS2} = 1 + V_{TH} = 1.4V \Rightarrow \text{headroom} = 1.8 - 1.4 - 0.25 = \underline{\underline{0.15V}}$$

Problem 6 [20 points]: MOSFET Cascode Stage and Current Mirror

 a) Consider the cascode amplifier stage below. M_1 and M_2 are each long-channel MOSFETs, with $\lambda \neq 0$.



i) What is the purpose of transistor M_1 ? [2 pts]

to boost the output impedance (and hence the gain) of this amplifier stage.

ii) Describe qualitatively how the gates should be DC biased. [4 pts]

- The gate voltage for M_2 should be set such that that $I_{D2} = I_1$
- The gate voltage for M_1 should be set such that $|V_{GS1}|$ results in $I_{D1} = I_1$ and $|V_{DS2}| \geq |V_{GS2} - V_{TH}|$

iii) Derive expressions for the voltage gain (A_v) and output resistance (R_{out}). [4 pts]


The ^{small-signal} resistance seen looking into the drain of M_1 is $\sim g_{m1} r_{o1} r_{o2}$

The current source is ideal, with infinite small-signal resistance.

$$R_{out} = g_{m1} r_{o1} r_{o2}$$

$$A_v = -g_{m2} R_{out} = -g_{m2} g_{m1} r_{o1} r_{o2}$$

 b) Consider the current mirror circuit below:



i) What is the purpose of the reference transistor M_{REF} ? [2 pts]

It generates the bias voltage needed for the mirror transistor (M_1) to produce a scaled copy of the reference current (I_{REF}).

ii) Derive an expression for I_1 in terms of I_{REF} , assuming that $\lambda = 0$. [4pts]

$$I_D \propto \frac{W}{L} (V_{GS} - V_{TH})^2 \Rightarrow \frac{I_1}{I_{REF}} = \frac{(W/L)_1}{(W/L)_{REF}} \text{ since } V_{GS1} - V_{TH} = V_{GS,REF} - V_{TH}$$

$$\Rightarrow \underline{I_1 = 2 I_{REF}}$$

iii) Suppose now that $\lambda \neq 0$. If M_1 is operating under the condition $V_{DS} > V_{GS}$, would I_1 be larger or smaller than I_{REF} ? Explain briefly. [4 pts]


I_D is increased by the factor $1 + \lambda (V_{DS} - V_{DS(sat)}) = 1 + \lambda (V_{DS} - V_{GS} + V_{TH})$

For M_{REF} , $V_{DS} = V_{GS}$ so this factor is $1 + \lambda V_{TH}$

For M_1 , $V_{DS} > V_{GS}$ so this factor is $> 1 + \lambda V_{TH} \Rightarrow \underline{I_1 > \text{ideal value}}$

 Problem 7 [20 points]: Frequency Response

Consider the amplifier stage below. Assume $\lambda \neq 0$, $g_m r_o \gg 1$, and saturation mode operation for each MOSFET.



- a) Write an expression for the low-frequency voltage gain from node X to node Y, i.e. $A_{v,XY}$. [3 pts]

$$A_{v,XY} \equiv \frac{v_X}{v_Y} = -g_{m1} \left(\frac{1}{g_{m2}} \right) \approx -1$$

- b) Write an expression for the low-frequency voltage gain of the entire stage, i.e. $A_v \equiv v_{out}/v_{in}$. [3 pts]

$$A_v = -g_{m1} (g_{m2} r_{o2} r_{o1} \parallel R_D) \approx -g_{m1} R_D$$

- c) Draw the MOSFET capacitances ($C_{GS1}, C_{GD1}, C_{SB1}, C_{DB1}, C_{GS2}, C_{GD2}, C_{SB2}, C_{DB2}$) on the circuit diagram above. [4 pts]
 d) Use Miller's theorem to derive an approximate expression for the bandwidth. Assume that the dominant pole is associated with node Y, $\omega_{p,Y}$. [7 pts]

Using Miller's theorem, C_{GD1} contributes a grounded capacitance to node Y with the value $C_{GD1} \left(1 - \frac{1}{A_{v,XY}} \right) \approx 2C_{GD1}$

The total grounded capacitance at node Y is therefore

$$C_{GS2} + C_{SB2} + C_{DB1} + 2C_{GD1}$$


The (small-signal) resistance seen between node Y and AC ground is

$$r_{o1} \parallel \frac{1}{g_{m2}} \approx \frac{1}{g_{m2}}$$

The dominant pole frequency (bandwidth) is thus


$$\frac{1}{g_{m2} [C_{GS2} + C_{SB2} + C_{DB1} + 2C_{GD1}]}$$

 - e) Sketch the Bode plot on the axes provided. Label the low-frequency voltage gain and bandwidth. [3 pts]



Problem 8 [20 points]: Differential Amplifiers

 a) Consider the basic differential amplifier circuit shown below. The MOSFETs are long-channel devices.




i) Why should the circuit be symmetric, ideally? [2 pts]

to achieve zero common-mode gain

ii) Can the differential voltage gain, $v_{out}/(v_{in1}-v_{in2})$, be adjusted by adjusting the tail current I_{SS} ? Explain briefly. [3 pts] **YES.**


The transistor bias currents are each equal to $\frac{I_{SS}}{2}$. Thus $g_m \propto \sqrt{I_D}$ and hence the voltage gain $\propto \sqrt{I_{SS}}$.

 b) Consider the amplifier stage shown below. Assume $\lambda \neq 0$, $g_m r_o \gg 1$, and saturation mode operation for each MOSFET.



i) Derive an expression for the differential voltage gain, $v_{out}/(v_{in1}-v_{in2})$. [4 pts]

half-circuit for AC analysis:

 

$$A_v = -g_{m1} \left(\frac{1}{g_{m3} \parallel r_{o1}} \right) \approx -\frac{g_{m1}}{g_{m3}} = \sqrt{\frac{(W/L)_1}{(W/L)_3}}$$

ii) Qualitatively, how would the differential voltage gain be affected if the current source (I_{SS}) were not ideal, i.e. it had finite resistance? [3 pts]

So long as the circuit is symmetric, the non-ideality of the tail current source will have no impact.

iii) Considering your answer to part (i), what is the best way to adjust the design of this amplifier to **increase the voltage gain**? (Consider the various options: adjustment in I_{SS} , V_{DD} , $(W/L)_1$ or $(W/L)_2$. Also, consider the trade-off (if any) with the maximum differential input voltage, $\Delta V_{in,max}$, which is proportional to $(V_{GS}-V_{TH})_{equil}$.) [4 pts]


From part (i), we see that A_v can only be adjusted by adjusting $(W/L)_1$ or $(W/L)_3$.

If $(W/L)_1$ is increased, $\Delta V_{in,max}$ decreases, which is undesirable.

Thus, the best way to increase A_v is to decrease $(W/L)_3 = (W/L)_4$.

 
c) What is the benefit of using an active load configuration, as shown to the right? [4 pts]

It allows a single-ended output voltage signal with higher gain and immunity to noise (in V_{DD} and V_{in1} & V_{in2}).



Problem 9 [20 points]: Advanced Topics

 a) Illustrate on the plot how the frequency response of an amplifier stage would change with negative feedback, for a loop gain of 10. Estimate the reduction in low-frequency gain. [4 pts]



- Negative feedback lowers the gain by $(1 + KA_1) \approx 10$
loop gain
- Negative feedback enhances the bandwidth by $(1 + KA_1)$

b) Indicate in the table below how CMOS technology parameters should evolve with technology advancement, in order to improve the speed (i.e. reduce the gate delay) of digital CMOS circuits. Assume that transistor channel dimensions W and L are scaled proportionately with the gate-oxide thickness. [4 pts]

CMOS Technology Parameter	Parameter should		
	increase	decrease	(doesn't matter)
Gate-oxide thickness, T_{ox}		✓	
Carrier mobility, μ	✓		
Threshold voltage, V_{TH}		✓	
Power supply voltage, V_{DD}	✓		

← note that this is not good for power density!

c) What is the benefit of using silicon-germanium (SiGe) in the base region of a BJT? Explain briefly. [4 pts]

SiGe has a smaller bandgap energy, hence much larger n_i , than Si.

$\beta \propto \frac{n_i^2 N_E}{n_i^2 N_B}$ is therefore enhanced if SiGe is used as the base material.

This allows large β to be achieved with large N_B , which is beneficial for reducing base-width modulation i.e. achieving large $r_o \rightarrow$ large $g_m r_o$

d) What is the benefit of using SiGe in the source and drain regions of a p-channel MOSFET? Explain briefly. [4 pts]

Since the lattice constant is larger for SiGe than for Si, SiGe in the source/drain regions induces compressive strain in the channel region, which enhances hole mobility and hence results in larger I_{DSAT} (hence smaller gate delay for digital CMOS) and larger transconductance (hence larger gain for amplifier applications).

e) Why have BJTs (rather than MOSFETs) been preferred, historically, for radio-frequency circuit applications? Why will this change in the future? [4 pts]

The cutoff frequency (f_T) is higher for BJTs than for MOSFETs.

As MOSFETs are scaled down in size, their gate capacitance (C_{gs}) decreases so that g_m/C_{gs} increases with each new generation of CMOS technology. Thus, MOSFETs are becoming suitable for RF applications.