

**EECS 105, Fall 1992
Final Exam
Professor R. T. Howe**

- Closed book; three 8 1/2" x 11" crib sheets (both sides)
- Do all work on exam pages.
- Default bipolar transistor parameters:

nnp: $\beta_n = 100$, $V_{An} = 100 \text{ V}$, $C_{[PI]} = 15 \text{ pF}$, $C_{\#181} = 1 \text{ pF}$.
pnnp: $\beta_p = 50$, $V_{Ap} = 50 \text{ V}$, $C_{[PI]} = 30 \text{ pF}$, $C_{\#181} = 2 \text{ pF}$.

- Default MOS transistor parameters:

NMOS: $\mu_n C' = 25 \text{ AV}^{-2}$, $[\text{LAMBDA}]_n = 0.01 \text{ V}^{-1}$, $V_{Tn} = 1 \text{ V}$.
PMOS: $\mu_p C'_{ox} = 10 \text{ AV}^{-2}$, $[\text{LAMBDA}]_p = 0.02 \text{ V}^{-1}$, $V_{Tp} = -1 \text{ V}$.

Problem #1 (Single-ended BJT amplifier) [20 points]
Picture of a circuit should be here!

Problem #1a [3 points]

Find the numerical value of the following resistors:

R_{E1}, R_{REF}, R_{E3}

such that the DC input voltage V_I , the DC output voltage V_O are both zero, and all bias currents are 100 μA .

Problem #1b [3 points]

Find the numerical value of the input resistance R_i of this amplifier. Use

$R_{E1} = 5 \text{ k}\Omega$

if you couldn't do part (a)--not the correct answer for part (a), of course.

Problem #1c [4 points]

Find the numerical value of the output resistance R_o of this amplifier. Use

$R_{E3} = 10 \text{ k}\Omega$

if you couldn't do part (a)--not the correct answer for part (a), of course.

Problem #1d [3 points]

Draw the 2-port small-signal model for this *three stage* amplifier. Label all input and output resistances and controlled sources.

Problem #1e [4 points]

What is the numerical value of the small-signal voltage gain, v_o / v_i ?

Problem #1f [3 points]

What is the maximum value the output voltage can reach and still have *all* devices operating in the forward active region?

Problem #2 (Electrostatics in Thermal Equilibrium) [18 points]
Picture of an n^+p - n layer and 2 graphs should be here!

Given: the above n^+p - n is in *thermal equilibrium*. The donor and acceptor doping concentrations are shown below the structure. You can assume that the n^+p depletion layer has a total width of $0.5 \mu\text{m}$ and that the p - n depletion layer is $1 \mu\text{m}$ wide in your sketches.

Problem #2a [6 points]

Sketch the electrostatic potential $\phi(x)$ along the x axis on the graph below; your values in the bulk regions (outside the depletion layers) should be accurate.

Problem #2b [6 points]

Sketch the electric field $E(x)$ along the x axis on the graph below. Your field values should be accurate in the bulk regions (*hint:* this shouldn't be too hard if you recall the definition of bulk silicon!) and qualitatively correct in the depletion regions.

Problem #2c [6 points]

Plot (note: must be accurate!) the charge density, normalized by the electron charge, on the log plot below. *Hint:* recall that the depletion layer widths are given, along with the doping concentrations.

Problem #3 (Frequency Response) [16 points]
Picture of a circuit should be here!

Problem #3a [3 points]

Redraw the schematic with the transistor current sources replaced current-source symbols and find numerical values for the source/sink currents.

Problem #3b [4 points]

Find the numerical value of the voltage gain $A_v = v_o / v_s$.

Problem #3c [5 points]

Find the numerical value of the corner frequency of this amplifier, f_c . Note that the transistor capacitances are given on the first page.

Problem #3d [4 points]

Given: the amplifier has a second pole at 6.4 MHz. Plot the magnitude of the amplifier voltage gain in dB as a function of frequency on the graph below.

Problem #4 ("Interesting" BiMOS Logic Gate) [14 points]
Picture of a circuit should be here!

$(W/L)=5$. Other transistor parameters are given on the first page.

Problem #4a [2 points]

Plot the load characteristic i_L as a function of v_O for the npn transistor on the graph below.

Problem #4b [4 points]

Plot the driver characteristics $|i_D|$ on the same graph below, for $v_I = 0, 1, 2, 3, 4,$ and 5 V.

Problem #4c [4 points]

From your results in part (b), plot the transfer curve v_O as a function of v_I on the graph below.

Problem #4d [4 points]

Label the operating regions for the p-channel MOSFET and for the npn BJT on the transfer curve. You need not find the exact breakpoints between the different segments, but the labels should be qualitatively correct.

Problem #5 (Two-stage differential amplifier) [20 points]
Picture of a circuit should be here!

Problem #5a [3 points]

Draw the 2-port small signal model for this op amp as a cascade of the two differential amplifiers. You need not evaluate all of the parameters in this part.

Problem #5b [3 points]

Find the numerical value for the transconductance of the first stage,

$$G_{m1}$$

Problem #5c [4 points]

Find the numerical value for the transconductance of the second stage,

$$G_{m2}$$

Problem #5d [3 points]

Find the numerical value of the differential input resistance of the second stage,

$$R_{id2}$$

Problem #5e [4 points]

Find the numerical value of the output resistance of the amplifier R_o .

Problem #5f [3 points]

Given that the two small-signal input voltage waveforms are:

$$v_{i1} = (-5 \times 10^{-1} \text{V}) \cos([s\text{OMEGA}]t) \text{ and}$$

$$v_{i2} = (-8.5 \times 10^{-1} \text{V}) \cos([s\text{OMEGA}]t).$$

Find the output waveform $v_o(t)$. You can assume that $[s\text{OMEGA}]$ is much less than the corner frequency of the differential amplifier.

Problem #6 (npn BJT and n-channel MOSFET Operating Regions) [12 points]

Problem #6a [6 points]

The plots below show the minority carrier concentrations in the emitter, base, and collector for six operating points, labeled *A-F* on the output characteristics. Fill in the table by correctly identifying which cross section corresponds with which operating point.

Picture of a bode plot, 6 cross sections and matching boxes should be here!

Problem #6b [6 points]

The device structures below show (qualitatively) the mobile electron charge $|Q_n(y)|$ in the channel of the MOSFET, along with the dotted outline of the edge of the depletion layer formed with the p-type substrate. Fill in the table by correctly identifying which device structure corresponds with which operating point *A-F* on the drain characteristics.

Picture of a bode plot, 6 device structures and matching boxes should be here!

**Posted by HKN (Electrical Engineering and Computer Science Honor Society)
University of California at Berkeley**

**If you have any questions about these online exams
please contact examfile@hkn.eecs.berkeley.edu.**