

NAME SOLUTIONS RW. BRODERSEN

MIDTERM

EECS 140
FALL 2000

USE THE FOLLOWING PARAMETERS
UNLESS STATED OTHERWISE

ASSUME ALL W/L'S ARE 10.

$$V_{TN} = V_{TP} = .5V$$

$$k'_n = k'_p = 100 \mu A/V^2$$


$$\lambda_n = \lambda_p = .01$$

$$\gamma_n = \gamma_p = 0$$

SHOW YOUR WORK! MAKE APPROXIMATIONS
TO WITHIN $\pm 10\%$.

1. V_B 1.95V
2. a) 10.5 k Ω
b) 225 M Ω
3. A_V -1000
4. a) 500 k Ω
b) 8.8 or 10

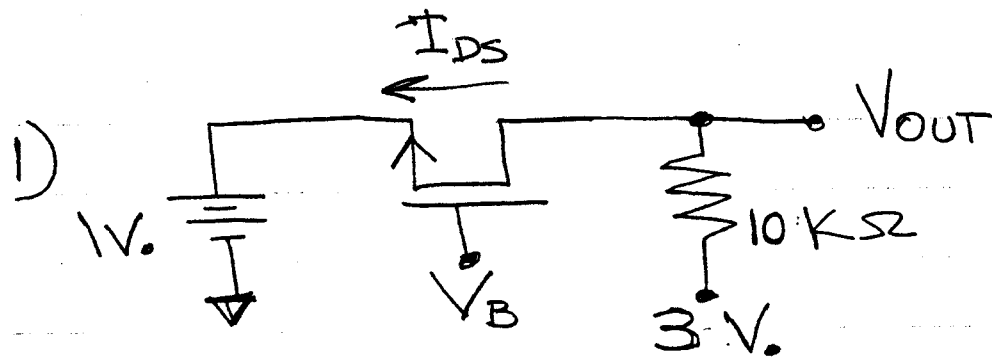5. 1.18 V
6. a) 1.55V
b) .45V
7. a) v_{max} .31
 v_{min} -.05
b) .1% or 1%




WHAT IS THE VOLTAGE AT V_B
 SO THAT V_{out} IS 2 VOLTS?
 V_B 1.95V

$$I_{DS} = \frac{3-2}{10k\Omega} = 100\mu A$$

$$= \frac{\mu_n C_{ox} W}{2L} (V_B - 1 - V_T)^2$$

$$= \frac{(10^{-4})10}{2} (V_B - 1 - .5)^2$$

$$V_B = 1.95V$$

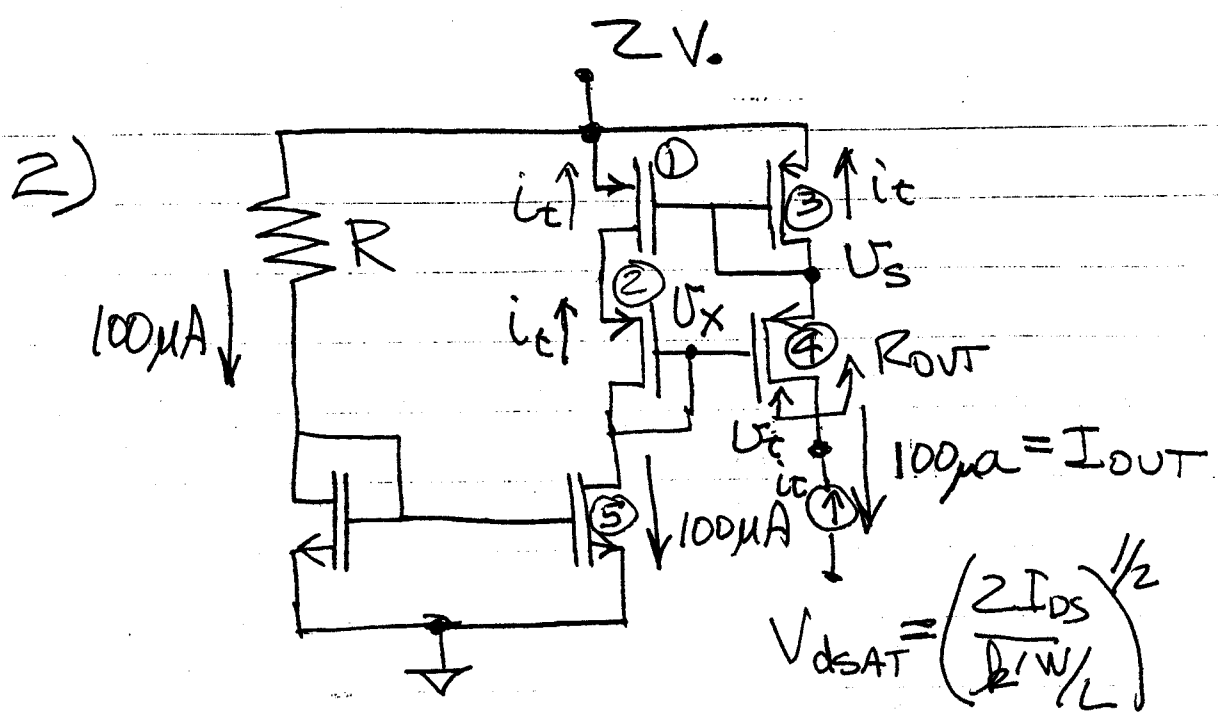

$$V_{dsAT} = \left(\frac{2I_{DS}}{\mu_n W/L} \right)^{1/2} = .45V$$

a) WHAT IS R SO THAT $I_{OUT} = 100 \mu A$? 10.5 kΩ

$$(100 \mu A)R = 2 - V_T - V_{dsAT} = 2 - .5 - .45 = 1.05V$$

$$R = 10.5 k\Omega$$


b) WHAT IS THE OUTPUT RESISTANCE, R_{OUT} ? 225 MΩ $V_S \approx 0$

WILSON SOURCE: $V_t = r_{o4}(i_t - g_{m4}V_x)$

$$V_x = -i_t(r_{o1} || r_{o5})$$

$$R_{out} = \frac{g_m r_o^2}{2} = 225 M\Omega$$
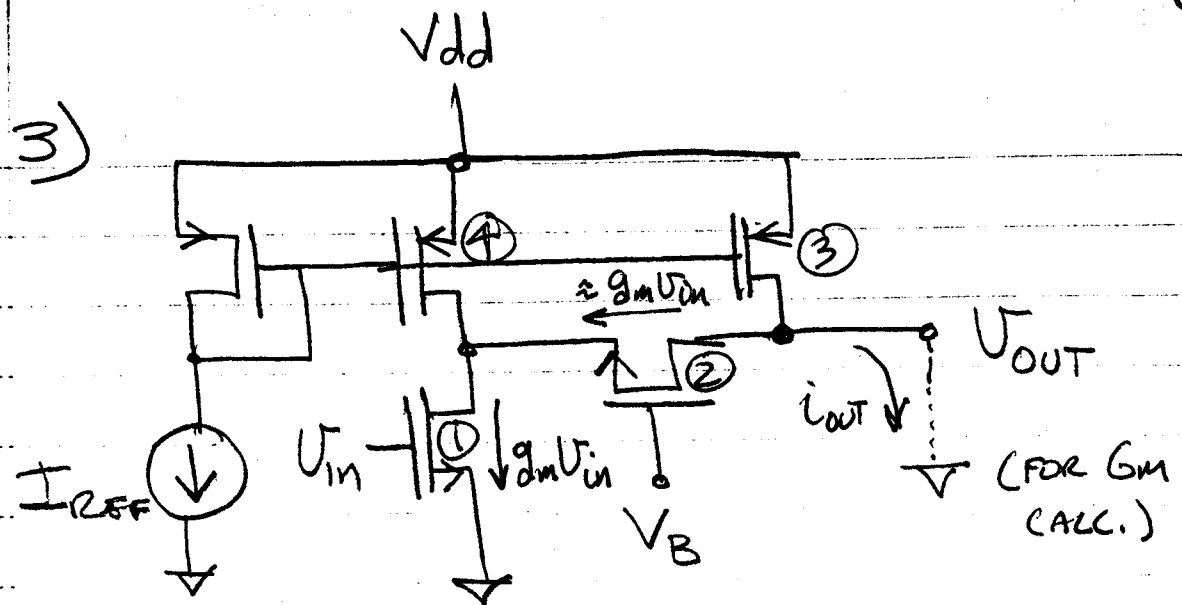
$$V_t = i_t r_{o0} \left(1 + g_m \frac{r_o}{2} \right) \approx g_m \frac{r_o^2}{2} i_t$$



ASSUME THE FOLLOWING SMALL SIGNAL PARAMETERS FOR ALL TRANSISTORS

$$g_m = .001 \text{ S} \quad \chi = .1$$

$$r_o = 1 \text{ M}\Omega$$


WHAT IS THE GAIN, $V_{out}/V_{in} \approx -1000$

$$V_{out} \approx -g_{m1} V_{in} \quad G_m = -g_{m1}$$

$$R_{out} = r_{o3} \parallel r_{o2} (1 + g_{m2} (r_{o2} \parallel r_{o1}))$$

$$\approx r_{o3}$$

$$A_v = -g_{m1} r_{o3} = -1000$$

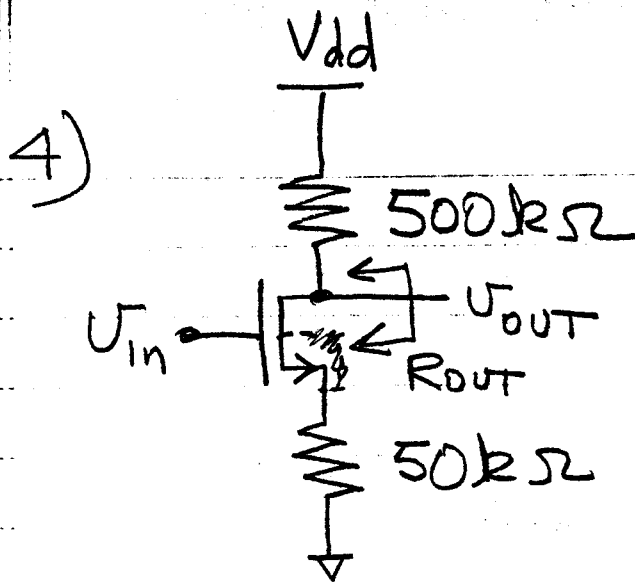

ASSUME

$$r_o = 1 \text{ M}\Omega$$

$$g_m = .001$$

$$\chi = .1$$

a) WHAT IS R_{OUT} ? $500 \text{ k}\Omega$

$$R_{OUT} = 500 \text{ k}\Omega \parallel r_o (1 + g_m (1 + \chi) 50 \text{ k}\Omega)$$

$$\approx 500 \text{ k}\Omega$$

55

b) WHAT IS THE GAIN? $8.8 \approx 10$


$$G_m = \frac{-g_m}{1 + g_m (1 + \chi) 50 \text{ k}\Omega} \approx \frac{-1}{55 \text{ k}\Omega}$$

$$A_v = G_m R_{OUT} = - \frac{500 \text{ k}\Omega}{55 \text{ k}\Omega} \approx 8.8$$

OR $\chi = 0$

$$A_v = 10$$

5)

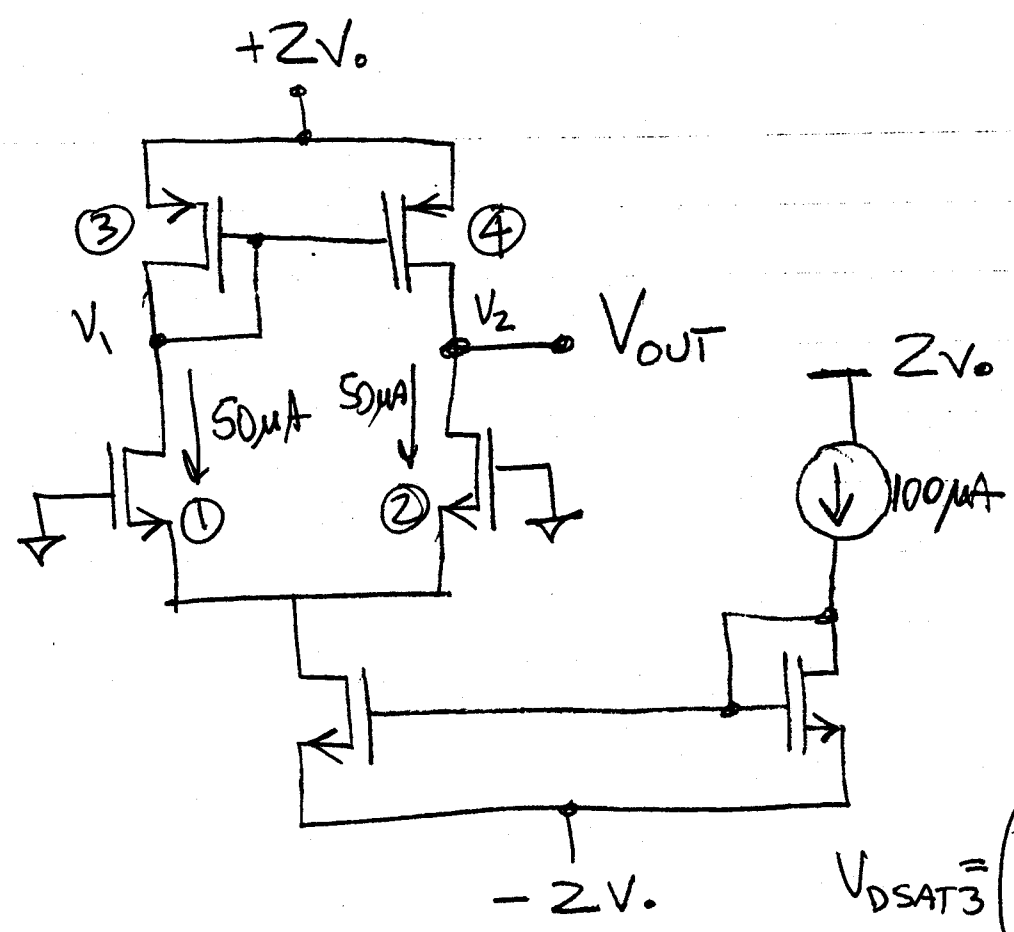


$$V_{DSAT3} = \left(\frac{2 (50\mu A)}{\mu' n / L} \right)^{1/2} = .32V$$

WHAT IS THE DC VOLTAGE AT V_{OUT} ? 1.18 V

Ⓑ SINCE $I_{DS1} = I_{DS2}$ THEN $V_1 = V_2$
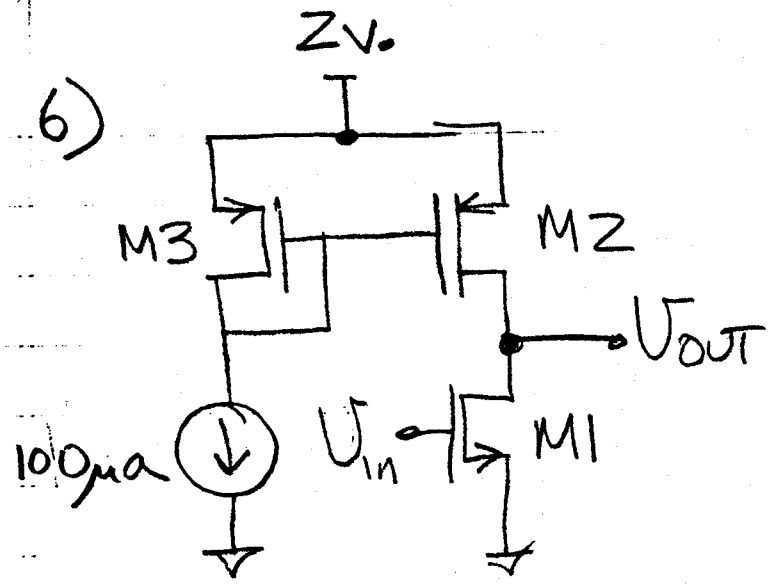
$$V_1 = 2 - V_{T3} - V_{DSAT3} = 2 - .5 - .32V = 1.18V$$



$$V_{DSAT} = \left(\frac{2(100\mu A)}{k_n' \mu/2} \right)^{1/2} = .45V.$$

WHAT IS THE MAXIMUM AND MINIMUM VOLTAGE AT V_{out} THAT KEEPS ALL DEVICES IN SATURATION?


- a) $V_{out,MAX}$ 1.55V. b) $V_{out,MIN}$.45V.

$V_{out,MAX}$ OCCURS WHEN M2 SATURATES

$$V_{out,MAX} = 2 - V_{DSAT2} = 1.55V.$$

$V_{out,MIN}$ OCCURS WHEN M1 SATURATES

$$V_{out,MIN} = V_{DSAT,1} = .45V.$$

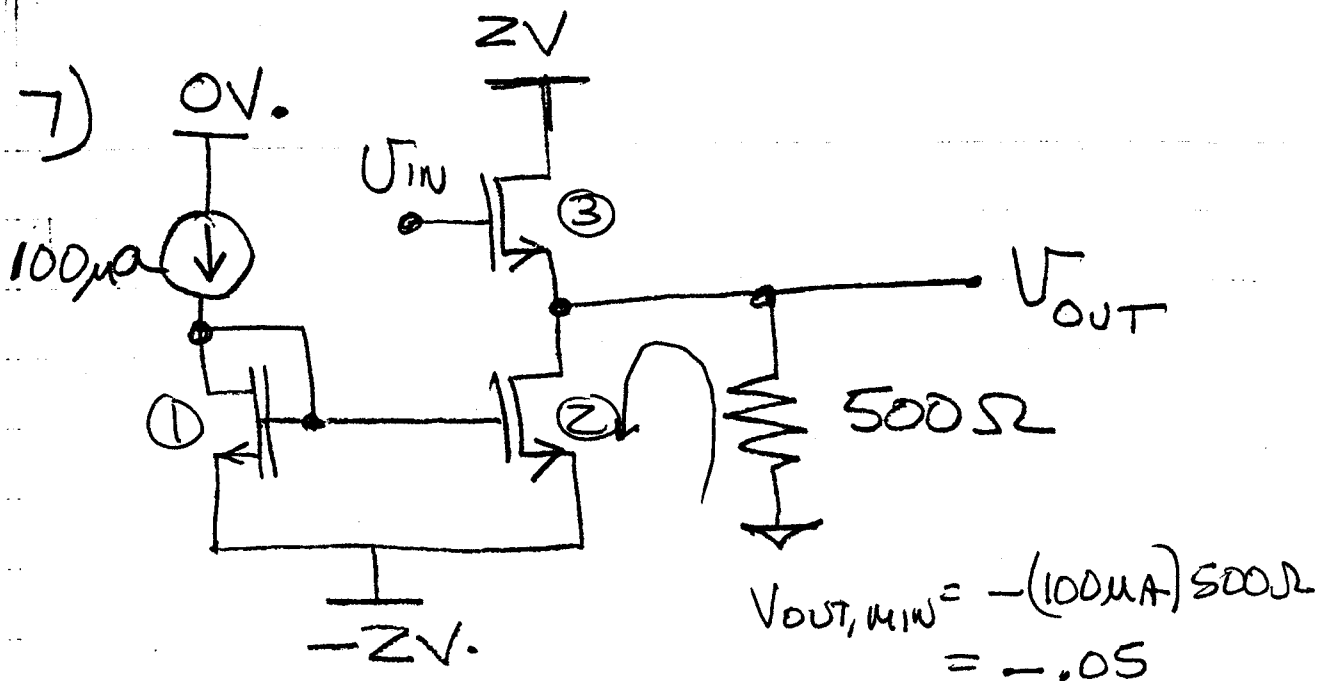

a) WHAT IS THE MAXIMUM & MINIMUM VOLTAGE AT V_{OUT}

$V_{OUT, MAX}$.31 , $V_{OUT, MIN}$ -.05

$$V_{OUT, MAX} = 2 - V_{T3} - V_{DSAT3} \quad (V_{IN} = V_{DD})$$

$$= 1.5 - \left(\frac{2(100\mu A + \frac{V_{OUT, MAX}}{R})}{k' \frac{W}{L}} \right)^{1/2}$$

$$V_{OUT, MAX}^2 - 7V_{OUT, MAX} + 2.05 = 0$$

$$V_{OUT, MAX} \approx .31$$

b) WHAT IS THE EFFICIENCY IN PERCENT INCLUDING ALL TRANSISTORS AND THE CURRENT SOURCE IF THE OUTPUT SWING IS A SINEWAVE WITH A 0.5 VOLT PEAK TO PEAK AMPLITUDE .1%

$$P_{SUPPLY} = (-2)(-I_{DS1}) + (-2)(-I_{DS2}) + 2 I_{DS3}$$

$$= 6(100\mu A) = 6 \times 10^{-4} \text{ W}$$

$$P_{LOAD} = \frac{1}{2} \frac{(.05/2)^2}{500} = .62 \times 10^{-6} \text{ W}$$

$$EFF = \frac{.62 \times 10^{-6}}{6 \times 10^{-4}} = .1\%$$