

Suggested Solutions for Mid-term Exam.

1 a) $I_{D1} = I_{D2} = I_{D6} = I_B/2$

$I_{D8} = N I_B/2$

$\Delta V_n = \sqrt{I_B / K_n' \frac{W}{L}}$ $n = 1, 2, \cancel{3}, \cancel{4}, 6, \cancel{7}, 8$

$\Delta V_q = \sqrt{I_B / K_q' \frac{W}{L}}$


$\Delta V_p = \sqrt{I_B / K_p' \frac{W}{L}}$ $p = 3, 4, 5, 7$

b) $V_{SS} + \Delta V_9 + V_{T1,2} + \Delta V_{1,2} < V_{Icm} < V_{DD} - |V_{T3,4}| - |\Delta V_{3,4}| + V_{T1,2}$

c) $V_{SS} + \Delta V_8 \leq V_o \leq V_{DD} - |\Delta V_7|$


d) $\therefore R_{out} = \frac{V_o}{i_o} \big|_{V_{in}=0}$

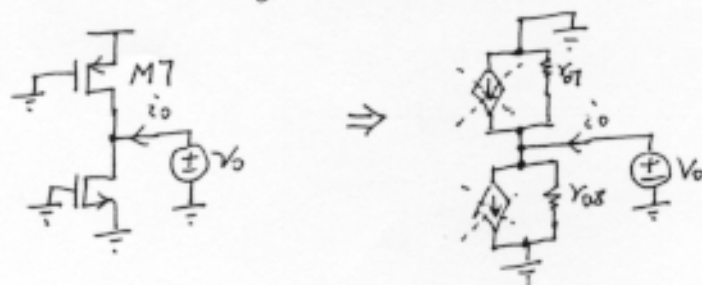\therefore The small signal model becomes.



$\therefore R_{out} = r_{o7} \parallel r_{o8}$

e). For a common source amplifier,

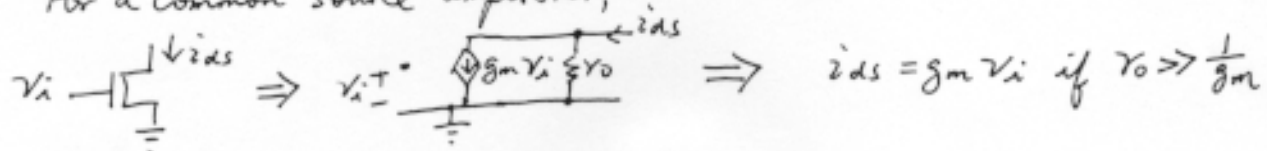

For differential mode input, $V_{i1} = \frac{V_d}{2}$, $V_{i2} = -\frac{V_d}{2}$,


and the drain of M9 is a.c. grounded (i.e. d.c. voltage is constant).

We can find $G_m = \frac{i_{out}}{V_d} \big|_{V_o=0}$ by using " $i_{ds} = g_m V_i$ "

and working from $M1 \rightarrow M3 \rightarrow M7$

& $M2 \rightarrow M4 \rightarrow M5 \rightarrow M6 \rightarrow M8$ as indicated in the

figure:

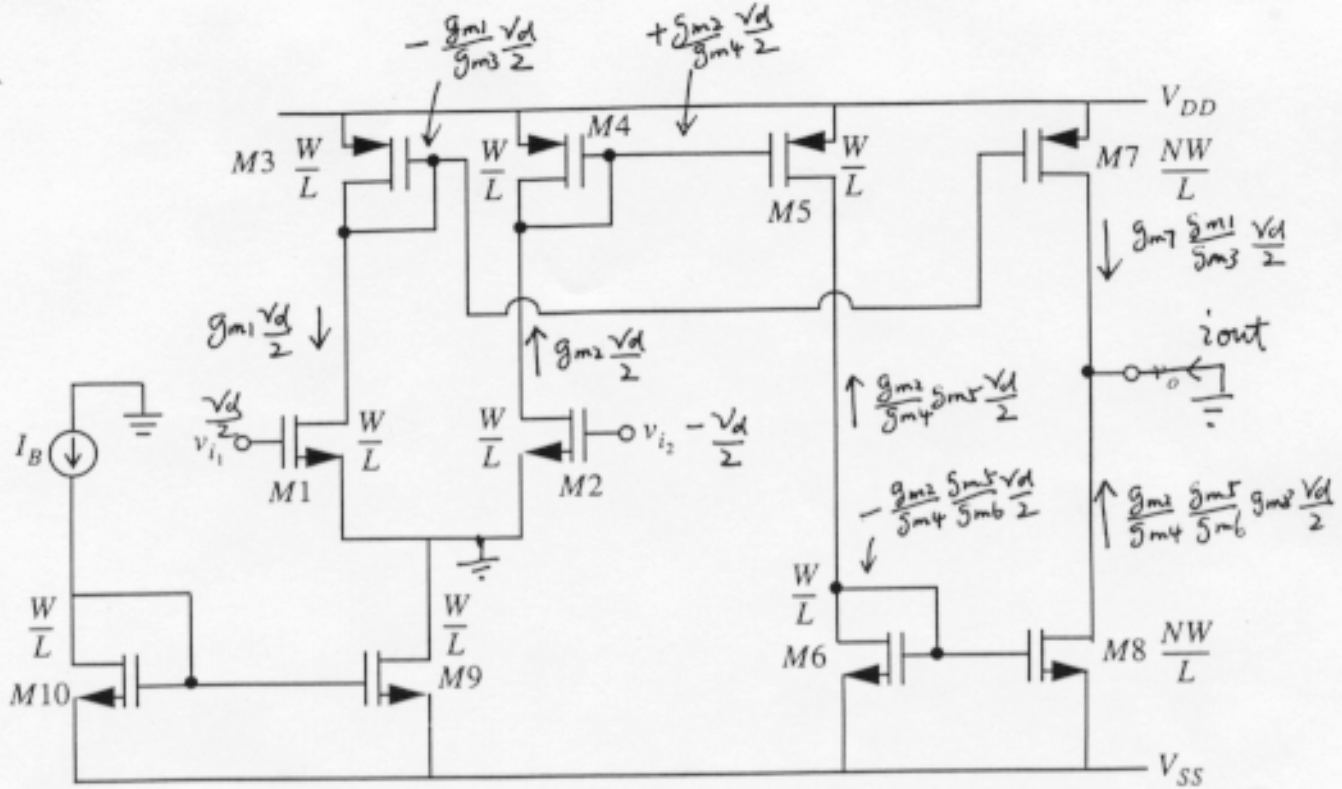

Therefore $i_{out} = - \left[g_{m7} \frac{g_{m1}}{g_{m3}} \frac{v_d}{2} + \frac{g_{m2}}{g_{m4}} \frac{g_{m5}}{g_{m6}} g_{m8} \frac{v_d}{2} \right]$

$\therefore g_{m1} = g_{m2} = g_{m1,2}, N g_{m3} = g_{m7}, g_{m4} = g_{m5}, g_{m6} = g_{m8}$

$\therefore G_m = -N g_{m1,2} \#$

f) For common mode input, the circuit is symmetric.

$M1 \rightarrow M3 \rightarrow M7 \rightarrow M8$ vs $M2 \rightarrow M4 \rightarrow M5 \rightarrow M6$

So, $V_{o8} = V_{o6} = V_{o16} = V_{o8}$, \Rightarrow M8 is diode connected in CM.

Use half circuit technique. we have


Since M9 is shared by the 2 half circuits,

$\therefore R_s = 2r_{o9}$

M1 then becomes a CS amplifier with degeneration,

$\therefore i_{sd7} \approx i_{sd1} N = \frac{g_{m1} V_{icm} N}{1 + g_{m1} 2r_{o9}}$

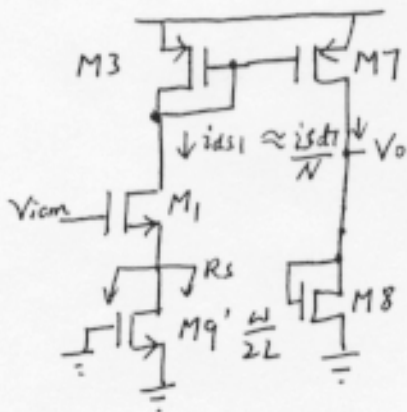$\therefore V_o = i_{sd8} \left(\frac{1}{g_{m8}} \right)$
 $= i_{sd7} \left(\frac{1}{g_{m8}} \right) = \frac{g_{m1} N}{g_{m8} (1 + 2g_{m1} r_{o9})} V_{icm}$
 $\therefore \frac{V_o}{V_{icm}} = \frac{1}{(1 + 2g_{m1} r_{o9})} \#$



$$2 a) I_{out} = I_{ref}$$

$$V_{GSn} = \sqrt{\frac{2 I_{ref}}{k' \left(\frac{W}{L}\right)}} + V_{Tn}, \quad n = 1, 2, 4, 5$$

$$V_{GSn} = \sqrt{\frac{2 I_B}{k' \left(\frac{W}{L}\right)}} + V_{Tn}, \quad n = 3, 6$$

$$b) V_{outmin} = \Delta V_2 + V_{GS3} = \Delta V_2 + V_{T3} + \Delta V_3$$

$$= \sqrt{\frac{2 I_{ref}}{k' \left(\frac{W}{L}\right)}} + \sqrt{\frac{2 I_B}{k' \left(\frac{W}{L}\right)}} + V_{T3}$$

c) Ignore body effect

$$\therefore \frac{V_2}{r_{o3}} = -g_{m3} V_1$$

$$\therefore V_2 = -g_{m3} r_{o3} V_1 \quad (1)$$


$$\text{Also, } \frac{V_1}{r_{o1}} = i_t \quad (2)$$

$$\frac{V_2 - V_1}{r_{o2}} + g_{m2}(V_2 - V_1) = i_t \quad (3)$$

$$\text{Sub (1) + (2) into (3)} \quad \frac{V_2}{r_{o2}} + g_{m2}(-g_{m3} r_{o3} r_{o1} i_t) - g_{m2} r_{o1} i_t - \frac{r_{o1} i_t}{r_{o2}} = i_t$$

$$\therefore R_{out} = \frac{V_t}{i_t} = r_{o1} + r_{o2} + g_{m2} r_{o1} r_{o2} + g_{m2} g_{m3} r_{o1} r_{o2} r_{o3}$$
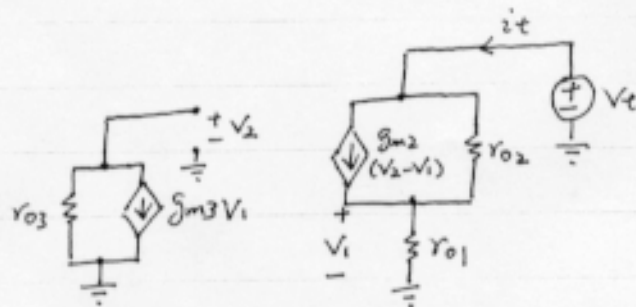
$$\approx r_{o1} r_{o2} r_{o3} g_{m2} g_{m3} \quad \#$$



d) Ensure $V_{04} = V_{01}$ so that $I_{out} = I_{ref}$ even there is channel length modulation.