

NAME SOLUTIONS

EECS 40 FALL 2003

RW BRODERSEN

ASSUME ALL  $\frac{W}{L}$ 'S = 10 UNLESS OTHERWISE SPECIFIED

$$k'_n = k'_p = 10^{-2} \text{ A/V}^2, V_{TN} = -V_{TP} = .3 \text{ V.}$$

$$2\phi_f = .6 \text{ V.}, \lambda = .05, \gamma = .1 \text{ V}^{1/2}$$

SHOW WORK. MAKE APPROX FOR  $\pm 10\%$  ACCURACY

(5) 1 a 2.6

(5) b .015

(10) 2 a 33k $\Omega$

(10) 3 a MAX 1.68V MIN .44V.

(5) b  $4 \times 10^6$

(5) 4 a 120  $\mu$ A

(10) b 40 %

(10) 5 a  $3.3 \times 10^5, 3.3 \times 10^5, 2.5 \times 10^6$  RAD/SEC

(10) b 6.8  $\mu$ f

(5) 6. a .0014 s.

(5) b 25

(5) c 366 $\Omega$

(5) 7 W  $10^{10}$  RAD/SEC


(5) R 100

(5) 8  $R_{out} = 3325$

(5)  $V_{out}/V_{in} = 1.11$



# PROBLEM 2. (10)

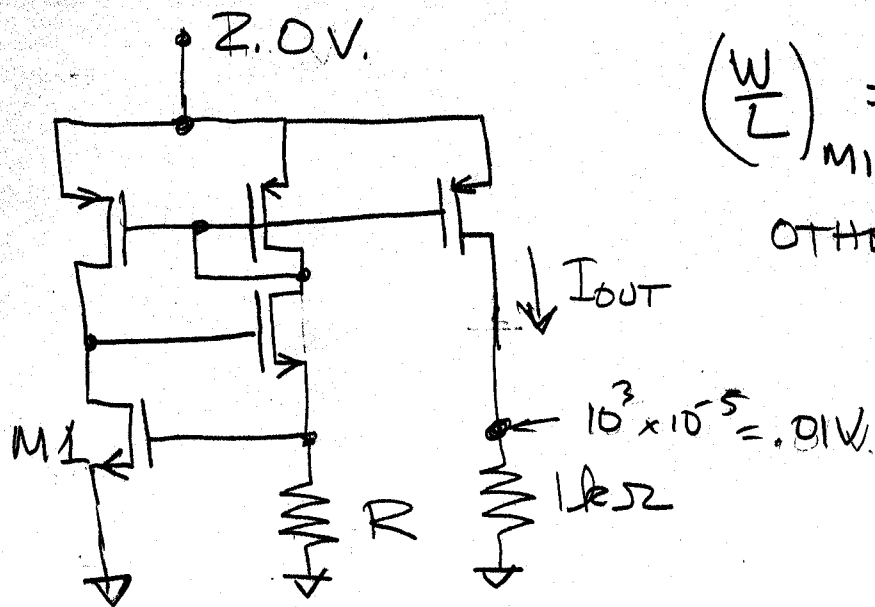

$$\left(\frac{W}{L}\right)_{M1} = 100$$

$$\text{OTHERS, } \frac{W}{L} = 10$$

- a) WHAT IS THE VALUE OF  $R$  SO THAT  $I_{OUT} = 10\mu A$ ?  $33k\Omega$

$$I_{OUT} = 10\mu A = (1 + \lambda V_{DS}) I_{OUT}^0$$

$$10\mu A = (1.1) I_{OUT}^0$$

$$I_{OUT}^0 = 9.09 \times 10^{-6}$$

$$R = \frac{V_T}{I_{OUT}^0} = \frac{.3}{9.09 \times 10^{-6}} = 33k\Omega$$

$$V_{DSAT} = \left( \frac{2 \times 9.1 \times 10^{-6}}{10^{-2} \times 10^2} \right)^{1/2} = 4.3 \times 10^{-3}$$

$\frac{W}{L} = 100$

SMALL ENOUGH TO NEGLECT


# PROBLEM 3 (15)

A WILSON SOURCE

2.0 V

$$V_{dsat} = 0.14V$$

$$\gamma = 0$$

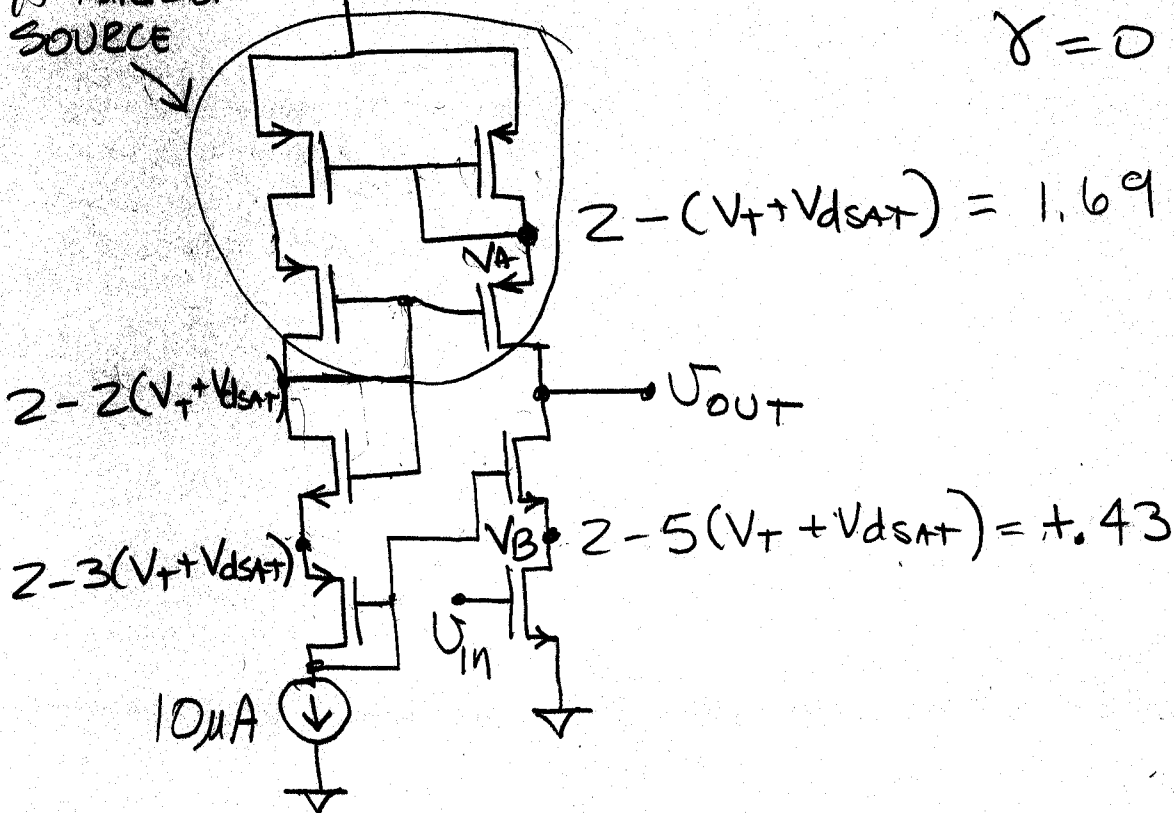

$$2 - (V_T + V_{dsat}) = 1.69$$

$$2 - 2(V_T + V_{dsat}) = V_A$$

$$2 - 5(V_T + V_{dsat}) = V_B$$

10µA

(10) a) WHAT IS THE VOLTAGE RANGE AT  $V_{OUT}$  FOR ALL TRANSISTORS TO BE IN SATURATION? 1.68 MAX .44 MIN


$$V_{MAX} = V_A - V_{dsat}$$

$$V_{MIN} = V_B + V_{dsat}$$

(5) b) WHAT IS THE GAIN,  $\frac{V_{OUT}}{V_{IN}}$ , IF  $V_{OUT}$  IS AT 1V.

$$A_v = g_m \left( \frac{g_m r_o^2}{2} \right) = 4 \times 10^6$$

PROBLEM 4 (15)

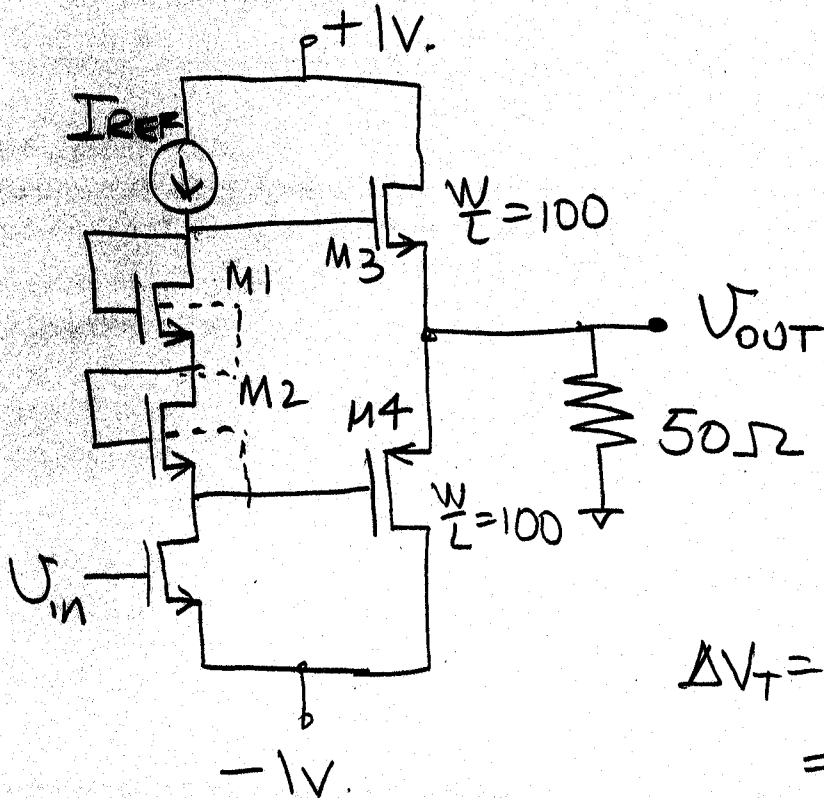

$$\Delta V_T = \sqrt{(.6 + 1)^{1/2}} - (.6)^{1/2} = -.049V$$

(5) a) WHAT IS  $I_{REF}$  SO THERE IS NO CROSSOVER DISTORTION AT  $V_{OUT} = 0V$ .

$$2(V_{TO, M1} + V_{DSAT, M1}) = 2(V_{TO} + \Delta V_T)_{M3} + 2V_{DSAT, M3}$$

(THE 2'S BECAUSE  $M1 = M2$  &  $M3 = M4$ ) = 0 WHEN  $V_{OUT} = 0$

$$V_{DSAT, M1} = \Delta V_T$$

$$\left(\frac{2I_{REF}}{\mu_n W/L}\right)^{1/2} = .049 \quad ; \quad I_{REF} = 120\mu A$$

(10) b) WHAT IS THE EFFICIENCY OF THIS CIRCUIT IF  $I_{REF} = 10\mu A$  (IGNORE CROSSOVER DISTORTION)

NEXT PAGE

# PROBLEM 4 (CONT.)

FIND  $V_{MIN}$

$$V_{MIN} = -1 + V_{DSAT}^{(10MA)} + V_T + V_{DSAT}^{I_{OUT}}$$

$$= -50(I_{OUT})$$

$$I_{OUT} = 1 - .014 - .3 - \frac{\Delta V_T}{V_T} - \left( \frac{2 I_{OUT}}{4} \right)^{1/2}$$

APPROX THIS BY  $\frac{.05}{2} = .025$

$$I_{OUT} = \frac{.66 - (2 I_{OUT})^{1/2}}{50}$$

$$= .0131 - .02 (2 I_{OUT})^{1/2}$$

GUESS	ANS
20ma	9ma
9ma	10.3
10.3	<u>10.1ma</u>

$$V_{NEG} = -(10.1ma) 50$$

$$= \underline{\underline{.51V}}$$

FOR PUSH PULL


$$EFFICIENCY = \frac{\pi}{4} \frac{\hat{V}_{O,PK}}{V_{DD}} = \underline{\underline{40\%}}$$

$$P_{LOAD} = \frac{\hat{V}_O^2}{2R}$$

$$P_{SUPPLY} = \frac{2}{\pi} V_{DD} \frac{\hat{V}_O}{R}$$

$$EFF = \frac{P_{LOAD}}{P_{SUPPLY}}$$

# PROBLEM 5 (20)

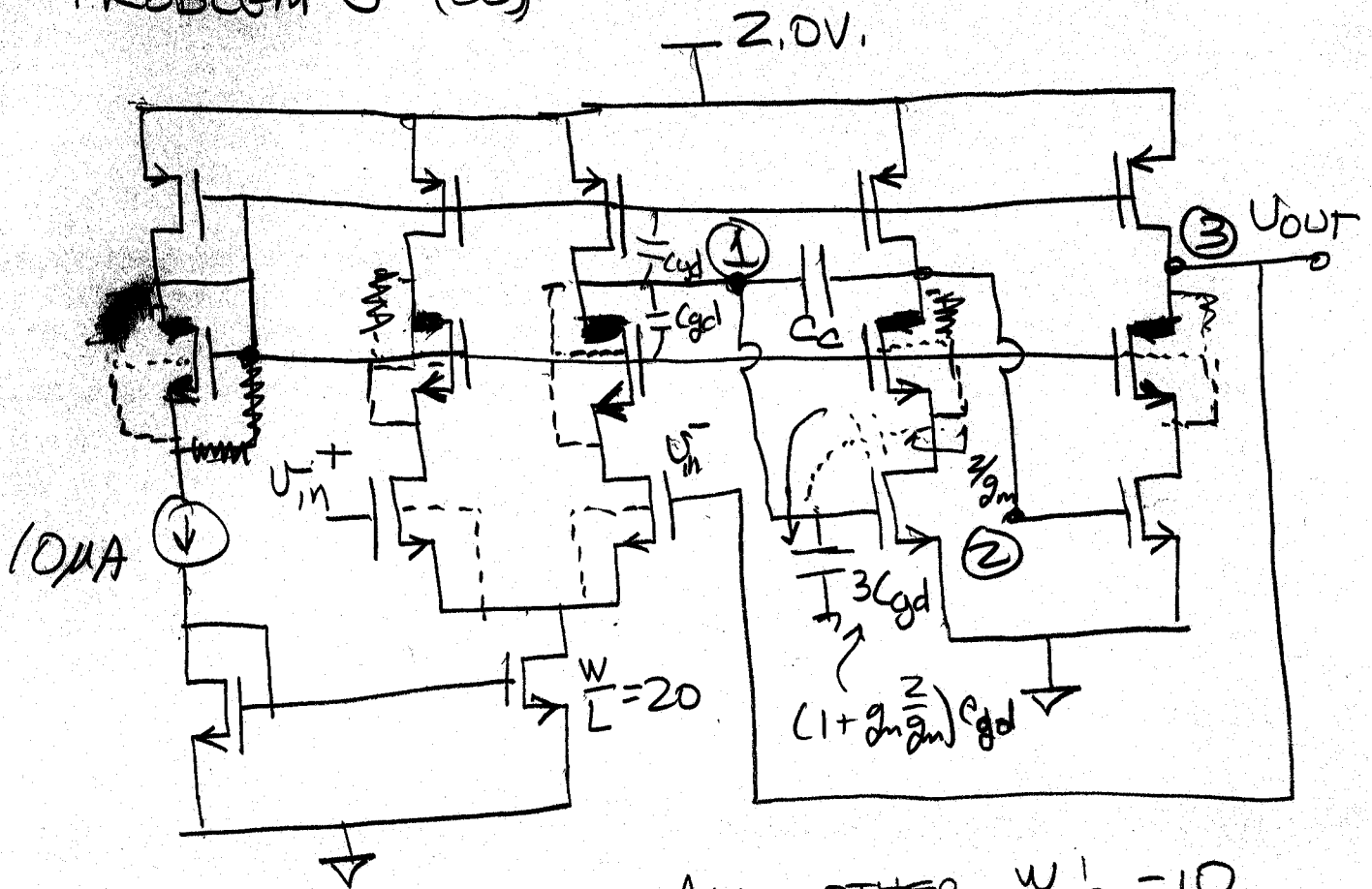

ALL OTHER  $\frac{W}{L}'s = 10$

$$C_{GS} = 1 \text{ pF}$$

$$C_{GD} = 0.1 \text{ pF}$$

ALL OTHER  $C's = 0$

ASSUME ALL DEVICES IN SAT.

- (10) a) OPEN THE LOOP  
(DISCONNECT THE CONNECTION TO  $V_{in}^-$ )  
WHAT ARE THE 3  
LOWEST POLES?

SET  $C_L = 0$ .

$$\omega_{p1} = \omega_{p2} = \frac{1}{(g_{m1} r_{o1} \parallel r_{o2}) (2C_{GD} + C_{GS} + 3C_{GD})}$$

$$\omega_{p3} = \frac{1}{(r_{o1} \parallel g_{m1} r_{o2}^2) (2C_{GD})}$$

$$= 2.5 \times 10^6 \text{ RAD/SEC}$$

$$= \frac{1}{2 \times 10^6 (1.5 \text{ pF})} = 3.3 \times 10^5 \frac{\text{RAD}}{\text{SEC}}$$

- (10) b) CLOSE THE LOOP AND WHAT IS THE  
VALUE OF  $C_L$  FOR  $45^\circ$  OF PHASE MARGIN

# PROBLEM 5 (CONT.)

$$a_{v1} = \frac{g_m r_o}{2} (g_m r_o)^2 = 11.3 \times 10^9$$

WITH FEEDBACK CONNECTION

NODE 3 POLE MOVES TO

$$\begin{aligned} \omega_{p3} &= \frac{1}{2 \times 10^6 (C_{gs} + 3C_{gd} + 2C_{gd})} \\ &= 3.3 \times 10^5 \text{ RAD/SEC} \end{aligned}$$

FROM  $V_{in}$  NODE

NODE 1 IS THE COMPENSATION POLE  
AND NODE 2 IS SPLIT - HAS  $\frac{1}{g_m}$  AS RESISTANCE

$$\omega_c = \frac{\omega_{p3}}{a_{v1}(1)} = 2.9 \times 10^{-5}$$

FOR 45° OF PHASE MARGIN


VERY LOW  
BECAUSE OF THE  
VERY HIGH GAIN  
- DIFFICULT TO  
MAKE STABLE

$$\omega_c = \frac{1}{(g_m r_o) C_c r_o}$$

$$C_c = \frac{1}{(2830) 2 \times 10^6 \times 2.9 \times 10^{-5}} = \underline{\underline{6.8 \mu f}}$$



# PROBLEM 6 (15)

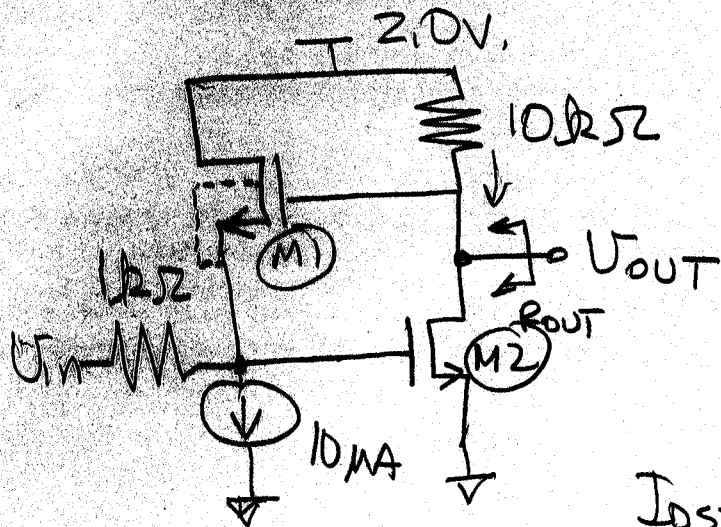

$$\frac{W}{L}'_S = 10$$


ASSUME  $V_{in}$  IS SET SO  $V_{out}$  IS AT 1.0V.

$$I_{DSS2} = 100\mu A \quad g_{m2} = 4.5 \times 10^{-3} \text{ S} \\ r_{o2} = 200k\Omega$$

USE FEEDBACK ANALYSIS TECHNIQUES.

(5) a) WHAT IS  $f$ ?

$$f = g_{m1} = .0014$$

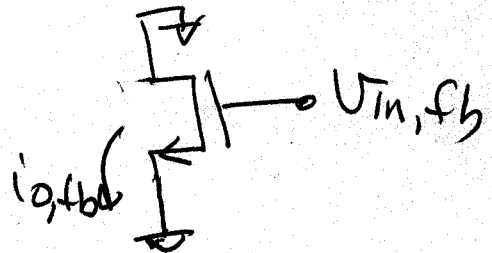

(5) b) WHAT IS THE LOOP GAIN WITH LOADING?


$$V_{out} = \frac{V_{out}}{i_{in}} = \left[ \frac{1}{g_{m1}} \parallel 1k \right] g_{m2} (10k \parallel r_{o2}) \\ = 17.8 \times 10^3 = a_R$$

(5) c) WHAT IS  $R_{out}$

$$T = a_R f_g = g_{m1} a_R \\ = 25$$

$$R_{out} = \frac{10k \parallel 200k\Omega}{1 + T} = 366\Omega$$


# PROBLEM 7 (10)

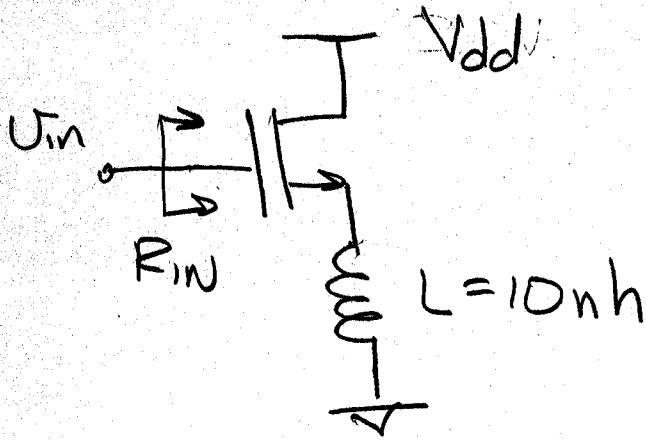

$C_{gs} = 1\text{pF}$   
 IGNORE OTHER C'S  
 $g_m = 10^{-2}\text{S}$   
 $r_o = 10^4\ \Omega$

AT WHAT FREQUENCY IS  $R_{in}$  PURELY RESISTIVE AND WHAT IS THE VALUE

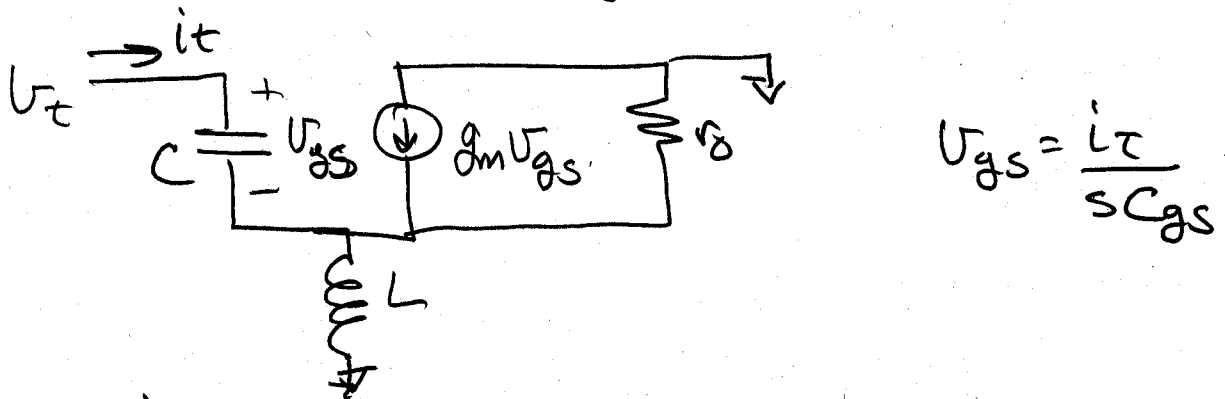(5)  $\omega_R = \underline{\hspace{2cm}}$  (5)  $R = \underline{\hspace{2cm}}$



$V_{gs} = \frac{i_t}{sC_{gs}}$

$V_t = \frac{i_t}{sC_{gs}} + g_m V_{gs} (sL || r_o) + i_t (sL || r_o)$

$= i_t \left( \frac{1}{sC_{gs}} + (sL || r_o) + g_m \left( \frac{sL || r_o}{sC_{gs}} \right) \right)$

LETS ASSUME  $|r_o| \gg |sL|$  LIKELY SINCE RF IMPEDANCES ARE ON THE ORDER OF 50 $\Omega$


$Z_{in} = \frac{1}{sC_{gs}} + sL + g_m \frac{L}{C_{gs}}$  ; IF  $\frac{1}{j\omega C_{gs}} + j\omega L = 0$  THEN

$Z_{in} = g_m \frac{L}{C_{gs}} = 100\ \Omega$

THIS HAPPENS  $\omega = \frac{1}{(LC)^{1/2}} = 10^{10}\ \text{RAD/SEC}$

CHECKING  $|sL| = |10^{10} \times 10^{-8}| = 100\ \Omega \ll r_o$

# PROBLEM 8

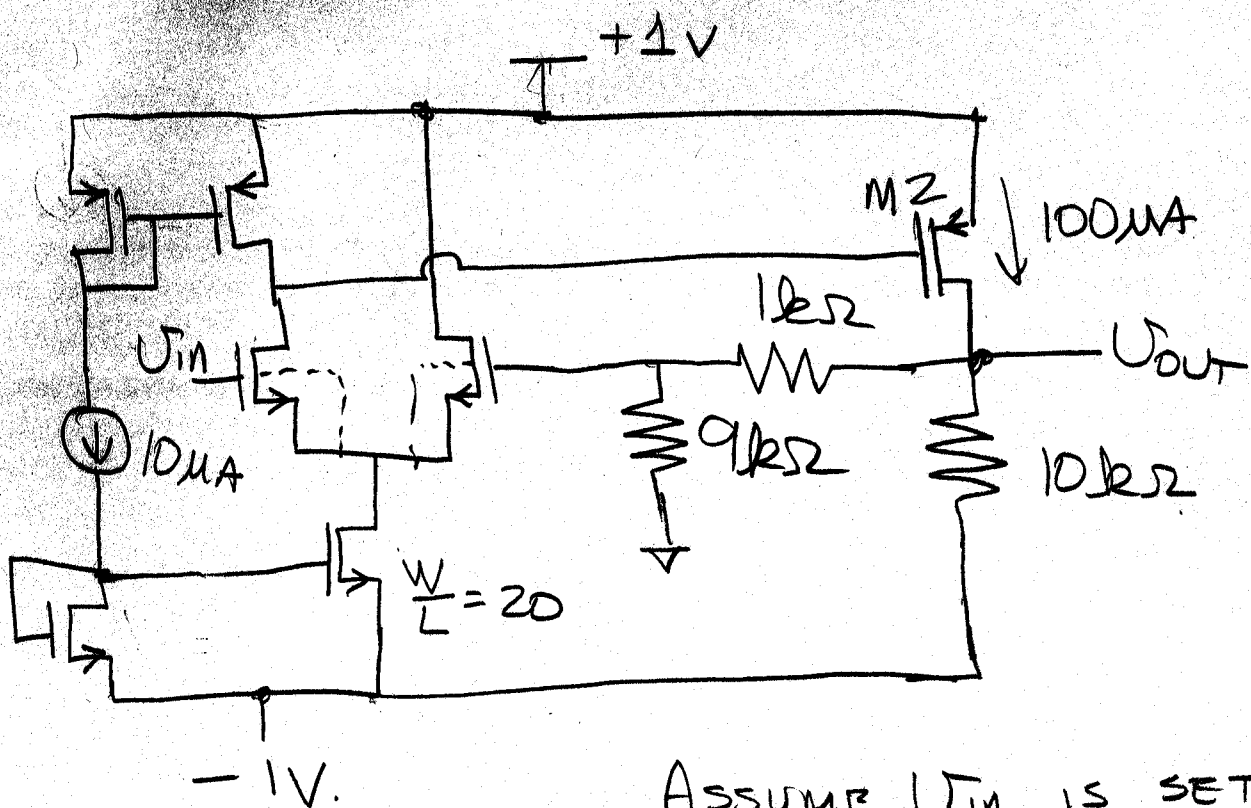

ASSUME  $V_{in}$  IS SET  
SO  $V_{out} = 0V$

(5) a) WHAT IS  $R_{out}$

$$R_{out} = \frac{10k \parallel 200k \parallel 10k}{1 + T}$$

$$= \frac{4.9k}{15 \times 10^3} = 333\Omega$$

$$f = \frac{9k}{1k + 9k} = 0.9$$

$$a_v = \left(\frac{g_m}{2}\right) \frac{1}{20} g_m (10k \parallel 10k \parallel 200k)$$

$$= 15.6 \times 10^3$$

$$T = a_v f = 14 \times 10^3$$

(5) b) WHAT IS  $\frac{V_{out}}{V_{in}}$

$$\frac{V_{out}}{V_{in}} = \frac{1}{f} \frac{T}{1 + T} = \frac{1}{0.9} = 1.11$$