

Name: SOLUTIONS

EECS 140

Midterm #1

Fall 1998

R.W. Brodersen

Use these values unless otherwise stated:

$$V_{TN} = .5V ; V_{TP} = -.5V$$

$$k_n = k_p = 100 \mu A/V^2$$

$$\lambda_n = \lambda_p = .01$$

$$\gamma = 0$$

1a) -1.74

b) 6.5k $\Omega$

2a) 122k $\Omega$

b) 1.72V, .72V

c) 76 $\Omega$

d) 10<sup>6</sup>

3a) 710

b) 14k $\Omega$

4a) -100

b) -4.2x10<sup>-7</sup>

5a) 1

b) .33 (.5OK)

c) -.5


6) 500 $\Omega$

7a) .027V

b) -.17V

c) .47% (-.67% OK)

1)

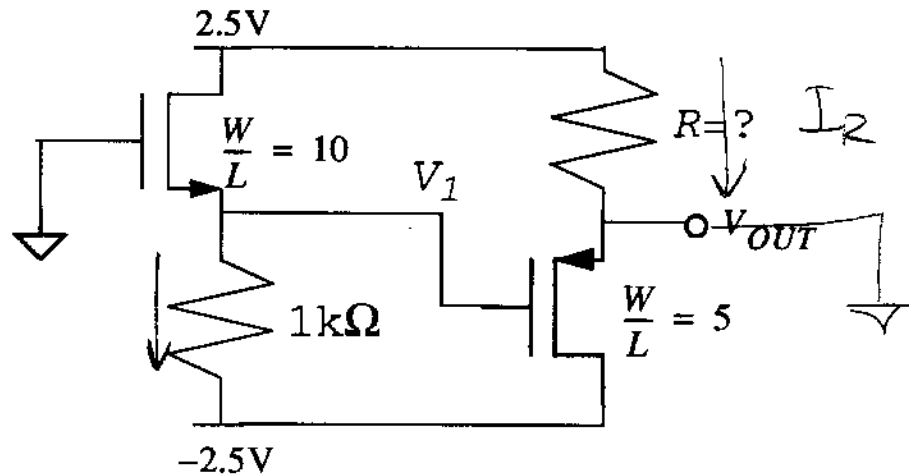

What is the voltage at  $V_1$ ?  $-1.74\text{V}$

$$\frac{V_1 - (-2.5)}{1\text{k}\Omega} = \frac{\mu_n C_{ox}}{2} 10 (0 - V_T - V_1)^2$$

$$.5V_1^2 - .5V_1 - 2.375 = 0$$

$$V_1 = -1.74 \quad (2.74)$$


What is the resistance  $R$ , which sets  $V_{OUT} = 0\text{V}$ ?

$$R = \underline{6.5\text{k}\Omega}$$

$$I_R = \frac{2.5}{R} = \frac{\mu_n C_{ox}}{2} 5 (0 - 1.74 + 1.5)^2$$

$$R = \frac{2.5}{3.8 \times 10^{-4}} = 6.5\text{k}\Omega$$

2)

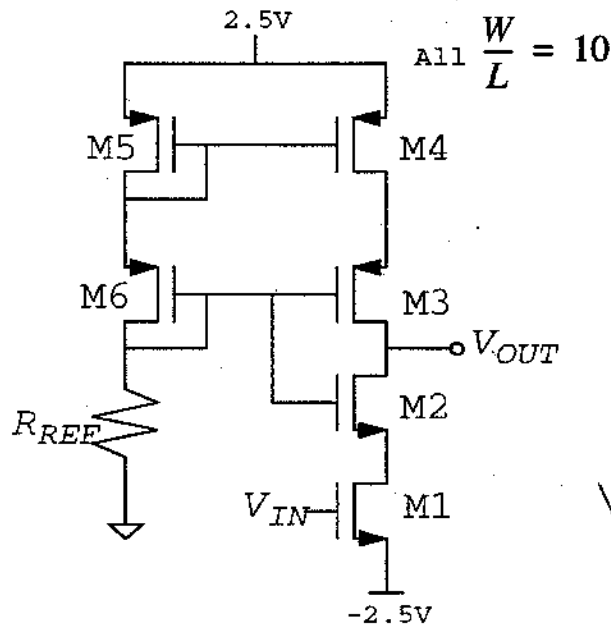

$$V_{DSAT5} = \left( \frac{2I_D}{\mu W/L} \right)^{1/2}$$

$$= \left( \frac{2 \cdot 10 \times 10^{-6}}{10^{-4} \cdot 10} \right)^{1/2} = 0.14$$

a) What is  $R_{REF}$  so that  $I_{DS} = 10 \mu A$ ?

$R_{REF}$  122 k $\Omega$

$$V_{G6} = V_{DD} - 2(V_T + V_{DSAT}) = 2.5 - 2(0.5 + 0.14) = 1.22 \text{ V}$$

$$R_{REF} = \frac{V_{G6}}{I} = \frac{1.22}{10 \mu A} = 122 \text{ k}\Omega$$

b) What is the maximum swing at

$V_{OUT}$  which has high gain?

$V_{OUT,MAX}$  1.72V,  $V_{OUT,MIN}$  -0.72V

$$V_{OUT,MAX} = V_{DD} - (V_T + V_{DSAT}) - V_{DSAT}$$

$$= 2.5 - (0.5 + 0.14) - 0.14 = 1.72 \text{ V}$$

$$V_{OUT,MIN} = V_{G6} - V_T = 1.22 - 0.5 = 0.72 \text{ V}$$

c) what is the output resistance?

$$R_{OUT} = \underline{76\Omega}$$

$$r_o = \frac{1}{\lambda I_D} = 10\text{M}\Omega$$

$$g_m = \frac{2I_D}{V_{dsAT}} = 141\frac{\mu\text{A}}{\text{V}}$$


$$\begin{aligned} R_{OUT} &= R_{o1} \parallel R_{o2} \approx r_{o3} r_{o4} g_{m3} \parallel g_{m2} r_{o2} r_{o1} \\ &\approx \frac{14.1\text{G}\Omega}{2} = 7\text{G}\Omega \end{aligned}$$

d) What is the gain?  $10^6$

$$G_m = -(1+\chi) g_m = -g_m$$

$$\begin{aligned} A_v &= -g_m R_{out} = 141\frac{\mu\text{A}}{\text{V}} \cdot 7\text{G}\Omega \\ &= 10^6 \end{aligned}$$

3)

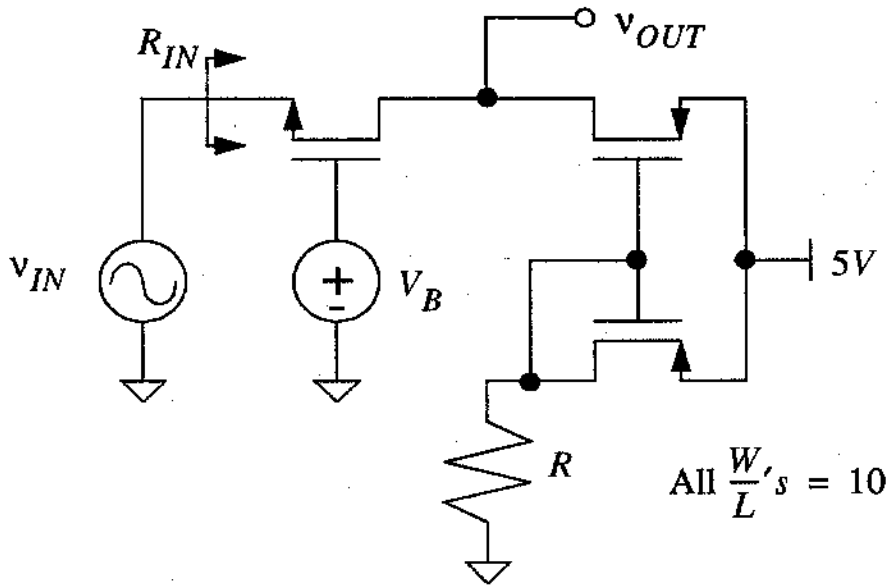

Assume  $R$  is chosen so that the currents are  $10 \mu\text{A}$  and  $V_B$  is chosen to set the DC voltage at  $v_{OUT} = 2.5 \text{ V}$

$$r_o = 10 \text{ M}\Omega$$

$$g_m = 141 \mu\text{A/V}$$

a) What is the gain  $v_{OUT}/v_{IN}$ ? 710

$$G_m = g_m$$


$$A_v = G_m R_{out} = 710$$

$$R_{out} = r_o \parallel r_o = 5 \text{ M}\Omega$$

b) What is  $R_{IN}$ ? 14.1 k $\Omega$

$$R_m = \frac{r_o + R_s}{1 + (1 + \beta) g_m r_o} = \frac{2r_o}{1 + g_m r_o} \approx \frac{2}{g_m} = 14.1 \text{ k}\Omega$$


4)

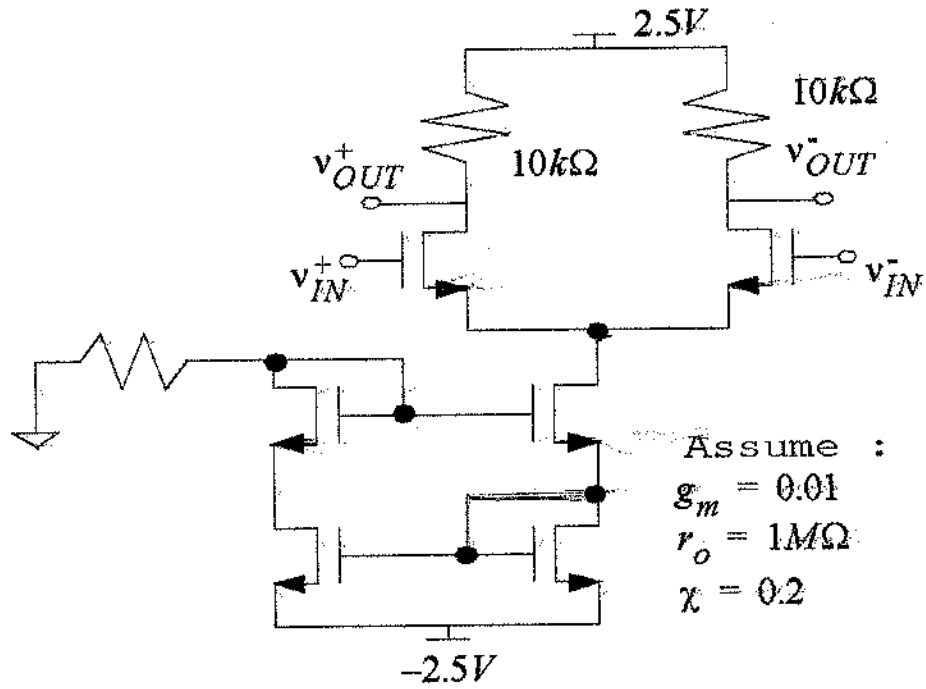

a)  $A_{cm} = \underline{-100}$

$$A_{dm} = -g_m R_{out} = -(0.01)(10k \parallel 1M\Omega) = -100$$

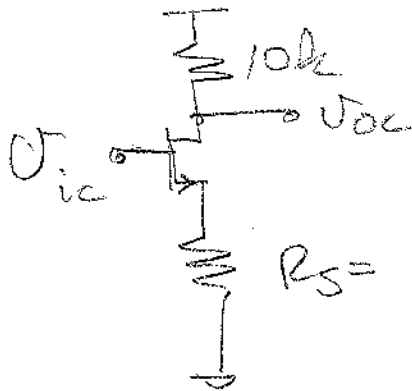b)  $A_{cm} = \underline{-4.2 \times 10^{-7}}$




$$G_m = \frac{-g_m}{1 + (1+\chi)g_m R_S} \approx \frac{.01}{(1.2)(0.01) \times 20 \times 10^9} = -4.2 \times 10^{-11}$$

$$R_S = 2(g_m r_o^2) = 20 \times 10^9 \Omega$$

↑  
 $R_{out}$  OF A WILSON SOURCE

$$A_{cm} = -G_m R_{out} = -(4.2 \times 10^{-11}) / (10^4) = -4.2 \times 10^{-7}$$


5)

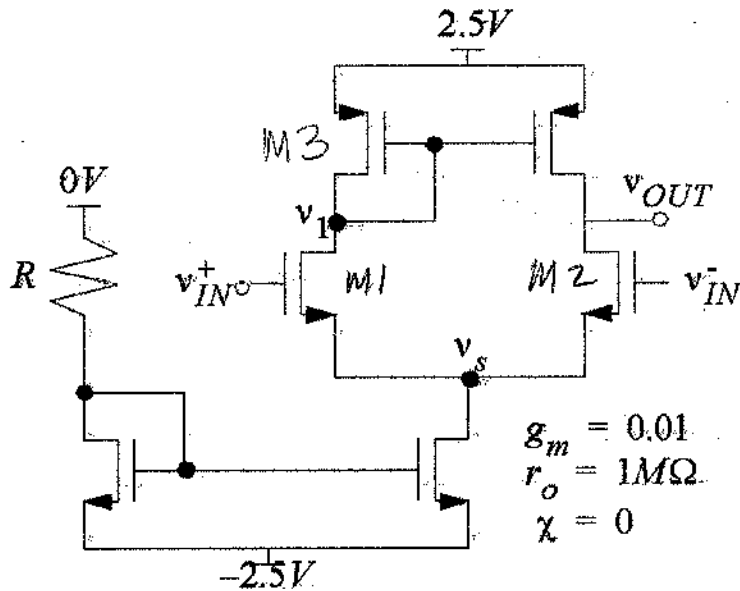

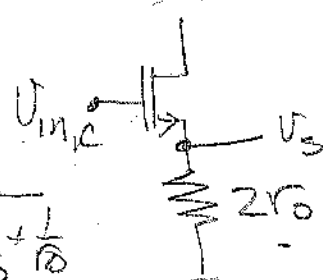a) If  $v_{IN}^+ = v_{IN}^- = v_{IN}$ , what is

$v_S/v_{IN}$ ? 1


$$\frac{v_S}{v_{in,c}} = \frac{g_m}{g_m(1+\lambda) + \frac{1}{R_s} + \frac{1}{r_o}} = \frac{.01}{.01 + \frac{1}{2r_o} + \frac{1}{r_o}} \approx 1$$



b) If  $v_{IN}^+ = 0V$  and  $v_{IN}^- = v_{IN}$ , what is

$v_S/v_{IN}$ ? .33

$$G_{m,out} = 0.33$$

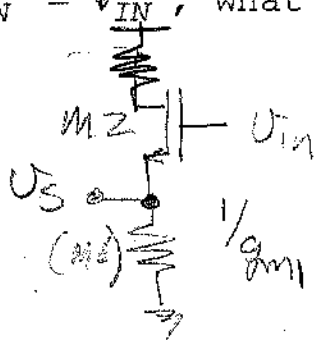

$$G_m = g_m$$


$$R_{out} = r_o \parallel \frac{1}{g_{m1}} \parallel \frac{2}{g_{m2}}$$


$$= \frac{.33}{g_m}$$

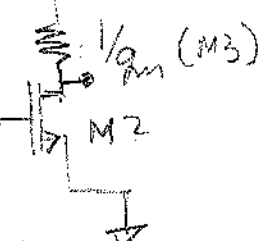c) If  $v_{IN}^+ = +v_{IN}/2$  and  $v_{IN}^- = -v_{IN}/2$ , what is

$v_1/v_{IN}$ ? -1

$$\frac{v_1}{v_{in}} = -g_{m1} R_{out} = -(0.01) \left( \frac{1}{0.01} \right) = -1$$



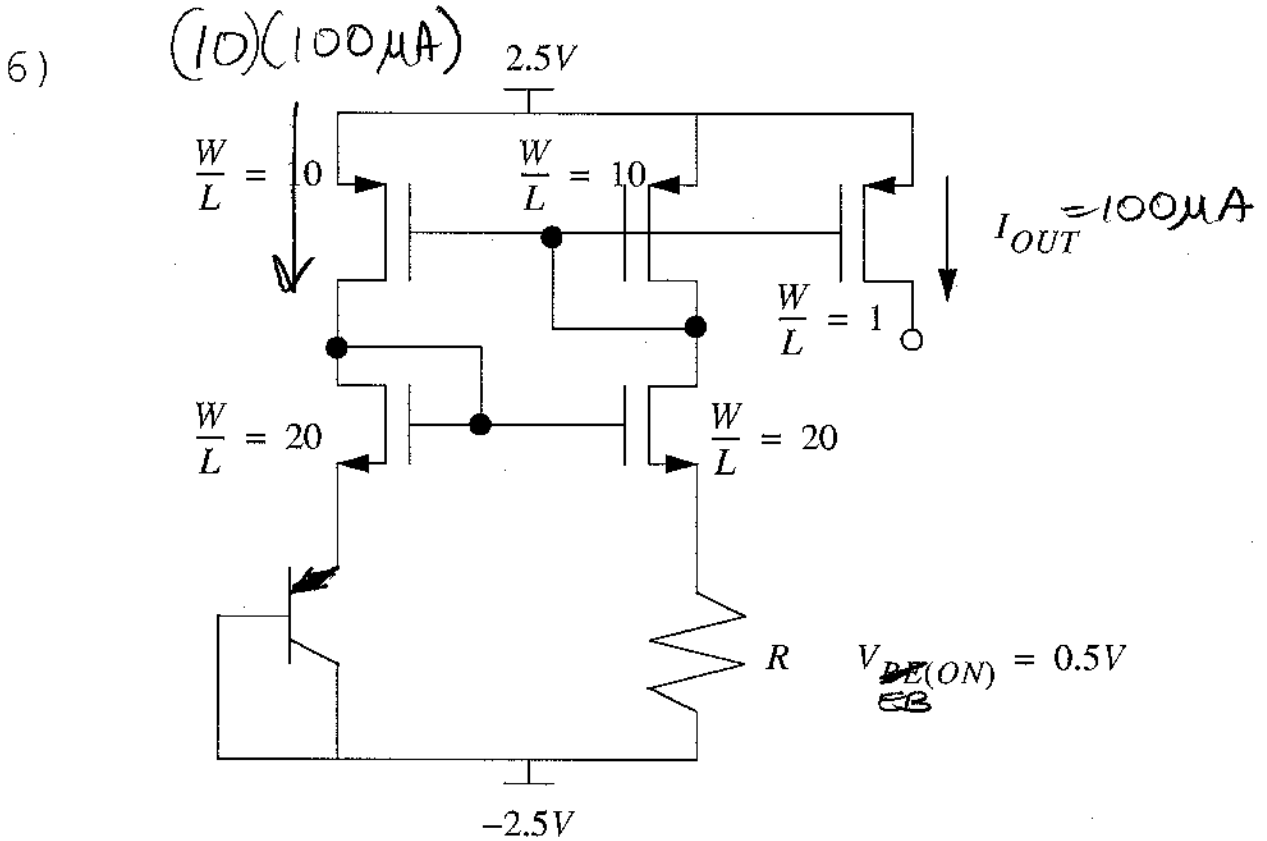

What is the value of  $R$  so that

$I_{OUT} = 100\mu A$ ?  $R$   $500\Omega$

$$R = \frac{V_{BE(ON)}}{(100\mu A)10} = \frac{.5}{.1 \times 10^{-4} \times 10} = 500\Omega$$




$$I_Q: -\frac{V_1}{R} = \frac{k'}{2} (V_1 - (-2.5) - V_T)^2$$

$$= \frac{k'}{2} (V_1 + 2)^2$$

$$V_1^2 + 24V_1 + 4 = 0 \quad V_1 = -17V$$

7)

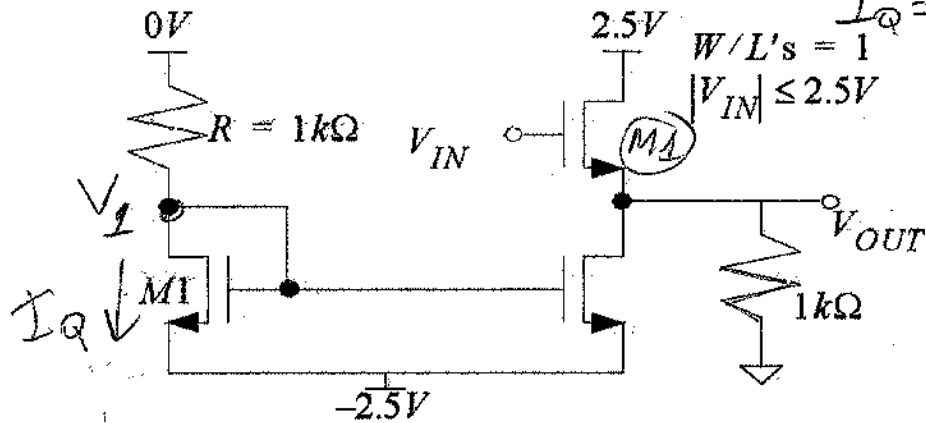

$$I_Q = 0.17 \text{ mA}$$

a) What is the most positive voltage that  $V_{OUT}$  can achieve? 0.027 Volts

$$V_{OUT,MAX} = V_{DD} - V_T - V_{DSAT,1} = 2 - \left[ \frac{2(I_Q + \frac{V_{OUT}}{1k})}{k'W/L} \right]^{1/2}$$

$$(2 - V_{OUT,MAX})^2 = \frac{2(I_Q + \frac{V_{OUT}}{1k})}{k'W/L}; \quad V_{OUT,MAX}^2 - 24V_{OUT,MAX} + 64 = 0$$

$$V_{OUT,MAX} = 0.027V$$

b) What is the most negative voltage that  $V_{OUT}$  can achieve? -0.17V

$$V_{OUT,MIN} = -I_Q R_L = -(0.17 \text{ mA}) (1k) = -0.17V$$

c) If R is chosen so the current through M1 is 0.1mA, what is the efficiency of this circuit? EFF = 0.47%  
(Assume the output must be centered around 0V)

$$(2 - V_{OUT,MIN})^2 = \frac{2(0.1 \times 10^{-3} + 10^{-3} V_{OUT})}{10^{-4}}$$

$$V_{OUT,MAX}^2 - 24V_{OUT,MAX} + 2 = 0$$

$$V_{OUT,MAX} = 0.084V$$

$$P_{SUPPLY} = 3(2.5)(0.1 \text{ mA}) = 0.75 \text{ mW}$$

$$P_{LOAD} = \frac{V_{OUT,MAX}^2}{2R_L} = \frac{(0.084)^2}{2 \times 10^3} = 3.5 \mu\text{W}$$