


EECS140 Midterm 2
Spring 2016

Prob.	Score
1	/10
2	/29
3	/16
4	/10
5	/15
Total	/80

Name _____

SID _____

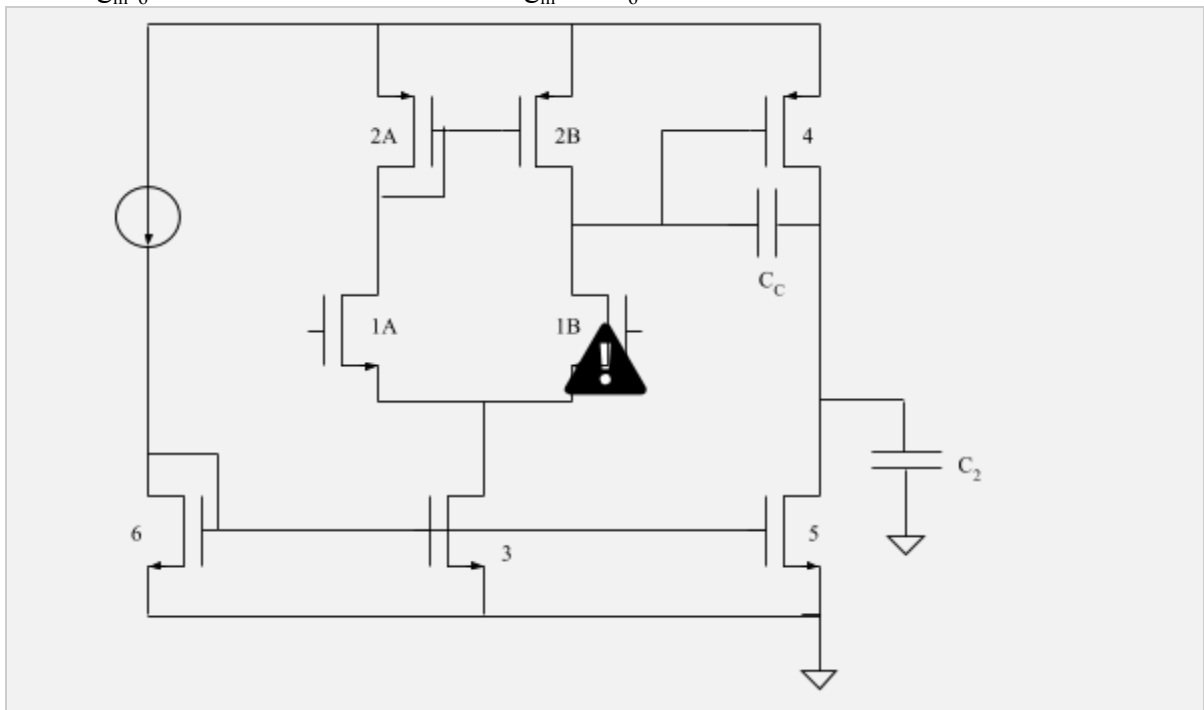1. For the op-amp below, assume that:
- All transistors are biased in saturation
 - All capacitors are assumed to be zero except C_C , C_2 , and C_{gs} for all transistors.
 - $g_m r_o \gg 1$ for all combinations of g_m and r_o



The same op-amp will be used in several different feedback circuits.

- a. [2] The spec requires that the output be able to swing to within 200mV of ground, and 150mV of the positive supply. List all constraints on overdrive voltages.

- b. [2] When used in feedback the closed-loop gain must be 5 +/- 1%. What is the constraint on the open-loop gain of the amplifier?
- c. [2] When used in feedback with a closed-loop gain of 5, the desired bandwidth is 200M rad/s. What is the constraint on the unity-gain bandwidth?
- d. The amplifier is also to be used in unity-gain feedback driving a 100pF load, and the desired open-loop phase margin is 70 degrees.
- i. [2] What is minimum possible value for g_{m4} ? (answer should be in Siemens)
- ii. [2] What are the constraints on g_{m1} and I_{tail} ? (in terms of other circuit values)

2. A particular design of the op-amp above has the following values for parameters. You may ignore the gain and phase associated with the current mirror for this problem.

G_{m1}	R_{o1}	G_{m2}	R_{o2}	C_2	C_C	C_{ps4}
1mS	1M	1mS	100k	100p	1p	0.1p


- a. [6] What are the low-frequency gains, and the locations of the uncompensated ($C_C=0$) poles, uncompensated second-stage unity gain frequency, and right-half-plane zero associated with C_c ?

$ A_{v1,0} $	$ A_{v2,0} $	ω_{p1}	ω_{p2}	ω_{u2}	$\omega_{z,RHP}$

On the following pages,


- b. [3] plot the magnitude of the second stage gain
- c. [6] plot the overall impedance seen at the first stage output,
- d. [2] plot the magnitude of the first stage gain,
- e. [6] plot the magnitude and phase of the overall gain. **Label any poles and zeros clearly.**
- f. [4] Estimate the unity-gain phase margin for this value of C_C . What value of feedback factor f gives a 45 degree phase margin?
- g. [2] Approximately what value of C_C is needed for a 45 degree phase margin if we can ignore $\omega_{z,RHP}$?

2B) Second stage gain – $|A_{v2,0}|$

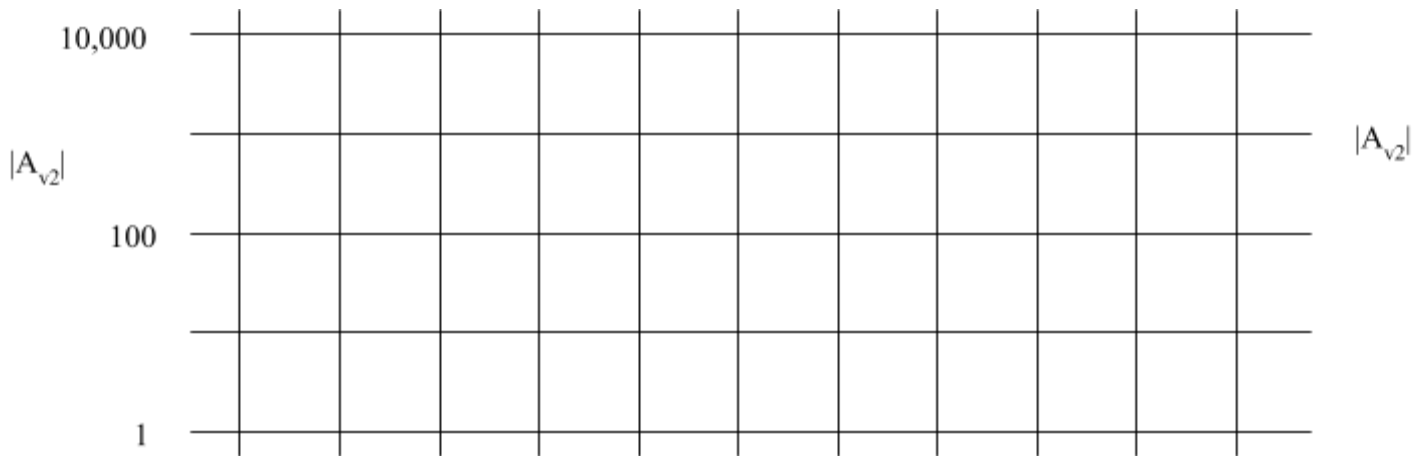


1 1k 1M 1G rad/s


2C) Impedance at first stage output, $|Z_{o1}|$

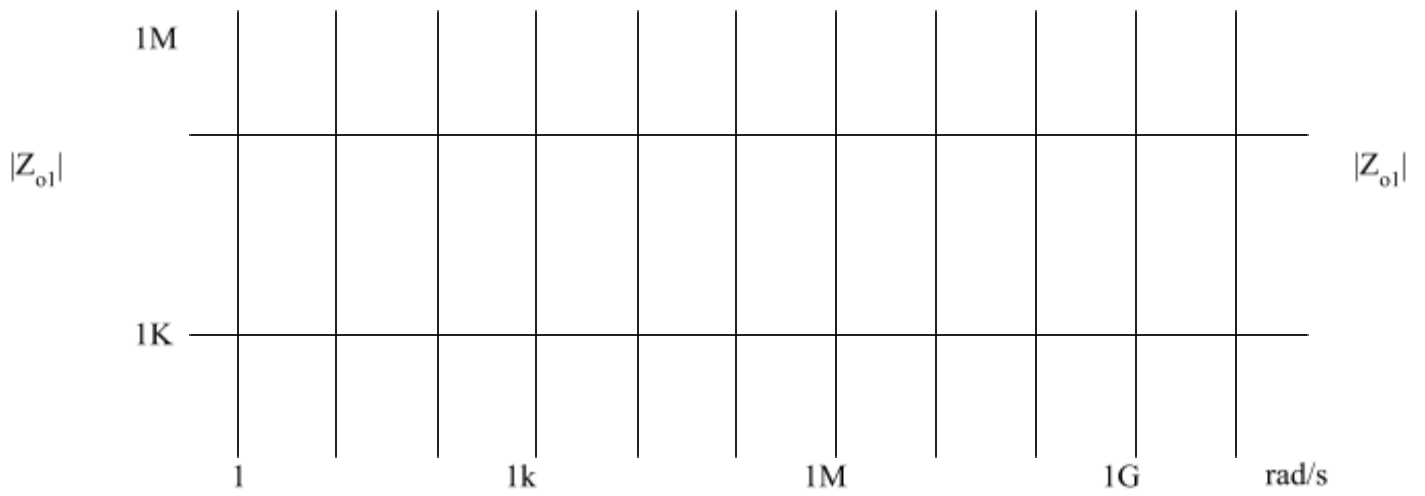


2D) First stage gain, $|A_{v1}|$

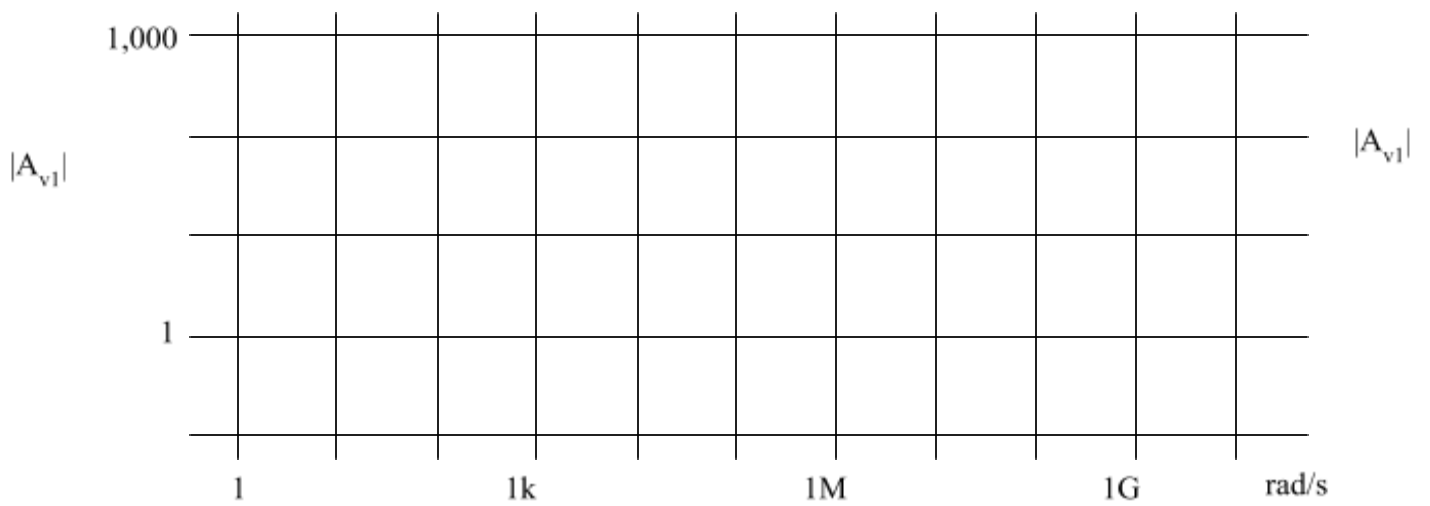

2E) op amp Bode plot

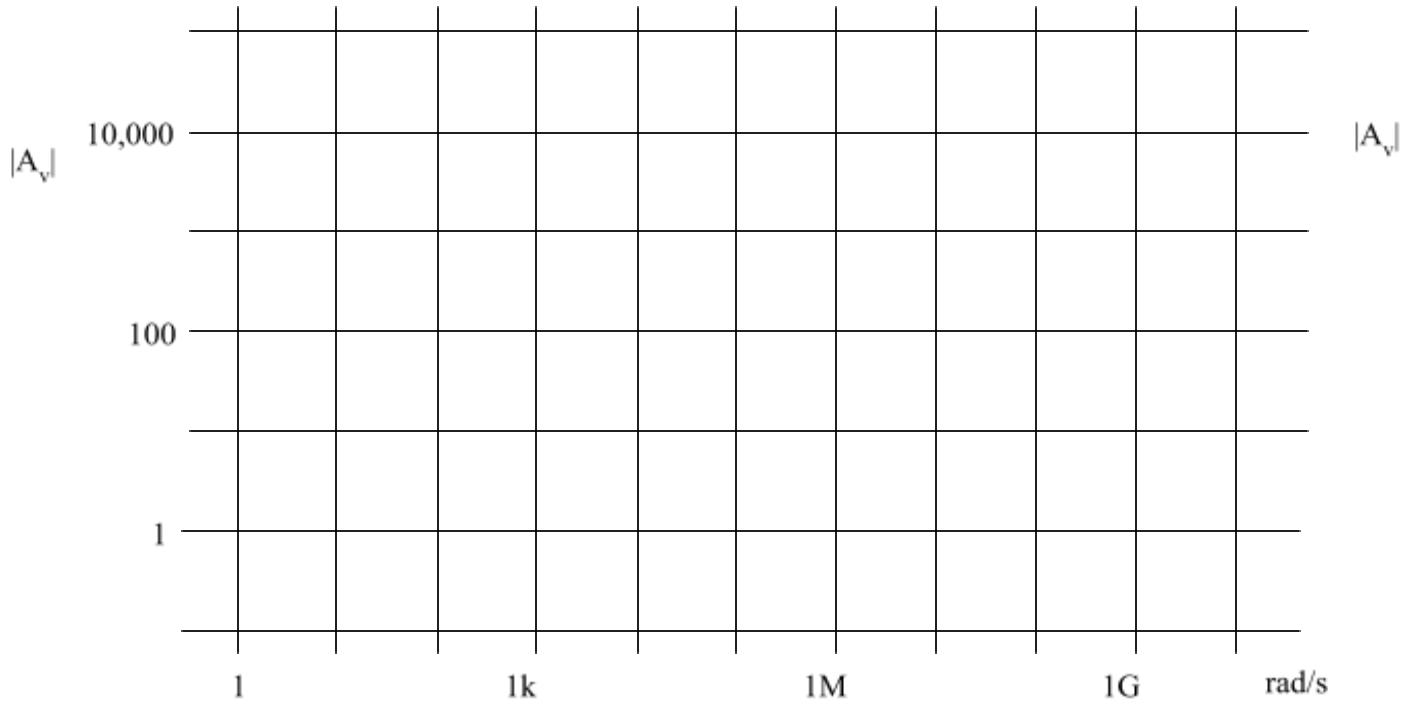


Label any poles and zeros clearly!

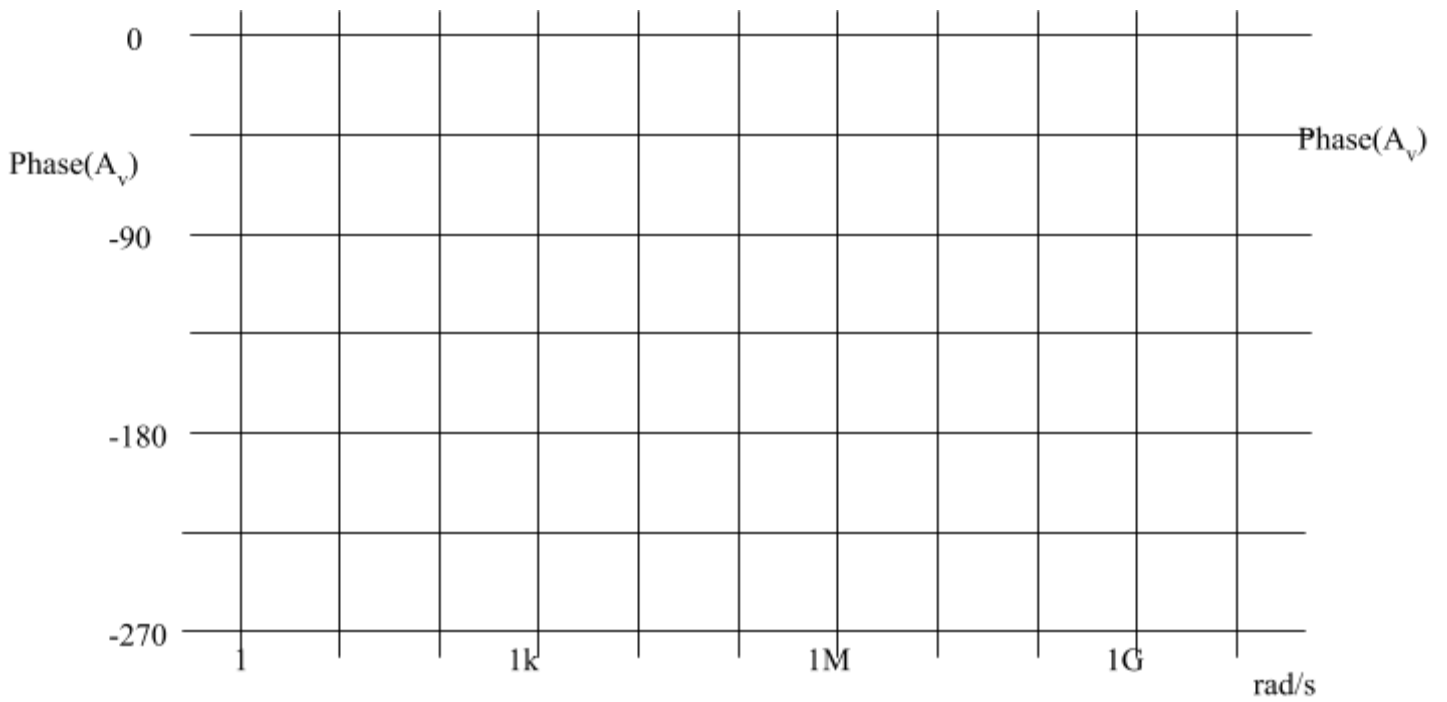

Don't forget RHP zero
Don't forget to answer 2f and 2g (phase margin questions)

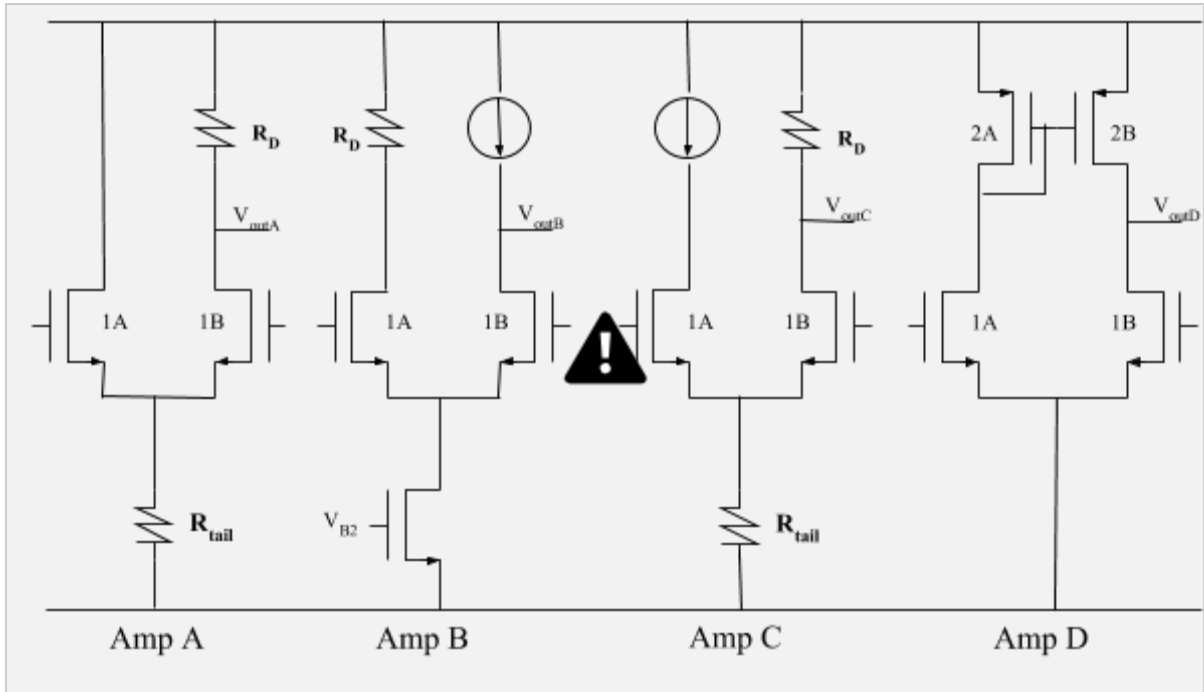3. [16] For the four differential amplifiers below, assume that $1/g_m \ll R \ll r_o$ for all configurations, and that current sources are ideal. Calculate the transconductance G_m and the output resistance R_o for each amplifier. Assume a **purely differential input**.




	G_m	R_o
Amp A		
Amp B		
Amp C		
Amp D		

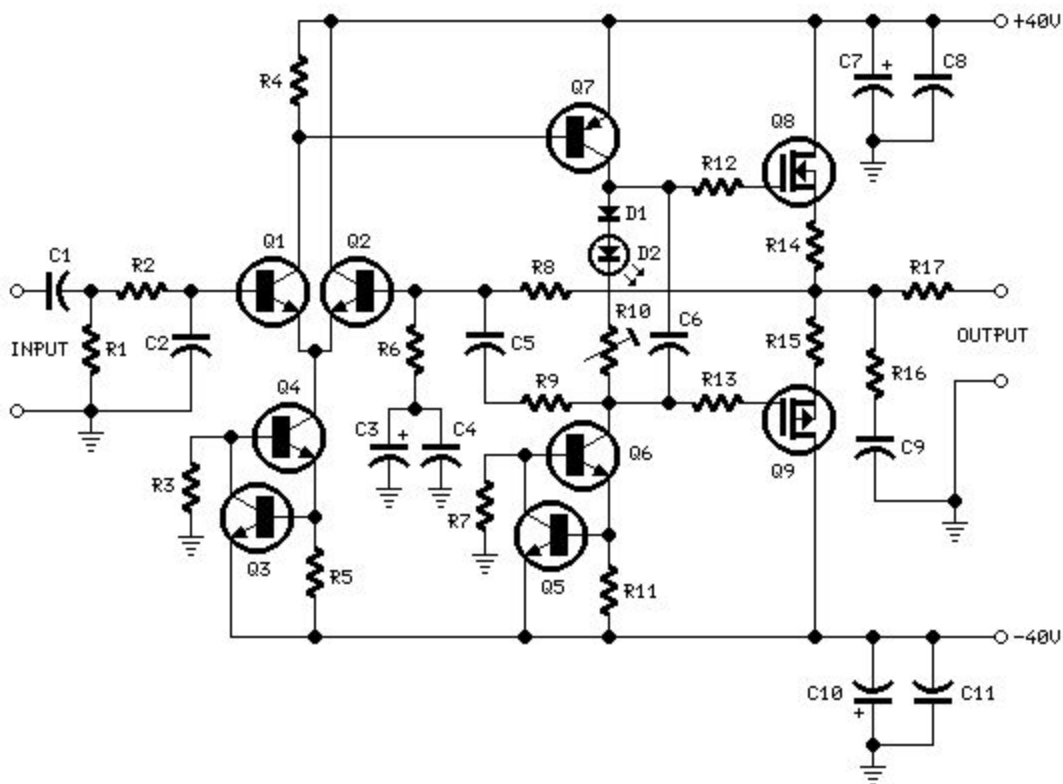- 4.

[10] The audio amplifier circuit below consists of a two-stage op-amp with an output stage. The op-amp is wired up in feedback.


- Which transistors make up the input differential pair?
- Estimate the tail current in terms of circuit parameters.
- Which transistors make up the second stage?
- Which capacitor provides Miller compensation?
- What component minimizes the effect of the right-half-plane zero associated with Miller compensation?
- What is the DC bias voltage on the base of Q1?
- What is the low-frequency feedback factor, f_{DC} ? (you may ignore finite BJT input impedance)
- What is the mid-frequency feedback factor, f_{audio} ?
- What RC time constant determines the transition from low-frequency to mid-frequency?



(source: eeweb.com/blog/circuit_projects)

5. For the amplifier in the figure to the right

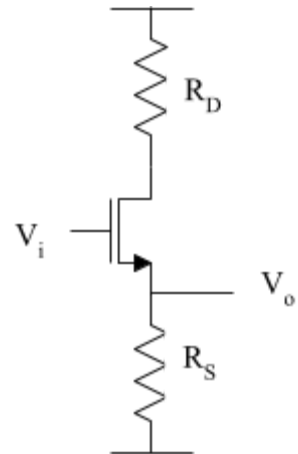a. [4] Draw the small signal model labeling the small signal variables v_i , v_o , i_o , v_d



b. [1] Write an expression for G_m as the ratio of two small signal parameters while a third is held equal to zero.

c. [1] Write v_d in terms of i_o

d. [4] Write KCL @ v_o and solve for G_m .

e. [3] Find the approximate value for G_m for each of three different values of R_D : much less than r_o , equal to r_o , and much greater than r_o .

f. [2] Write the full expression for R_o . (you don't need to derive it)