

Thursday, April 6, 1995

Name: ...

This exam has 3 problems with equal weights. Show how you arrived at each result to get credit. Please mark results clearly with a box around them. Write the answers directly on the exam sheets.

Device Parameters: (unless otherwise indicated)

NPN: $I_s = 5 \times 10^{-15} \text{A}$, $\beta = 100$, $V_A = 100 \text{V}$, $V_{BE(on)} \approx 0.7 \text{V}$, $V_{CE(sat)} = 0.2 \text{V}$,
 $C_{je0} = 1 \text{pF}$, $\tau_f = 0.3 \text{ns}$, $C_{\mu} = 0.5 \text{pF}$

PNP: $I_s = 2 \times 10^{-15} \text{A}$, $\beta = 50$, $V_A = 50 \text{V}$, $V_{BE(on)} \approx 0.7 \text{V}$, $V_{CE(sat)} = -0.2 \text{V}$,
 $C_{je0} = 0.5 \text{pF}$, $\tau_f = 20 \text{ns}$, $C_{\mu} = 0.5 \text{pF}$


NMOS: $\mu C_{ox} = 50 \mu\text{A}/\text{V}^2$, $V_{th0} = +0.7 \text{V}$, $\lambda = 0.02 \text{V}^{-1}$ @ $L = 4 \mu\text{m}$, $\gamma = 0.4 \sqrt{\text{V}}$, $2\phi = 0.6 \text{V}$

PMOS: $\mu C_{ox} = 25 \mu\text{A}/\text{V}^2$, $V_{th0} = -0.7 \text{V}$, $\lambda = 0.05 \text{V}^{-1}$ @ $L = 4 \mu\text{m}$, $\gamma = 0.6 \sqrt{\text{V}}$, $2\phi = 0.6 \text{V}$
 $V_T = 26 \text{mV}$ (300 K)

Problem #1

In the amplifier shown below a dc biasing circuit (no shown) makes that the large signal output voltage is $V_o = 1 \text{V}$. C_i is a large coupling capacitor. Assume that the circuit is compensated to ensure stability.

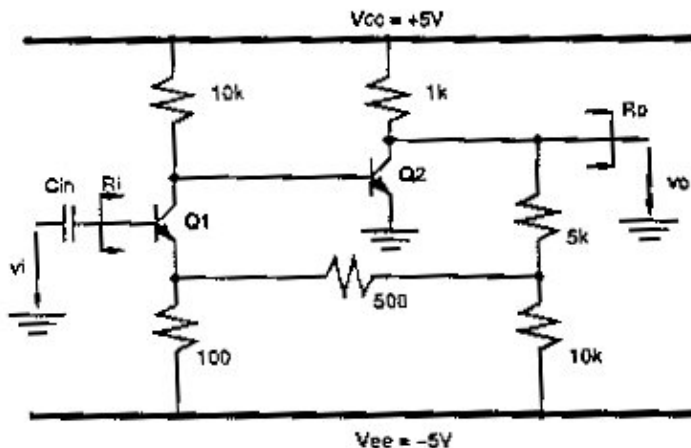- (a) what is the type of feedback used?
- (b) what is the feedback factor, f ?
- (c) what is the loop gain, T , at low frequency?
- (d) what is the low-frequency, small-signal voltage gain v_o/v_i of the circuit?
- (e) what is the low frequency input resistance, R_i ?
- (f) what is the low frequency output resistance, R_o ?




Problem #2

For the circuit below, find

- (a) the low-frequency transresistance $R_x = v_o/i_{sig}$, and
- (b) the bandwidth f_{-3db} (use zero valued time constants).

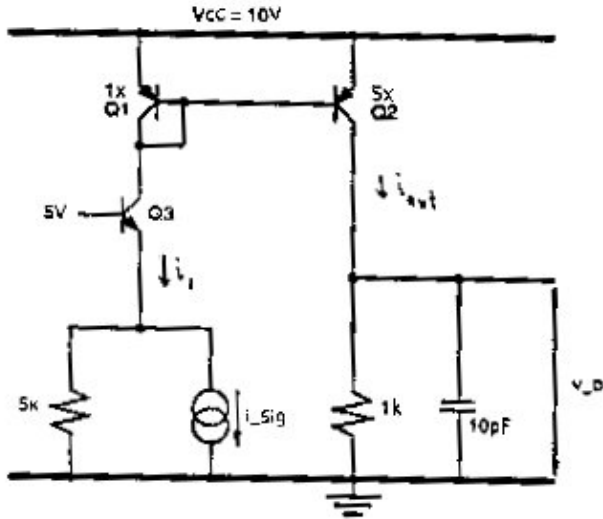
(c) write an expression for the frequency response $V_o(s)/I_{sig}(s)$ (polynomial in s). Include only the dominant pole and ignore zeroes.



Problem #3

In the amplifier below you may neglect base currents when determining dc conditions.

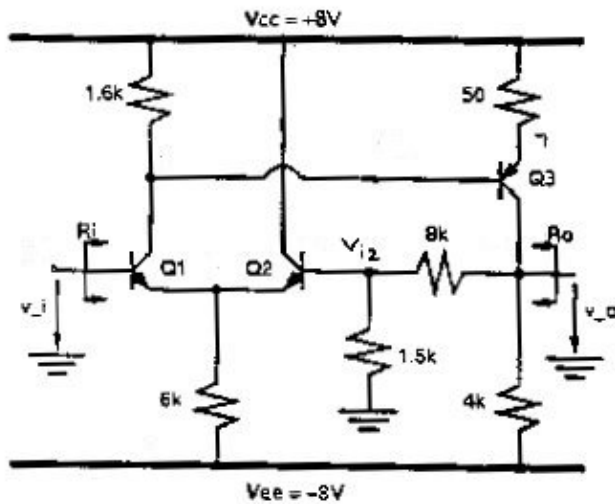- (a) What is the overall feedback used?
- (b) Find the low-frequency loop-gain T_o .
- (c) Determine the closed-loop voltage gain, v_o/v_i at low frequencies.
- (d) Determine the closed-loop input and output resistances R_i and R_o .



Posted by HKN (Electrical Engineering and Computer Science Honor Society)
University of California at Berkeley

If you have any questions about these online exams please contact examfile@hkn.eecs.berkeley.edu.