



University of California
 College of Engineering
 Department of Electrical Engineering
 and Computer Science

J. M. Rabaey

203 McLaughlin

MWF 10-11am

e141@zabriskie

EECS 141: FALL 95—MIDTERM 1

For all problems, you can assume the following transistor parameters:

NMOS:

$$V_{Tn} = 0.75V, k'_n = 20 \mu A/V^2, \lambda = 0, \gamma = 0.5 V^{1/2}, 2\Phi_F = -0.6V$$

PMOS:

$$V_{Tp} = -0.75V, k'_p = 7 \mu A/V^2, \lambda = 0, \gamma = 0.5 V^{1/2}, 2\Phi_F = -0.6V$$

For all problems, you may assume that the transistor lengths indicated are the effective lengths (L_{eff}) or, equivalently, that $LD = 0$.

NAME	<div style="display: flex; justify-content: space-between;"> Last First </div>
-------------	--

GRAD/UNDERGRAD	
-----------------------	--

Problem 1:

Problem 2:

Total	
--------------	--

PROBLEM 1: MOS Inverter

Consider the fictitious gate of Figure 1. The I-V characteristic of the load device L_1 is given in the Figure as well.

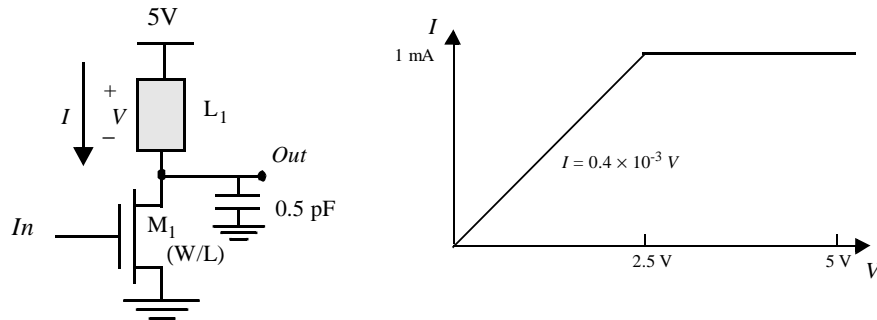


FIG. 1 MOS Inverter

- a. Determine $(W/L)_{M_1}$ such that a V_{OL} of 1V is obtained.

$W/L =$

- b. Write down the equation(s) you would use to solve for V_{IH} .

Eq. 1:
(Eq. 2:)

c. Find t_{pHL} .

$$t_{pHL} =$$

d. Determine the average static power consumption, assuming that the input is high 75% of the time.

$$P_{stat} =$$

f. Figure 2 shows the load-lines of two possible load devices. Determine which one is better (a or b) for each of the following gate properties and explain in ONE line why.

 


FIG. 2 Load lines of two load devices (a) and (b).

Property	(a) or (b)	Why
V_{OL}		
t_{pLH}		
t_{pHL}		
P_{stat}		

Problem 2: Combinational Logic

The gate below has the advantage of being simple and requiring the minimum number of transistors for the function intended.

 


FIG. 3 : Complex Gate

a. Derive the boolean expression for F . What logic function does this gate implement?

F =

Logic function:

b. Determine the **exact** output voltage for each of the following conditions (assume that the supply rails — and the logic levels at the inputs — are set at 0 V and 3.3 V):

$A = 0; X = 1, Y = 1$	$V_{out} =$
$A = 1; X = 1, Y = 1$	$V_{out} =$
$B = 0; X = 0, Y = 1$	$V_{out} =$
$B = 1; X = 0, Y = 1$	$V_{out} =$
$D = 0; X = 0, Y = 0$	$V_{out} =$
$D = 1; X = 0, Y = 0$	$V_{out} =$

c. Determine t_{pLH} and t_{pHL} between node B and the output for $X = 0$ and $Y = 1$. You may assume an equivalent resistance of $10\text{ k}\Omega$ for an NMOS transistor and $25\text{ k}\Omega$ for a PMOS. The capacitance at nodes m and n equals 100 fF , while node F is loaded with 300 fF .

$t_{pLH} =$

$t_{pHL} =$