

Name (Last, First) _____ Student ID number _____

UNIVERSITY OF CALIFORNIA

College of Engineering
Electrical Engineering and Computer Sciences Department

EECS 145M: Microcomputer Interfacing Laboratory

Spring Midterm #1 (Closed book- equation sheet provided- calculators OK)

Full credit can only be given if you show your work.

Monday, March 3, 2003

PROBLEM 1 (20 points)

Describe the characteristics of the following circuits

1a (10 points) The transparent latch

1b (10 points) The tri-state buffer

Name (Last, First) _____ Student ID number _____

PROBLEM 2 (25 points)

2a (10 points) Sketch the successive approximation analog to digital conversion circuit. Label each component and data line. (For example, a D/A would be drawn as a single labeled box with labeled I/O lines.) Use part 2b below to describe any complex operations.

2b Describe the operation of the successive approximation analog to digital converter. You may use words or a flow chart, provided that you describe its operation clearly.

Name (Last, First) _____ Student ID number _____

PROBLEM 3 (25 points)

How would you use electronic components, a computer with a digital I/O port, and statistical analysis to determine whether racecar drivers or jet fighter pilots have the faster reaction time? List all the steps that you need to accomplish to make a valid determination.

PROBLEM 4 (30 points)

Design a system for simultaneously digitizing (within a few ns) two different analog waveforms exactly once per second using two 12-bit A/D converters that are read with a *single* 16-bit digital input port. Assume:

- Your computer program determines when the two waveforms are digitized, waits for completion, and then stores each value.
 - Your program can read a 1 kHz timer using the command "time=get_tick_count"
 - You have two 12-bit A/D converters with “start conversion” and “data available” handshaking lines
 - Each A/D converter is started by making its “start conversion” line HIGH (5V)
 - When conversion is complete, each A/D converter makes its “data available” line HIGH
 - The A/D output data are valid until “start conversion” is brought LOW which makes the A/D converter bring “data available” LOW
 - The computer has a 16-bit digital output port that your program can write to using the command "put_single_value (dataout)"
 - The 16-bit digital input port can be read using the command "datain = get_single_value"
 - You may use any components discussed in the 145M course, but keep it simple
- 4a.** (15 points) Draw a block diagram of your system, showing and labeling all essential components, connections, and signals.

Name (Last, First) _____ Student ID number _____

- 4b.** (15 points) List the steps (hardware and software) to simultaneously digitize the two analog voltages, sequentially read them into computer memory, and repeat the entire process exactly once per second.