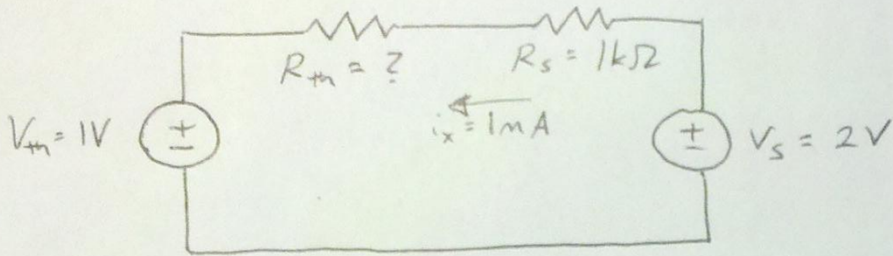


Problem 1

$$V_{th} = V_{oc} = 1V$$



$$\text{KVL} : 2 - (1mA)(1k\Omega) - (1mA)R_{th} - 1 = 0$$

$$2 - 1 - 1 - i_x R_{th} = 0 \rightarrow \therefore R_{th} = 0$$

$$V_{th} = 1V$$
$$R_{th} = 0\Omega$$

Problem 2

7 nodes + 2 unknown variables (v_x, v_y)
→ 9 equations total

① $V_x = V_4 - V_5$

② $V_y = V_7 - V_6$

KCL for rest!

③ Node 1: $\frac{V_1 - V_5 - V_7}{R_1} + \frac{V_1 - V_2}{R_2} + \frac{V_1 - V_3}{R_3} = 0$

④ SuperNode 2/4: $\frac{V_2 - V_1}{R_2} + \frac{V_2 - V_3}{R_4} + \frac{V_4 - V_3}{R_5} + \frac{V_4 - V_5}{R_6} = 0$

→ auxiliary eqn needed: ⑤ $V_2 - V_4 = \beta V_y$

⑥ Node 3: $\frac{V_3 - V_1}{R_3} + \frac{V_3 - V_2}{R_4} + \frac{V_3 - V_4}{R_5} - \alpha V_x = I_s$

⑦ Node 5: $-\frac{V_x}{R_6} + \alpha V_x + \frac{V_5 - V_6}{R_7} = 0$

⑧ Node 6: $\frac{V_6 - V_5}{R_7} + I_s - \frac{V_y}{R_8} = 0$


⑨ Node 7: $\frac{V_7 - V_6}{R_8} + \frac{V_5 - V_1}{R_1} = 0$

OK if you plugged in ground, but set of equations must be same if we set above equations with same ground.

OK if you plugged in ~~the~~ v_x, v_y , but only if you stated what v_x & v_y equal in terms of nodes.

Problem 3

supermesh
(2 aux. needed)

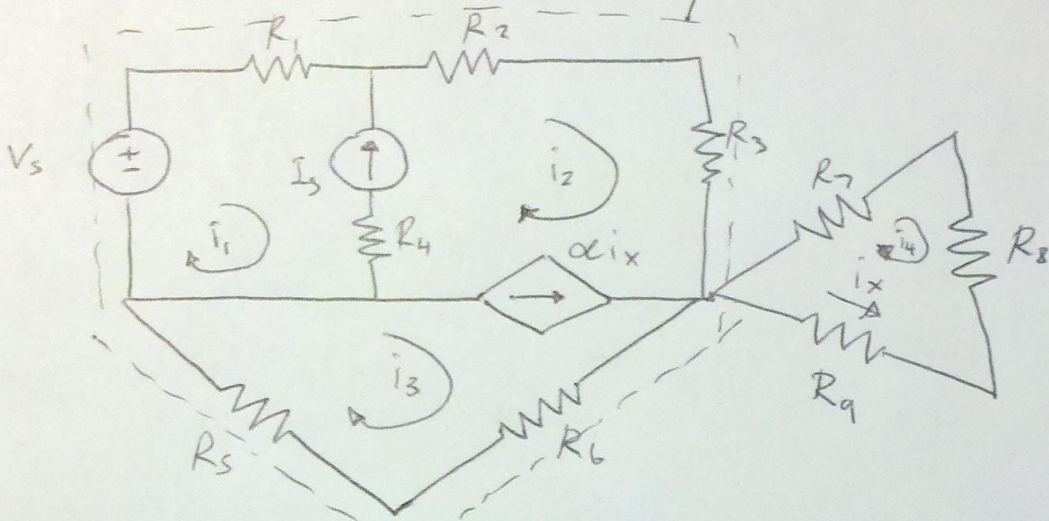

4 meshes & i_x \longrightarrow 5 equations to be complete.

① $i_4 = -i_x$ (Mesh 4)

② $i_x = 0$ since $-i_x (R_7 + R_8 + R_9) = 0$ (Mesh 4)

③ (supermesh 1/2/3)

$$-V_s + R_1 i_1 + R_2 i_2 + R_3 i_2 + R_6 i_3 + R_5 i_3 = 0$$

2 aux: $\alpha i_x = i_2 - i_3 \longrightarrow \therefore i_2 = i_3$ ④

Also, $I_3 = i_2 - i_1$ ⑤


Problem 4

(a) Voltage divides in parallel:


$$V_a = V_s / 2 \quad V_b = V_s \frac{R_s}{R + R_s}$$

$$V_{th} = V_{oc} = V_a - V_b \quad \therefore \boxed{V_{th} = V_s \left(\frac{1}{2} - \frac{R_s}{R + R_s} \right)}$$


Equivalent resistance:

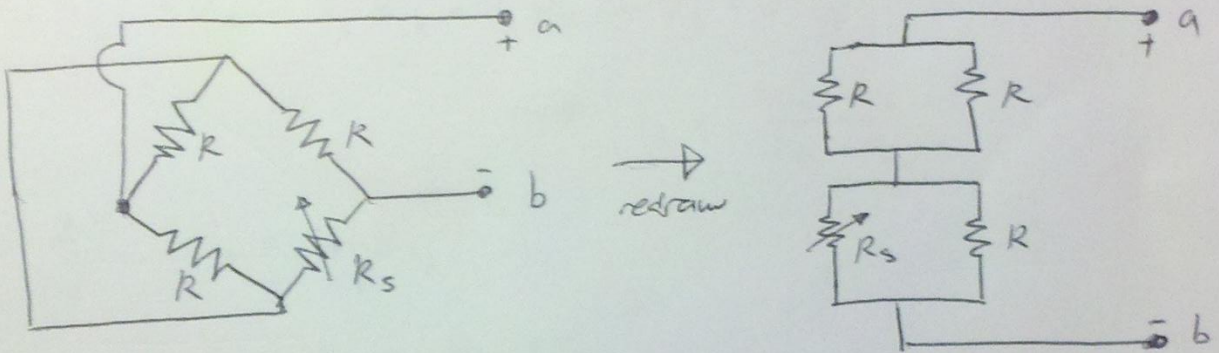
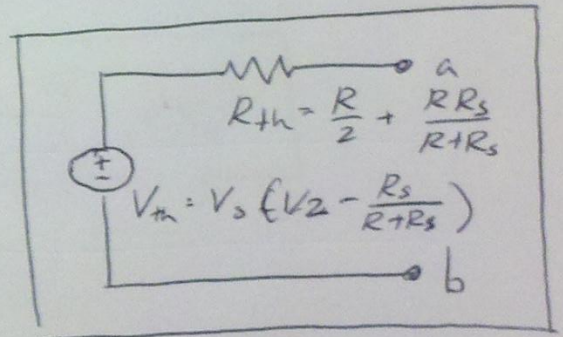
$$\therefore \boxed{R_{th} = \frac{R}{2} + \frac{R R_s}{R + R_s}}$$



(b)

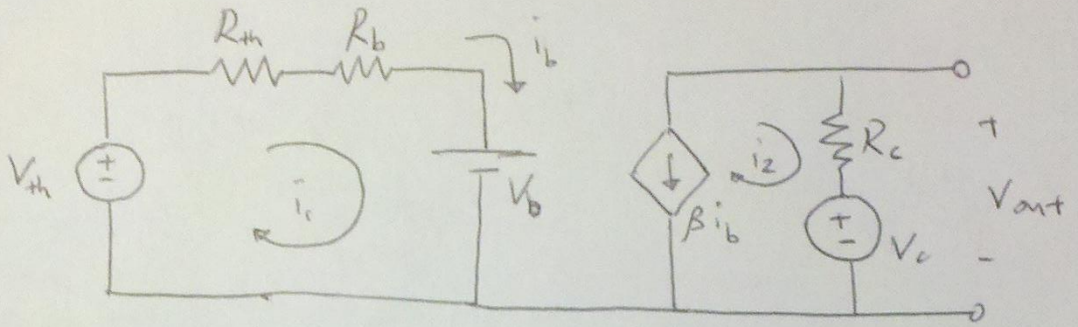

$$i_1 = i_b$$

$$\text{Mesh 1: } -V_{th} + i_b R_b + i_b R_{th} + V_b = 0$$

$$\rightarrow i_b = \frac{V_{th} - V_b}{R_{th} + R_b}$$

$$\text{Mesh 2: } i_2 = -\beta i_b$$

$$V_{out} = i_2 R_c + V_c$$

$$\therefore \boxed{V_{out} = -\beta R_c \frac{V_{th} - V_b}{R_{th} + R_b} + V_c}$$