

Department of Electrical Engineering and Computer Sciences
College of Engineering
University of California, Berkeley

SR Sanders

Spring 2002

EECS40 - Midterm #1
Feb. 26, 2002

Name: _____
Last, First

SID# _____

Signature: _____

TA:

Guidelines

1. Closed book, except 2 sheets of your own notes.
2. You may use a calculator.
3. Do not unstaple the exam.
4. Show all your work and reasoning on the exam to receive full or partial credit.
5. The exam has 4 problems.

Problem	Points possible	Your score
1	20	
2	20	
3	30	
4	30	
total		

1. Consider the Boolean expression:

$$F = (X + \bar{Y})(Y + Z)$$


(10) a) Write a truth table for this expression.

X	Y	Z	F
0	0	0	
0	0	1	
0	1	0	
0	1	1	
1	0	0	
1	0	1	
1	1	0	
1	1	1	

(10) b) Express F in sum of products form. Do not simplify.

(10) c) Draw a realization for your expression in (b) using NAND logic.

4.

 

The circuit shown here is at equilibrium with $v_c = 0$ at $t = 0$. At $t = 0$, switch A is moved as shown in the diagram. Then at time $t = 10 \mu\text{s}$, switch B is closed.

(6) a) For time $0 < t < 10 \mu\text{s}$, determine the circuit time constant.

(6) b) Determine an expression for the capacitor voltage for time $0 < t < 10 \mu\text{s}$.

(6) c) For time $t > 10 \mu\text{S}$, determine the circuit time constant.

(6) d) Determine an expression for the capacitor voltage $v_c(t)$ for $t > 10 \mu\text{S}$.

(6) e) Graph $v_c(t)$ for $t > 0$ on the axes below.

