

Professor Oldham

Fall 2000

EECS 40 — FINAL EXAM

Saturday, 16 December 2000, 8:00 - 11:00 a.m.

Name: _____
Last, First

Student ID: _____

Signature: SOLUTIONS

TA: Ben
 Warren
 Naratip

Guidelines:

1. Closed book and notes except 1 page of formulas.
2. You may use a calculator.
3. Do not unstaple the exam.
4. Show *all your work and reasoning on the exam* in order to receive full or partial credit.
5. **Caution:** NO CREDIT will be given for answers not in answer boxes.
6. This exam contains 8 problems and corresponding worksheets plus the cover page.


| Problem | Points Possible | Your Score |
|--------------|-----------------|------------|
| 1 | 12 | |
| 2 | 12 | |
| 3 | 12 | |
| 4 | 12 | |
| 5 | 14 | |
| 6 | 12 | |
| 7 | 12 | |
| 8 | 14 | |
| Total | 100 | |

$$\epsilon_0 = 8.85 \times 10^{-14} \text{ F/cm}$$

$$\begin{aligned} f &= 10^{-15} \\ p &= 10^{-12} \\ n &= 10^{-9} \\ \mu &= 10^{-6} \\ m &= 10^{-3} \\ K &= 10^3 \\ M &= 10^6 \end{aligned}$$

Problem 1 (12 points)

(a)

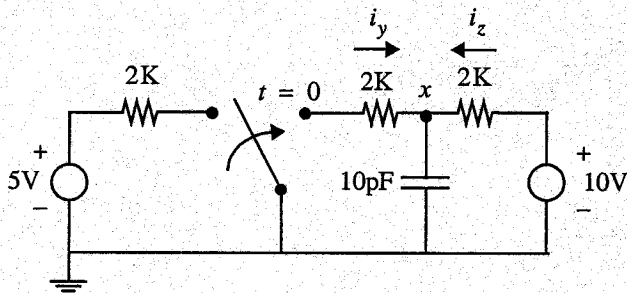

The switch closes at $t = 0$.

(a.1) What is V_x at $t = 0^+$?

a.1

$$V_x(t = 0^+) = 10V$$

(a.2) What is i_y at $t = 0^+$?

$$i_y(t=0^+) = \frac{0 - V_x(t=0^+)}{2k}$$

$$= \frac{-10}{2k} = -5mA$$

a.2

$$i_y(t = 0^+) = -5mA$$

(a.3) What is i_z at $t = 0^+$?

$$i_z(t=0^+) = \frac{10 - V_x(t=0^+)}{2k} = \frac{10 - 10}{2k}$$

$$= 0$$

a.3

$$i_z(t = 0^+) = 0mA$$

(a.4) What is $\frac{dV_x}{dt}$ at $t = 0^+$?

$$C \frac{dV_x}{dt} = i_y + i_z \Rightarrow \frac{dV_x}{dt} \Big|_{t=0^+} = \frac{-5 + 0}{10 \times 10^{-12} F} = -5mA$$

a.4

$$\frac{dV_x}{dt} \Big|_{t=0^+} = -5 \times 10^8 \left(\frac{V}{sec} \right)$$

(a.5) Draw very neatly the graph of V_x versus time on the axes provided opposite. (You MUST put scales on the axes to receive full credit.)


(a.6) Write an equation for $V_x(t)$.

a.6

$$V_x(t) = 5 + 5 \exp(-t/10^{-8})$$

Problem 1 (Cont.)


(a.5)

 

The * shows the
value of V_x at
 $t = \text{time constant}$
 $= 10 \text{ ns}$

Problem 2 (12 points)

(a)

 

| PMOS Device Parameters | |
|------------------------|-----------------------|
| $ V_T $ | $= 0.5V$ |
| $\frac{W}{L} _p$ | $= \frac{0.75}{0.25}$ |
| R_p | $= 3K$ |
| C_{Dp} | $= 1fF$ |
| C_{Gp} | $= 6fF$ |
| NMOS Device Parameters | |
| $ V_T $ | $= 0.5V$ |
| $\frac{W}{L} _n$ | $= \frac{0.75}{0.25}$ |
| R_n | $= 1.5K$ |
| C_{Dn} | $= 1fF$ |
| C_{Gn} | $= 6fF$ |

(a.1) Fill out the Truth Table. (Define logic "1" as $\sim V_{DD}$ and logic "0" as $\sim 0V$.)

a.1


| A | B | C | F |
|---|---|---|---|
| 0 | 0 | 0 | 1 |
| 0 | 0 | 1 | 1 |
| 0 | 1 | 0 | 1 |
| 0 | 1 | 1 | 1 |
| 1 | 0 | 0 | 1 |
| 1 | 0 | 1 | 1 |
| 1 | 1 | 0 | 1 |
| 1 | 1 | 1 | 0 |

(a.2) What is the logic function (F in terms of A, B, C)?

a.2

$$F = \overline{A \cdot B \cdot C}$$

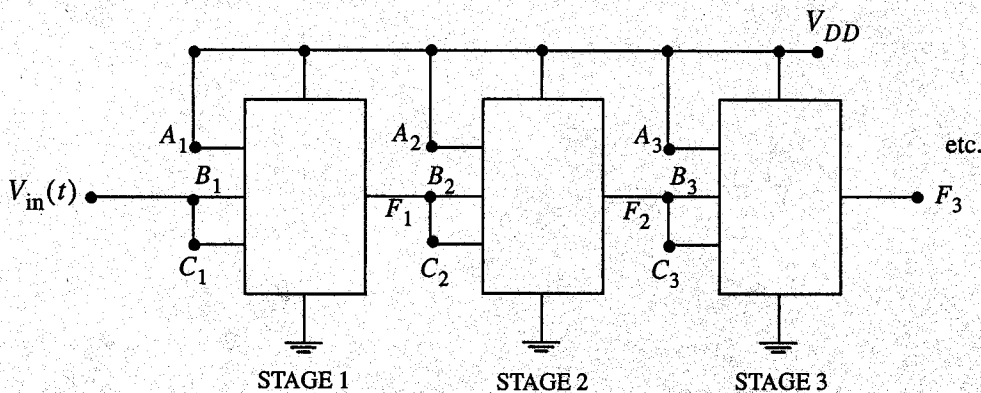(b) A number of these gates are hooked up as follows:



Problem 2 (Cont.)

(b.1) If $V_{in}(t)$ is initially zero and suddenly jumps to V_{DD} , can you write an expression for the stage delay τ_{DHL} , i.e., the time it takes F_1 to go from V_{DD} to $V_{DD}/2$ (in terms of device parameters $R_n, R_p, C_{Dn}, C_{Dp}, C_{Gn}, C_{Gp}$)? **Note:** Ignore wiring capacitance and do not evaluate numerically.

b.1

$$\tau_{DHL} = 0.69 \cdot R \cdot C \quad \text{where}$$

$$R = 3R_n \quad \text{and}$$

$$C = 3C_{Dp} + C_{Dn} + 2C_{Gp} + 2C_{Gn}$$

(formulas only)

(b.2) In the same circuit above $V_{in}(t)$ is a square wave going from 0 to V_{DD} to 0, etc. We are interested in worst case delay. Which transient is slower: τ_{DHL} or τ_{DLH} ? Answer the question by checking one of the three boxes.

b.2

$\tau_{DLH} > \tau_{DHL}$

$\tau_{DLH} < \tau_{DHL}$

$\tau_{DLH} = \tau_{DHL}$


(b.3) Why? (Explain answer to b.2.)

b.3

$$3R_n > R_p$$

Problem 3 – Circuit Analysis (12 points)

(3 marks)
(a)

 


Find V_B in terms of V_1, I_1, R_1, R_2 .

$$I_1 = \frac{V_A}{R_1} + \frac{V_B}{R_2}$$

$$V_A = V_1 + V_B$$

$$V_B = \frac{(I_1 R_1 - V_1) R_2}{R_1 + R_2}$$

(3 marks)
(b)

 


$$V_x = I_2 R_C$$

Check "Yes" or "No" for each item in the following table:

| | Yes | No |
|--------------------------|-----|----|
| V_x depends on V_1 ? | | x |
| " R_1 ? | | x |
| " R_2 ? | | x |
| " R_A ? | | x |
| " R_B ? | | x |
| " R_C ? | ✓ | |

(2 marks)
(c)

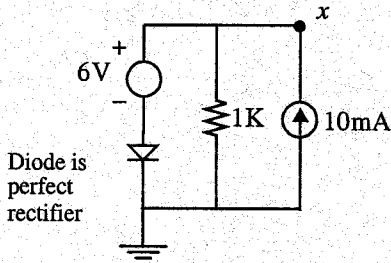


Diode is perfect rectifier

Find V_x .

Since diode is a perfect rectifier, no voltage drop can exist across it.

$$V_x = 6V \quad (V)$$

(2 marks)
(d)

 


Find V_y .

Apply KVL on the outermost loop.

$$V_y = -5V \quad (V)$$

(2 marks)
(e)

 

Find V_o in terms of V_{in}, R_1, R_2 .


$$V_{in} = V_a + 5V_a = 6V_a$$

$$V_o = 5V_a$$

$$V_o = \frac{5}{6} V_{in}$$

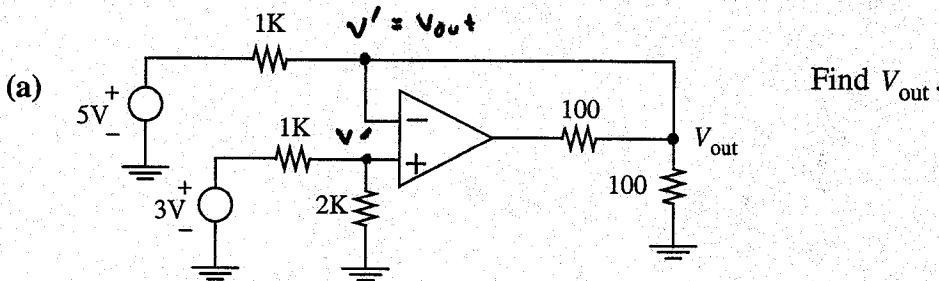Problem 4 – Op-Amp Circuits (12 points)

Note: Assume that all op-amps are ideal except that they have rails of $\pm 5V$.




Find V_{out} .

$V_{out} = 2 \text{ (V)}$

$V' = \frac{(3V)(2K)}{1K + 2K} = 2V$ (Voltage divider)

$V' = V_{out} = 2V$

 



Fill out the table:

| V_A | V_B | V_C (V) | V_{out} (V) |
|-------|-------|-----------|---------------|
| 0 | 0 | 0 | 0 |
| 0 | 0 | 2 | 0.5 |
| 0 | 2 | 0 | 1.0 |
| 0 | 2 | 2 | 1.5 |
| 2 | 0 | 0 | 2.0 |
| 2 | 0 | 2 | 2.5 |
| 2 | 2 | 0 | 3.0 |
| 2 | 2 | 2 | 3.5 |



$$V' = -\left(\frac{V_A}{1K} + \frac{V_B}{2K} + \frac{V_C}{4K}\right)(1K) = -V_A - \frac{1}{2}V_B - \frac{1}{4}V_C$$

$$V_{out} = -V' = V_A + \frac{1}{2}V_B + \frac{1}{4}V_C$$

 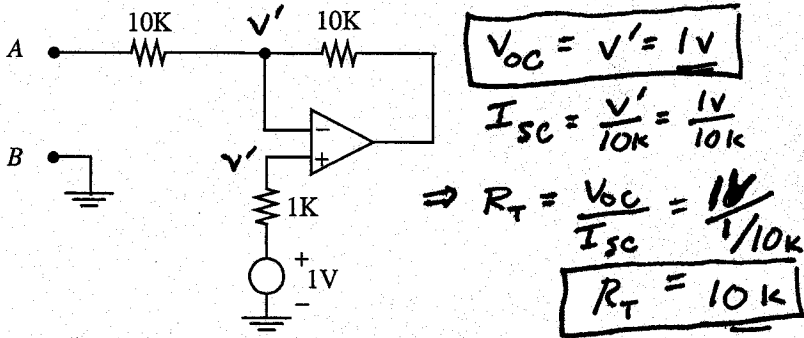(c) Find and sketch the Thévenin Equivalent of this op-amp circuit (from terminals A-B).



 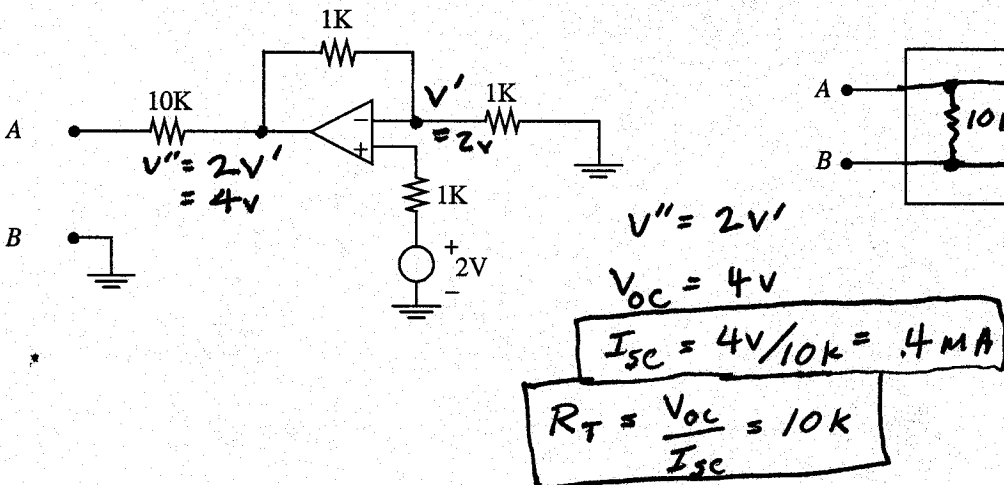(d) Find and sketch the Norton Equivalent of this op-amp circuit (from terminals A-B).



Problem 5 (14 points)

A CMOS process is listed below:

- (1) Start with p-type wafer.
- (2) Deposit $0.5\mu\text{m}$ oxide. Note: This and all oxides have relative dielectric constant of 3.9. (ϵ_0 is on cover page.)
- (3) Pattern with well mask. (LIGHT GRAY, DARK FIELD)
- (4) Implant n well and drive to $1\mu\text{m}$ depth.
- (5) Remove all oxide and deposit $0.5\mu\text{m}$ oxide.
- (6) Pattern with active area mask. (BLACK RECTANGLE, DARK FIELD)
- (7) Grow 10nm gate oxide.
- (8) Deposit $0.5\mu\text{m}$ polysilicon.
- (9) Pattern polysilicon (gates). (DARKER GRAY, CLEAR FIELD)
- (10) Apply resist and pattern with select mask. (NOT SHOWN)
- (11) Implant p-type source drains and anneal to get $0.1\mu\text{m}$ junction depth.
- (12) Apply resist and pattern with second select mask. (NOT SHOWN)
- (13) Implant n-type source drains and anneal to get $0.5\mu\text{m}$ junction depths for both p-type and n-type source drains.
- (14) Deposit $0.5\mu\text{m}$ oxide.
- (15) Pattern for contacts. (LIGHTER SQUARES IN ACTIVE AREA, DARK FIELD)
- (16) Deposit $1\mu\text{m}$ Al metal.
- (17) Pattern metal. (DOTS, CLEAR FIELD)

We do not show the layout for the entire circuit, but just one PMOS device on page opposite.

- (a) Draw a sketch on the axes provided (on the facing page) of the cross-section through the device along the line A-A (after step 17). Note: The sketch must be to scale and neat to receive full credit.



- (b) What is the gate capacitance in fF of this device? (Put answer in box provided on facing page.)

$$C_G = \frac{\epsilon_r \epsilon_0}{t_{ox}} \cdot W \cdot L = \frac{3.9 \cdot 8.85 \times 10^{-14}}{10^{-6}} \cdot 1 \times 10^{-4} \cdot 0.5 \times 10^{-4} = 3.4 \times 10^{-15} \text{ F}$$

- (c) What is the metal to substrate capacitance per unit area ($\text{fF}/(\mu\text{m})^2$)? (Put answer in box provided on facing page.)

$$C_{MA} = \frac{\epsilon_r \epsilon_0}{t_{field}} = \frac{3.9 \cdot 8.85 \times 10^{-14}}{1 \times 10^{-4}} = \frac{0.034 \times 10^{-15} \text{ F/cm}^2}{10^{-8}} = 0.034 \times 10^{-15} \text{ F/cm}^2$$

Problem 5 Answer Sheet

  


(b) $C_{Gp} = 3.4 \text{ fF}$


(c) $C_{MA} = 0.034 \text{ fF}/\mu\text{m}^2$


NOTE - 0.5 μm JUNCTION DEPTH IS TOO DEEP! THEY WILL SHORT UNDER GATE

Problem 6 (12 points)


Find the Thévenin equivalent circuits of the following. (You must draw solution in box provided.)

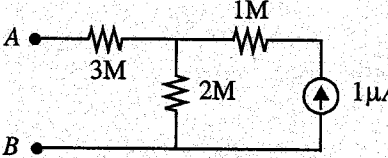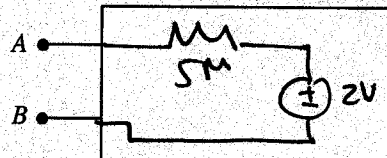
a)  $R_{TH} = 3M + 2M = 5M$
 $V_{TH} = (2M)(\mu A) = 2V$



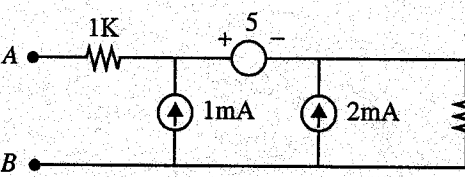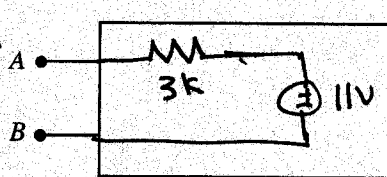
b)  (Hint: Use Superposition)


$R_{TH} = 1k + 2k = 3k$
 V_{TH} by Superposition
 $1mA \rightarrow 2V$
 $2mA \rightarrow 4V$
 $5V \rightarrow 5V$
 $V_{TH} = 11V$



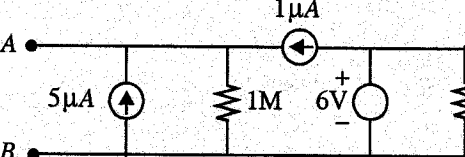
c) 


$R_{TH} = 1M$
 $V_{TH} = (5+1)(1) = 6$

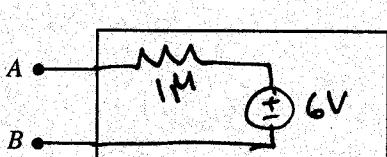

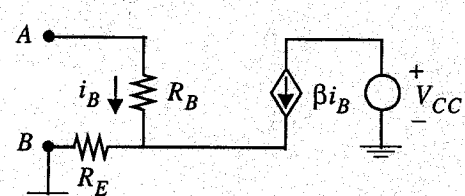
d) 

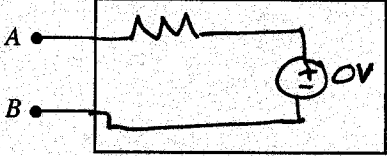$\frac{V_{TH}}{i_b=0} \Rightarrow V_{AB}=0$
 R_{TH}
 Use 1V test
 $R_{TH} = 1/I_B$
 $I_B = \frac{1 - (\beta+1)I_B R_E}{R_B + (\beta+1)R_E}$



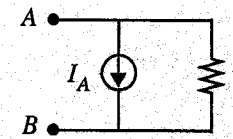e) 

$R_{TH} = R_A$
 $V_{TH} = -I_A R_A$

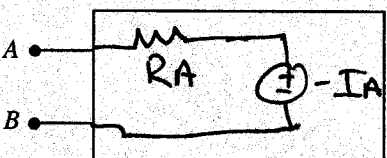


Problem 7 – Power and Energy (12 points)

 (a) The switch closes at $t = 0$. Then we wait a long time. Find the energy:

- (a.1) delivered by the power supply.
- (a.2) dissipated in the resistor.
- (a.3) delivered to the capacitor.

(Answers must appear in answer boxes and must have units.)



$$CV^2 = 0.1 \text{ mJ}$$


a.1 0.1 units mJ

$$\frac{1}{2} CV^2 = 0.05 \text{ mJ}$$

a.2 0.05 units mJ

$$\frac{1}{2} CV^2 = 0.05 \text{ mJ}$$

a.3 0.05 units mJ

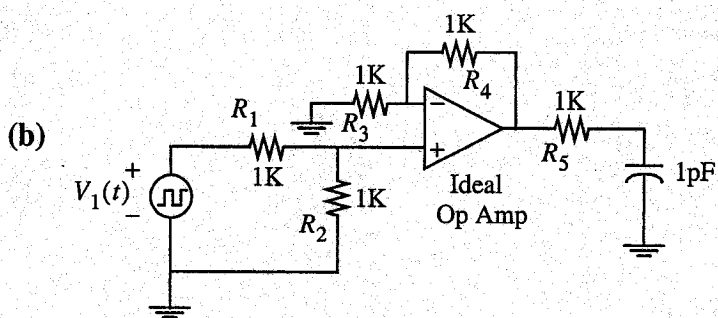

$V_1(t)$ is a square wave switching every $1 \mu\text{sec}$. It is going from $+2\text{V}$ to 0V , back to $+2\text{V}$, etc. (Period is $2 \mu\text{sec}$.)

(b.1) What is the average power delivered by V_1 in mW?

$$P_{\text{av}} = \frac{1}{2} \frac{V^2}{(R_1 + R_2)} = \frac{1}{2} \frac{(2)^2}{2\text{K}} = 1 \text{ mW}$$

b.1 $P = \underline{1} \text{ mW}$

(b.2) What is the average power dissipated in each of the resistors R_1 to R_5 ?

R_1, R_2, R_3, R_4 have same voltage drops.

$$P_{R1-R4} = \frac{1}{2} \frac{V^2}{R} = \frac{1}{2} \frac{(1)^2}{1\text{K}} = 0.5 \text{ mW}$$

op amp output voltage is a square wave 0 to 2V

$$P_{R5} = \frac{1}{2} CV^2 f = \frac{1}{2} (1\text{p})(2)^2 (10^6) = 2 \mu\text{W}$$

b.2

$P_{R1} = \underline{0.5} \text{ mW}$

$P_{R2} = \underline{0.5} \text{ mW}$

$P_{R3} = \underline{0.5} \text{ mW}$

$P_{R4} = \underline{0.5} \text{ mW}$

$P_{R5} = \underline{0.002} \text{ mW}$

(b.3) What is the average power dissipated in the capacitor? $= 2 \mu\text{W}$

Capacitor does not dissipate any (average) power.

b.3 $P = \underline{0} \text{ mW}$

(b.4) Where does the energy dissipated in R_3 come from?

b.4

op amp power supply ?

Problem 8 – Drain I-V (14 points)

The drain I-V characteristics of one of the Berkeley world record-setting PMOS "FinFet" devices are given opposite. The device has a channel length of only 40 nm. This device has a width of $1\mu\text{m}$ and a gate oxide thickness of 2 nm. If we assume a (-0.25V) threshold, we note that in saturation it seems to obey our model equation:

$$I_D = I_{DS}(1 + \lambda|V_{DS}|)$$

where

$$I_{DS} = k_V \frac{W}{L} (V_{GS} - V_T). \quad (\text{Note: } V_{GS}, V_{DS}, I_D, I_{DS}, V_T \text{ are all negative for PMOS.})$$

We intend to use this device in a circuit with logic values corresponding to $\sim 0\text{V}$ and $\sim 1\text{V}$, using, of course, a 1V power supply.


(a) Device parameters: a.1) What is k_V for this device (20% accuracy)?

$$k_V = \underline{16} \text{ units } \underline{\mu\text{A/V}}$$

a.2) What is λ (20% accuracy)?


$$\lambda = \underline{0.1} \text{ units } \underline{\text{V}^{-1}}$$

 (b) Basic inverter: In the absence of an NMOS device we can still make an inverter with a resistor and power supply. Suppose we hook up the device as follows:



(b.1) For this inverter you are to estimate the output voltage at several values of input voltage; in particular, fill out the table opposite. An accuracy of .05 V is adequate.

 In order to estimate the performance of this CMOS inverter, we consider a chain of identical inverters. Stage 1 and 2 are shown at the right. Suppose the input to stage 1 is low ($\sim 0\text{V}$).



(b.2) The Berkeley designers believe that for this inverter a sensible logic "0" range might be $0 < V < 0.25\text{V}$. What might be a sensible voltage range to define as "1"?

b.2

$$\underline{0.75 < V < 1}$$

(b.3) Now we want to consider the transient. If we ignore interconnect and drain capacitances, what is the capacitance loading the output node of stage 1? Give both a formula in terms of the circuit capacitances and evaluate for the numerical value.


b.3

$$C = \frac{2\epsilon t}{F} \cdot W \cdot L \quad (\text{formula})$$

$$C = \underline{0.69} \quad (\text{fF}) \quad (\text{numerical value})$$

(b.4) The input to stage 1 is suddenly switched from 0V to 1V. We expect the output of stage 1 to go from high to low. You have already computed the capacitance in question (b.3); now compute the resistance governing this transient. And compute the time for the output to reach 0.25V (formula and value). PLEASE NOTE ANSWER BOXES OPPOSITE.

Problem 8 (Cont.)

 

(b.1)

| V_{in} | V_{GS} | V_{out} |
|----------|----------|-----------|
| 0 | 1 | 0.75 |
| 0.25 | 0.75 | 0.6 |
| 0.5 | 0.5 | 0.35 |
| 0.75 | 0.25 | 0 |
| 1.0 | 0 | 0 |

(b.4)

$R = \underline{\quad 3K \quad} \text{ ohms}$

$\Delta t = \underline{\quad -RC \ln \frac{V_{OL}}{V_{OH}} \quad} \text{ (formula)}$

$\Delta t = \underline{\quad 2.8 \times 10^{-12} \quad} \text{ (sec)}$