

Professor Oldham

Spring 2001

**EECS 42 — MIDTERM #2**

5 April 2001

**Name:** \_\_\_\_\_  
Last, First

**Student ID:** \_\_\_\_\_

**Signature:** \_\_\_\_\_





**Guidelines:**

1. Closed book. A 3-page summary with formulas is provided at the end of the exam.
2. Show *all your work and reasoning on the exam* in order to receive credit.
3. **Warning:** Some problems will be graded with no partial credit, so check your answers.
4. You may use a calculator.
5. Do not unstaple the exam.
6. This exam contains 5 problems worth 20 points each, and corresponding worksheets plus the cover page and the 3-page summary with formulas.
7. **Please do not ask questions** except to point out possible errors or typographical mistakes.

<b>Problem</b>	<b>Points Possible</b>	<b>Your Score</b>
1	20	
2	20	
3	20	
4	20	
5	20	
<b>Total</b>	<b>100</b>	

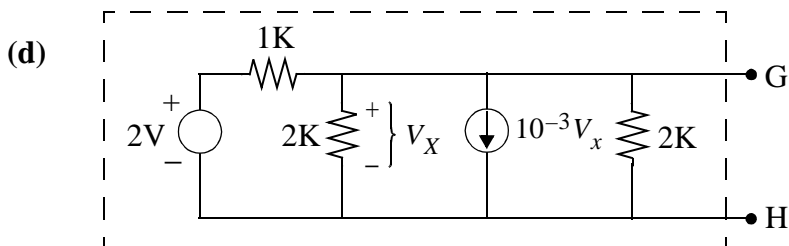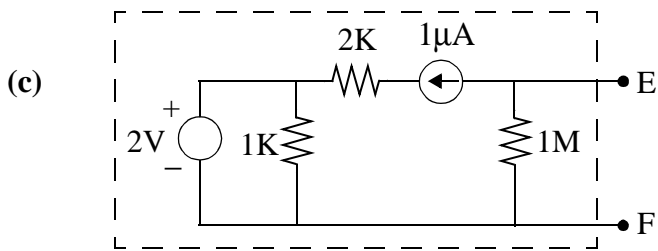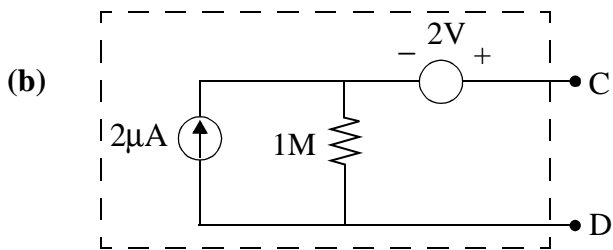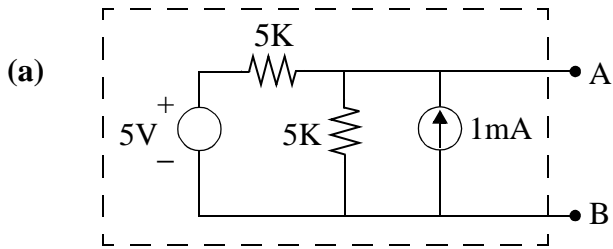
**Problem 1 (20 points)**

You are to find the Thévenin equivalent circuit for each of the following circuits. NOTE: You must fill in the answer boxes on the page opposite to receive full credit. Show the Thévenin equivalent circuit and indicate the values of  $R_T$  and  $V_T$ .



**Problem 1 Answer Sheet**

(a)

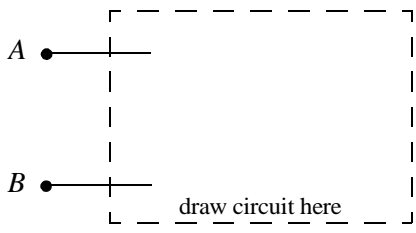


draw circuit here

$R_T = \text{_____} \Omega$

$V_T = \text{_____} \text{V}$

(b)

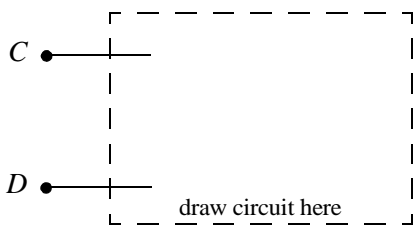


draw circuit here

$R_T = \text{_____} \Omega$

$V_T = \text{_____} \text{V}$

(c)

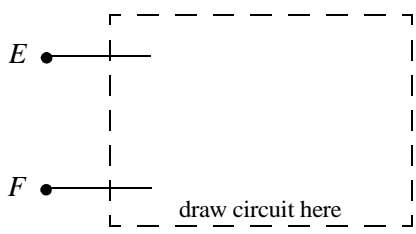


draw circuit here

$R_T = \text{_____} \Omega$

$V_T = \text{_____} \text{V}$

(d)

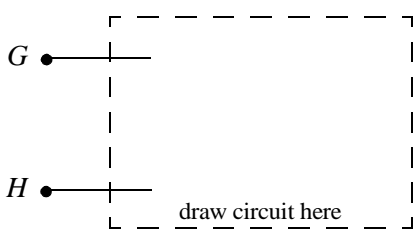

draw circuit here






$R_T = \text{_____} \Omega$

$V_T = \text{_____} \text{V}$

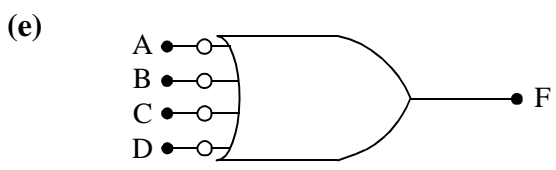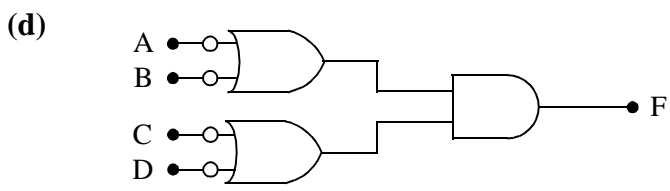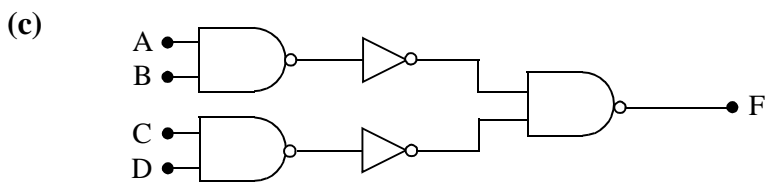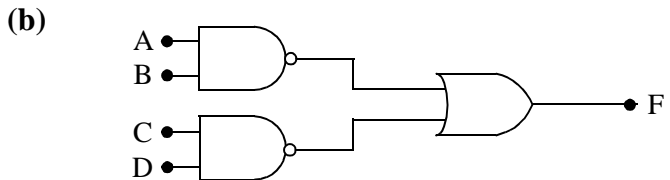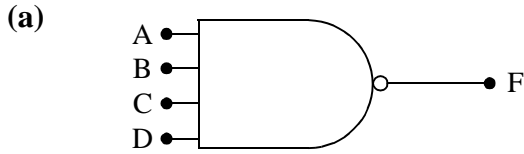**Problem 2 (20 points)**

As you know, sometimes two quite different circuits are equivalent. Consider the five following circuits. Indicate by circling which circuits are equivalent to each other.


NOTE: Do not guess; you MUST actually demonstrate that the circuits are equivalent. If you do not show the basis for your assertions of equivalence, you cannot receive credit. (Please do not ask a question of how to demonstrate equivalence—you are responsible for knowing that.) The grading will reward for correct answers with appropriate basis for the choices and will subtract for wrong answers.



## **Problem 2 Worksheet**

**Problem 3 (20 points)**

Consider the following logic circuit:

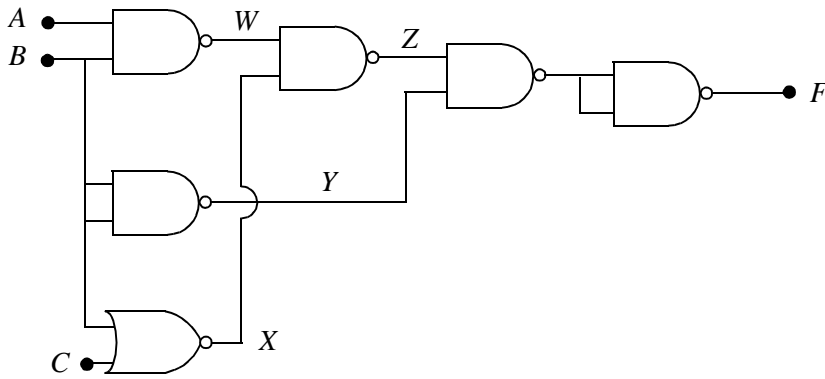

(a) Fill out the truth table (opposite), showing the intermediate values  $W, X, Y, Z$  as well as the output  $F$ .

(b) Write an expression for  $F$  in the “sum of products” form (in terms of inputs  $A, B, C$ ).

(c) Simplify the expression (if you can).

(d) Implement (synthesize) the function for  $F$  with NAND gates (show the NAND-gate circuit).

**Problem 3 Answer- and Worksheet**

(a)

A	B	C	W	X	Y	Z	F
0	0	0					
0	0	1					
0	1	0					
0	1	1					
1	0	0					
1	0	1					
1	1	0					
1	1	1					

(b)

$F =$ _____
-------------


(c)

$F =$ _____
-------------

(d)

**Problem 4 (20 points)**

(a) Consider the circuit below:

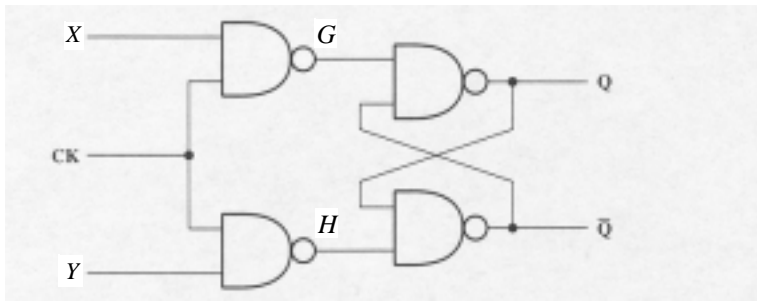


Fill in the value for  $Q$  in the timing diagram opposite. But to show your work, you must also show values for  $G$  and  $H$ . Note that the initial value of  $Q$  is 0, as shown by heavy dark line on the timing diagram. Ignore stage delay.

(b) For the same circuit, fill in the table, opposite.



**Problem 4 Answer Sheet**

(a)

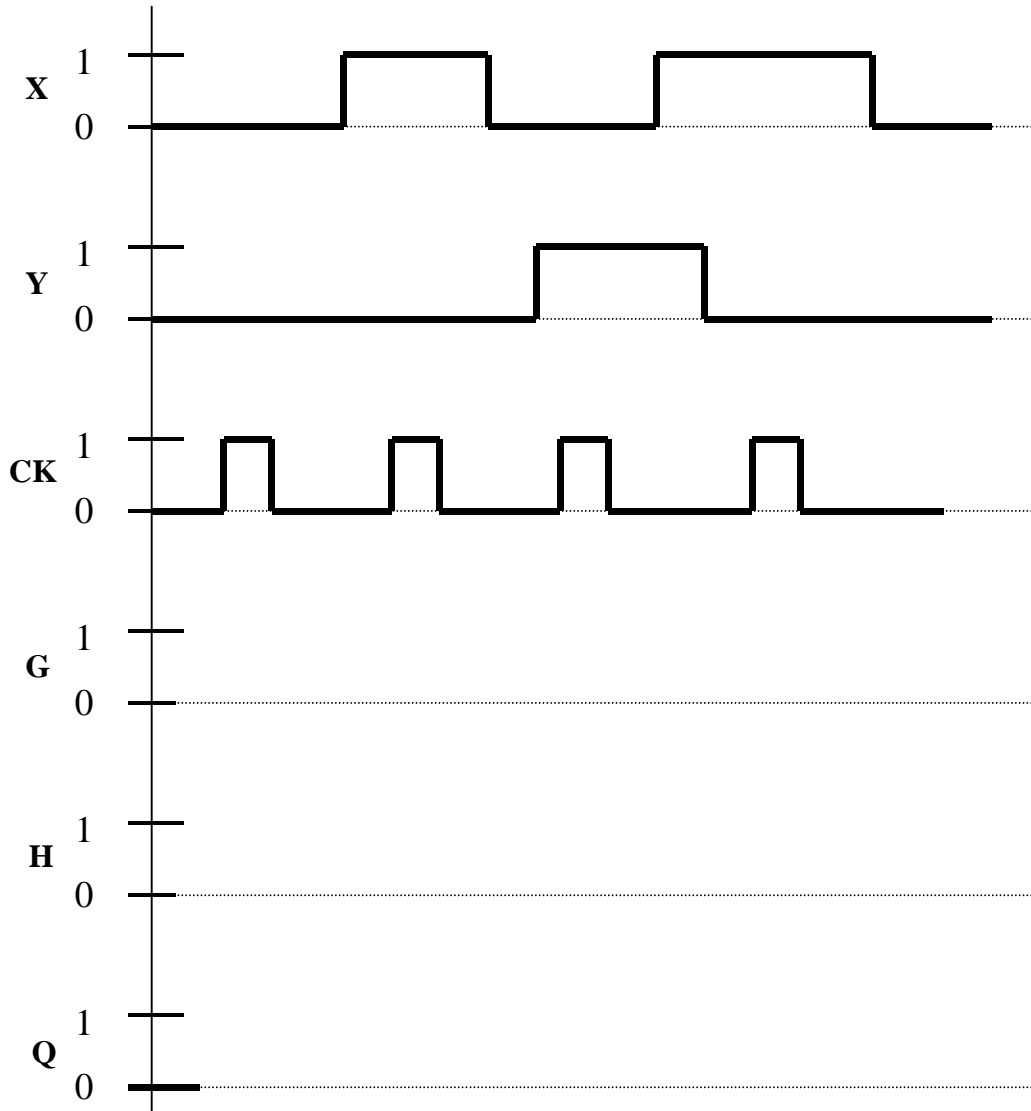


(b) The table below is intended to show the value of  $Q$  after CK goes high. Fill in the “Q” column with 0 or 1 or “ $Q_{old}$ ”.



$X$	$Y$	$Q$ (after CK=1)
0	0	
0	1	
1	0	

**Problem 5 (20 points)**


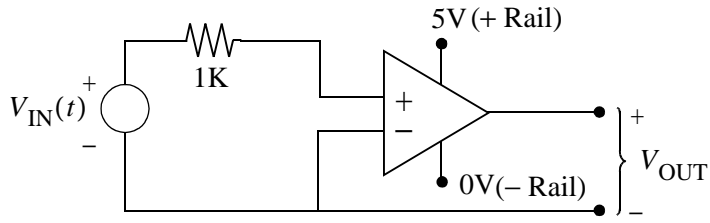
(a) For the circuit below and the input shown, neatly sketch the output voltage waveform on the axes provided.



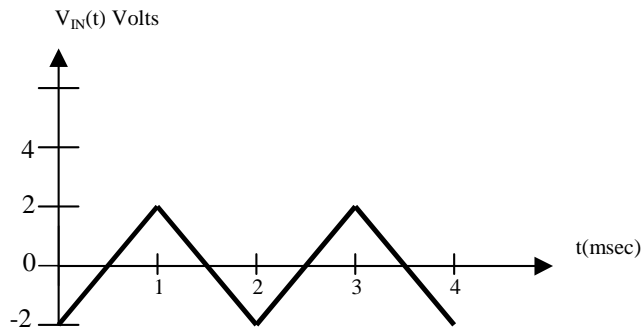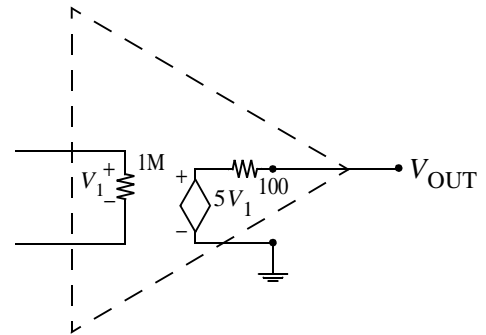Circuit Model for Linear Range of Amplifier:




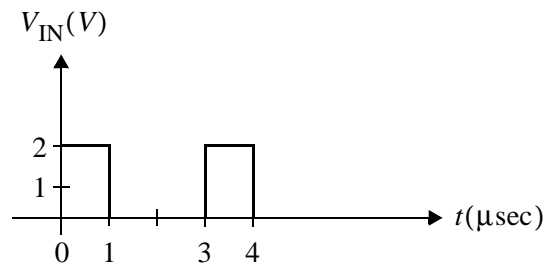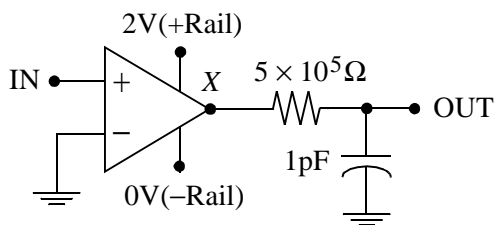(b) For the circuit shown below, neatly and carefully sketch the voltage at node X and the output on the page opposite. The amplifier is a high-gain amplifier with a gain of greater than a million, an input resistance of greater than  $1\text{M}\Omega$ , and an output resistance of less than  $100\Omega$ .



**Problem 5 Worksheet and Answersheet**

**(a)**

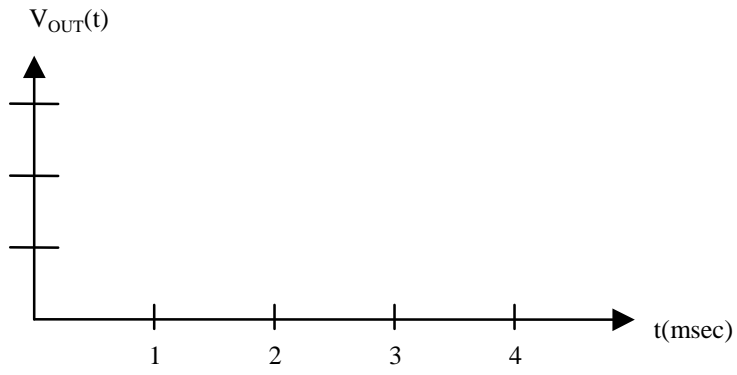

**(b)**

