

EECS 42 Spring 1995 Final Exam

Professor Paul Hagouel

May 16, 1995

100 Points Total

Problem 1

: (DC analysis, resistor combinations, Thevenin and Norton equivalent circuits): For each circuit, find the specified current, voltage and/or equivalent circuit. Hint: you may use source transformations where and if appropriate. (5 points each).

a. Find the current i and the voltage v (no mesh or nodal analysis).

b. Find R_{eq} . All resistances are in Ohms. (NO mesh or nodal analysis).

c. Find the voltage v_1 .

d. Find the Thevenin equivalent circuit at terminals a-b.

Problem 2

: (Operational amplifiers, ideal op-amp techniques): Find v_0/v_s for the circuit shown below (13 points). Assume that the operational amplifiers are ideal and that an ideal amplifier has an

$A = \infty$ (infinite). State the properties of an ideal operational amplifier (2 points).

Problem 3

: (Capacitor voltage initial condition, forced and transient response): For the circuit shown below, find $i(t)$ for $t > 0$. Assume the circuit is in steady state at $t = 0$. Hint: Voltages across capacitors can not change instantaneously. 0^+ denotes time and $t = 0^+$. The current source $10u(t)$ mA signifies that its value (i.e. the value of the source current) is equal to 0 A (or alternatively the source is "dead") for time $t \leq 0$, and equal to a 10 mA source for $t > 0$. (15 points)

Problem 4

: (Sinusoidal steady-state analysis including phasors and impedances. Frequency response and Bode asymptotic plots):

a. A circuit is shown below with a voltage source equal to $v_s=100\cos 1000t$ V. (8 points no partial credit)

For the circuit shown find:

- (a₁) the impedance \mathbf{Z}
- (a₂) using \mathbf{Z} , find the phasor current \mathbf{I}
- (a₃) find $i(t)$

b. An operational amplifier circuit is shown below. Find the ratio $\mathbf{V}_o/\mathbf{V}_s$ as a function of

ω (4 points) and sketch the asymptotic Bode plot when $R_2=10R_1$ and $R_2C=0.1$. (it should show the corner frequency ω_c and the frequency ω_m where it crosses the ω axis). (4 points)

Problem 5

: (Combinatorial logic, truth table, Karnaugh map, logic circuit realization): Minority checker. A minority function is generated in a combinational circuit when the output is equal to 0 if the input variables have more 1s than 0s. The output is 1 otherwise. Design a 3-input minority function. (5 points each: if the implementation is not done with two-input NAND gates then 2 points)

a. Fill the following truth table (5 points)

b. Use the Karnaugh map to find the minimum function F.

c. Implement using only two-input NAND gates (i.e. the gate has only two inputs). You can assume that the input complements are available. (5 points)

Problem 6

: (Sequential logic with **D** flip-flops, state table, state diagram, timing diagram): A sequential circuit with two **D** - type flip flops A and B (i.e. with inputs D_A , D_B and respective outputs **A** and **B**), two input variables **X** and **Y**, and one output variable **Z** is specified by the following input equations:

D

$A = (\overline{X})Y + XA$, $D_B = (\overline{X})B + XA$, and $Z = B$.

a. Draw the logic diagram of the circuit (6 points)

b. Fill up the state table (7 points). Hint: Take all possible combinations of inputs and initial states.

c. (you can either do c_1 or c_2) [c_1] draw the state diagram or [c_2] fill in the timing diagram. (7 points)

c_1

c_2

Solutions:

1a) $i = 3.33 \text{ A}$, $v = -13.33 \text{ V}$

b) $R_{eq} = 14 \text{ Ohms}$

c) $v_1 = 10 \text{ V}$

d) $V_T = 16 \text{ V}$, $R_T = 16/3 \text{ Ohms}$

2) $(V_o/V_s) = 22$

3) $i(t) = -2 + (10/3)e^{-2000t} \text{ mA}$

4a₁) $Z = 2 + j = 5^{1/2} \angle 26.7^\circ \text{ Ohms}$

a₂) $447 \angle -26.7^\circ \text{ A}$

a₃) $i(t) = 44.7 \cos(1000t - 26.7^\circ) \text{ A}$

b) $(V_o/V_s) = 1/(1 + j\omega R_2 C)$

5a)

Truth table:

A B C F

0 0 0 1

0 0 1 1

0 1 0 1

0 1 1 0

1 0 0 1

1 0 1 0

1 1 0 0

1 1 1 0

b) K map for F:

c\AB 00 01 11 10

0

1 1 0 1

1

1 0 0 0

c) A----**D**----\

| **D** -----= **D** \

B--**D**---/ /

| | **D** - F

C---| /

| /

D -----/