

Score summary  
(leave blank):

P1: \_\_\_\_\_

P2: \_\_\_\_\_

P3: \_\_\_\_\_

P4: \_\_\_\_\_

P5: \_\_\_\_\_

Total: \_\_\_\_\_

Name: SOLUTIONS

SID: \_\_\_\_\_

Name of student behind you:  
\_\_\_\_\_

Name of student in front of you:  
\_\_\_\_\_

**UNIVERSITY OF CALIFORNIA**  
**College of Engineering**  
**Department of Electrical Engineering**  
**and Computer Sciences**


**Midterm 2**

**EECS 42/100**  
**FALL 2007**

**B. E. BOSER**

- *Closed book, closed notes.*
- *No calculators.*
- *Leave packs and with books and cell phones in isle.*
- *Copy your answers into marked boxes on exam sheets.*
- *Simplify numerical and algebraic results as much as possible.*  
*Up to 10 points penalty for results that are not reasonably simplified.*
- *Mark your name and SID at the top of the exam and all extra sheets.*
- *Be kind to the graders and write legibly. No credit for illegible results.*
- *No credit for multiple differing answers for same problem.*

Problem 1 [20 points]

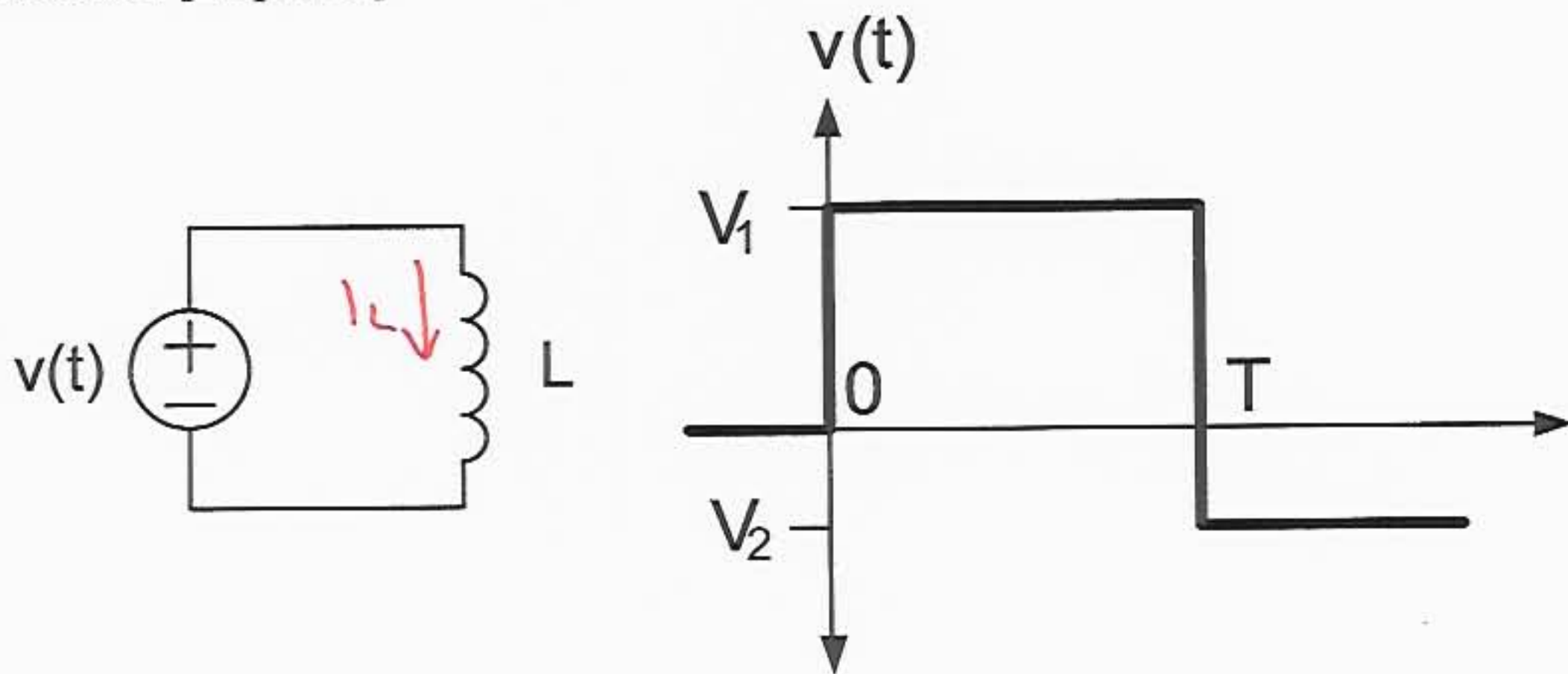

The voltage source  $v(t)$  in the diagram above applies a voltage  $V_1$  for  $0 \leq t \leq T$  and  $V_2$  for  $t > T$ . For  $t < 0$  the voltage is zero and the inductor current is zero. Derive algebraic equations for the power  $p_1(t)$  delivered by the source for  $0 \leq t \leq T$  and the power  $p_2(t)$  delivered for  $t > T$ .

$$p_1(t) = V_1^2 t / L$$

$$p_2(t) = \frac{V_2^2 (t-T)}{L} + \frac{V_1 V_2 T}{L}$$

$$V(t) = L \frac{di_L}{dt}$$

$$\int_0^t \frac{V(\tau)}{L} d\tau = i_L(t)$$

For  $0 < t < T$   
 $V(t) = V_1$

$$i_L(t) = V_1 t / L$$

For  $t > T$   $V(t) = V_2$

$$i_L(t) = \int_T^t \frac{V(\tau)}{L} d\tau + i_L(T) = \int_T^t \frac{V_2}{L} d\tau + \frac{V_1 T}{L}$$


$$= \frac{V_2 (t-T)}{L} + \frac{V_1 T}{L}$$

$$P = i \cdot v$$

$$P_1(t) = V_1 \cdot V_1 t / L = V_1^2 t / L$$

$$P_2(t) = V_2 \left[ \frac{V_2 (t-T)}{L} + \frac{V_1 T}{L} \right] = \frac{V_2^2 (t-T)}{L} + \frac{V_1 V_2 T}{L}$$

Problem 2 [20 points]

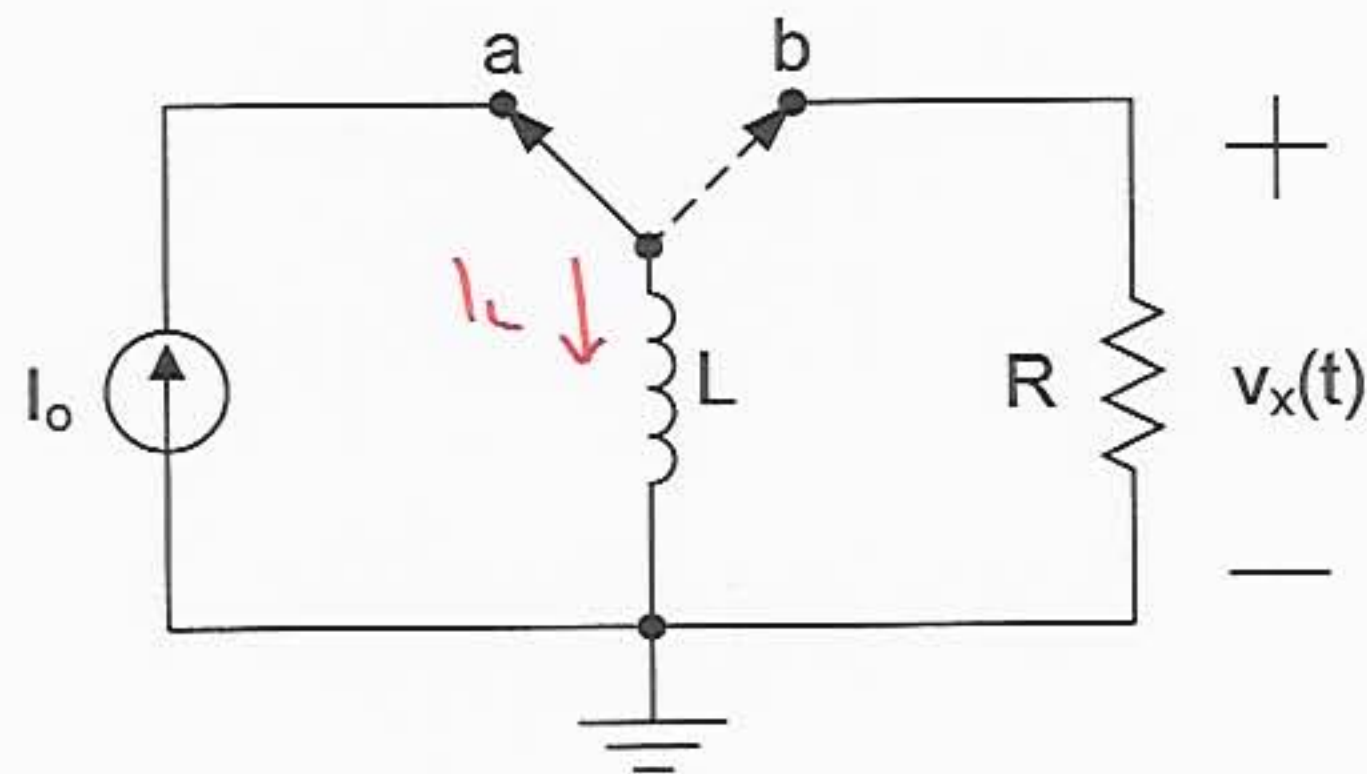

In the circuit shown above the switch is in position (a) for  $t < 0$  and in position (b) for  $t \geq 0$ . Find an algebraic expression for  $v_x(t)$  for  $t \geq 0$ .

$$v_x(t) = -R I_0 e^{-tR/L}$$

$$t < 0, I_L = I_0$$

$$t > 0$$


$$V_x = -R I_L, \quad V_x = L \frac{dI_L}{dt}$$

$$I_L \text{ of form } A e^{-t/\tau} \text{ with } A = I_0, \tau = L/R$$

$$I_L = I_0 e^{-tR/L}$$

$$V_x = -R I_0 e^{-tR/L}$$

Problem 3 [20 points]

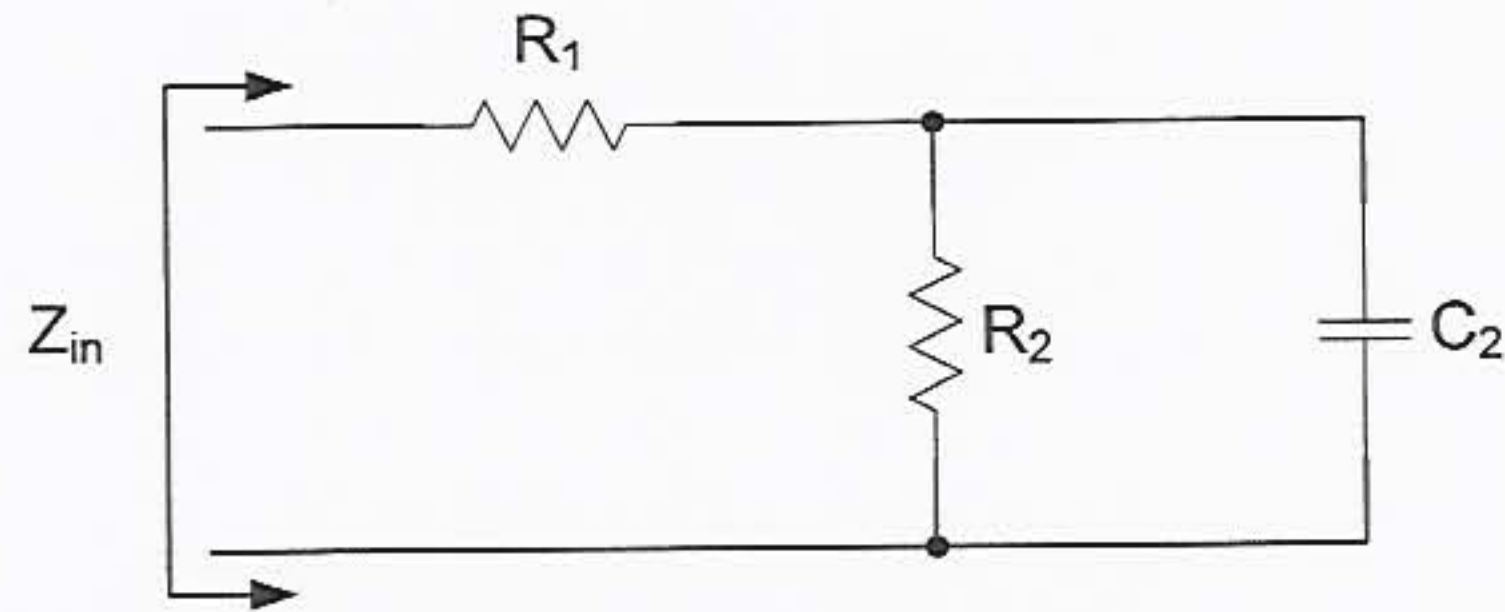

Find an algebraic equation for the imaginary part of  $Z_{in}(j\omega)$ .

$$\text{Im}\{Z_{in}\} = \frac{-\omega R_2^2 C_2}{1 + \omega^2 R_2^2 C_2^2}$$

$$Z_{in} = R_1 + R_2 // Z_{C_2}$$

$$= R_1 + \frac{R_2 Z_{C_2}}{R_2 + Z_{C_2}} = R_1 + \frac{R_2 / s C_2}{R_2 + 1/s C_2}$$


$$= R_1 + \frac{R_2}{1 + s R_2 C_2}$$

$$= R_1 + \frac{R_2}{1 + s R_2 C_2} \cdot \frac{1 - s R_2 C_2}{1 - s R_2 C_2}$$

$$= R_1 + \frac{R_2 - s R_2^2 C_2}{1 + \omega^2 R_2^2 C_2^2} = R_1 + \frac{R_2 - j\omega R_2^2 C_2}{1 + \omega^2 R_2^2 C_2^2}$$

$$\text{Im}(Z_{in}) = \frac{-\omega R_2^2 C_2}{1 + \omega^2 R_2^2 C_2^2}$$

Problem 4 [20 points]

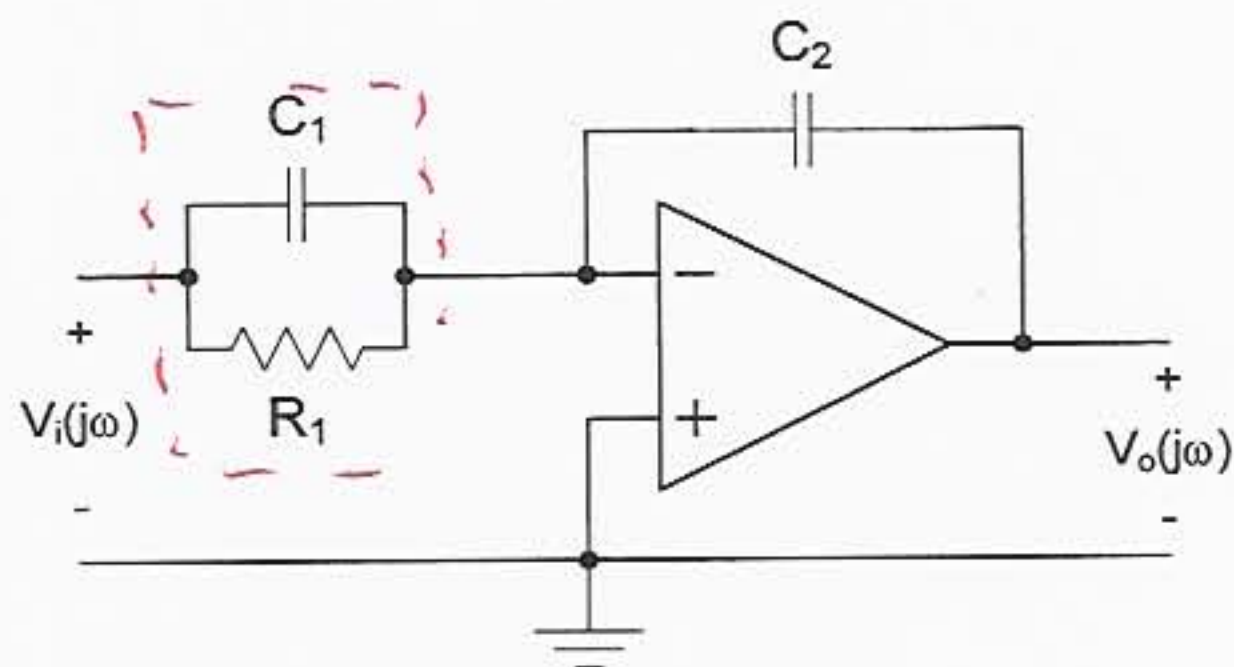

Derive an equation for the transfer function  $H(j\omega) = \frac{V_o(j\omega)}{V_i(j\omega)}$ .

$$H(j\omega) = - \frac{1 + j\omega R_1 C_1}{j\omega R_1 C_2}$$

$$V_- = V_+ = 0$$

KCL @  $V_-$       CURRENTS ENTERING THE NODE

$$\frac{V_i}{R_1} + V_i \cdot s C_1 + V_o \cdot s C_2 = 0$$

$$V_i \left( \frac{1}{R_1} + s C_1 \right) + V_o s C_2 = 0$$

$$-V_i \left( \frac{1 + s R_1 C_1}{R_1} \right) = V_o s C_2$$

$$H(s) = \frac{V_o}{V_i} = - \frac{1 + s R_1 C_1}{s R_1 C_2}$$

$$H(j\omega) = - \frac{1 + j\omega R_1 C_1}{j\omega R_1 C_2}$$

**Problem 5 [20 points]**

Draw the Bode plot (magnitude and phase) of the following transfer function:

$$H(s) = \frac{Ks}{1 - \frac{s}{p_1}}$$

for  $K = \frac{1}{1 \text{krad/s}}$  and  $p_1 = -10 \text{krad/s}$  in the semilog paper provided below. Mark the axes (units and tick values).

