

Professor Fearing

Fall 1999

EECS 150 – QUIZ #2

Tuesday, 4 November 1998, 2:10-3:30 p.m.

Name: _____

ID#: _____

- Closed book. No notes. No calculators.
- There are 4 problems worth 100 points total. There is little room for partial credit—it's better to do half the test carefully than to do the entire test sloppily.

Problem	Points	Your Score
1	16	
2	20	
3	50	
4	14	
Total	100	



In the real world, unethical actions by engineers can cost money, careers, and lives. The penalty for unethical actions on this exam will be a grade of zero.

Problem 1 (16 points)

List the ROM contents in **hexadecimal** to implement the FSM shown below. The inputs A and B are synchronized. The states are assigned numerical order, e.g., for state S4, $Q_2Q_1Q_0 = 100_2$. (Follow normal state diagram assumptions: holding in the same state is implicit, etc.).


Fill in ROM contents in hexadecimal. (Binary answers will receive no credit.)

Address	Data	Address	Data	Address	Data	Address	Data
0		8		10		18	
1		9		11		19	
2		A		12		1A	
3		B		13		1B	
4		C		14		1C	
5		D		15		1D	
6		E		16		1E	
7		F		17		1F	

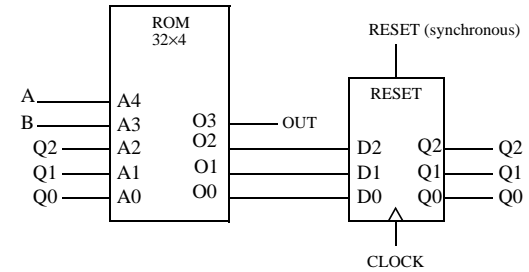 


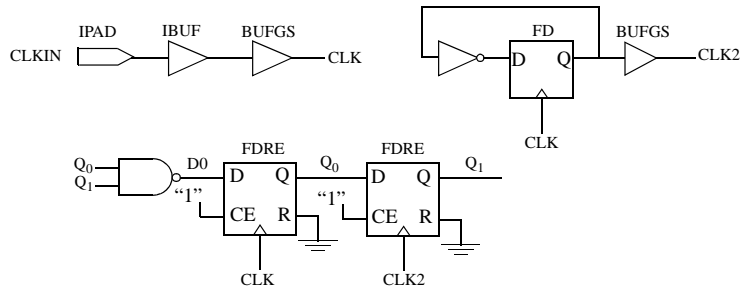Problem 2 (20 points)

Your lab partner has designed the following Xilinx XC4000 circuit and tells you it works fine in unit delay simulation, but won't work when downloaded to the Xilinx chip. Given $CLKIN=1MHz$, $T_{ckomax}=2.8ns$, $T_{su}=2.4ns$.



 [12 pts.] a) Complete the timing diagram (considering propagation and interconnect delays) to show why the circuit does not operate as intended.



[4 pts.] b) Circle the problem area(s) in the timing diagram, and briefly explain in a full sentence what the problem is.

[4 pts.] c) Modify the design above so it will work as intended. Do not add any gates or FF.

Problem 3 (50 points)

You are given the 8-bit data path below. The SRAM is 256×8 , but has the same operating characteristics as the static RAM used in lab. 8-bit binary counter CB8RE has synchronous reset.

