

CS152: Computer Architecture and Engineering
Fall, 2000
Midterm 1

Professor W. Brodersen


Problem 1: Single-cycle Processor Performance (35 points)

We have a single cycle processor as we learned in class. Besides the instructions R-format, lw, sw, and beq that the processor already implemented, the designer figured that certain software does the following instructions extensively

cs \$t \$s1 \$s2 **cslw** \$t \$s1 \$s2 **cslwcs** \$t \$s1 \$s2


Besides the usual PC handling and instruction fetch as before,

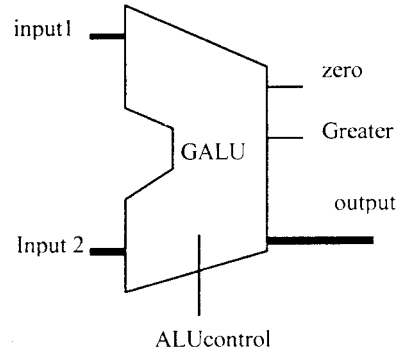- the **cs** instruction is described as:
\$t <= max(\$s1, \$s2)
- The **cslw** does the following:
\$t <= memory [max(\$s1,\$s2)]
- The **cslwcs** instruction the following:
\$t <= max{\$s1, memory[max (\$s1, \$s2)]}



So now you see that **cs** and **lw** in above names stand for “compare select” and “load word”.

The designer plans to modify the datapath and control signal based on the processor showed in next page. It's a textbook processor with some missing blocks and wiring to fill in. The components that can be used are any of the blocks *already present* in the design and the generalized GALU (showed above) with an additional output GREATER that equals to 1 if Input1-Input2 >0, and equals to 0 if Input1-Input2 =< 0.

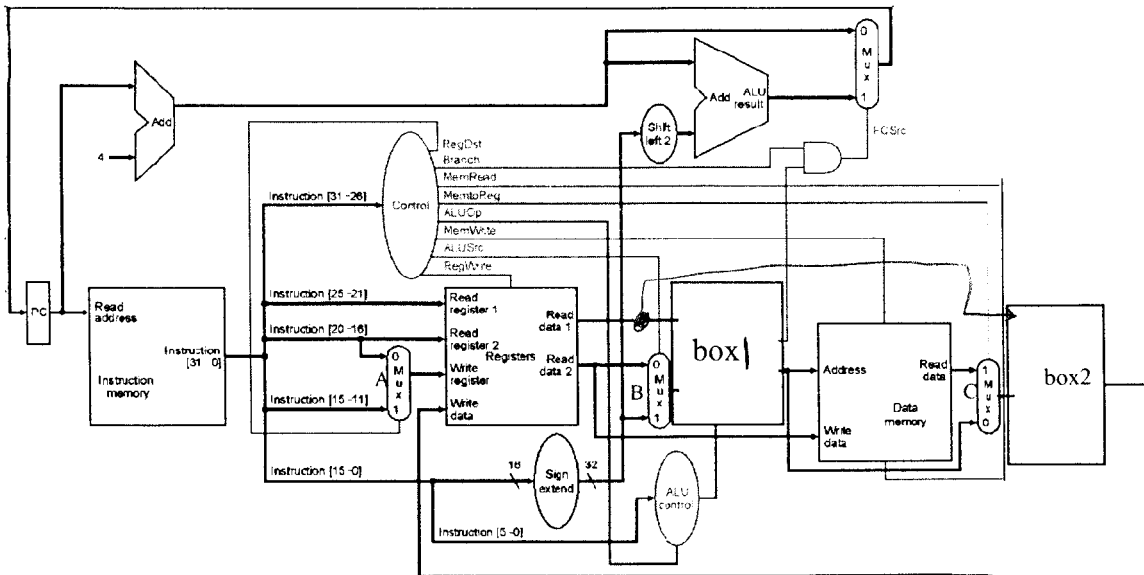


A) [10 points] **Describe below in words and draw in box 1** the blocks that need to be added in order to implement the **cs** and **cslw** instructions. **Furthermore, draw in box 2** any additional blocks to implement the **cslwcs** instruction. (*Hint: think about doing so by adding GALU(s), MUX(es), AND(s), and possibly new control signal(s)*)

i) For **cs** and **cslw**:

Box 1



ii) For **cslwcs**:

 

B) [7 points] Fill in the control table below with X, 0 or 1. Add in new columns) if you need new control signal(s). You may not need all three columns.

Instruction	ALUsrc	Mem-ToReg	RegWr	Mem-Read	Mem-Write			
SW	1		0	0	1			
R-format	0	0		0				
cslw								
cslwcs								

C) [9 points] You will point out the *critical path*, calculate the *critical path delay in ns*, and hence determine the *fastest clock rate in MHz*. Finally, you will use some program features to *calculate the execution time of the processor*. Use the following delay parameters (ignore hold time and regard the register delay as clock-to-Q):

- ALU or GALU, delay = 15 (ns)
- Sign/zero extender, delay = 3(ns)
- 2-1 Mux, delay = 2 (ns)
- Memory, delay (both write and read) = 10 (ns)
- Register, delay = 1 (ns)
- Register files, read delay =10 (ns), write setup time=10 (ns)

All other components' delays are ignored (i.e. zero).

i) The critical, path is (write down the components' names in order):

ii) The critical path delay in ns and the fastest clock rate in MHz:

iii) Now use a program to evaluate the performance of the processor. The program has 10% **lw** instructions, 10% **beq**, 10% **sw**, 20% R-format, 25% **cs**, 15% **cslw**, 10% **cslwcs**. The program contains 1,000,000 instructions in total. How much time is needed to run this program?

D) [9 points] *Please write down as simply as possible the decomposition* of the **cslwcs** instruction in terms of **cs**, **cslw**, **lw**, **sw** and/or **R-format** instructions. Thus the original processor can be modified only to run additional **cs** and **cslw** instructions in one cycle and use multiple cycles for **cslwcs**. *Estimate the critical path delay* for this processor, and hence *evaluate the time needed* to run the same program in part C.iii above.

i) Define **cslwcs \$t \$s1 \$s2**, in terms of **cs**, **cslw**, **lw**, **sw** and **R-format** instructions:

ii) The new critical path delay:


iii) The new execution time of the program:

Problem 2: Bus-based Multicycle Processor (30 points)

The datapath below forms a multicycle processor which uses two time-multiplexed buses for communication rather than point-to-point connections and muxes. What are the pros and cons of such an architecture? Is it a good idea? This problem will get you started toward a decision...

You can make the following assumptions:

- The next PC logic will automatically increment the PC when you fetch a new instruction
- Both the sign-extended and zero-extended forms of the immediate field are available to Bus B
- The register specifiers Rs, Rt, and Rd are always correctly passed to the register file (data written into the register file is passed from BusB)
- Both the register file and the memory have purely combinational (asynchronous) reads
- The register file, memory, and all registers are triggered by the same clock edge (with no skew)

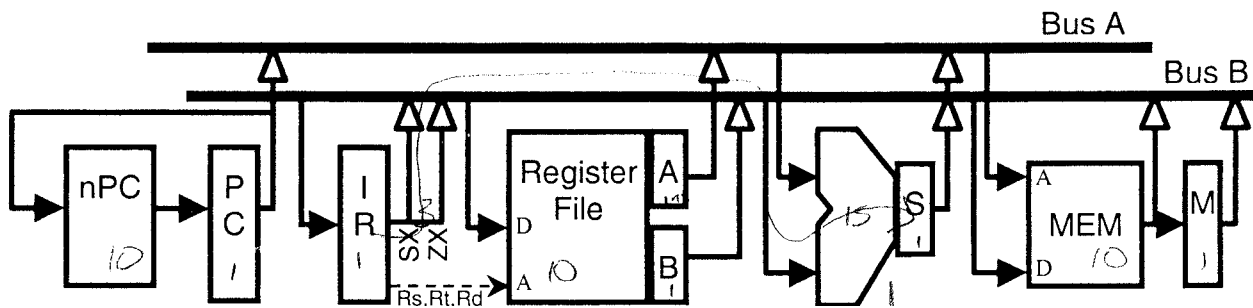

You can use the rest of this page for scratch space. The first question begins on the next page...

A) [10 points] Microprogram the following instructions by filling in the table. The **SrcA** and **SrcB** fields specify which signals will be assigned to BusA and BusB, respectively. The **WrDest** field specifies what component is written at the end of the cycle. This can be any one of the state registers (A and B can be paired together in one cycle), the register file, or memory. It is implied that all other components will not be written accidentally. The **Sequence** field behaves as presented in class: it specifies whether the microprogram should return to the fetch stage to start a new macroinstruction, dispatch to a location specific to the current opcode, or proceed in order. You should ignore the BNE instruction for now - it is only provided for part (C). *Hint: you do not need to fill all the rows.*

μ Addr	Instruction	SrcA	SrcB	ALUOp	WrDest	Sequence
00	Fetch					
01	Decode					
02	ADD					
03						
04						
05						
06	ADDI					
07						
08						
09						
0A	LW					
0B						
0C						
0D						
0E	SW					
0F						
10						
11						
12	<i>BNE</i>	<i>A</i>	<i>B</i>	<i>Sub</i>	<i>--</i>	<i>If ALUZero Then Next Else Fetch</i>
13		<i>PC</i>	<i>SX</i>	<i>Add</i>	<i>PC*</i>	<i>Fetch</i>

B) [10 points] One of the major drawbacks to using large buses is the massive loading caused by so many components all connected to the same node. To approximate the effect of the increased loading, assume that it takes an additional 10ns just to drive a signal on a bus (in other words, assume the hollow arrowheads in the datapath schematic have a delay of 10ns). Each component delay is copied below for your reference (you'll notice they all match the other problems). *Neglecting the BNE instruction, what is the maximum clock frequency of this processor?*

Registers (clk-to-Q)	1ns
Register File	10ns
Extender	3ns
ALU	15ns
Memory	10ns
nPC Logic	10ns

C) [10 points] Calculate the execution time of the following assembly program, which adds two 1000-element integer vectors. The base pointers of the source vectors and the destination vector are initially stored in \$4, \$5, and \$6 respectively. *Give your reasoning and/or equations in words, and clearly substitute each term with its actual numerical value!*

```

        ADDI $0, $8, 1000
top:    LW    $10, 0($4)
        LW    $11, 0($5)
        ADD  $12, $10, $11
        SW   $12, 0($6)
        ADDI $4, $4, 4
        ADDI $5, $5, 4
        ADDI $6, $6, 4
        ADDI $8, $8, -1
        BNE $8, $0, top

```

Problem 3: MIPS 5 Stage Pipelined Processor (35 points)

The processor shown on the next page is one implementation of a standard MIPS 5 stage pipelined processor. The specifications of the processor are as follows:

- Five pipeline stages: IF, ID, EX, MEM, WB.
- The processor does not have forwarding nor hazard implemented yet.
- Control signals are represented by dotted lines. **Control bus values represent the actual control bits top-down.** Control signal values are in **binary format**. Data signal values are in **decimal format**.
- RegisterFile **writes in the first half of the cycle**, and **reads in the second half**.
- Both instruction and data memory reads asynchronously; data memory writes synchronously. Both memories are **byte addressed**. Data memory size is 16 words and only the least significant bits are used to address the memory. Each component has been labeled with a **worst-case delay**. Registers only have clock-to-Q delay, and **zero setup/hold time**. **Assume no clock skew**.
- The diagram of the processor also includes a snapshot of the processor **at the beginning of the cycle**, with necessary signal values labeled.
- Tables 1 & 2 show the contents of the register file and data memory at the snapshot time. **Assume the register file and memory have been correctly updated in the previous cycle, but all writes in the current cycle have not taken place yet.** Table 3 shows the ALU control truth table. A MIPS R3000 opcode table is also attached at the end.

A) [5 points] How many branch delay slot(s) does this processor have?

B) [5 points] What is the minimum clock period of the processor?

C) [7 points] In MIPS assembly language, determine exactly what instruction is being executed in ID stage? What are the changes to the register file and data memory after the completion of the instruction?

D) [7 points] In MIPS assembly language, determine exactly what instruction is being executed in EX stage? What are the changes to the register file and data memory after the completion of the instruction?

E) [11 points] Now implement only the hazard detection unit without forwarding, such that from the software's perspective, the processor has exactly one branch delay slot, exactly one load delay slot, and all hazards are resolved at the hardware level. You are only allowed to add write enable control signals to any of the five pipeline registers, along with necessary control logic.

i. In order to stall the pipeline, some of the five pipeline registers should have write enable control signal. Fill in the following table. ('Y' means yes needed, 'N' means not necessary)

	PC	IF/ID	ID/EX	EX/MEM	MEM/WB
Need Write En?					

ii. Describe in words, or pseudocode, under what condition each of the pipeline registers should be write disabled, and for **how many processor cycles** in each case.

Pipeline Register	Write Disable Condition	Number of Cycles
PC		
IF/ID		
ID/EX		
EX/MEM		
MEM/WB		

Table 1: Register File Contents


Register Address	Content
0	0
1	1
2	2
3	3
4	4
5	5
6	6
7	7
8	8
9	9
10	10
11	11
12	12
13	13
14	14
15	15
16	16
17	17
18	18
19	19
20	20
21	21
22	22
23	23
24	24
25	25
26	26
27	27
28	28
29	29
30	30
31	31

Table 2: Data Memory Contents

Word Address	Content
0	24
1	78
2	46
3	184
4	169
5	23
6	78
7	40
8	80
9	36
A	85
B	42
C	56
D	72
E	81
F	100

Table 3: ALU control truth table

ALU opcode	ALU operation
00	Add
01	Sub
10	R-format

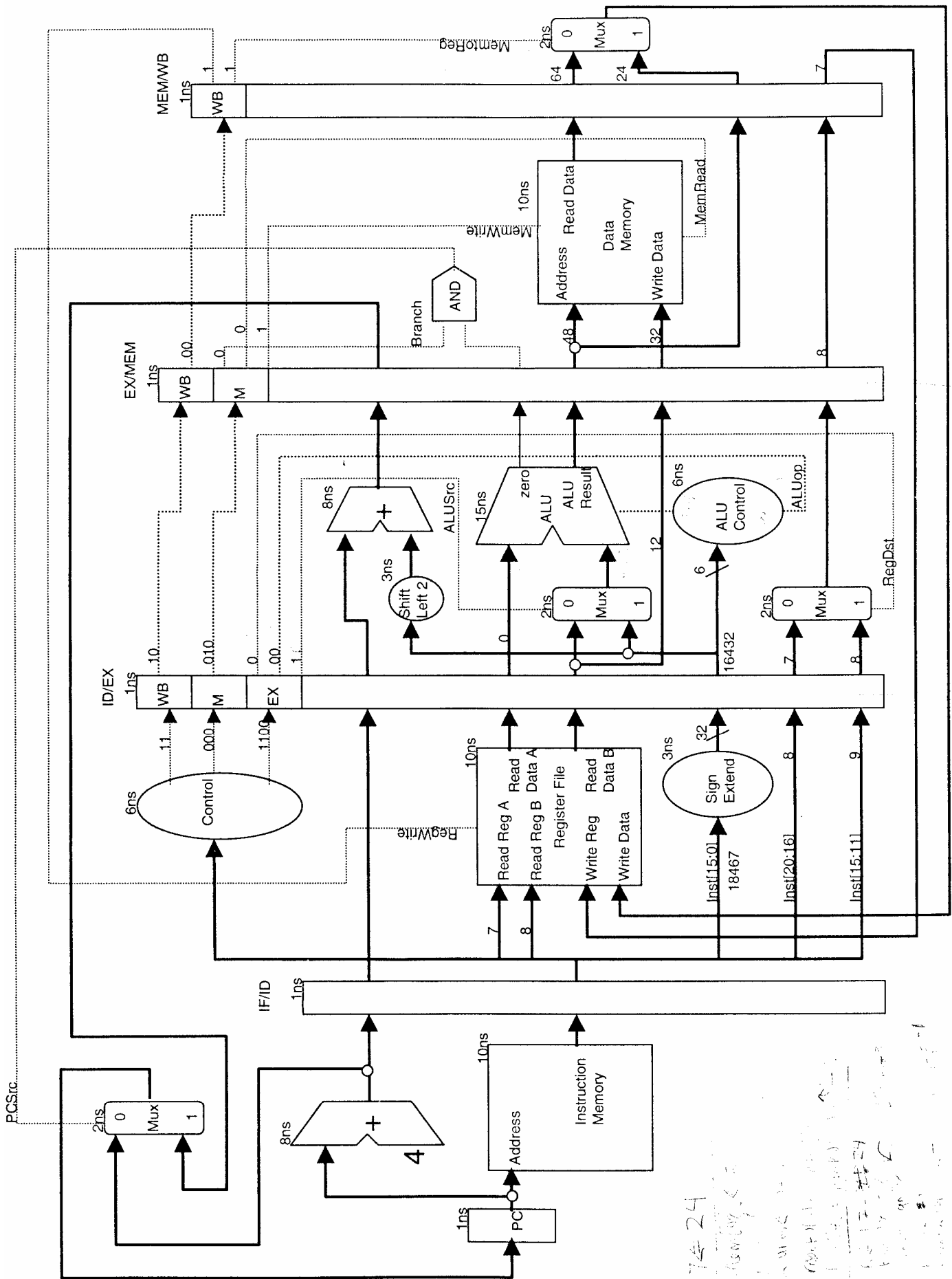

174 24
 Memory
 (80486) (80486) (80486)
 (80486) (80486) (80486)
 (80486) (80486) (80486)
 (80486) (80486) (80486)

10	16	op(31,26)	rs	(25,21)	bc	(16,15)	funct	(4,0)	rt	(20,16)	funct(5,0)	funct(5,0)
0	00	*									sll	add
1	01	*										sub
2	02	j									srl	mul
3	03	jal									sra	div
4	04	beq										
5	05	bne										abs.
6	06	blez									srlv	mov.
7	07	bgtz									sra v	neg
8	08	addi									jr	
9	09	addiu									jalr	
10	0a	sth										
11	0b	srtu										
12	0c	andi									syscall	
13	0d	ori									break	
14	0e	xori										
15	0f	lui										
16	10	* = 0 *									mthi	
17	11	* = 1 *									mthi	
18	12	* = 2 *									mflo	
19	13	* = 3 *									mtlo	
20	14											
21	15											
22	16											
23	17											
24	18										mult	
25	19										multu	
26	1a										div	
27	1b										divu	
28	1c											
29	1d											
30	1e											
31	1f											
32	20	lb	0	mfc	0	bc f	0	tlbr	0	bltz	add	cvf.s
33	21	lh	1		1	bc t	1	tlbw	1	bgez	addu	cvf.d
34	22	lwl	2	cfc			2		2		sub	
35	23	lwr	3				3		3		subu	
36	24	lbu	4	mfc			4		4		and	cvf.w
37	25	lhu	5				5		5		or	
38	26	lwr	6	ctc			6	tlbwr	6		xor	
39	27		7				7		7		nor	
40	28	sb	8				8	tlbp	8			
41	29	sh	9				9		9			
42	2a	swl	10				10		10		sll	
43	2b	sw	11				11		11		sll	
44	2c		12				12		12		sll	
45	2d		13				13		13		sll	
46	2e	swr	14				14		14			
47	2f		15				15		15			
48	30	lwc0	16	cop			16	rte	16	bltzal		cvf.l
49	31	lwc1	17	cop			17		17	bgezal		cvf.un
50	32	lwc2	18				18		18			cvf.eq
51	33	lwc3	19				19		19			cvf.ueq
52	34		20				20		20			cvf.olt
53	35		21				21		21			cvf.olt
54	36		22				22		22			cvf.ole
55	37		23				23		23			cvf.ole
56	38	swc0	24				24		24			cvf.st
57	39	swc1	25				25		25			cvf.ngle
58	3a	swc2	26				26		26			cvf.seq
59	3b	swc3	27				27		27			cvf.ngl
60	3c		28				28		28			cvf.lt
61	3d		29				29		29			cvf.nge
62	3e		30				30		30			cvf.le
63	3f		31				31		31			cvf.ngt