

PRINT NAME (Last, First):

POOLLA

SIGN YOUR NAME: _____

STUDENT ID #: _____

# 1	# 2	# 3	# 4	SUBTOTAL
7	8	6	14	35


# 5	# 6	# 7	# 8	SUBTOTAL	TOTAL
15	10	21	4	50	85

Instructions:

- 1 Print and sign your name and enter your student ID number above.
- 2 Read the questions carefully.
- 3 Write your solution clearly.
- 4 You must show your work to get full credit.
- 5 This exam has 8 questions worth 85 points, so you should proceed at approximately 1 point per minute.

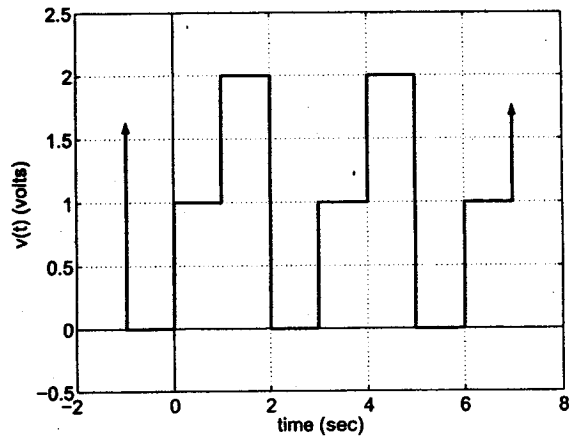Problem # 1 (1+2+2 = 5 points)

Consider the periodic voltage waveform $v(t)$ shown below.



Find the following:

◇ Period

3 seconds

Period = 3 seconds

◇ DC Voltage

DC Voltage = 1 volt

◇ RMS Voltage

$$\sqrt{\frac{1}{3} \int_0^3 v^2 dt}$$
$$= \sqrt{\frac{1}{3} [1+4]} = \sqrt{\frac{5}{3}}$$

RMS Voltage = $\sqrt{\frac{5}{3}}$ volts

Problem # 2 (2 + 2 + 2 + 2 = 8 points)

Convert the following phasors to sinusoids. Assume the frequency is ω .

(a) $5 \exp(j\pi/2)$

$$5 \cos(\omega t + \frac{\pi}{2})$$

Answer = $5 \cos(\omega t + \frac{\pi}{2})$
 $-5 \sin(\omega t)$

(b) $3 + 4j$

Answer = $3 \cos(\omega t) - 4 \sin(\omega t)$
 $5 \cos(\omega t + 53.1^\circ)$.921
 $5 \sin(\omega t + 143.1^\circ)$

Convert the following sinusoids to phasors.

(c) $3 \cos(\omega t) + 4 \sin(\omega t)$

Answer = $3 - 4j$
 $5 \angle -53.1^\circ$

 $3 + 4j$

(d) $\sqrt{2} \sin(\omega t - 45^\circ)$



Answer = $-1 - j$
 $\sqrt{2} \angle -135^\circ$

$$\sqrt{2} \sin(\omega t) \leftrightarrow -j\sqrt{2}$$

$$\sqrt{2} \sin(\omega t - \frac{\pi}{4}) \leftrightarrow -j\sqrt{2} e^{-j\pi/4}$$

$$= -j\sqrt{2} \left(\frac{1}{\sqrt{2}} - \frac{j}{\sqrt{2}} \right)$$

$$= -1 - j$$

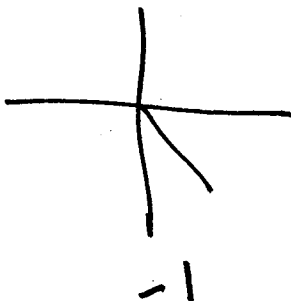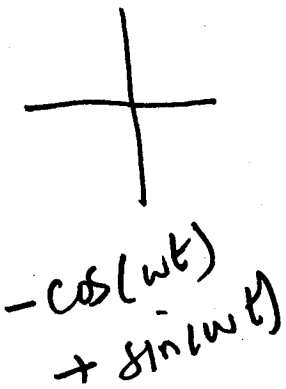

Problem # 3 ($6 * 1 = 6$ points)

Circle the most appropriate answers.

Incorrect answers receive -1 points.

No explanations are necessary.

The internal resistance R of a practical current source is in series / parallel with the source.


For a well designed circuit with a practical current source, this internal resistance R should be much larger / smaller than the load resistance.

A circuit element that requires an external power supply is called active / passive.

We can / cannot find the Thevenin equivalent of a circuit containing diodes.

The input resistance of an ammeter is very low / very big

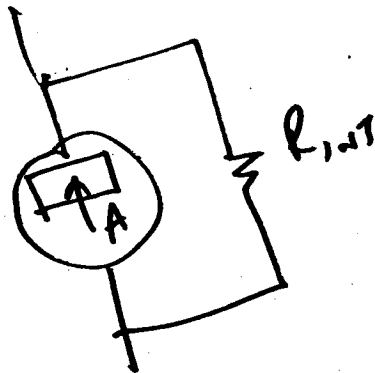
An oscilloscope can easily be used / not be used to measure magnetic field strength.



Problem # 4 (5 + 5 + 2 + 2 = 14 points)

A 10 volt battery with internal resistance R_1 is connected to a resistive load R_L . The voltage across the load is measured with a voltmeter whose internal resistance is R_2 .

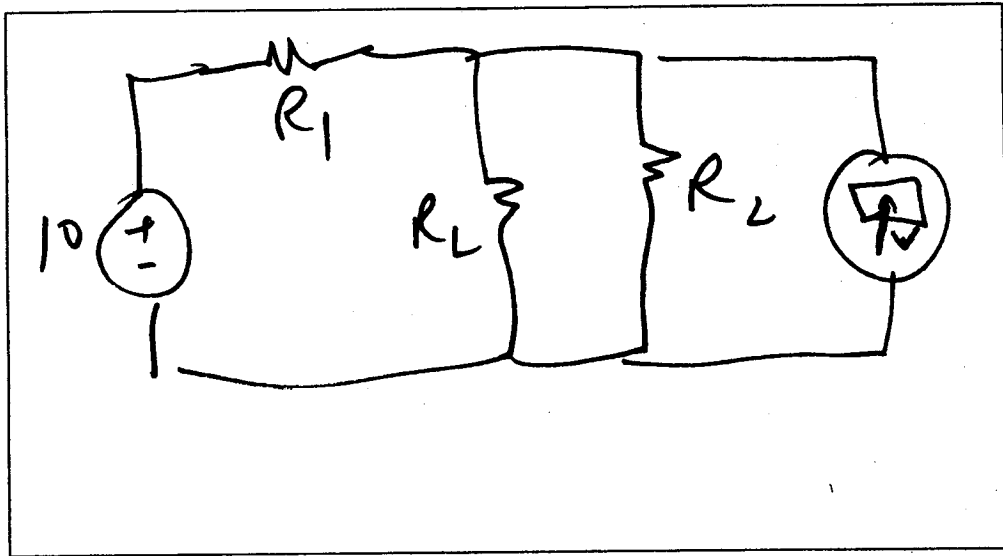(a) Draw a circuit diagram for this problem in the box below.



(b) Find an expression for the voltage recorded by the voltmeter in terms of R_1, R_2, R_L .

$$\frac{R_2 \uparrow \uparrow R_L}{R_1 + R_2 \uparrow \uparrow R_L} \quad 10$$

Voltmeter Reading = $10 \frac{R_2 R_L}{R_2 R_1 + R_L R_1 + R_2 R_L}$


(c) Ideally, would you want $R_1 \gg R_L$ or $R_1 \ll R_L$? (circle your answer)

(d) Ideally, would you want $R_2 \gg R_L$ or $R_2 \ll R_L$? (circle your answer)

4+4+4+3

Problem # 5 (4+8+1+2 = 15 points)

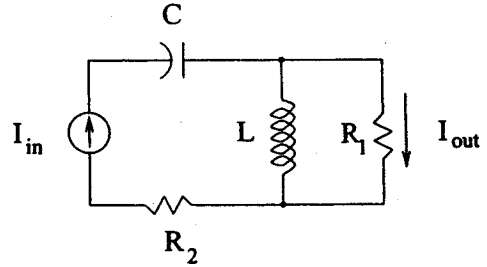- (a) Consider the circuit shown here. Let I_{in} and I_{out} be the phasors of the input current I_{in} and the output current I_{out} respectively. Find I_{out} in terms of R_1, R_2, L, C, ω and I_{in} .



Current divider


4 pts

$$\frac{j\omega R_1 L + \omega^2 L^2}{R_1^2 + \omega^2 L^2} I_{in}$$

$$I_{out} = \frac{j\omega L}{R_1 + j\omega L} I_{in}$$

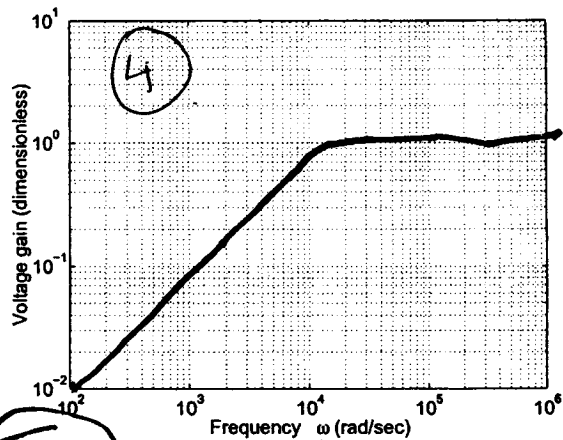- (b) With $R_1 = 1 \text{ K}\Omega, R_2 = 5 \text{ k}\Omega, L = 100 \text{ mH}, C = 3 \mu\text{F}$, sketch the frequency response of the current magnitude gain from I_{in} to I_{out} . Use the log-log scale graph-paper supplied below.

$$\frac{j\omega}{j\omega + \frac{R_1}{L}} \approx \frac{10^3}{0.1} = 10^4$$



$$\frac{\omega L}{\sqrt{R_1^2 + \omega^2 L^2}}$$

- (c) Is this a low-pass or band-pass or high-pass filter?
(circle your answer)

3

4

$$\frac{\omega}{\sqrt{\omega^2 + \frac{R_1^2}{L^2}}}$$


Problem # 6 (3 + 3 + 4 = 10 points)

Consider the circuit shown below.

Let V_a and V_b be the voltages at nodes a and b respectively.

Here, you will use the nodal method to find the voltage V_a .

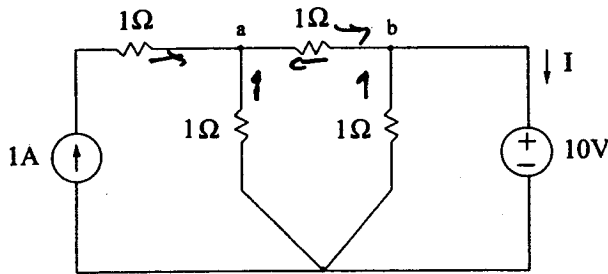Let the unknown quantities be the node voltages V_a , V_b and the current I .



- (a) Write KCL at node a in terms of the unknown quantities only.

$$\text{KCL at node } a: 1 + V_b - V_a - V_a = 0$$

- (b) Write KCL at node b in terms of the unknown quantities only.

$$\text{KCL at node } b: V_a - V_b - V_b - I = 0$$

- (c) Solve for V_a . You will need one more equation here.

$$V_b = 10$$

$$V_a = 5.5 \text{ volt}$$

$$V_b + 1 = 2V_a$$

$$V_a = \frac{11}{2}$$


Problem # 7 (9 + 8 = 17 points)

Consider the circuit shown here.
The source voltage $v_s(t)$ is given by:

$$v_s(t) = \begin{cases} -4 \text{ volts} & t \leq 0 \\ 6 \text{ volts} & t > 0 \end{cases}$$


Here, $R_1 = 2k\Omega$, $R_2 = 2k\Omega$, $R_3 = 3k\Omega$, $C = 2.5\mu F$.

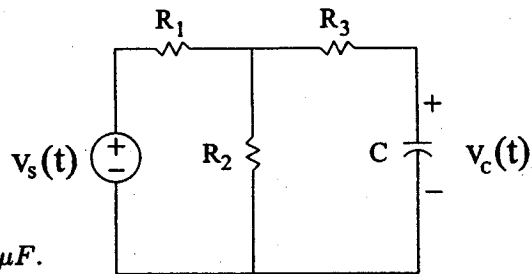The problem is to find the voltage $v_c(t)$ for $t > 0$.



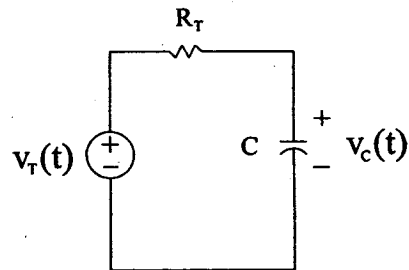- (a) (4+4+3 = 11 points) Find the Thevenin equivalent for the circuit above. In other words, find the voltage $v_T(t)$ and the resistance R_T for the equivalent circuit shown below.

$$\begin{aligned} R_T &= R_3 + R_1 \parallel R_2 \\ &= 3 + 1 \\ &= 4 \text{ k}\Omega \end{aligned}$$



@ $t = 0^-$ $V_S = -4$

voltage divider $V_T(0^-) = -2$

@ $t = 0^+$
 $V_S = 6$

$$v_T(t) = \begin{cases} -2 & \text{volts } t \leq 0 \\ 3 & \text{volts } t > 0 \end{cases}$$

$$R_T = 4 \text{ k}\Omega$$

(b) (2 + 4 + 4 = 10 points) For the rest of the problem use the following values. These values are **not** correct but will enable you to finish the problem even if you made a mistake in part (a).

Values you should use:


$$v_T(t) = \begin{cases} -3 \text{ volts} & t \leq 0 \\ 5 \text{ volts} & t > 0 \end{cases} \quad R_T = 6k\Omega$$

Find the time constant of the circuit.

Find $v_C(t)$ for $t > 0$.

Sketch $v_C(t)$ on the graph below.
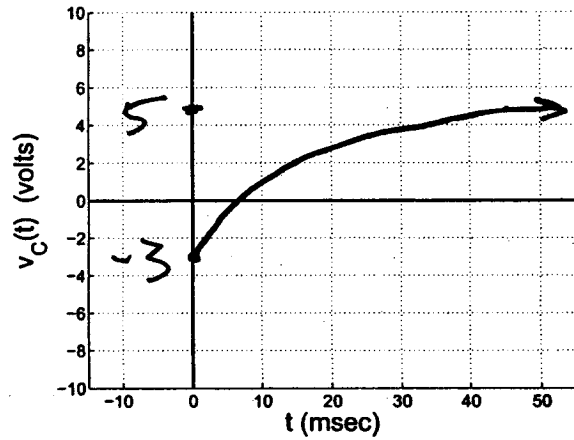
$$R_T C = 6 \times 10^3 \times 2.5 \times 10^{-6} = 15 \text{ msec.}$$



time constant = 15 ms

for $t > 0$, $v_C(t) =$

$$5 + (-3 - 5)e^{-t/15}$$

Problem # 8 (4 points)

You have two resistors R_1 and R_2 . Using these in various combinations you can make resistances of 4, 6, 12, and 18Ω .

Find R_1, R_2 .

$$R_1 = 6$$

$$R_2 = 12$$

$$2$$

$$2$$