

**Microelectronic Devices and Circuits- EECS 105**

**Second Midterm Exam**

Wednesday, November 15, 2000

Costas J. Spanos

University of California at Berkeley

College of Engineering

Department of Electrical Engineering and Computer Sciences

Your Name: \_\_\_\_\_  
(last) (first)

Your Signature: \_\_\_\_\_

1. Print and sign your name on this page before you start.
2. You are allowed two 8.5"x11" handwritten sheets with formulas. No books or notes!
3. Do everything on this exam, and make your methods as clear as possible.

Problem 1 \_\_\_\_\_ / 30

Problem 2 \_\_\_\_\_ / 40

Problem 3 \_\_\_\_\_ / 30

**Problem 1 of 3 Answer each question briefly and clearly. Sketch a simple drawing if it helps you make your point. (30 points)**


What is the physical mechanism limits the maximum  $f_T$  of a BJT? (6 pts)

What is "base-width modulation" and how does it affect the behavior of BJT? (6pts)

You are given a 2-port, which has  $R_{in} = 1K\Omega$ ,  $R_{out} = 100K\Omega$ , and an open circuit voltage gain  $A_v = -10$ . Please draw the equivalent transconductance 2-port and calculate its  $R_{in}$ ,  $R_{out}$ , and  $G_m$ . (6 pts)

consider a CE amplifier. What is (are) the benefit(s) of using an ideal current source versus a resistor connected to the supply to bias the collector? (6 pts)

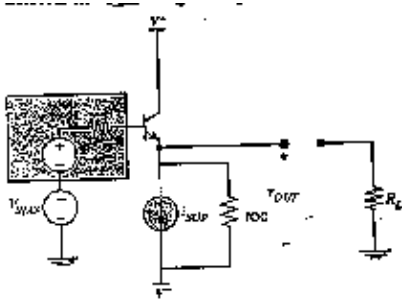
Sketch the small signal equivalent of the following amp (ignore all capacitors) (6 pts):



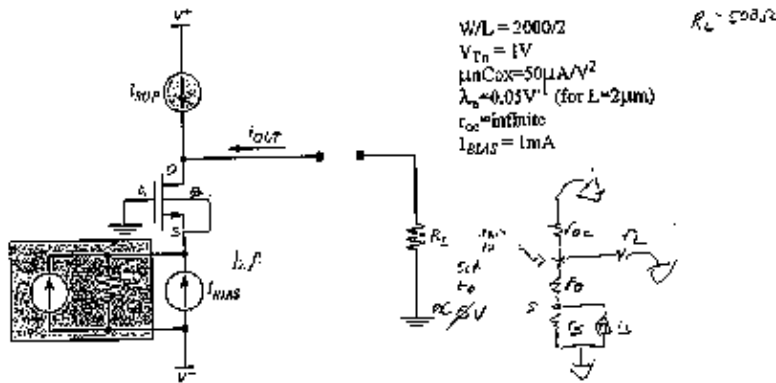**Problem 2 of 3 (40 points)**

For each of the following questions, make sure that you show the expressions *before* you plug in the specific values. A correct expression is worth 70% of the credit, even if the numerical calculation is incorrect!

We want to "match" a car radio antenna to the radio input. The antenna acts as a small signal current source with an  $R_s = 50\Omega$ . The radio input "looks" like an ohmic load with  $R_i = 500\Omega$ . We will use the following CG MOS amplifier in order to achieve decent current gain from the signal source to the load. Note that the bulk is shorted to the source ( $V_{bs} = 0V$ ). Ignore all caps in answering the following questions




a) Draw the equivalent small signal circuit of this amplifier (10pts)

a) draw the equivalent small signal circuit of this amplifier (10 pts)

b) Sketch the 2-port Current Amp equivalent, and write expressions for  $R_{in}$ ,  $R_{out}$ , and  $A_i$ . Assume that  $r_o \gg R_s$  and  $r_o \gg R_L$ . (10 pts).

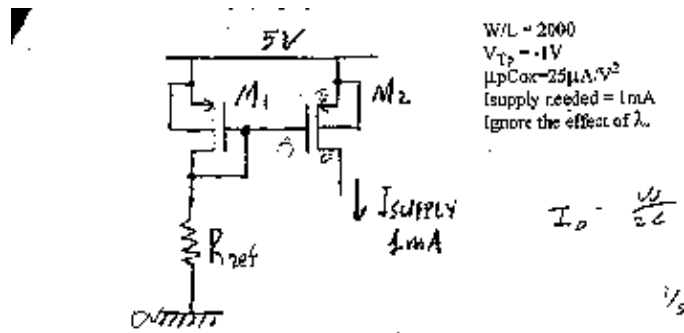c) Calculate the overall (loaded) current gain, (note that  $V_{bs} = 0$  V). (10pts)


M1 and M2 have both the same W/L. Find the value of  $R_{ref}$  so that this current source delivers the 1 mA of supply current that is needed (for this part of the problem assume that the load draws no DC current). (10pts).



Problem 3 of 3 (30 points)

For each of the following questions, make sure that you show the expressions before you plug in the specific values. A correct expression is worth 70% of the credit, even if the numerical calculation is incorrect!

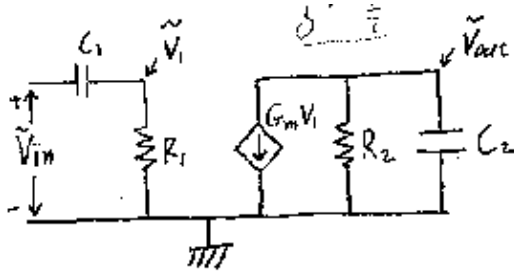a) Derive the transfer function  $V_{out}/V_{in}$  expression of the following amplifier (10 pts).



b) Plot amplitude and phase Bode plots when  $R_1 = 10\text{K}\Omega$ ,  $C_1 = 0.01\ \mu\text{F}$ ,  $R_2 = 1\text{K}\Omega$ ,  $C_2 = 0.001\ \mu\text{F}$ ,  $G_m = 0.01\ \text{S}$ . (10 pts for each plot).

