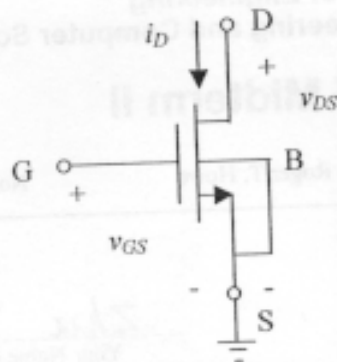


1. Short-Channel MOSFET Model [17 points].




Device parameters:

$$\begin{aligned}
 C_{ox} &= 4 \text{ fF}/\mu\text{m}^2 \\
 W &= 2.5 \mu\text{m} \\
 L &= 0.1 \mu\text{m} \\
 V_{Tn} &= 1 \text{ V} \\
 V_{DS,sat} &= 0.75 \text{ V} \\
 \lambda_n &= 0.05 \text{ V}^{-1} \\
 v_{sat} &= 10^7 \text{ cm/s}
 \end{aligned}$$

An improved model for the velocity-saturated MOSFET is:

$$\begin{aligned}
 i_D &= C_{ox} W v_{sat} (v_{GS} - V_{Tn}) \left( \frac{v_{DS}}{V_{DS,sat}} \right) \left( 1 - \frac{v_{DS}}{2V_{DS,sat}} \right) \text{ when } v_{DS} \leq V_{DS,sat} = 0.75 \text{ V (triode region)} \\
 &= C_{ox} W v_{sat} (v_{GS} - V_{Tn}) \left( \frac{v_{DS}}{V_{DS,sat}} - \frac{v_{DS}^2}{2V_{DS,sat}^2} \right) \\
 i_D &= \left( \frac{1}{2} \right) C_{ox} W v_{sat} (v_{GS} - V_{Tn}) \left[ \frac{1 + \lambda_n v_{DS}}{1 + \lambda_n V_{DS,sat}} \right] \text{ when } v_{DS} > V_{DS,sat} = 0.75 \text{ V (saturation region)}
 \end{aligned}$$

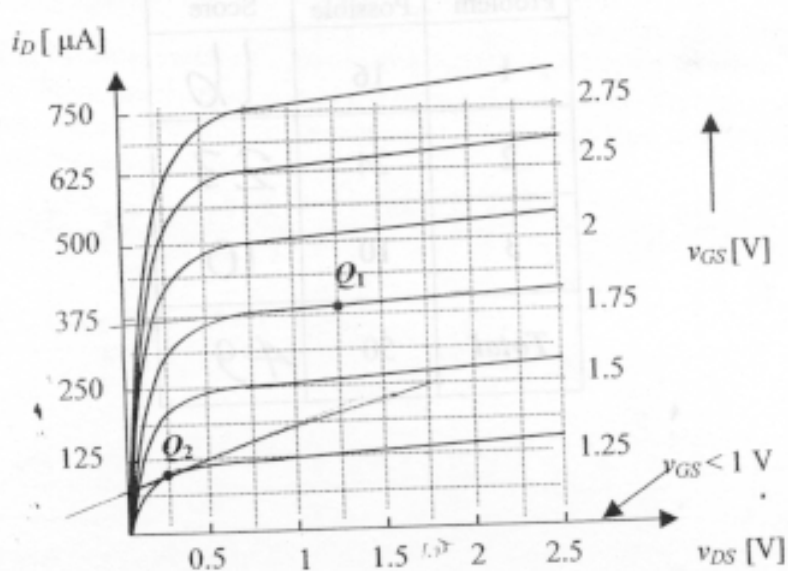The drain characteristics for this short-channel MOSFET model are:




(a) [4 pts.] What is the small-signal transconductance  $g_m$  at the operating point  $Q_1$  in  $\mu\text{S}$ ? You can find the answer either from the drain current equations or graphically: in either case, be sure to explain your method clearly.

(b) [4 pts.] What is the small-signal drain resistance  $r_o$  at the operating point  $Q_1$  in  $\text{k}\Omega$ ? For this parameter at this operating point, graphical techniques don't give a sufficiently accurate answer.

(c) [4 pts.] What is the transconductance  $g_m$  at the operating point  $Q_2$  in  $\mu\text{S}$ ? You can find the answer either from the drain current equations or graphically: in either case, be sure to explain your method clearly.

(d) [4 pts] What is the small-signal drain resistance  $r_o$  at the operating point  $Q_2$  in  $\text{k}\Omega$ ? You can find the answer either from the drain current equations or graphically: in either case, be sure to explain your method clearly.

2. BJT voltage buffer [18 pts.]

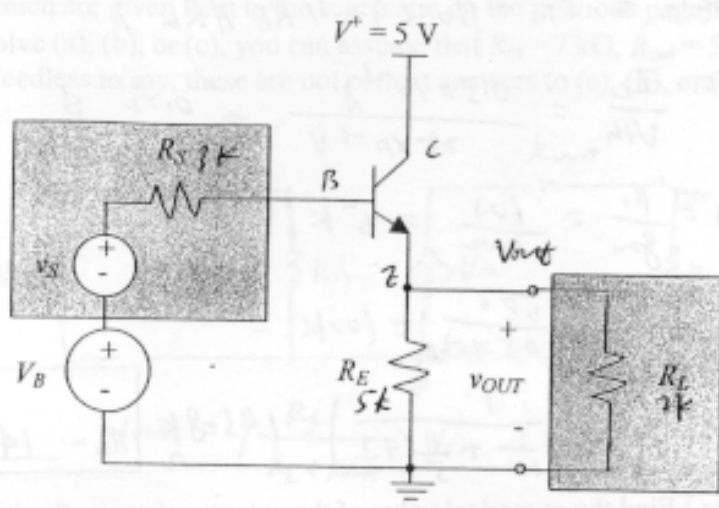

Given:  
 $\beta_o = 100$   
 $V_{th} = 25\text{ mV}$   
 $V_A = 50\text{ V}$   
 $V_{CEsat} = 0.1\text{ V}$   
 $R_S = 3\text{ k}\Omega$   
 $R_E = 5\text{ k}\Omega$   
 $R_L = 2\text{ k}\Omega$

- (a) [3 pts.] Find the numerical value of  $V_B$  such that  $V_{OUT} = 2.5\text{ V}$ . Your answer should be accurate to  $\pm 5\%$ . Notes: (i) the gray boxes indicate small-signal elements that can be neglected for the DC bias analysis and (ii) the DC base current  $I_B$  of the bipolar transistor can be neglected for the bias solution.

- (b) [3 pts.] What is the numerical value of the DC collector current  $I_C$  for this amplifier?

(c) [4 pts.] Find the numerical value of the input resistance  $R_{in}$  of this amplifier in  $k\Omega$ .


(d) [4 pts.] Find the numerical value of the output resistance  $R_{out}$  in  $k\Omega$ .

(e) [3 pts.] Find the numerical value two-port parameter  $A_v$ , the open-circuit voltage gain, for this amplifier.

- (f) [4 pts.] Find the overall voltage gain  $v_{out} / v_s$  with  $R_S$  and  $R_L$  present (values of which are given next to the schematic on the previous page). If you couldn't solve (a), (b), or (c), you can assume that  $R_{in} = 7 \text{ k}\Omega$ ,  $R_{out} = 5 \text{ k}\Omega$ , and  $A_v = 0.8$ . Needless to say, these are not correct answers to (a), (b), or (c).

- (g) [3 pts.] Suppose that the input voltage  $v_s(t) = \hat{v}_s \cos(\omega t)$ . What is the maximum amplitude  $\hat{v}_s$  for which the small-signal, two-port model you've derived in parts (b)-(c) is reasonably accurate? You can assume that the frequency of  $v_s(t)$  is low enough that capacitors can be neglected. *Justify your answer.*

3. npn bipolar transistors [10 pts.]

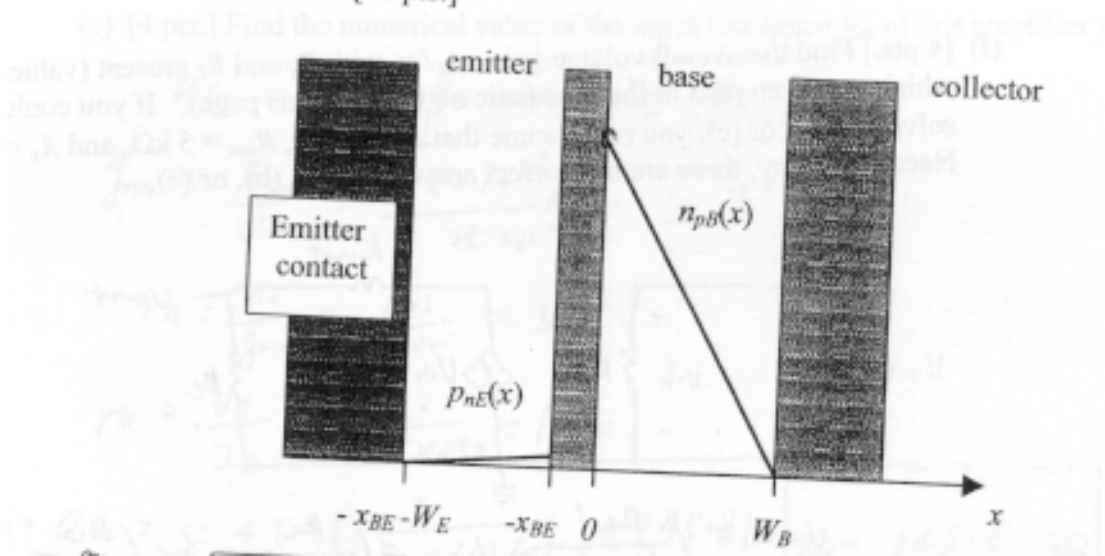

Given:

Base width =  $W_B = 150 \text{ nm} = 0.15 \text{ } \mu\text{m}$

Emitter-base junction area =  $A_E = 25 \text{ } \mu\text{m}^2$

Emitter width =  $W_E = 100 \text{ nm} = 0.1 \text{ } \mu\text{m}$

Base-collector junction area =  $A_C = 50 \text{ } \mu\text{m}^2$

Electron diffusion constant in base:  $D_n = 20 \text{ cm}^2/\text{s}$

Hole diffusion constant in emitter:  $D_p = 7 \text{ cm}^2/\text{s}$

Electron charge:  $q = -1.6 \times 10^{-19} \text{ C}$

Intrinsic concentration:  $n_i = 10^{10} \text{ cm}^{-3}$

- (a) [4 pts.] The collector current for this forward-active npn bipolar transistor is  $I_C = 25 \text{ } \mu\text{A}$ . From the cross section of the device shown above, find the numerical value of the minority electron concentration at  $x = 0$ , at the base side of the emitter-base depletion region.

(b) [3 pts.] For the bias conditions in part (a), the base-emitter voltage  $V_{BE} = 697.5$  mV. What is the doping concentration  $N_A$  in the base? If you couldn't solve part (a), you can use  $n_{pB}(0) = 8 \times 10^{14} \text{ cm}^{-3}$ , which is not the correct answer to part (a), of course.

(c) [3 pts.] The minority hole concentration in the emitter at the edge of the emitter-base depletion region is  $(0.04) \times (\text{your answer to part (a)})$ . What is the forward-active DC current gain  $\beta_F$  for this transistor? Note that you don't need to have answered part (a) in order to answer this part!