

Microelectronic Devices and Circuits- EECS105
Second Midterm Exam

Wednesday, April 16, 2003

Costas J. Spanos
 University of California at Berkeley
 College of Engineering
 Department of Electrical Engineering and Computer Sciences

Your Name: Official Solutions
 (last) (first)

Your Signature: _____

1. Print and sign your name on this page before you start.
2. You are allowed two, 8.5"x11" handwritten sheet. No books or notes!
3. A correct expression is worth 70% of the credit. The calculation gets you the rest.
4. You have until 4/25/03 to bring any grading issues to Prof. Spanos' attention.

Problem 1 _____ / 48
 Problem 2 _____ / 16
 Problem 3 _____ / 16
 Problem 4 _____ / 20
 TOTAL $\mu = 75$ $\sigma = 16$ / 100

MOS Device Data¹ (you may not have to use all of these...)

$\mu_n C_{ox} = 50 \mu A/V^2$, $\mu_p C_{ox} = 25 \mu A/V^2$, $V_{Tn} = -V_{Tp} = 1V$, $L_{min} = 2 \mu m$, $V_{BS} = 0$.
 $\lambda_n = \lambda_p = 0.1 V^{-1}$ when $L = 1 \mu m$, and it is otherwise proportional to $1/L$
 $C_{ox} = 2.3 fF/\mu m^2$, $C_{jn} = 0.1 fF/\mu m^2$, $C_{jp} = 0.3 fF/\mu m^2$, $C_{jswn} = 0.5 fF/\mu m$,
 $C_{jswp} = 0.35 fF/\mu m$, $C_{ovn} = 0.5 fF/\mu m$, $C_{ovp} = 0.5 fF/\mu m$

BJT Device Data¹ (you may not have to use all of these...)

$\beta_F = \beta_o = 100$, $I_S = 10^{-17} A$, $V_{CE SAT} = 0.1V$, $V_A = 25V$, $\tau_F = 50ps$, $C_{je} = 15 fF @ V_{BE} = 0.7V$,
 $C_{\mu} = 10 fF @ V_{BC} = -2.0V$

¹ Except as indicated on the particular problem...

Problem 1 of 4: Answer each question briefly and clearly. (6 pts each, 48 total)

1.1 What are the *typical* values of R_{in} , R_{out} for a decent CC voltage buffer?

R_{in} 5-10 Ω 100-1000 Ω 10-20 $k\Omega$ 100-300 $k\Omega$ 1-10 $M\Omega$ $r_n + \beta_o (2d/2oc/R_c)$
 R_{out} 5-10 Ω 100-1000 Ω 10-20 $k\Omega$ 100-300 $k\Omega$ 1-10 $M\Omega$ $1/g_m + \frac{R_s}{\beta_o}$

1.2 Why is it important to make the base of a BJT as short as possible? (choose one)

- So that the transistor occupies less space
- So that there are no ohmic losses in the base
- So that almost all injected minority carriers make it across
- So that holes and electrons stay uniformly distributed

1.3 What happens when the base of a BJT is very short? (choose one)

- The transconductance drops in value
- The beta drops in value
- The r_o drops in value
- The Early voltage gets delayed

Provide a brief explanation of the mechanism responsible for the above:

Base width modulation due to the CB depletion region making the base even shorter (decreases $|V_A|$)


1.4 What happens when the channel of a MOSFET is very long? (choose one)

- The transconductance increases
- Velocity saturation kicks in
- The transistor gets too hot
- The r_o increases in value

Provide a brief explanation of the mechanism responsible for the above:

Channel length modulation is less of a problem for long transistors (decreases λ)

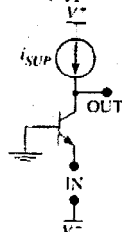- 1.5 Why it is important to have a current supply with a huge (i.e. tens of MOhms) internal resistance when you design a current buffer utilizing a Common Base BJT? (Typical r_o for a BJT is 100kOhms)




because a CB is meant to have a huge output resistance and you do not want the r_{oc} to limit it!

$$r_{oc} \parallel \left[(1 + g_m (r_o \parallel \beta_o)) r_o \right]$$

↑
HUGE

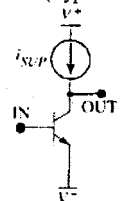
- 1.6 Why it is NOT so important to have a current supply with an internal resistance greater than $\sim 1\text{M}\Omega$ when you are designing a Common Emitter amplifier? (Typical r_o for a BJT is 100kOhms)



Because r_{oc} goes in parallel to r_o and r_o limits the R_{out} value. A very large r_{oc} will be wasted...

$$R_{out} = r_o \parallel r_{oc}$$

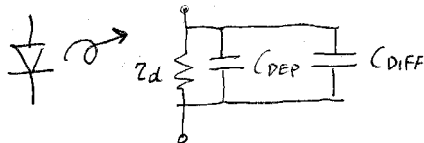- 1.7 Draw the small signal model of the forward biased diode. Name all distinct capacitive components.




- 1.8 Provide a brief definition of the transition frequency ω_t of the BJT transistor.

the frequency at which a CE amp with shorted output has a current gain of -1 .

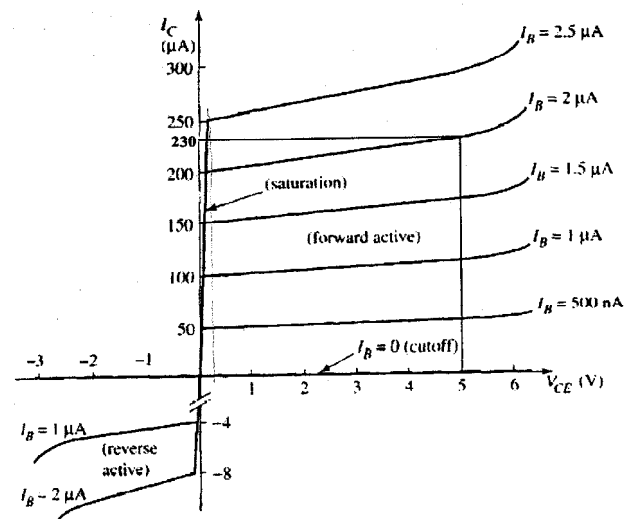Problem 2 of 4: Answer each question briefly and clearly. (16 points)

From the graph below, please estimate β_F and β_R , as well as r_o . Also, estimate g_m , r_π and $V_{CESAT\ min}$ when $I_B = 2\mu\text{A}$ at room temperature ($V_{th} = 0.025\text{mV}$). Do NOT use the default BJT values on the front page of this exam for this question. Hint: in reverse active mode the role of the collector and emitter are reversed. Mark the graph to clarify your method as needed.)




expression	value & units	
$\beta_F = I_C / I_B = 200\mu\text{A} / 2\mu\text{A}$	100	2
$\beta_R = I_E / I_B = I_C - I_B / I_B = \frac{8-2}{2}$	3	2
$r_o = \frac{1}{SLOPE} = \frac{1}{30\mu\text{A}/5\text{V}} = \frac{5\text{V}}{30\mu\text{A}} = \frac{5\text{V}}{3 \cdot 10^{-5}\text{A}}$	167 k Ω	3

Assuming $I_B = 2\mu\text{A}$:

$g_m = \frac{I_C}{V_{th}} = \frac{\beta_F \cdot I_B}{V_{th}} = \frac{200\mu\text{A}}{25\text{mV}} = \frac{2 \cdot 10^{-4}}{25 \cdot 10^{-3}} = 0.8 \cdot 10^{-2}$	8 mS	3
$r_\pi = \beta_F / g_m = 100 / 8 \cdot 10^{-3}$	12.5 k Ω	3
$V_{CESAT\ min} = \sim 0.2\text{V}$ (from the graph)	0.2V	3

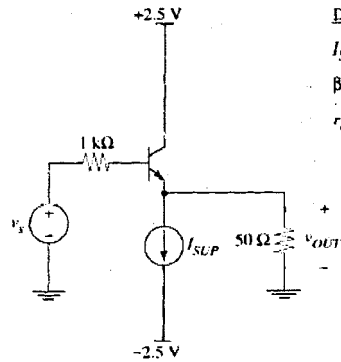Problem 3 of 4: Answer each question briefly and clearly. (16 points)



Device Data

$$I_S = 10^{-17} \text{ A}$$

$$\beta_F = \beta_o = 100$$

$$r_{ik} \rightarrow \infty$$

You are given the above Common Collector amplifier, with an ideal current supply source, and with values as shown above. Please do the following:


- 3.1 Calculate the output voltage swing, assuming that the I_{SUP} needs a minimum of 0.5Volts across it in order to operate properly, and $V_{CE\text{SATmin}}$ is 0.1V.

$V_{out\text{max}}$ = limited by BJT staying in F.A.M

$V_{out\text{min}}$ = limited by I_{sup} staying functional


Expression	Value
$V_{OUT\text{max}} = V^+ - V_{CE\text{SATmin}} = 2.5 - 0.1$	2.4V
$V_{OUT\text{min}} = V^- + V_{sup\text{min}} = -2.5 + 0.5$	-2.0V

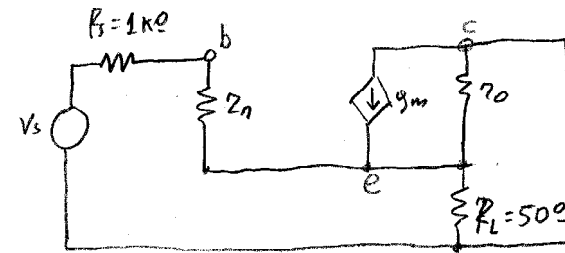- 3.2 Draw the equivalent small signal circuit of the common collector amplifier shown on the preceding page.



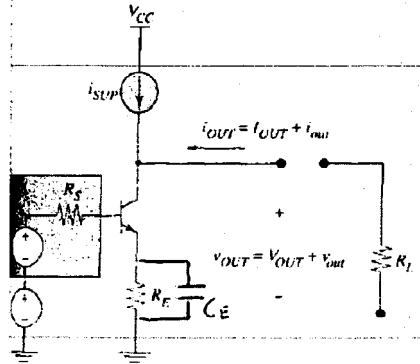Problem 4 of 4: Answer each question briefly and clearly. (20 points)

You are given a common emitter amplifier with R_E (degeneration emitter resistor), and an extra capacitor C_E connected across that resistor.



Recall that without the capacitance C_E , the formulae for this amplifier are:

$$G_m = \frac{g_m}{1 + g_m R_E} \quad R_{in} = r_{\pi} (1 + g_m R_E) \quad R_{out} = r_o [1 + g_m R_E] \parallel r_{oc}$$

4.1 Write expressions for R_{in} , R_{out} and G_m as a function of ω when C_E is present (neglect all the transistor small signal capacitances).

All I have to do is to replace R_E with $Z_E = R_E \parallel Z_{CE}$
 where $Z_{CE} = \frac{1}{j\omega C_E}$ so $Z_E = \frac{R_E / j\omega C_E}{R_E + \frac{1}{j\omega C_E}} = \frac{R_E}{1 + j\omega R_E C_E}$

expression

$G_m = \frac{g_m}{1 + g_m Z_E} = \frac{g_m (1 + j\omega R_E C_E)}{1 + j\omega R_E C_E + g_m R_E}$
$R_{in} = r_{\pi} (1 + g_m Z_E) = r_{\pi} \left(1 + \frac{g_m R_E}{1 + j\omega R_E C_E}\right)$
$R_{out} = r_o (1 + g_m Z_E) \parallel r_{oc} = r_o \left(1 + \frac{g_m R_E}{1 + j\omega R_E C_E}\right) \parallel r_{oc}$

4.2 Given the following values: $R_E = 10k\Omega$, $g_m = 0.9mS$, and $C_E = 100nF$, write the expression $G_m(\omega)$, restate it to show its pole(s) and zero(es) and plot it on a Bode Plot, whose vertical axis is in units of $20\log_{10}(|G_m/mS|)$. (These units are actually dBmS with reference of 1mS, i.e. a value of 1mS will show as 0db, 10mS will show as 20db, etc.)

$$G_m = \frac{g_m}{1 + g_m (R_E \parallel \frac{1}{j\omega C_E})} = \frac{g_m (1 + j\omega R_E C_E)}{1 + j\omega R_E C_E + g_m R_E} = \frac{g_m}{1 + g_m R_E} \left[\frac{1 + j\omega R_E C_E}{1 + j\omega R_E C_E + g_m R_E} \right]$$

$$Z_1 = \frac{1}{R_E C_E} \quad P_1 = \frac{1 + g_m R_E}{R_E C_E}$$

Expression	Value
$G_m(\omega) = \frac{g_m}{1 + g_m R_E} \left[\frac{1 + j\omega R_E C_E}{1 + j\omega R_E C_E + g_m R_E} \right]$	
G_m when ω very low = $\frac{g_m}{1 + g_m R_E}$	0.09mS \approx (-21dbmS)
G_m when ω very high = g_m	0.9mS \approx (-1dbmS)

