

<b>Name:</b>	<b>Student ID #:</b>
--------------	----------------------

**University of California at Berkeley  
Electrical Engineering and Computer Science  
EE105 Midterm Examination #1  
March 5, 2014  
(50 minutes)**

**CLOSED BOOK;** Two standard 8.5" x 11" sheet of notes (both sides) permitted

---

**IMPORTANT NOTES**

- Read each problem completely and thoroughly before beginning to work on it
  - Summarize all your answers in the boxes provided on these exam sheets
  - Show your work in the space provided so we can check your work and scan for partial credit
  - Remember to put your name in the space above
- 


<b>Problem #</b>	<b>Points Possible</b>	<b>Score</b>
1	20	
2	40	
3	40	
<b>Total</b>	100	

**1. True/False questions (20 points)**

For each of the following statements, state “T” for true or “F” for false. No explanation necessary. Correct answers are worth +2 point and incorrect answers yield -2 point. 0 points for unanswered questions. Your minimum total score on this problem is zero points.

(a) The input resistance of a common-base stage depends on the load resistance, $R_L$ . (Include $r_o$ )	
(b) Assuming a constant current source load, the voltage gain, $A_V$ , of a cascode common-emitter amplifier is twice as large as that of a common-emitter amplifier without cascode.	
(c) The Early voltage of a BJT can be increased by increasing the doping density in the base region.	
(d) In an abrupt-junction pn diode, the depletion region is greater on the more lightly doped side.	
(e) In an abrupt-junction pn diode, the potential drop is greater on the more lightly doped side.	
(f) In a common-emitter amplifier with a fixed load resistance, $R_L$ , properly biased for maximum signal swing at the output, the voltage gain is doubled as the power supply voltage, $V_{CC}$ , is doubled. Assume $V_{CE(sat)} = 0V$	
(g) Cascoding can be used to increase the small-signal output resistance of a common-emitter stage.	
(h) In a common-collector amplifier with an ideal current source connected from the emitter to ground, the small-signal input resistance is $r_\pi$ .	
(i) The combination of a degenerated common-emitter amplifier cascaded with a common-collector amplifier is suitable for current amplification.	
(j) Oski got his/her undergraduate degree at Stanford.	

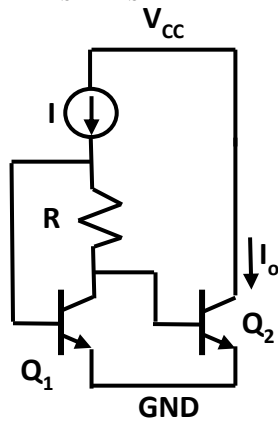2. **DC Bias Circuits (40 points).** In the circuit below, all devices operate in the forward-active region (FAR). In all cases, assume  $I_{S1} = I_{S2} = 10^{-17}$  A,  $I = 1$  mA and  $R = 100 \Omega$ .



(a) Find the value of  $I_o$  with  $\beta_1 = \beta_2 = \infty$ .

(a) $I_o =$	
-------------	--

(b) Find the value of  $I_O$  with  $\beta_1 = 100$  and  $\beta_2 = \infty$ .


(b) $I_O =$	
-------------	--

(c) Find the value of  $I_O$  with  $\beta_1 = \infty$  and  $\beta_2 = 100$ .

(c) $I_O =$	
-------------	--

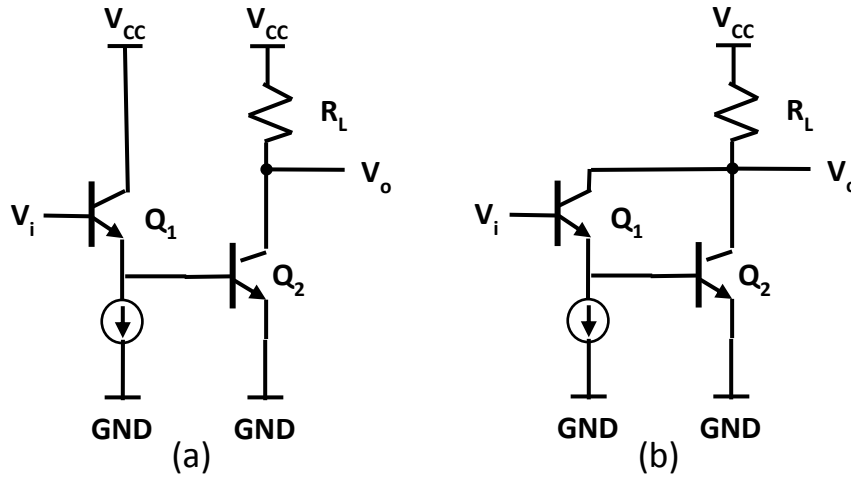3. (40 points) **Small-signal gain calculations.** In the circuits below, all devices operate in the forward-active region (FAR). In both cases, assume for DC  $V_{BE1} = V_{BE2}$ ,  $\beta_1 = \beta_2 = \infty$  and  $V_{A1} = V_{A2} = \infty$ .

Derive expressions for the small-signal voltage gains,  $A_V = V_O/V_i$  and compute the value of the ratio of the two gains,  $A_V(b)/A_V(a)$ .



Blank Work Sheet for Problem #3.

<b><math>V_o/V_i(a) =</math></b>	
<b><math>V_o/V_i(b) =</math></b>	
<b>Gain Ratio =</b>	