

UNIVERSITY OF CALIFORNIA  
College of Engineering  
Department of Electrical Engineering  
and Computer Sciences

Professor Oldham

Spring 1999

**EECS105 — Midterm 2**

**Thursday, 8 April 1999**

**Your name:** \_\_\_\_\_  
first last


**Your discussion TA:**  Allan Chang  Lily Tam

- This is a closed book exam, but you may use your 2 pages of notes.
- Please do all your work on the pages of this exam. Ask if you need extra paper.
- Full credit will be given only when you indicate the source of your answer, such as a table, graph, or calculation.
- Please write your name in the above space
- **SPECIAL NOTES:**
  1. **QUESTIONS:** Because it is disturbing to others in the exam when we pass by to answer questions, we must ask you to please limit your questions. Re-read the exam question and be sure that the data or equation you need is not already provided.
  2. **GRAPHS AND FORMULAS PROVIDED:** At the back of the exam are several pages of formulas, and data in the form of graphs. Please look for information here rather than asking a question.  
 Yes, I have looked these over. (Check box)
  3. **SOME PARTS OF THE EXAM ARE GRADED WITH NO PARTIAL CREDIT.** They are noted. You may wish to double check your answers on those parts.
  4. **DEVICE PROPERTIES:** Unless otherwise specified, assume n-channel transistors have  $V_{tn} = 0.5 \text{ V}$ ,  $\mu C_{ox} = 50 \mu\text{A}/\text{V}^2$ , and p-channel transistors have  $V_{tp} = -0.5 \text{ V}$ ,  $\mu C_{ox} = 25 \mu\text{A}/\text{V}^2$ . In small-signal calculations assume a lambda of 0.05 for both types. Assume bipolar transistors have beta of 100 and  $I_{ES}$  of 10-15 A (both npn and pnp transistors). In small-signal calculations assume the Early voltage is 20 V. You are to ignore lambda and Early voltage in biasing calculations.

	<b>SCORE</b>
Problem 1 (15 pts.)	
Problem 2 (15 pts.)	
Problem 3 (20 pts.)	
Problem 4 (25 pts.)	
Problem 5 (25 pts.)	
<b>TOTAL</b> (100 pts.)	

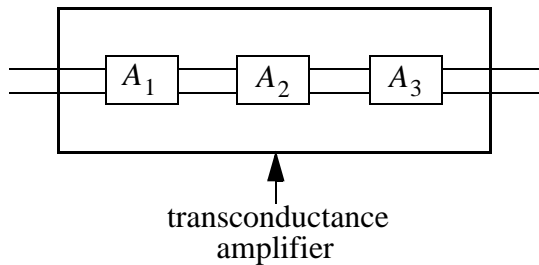**Problem 1 (15 pts., NO Partial Credit)**

You buy three voltage amplifiers with the following specifications:  $R_{in} = 10^5$ ,  $R_{out} = 10^5$ ,  $A = 10$ . You hook them up in series (i.e., output 1 = input 2, etc.), and place them in a black box. You are going to sell this box as a transconductance amplifier. What are the specifications of the transconductance amplifier?




$G_m =$  \_\_\_\_\_

$R_{in} =$  \_\_\_\_\_

$R_{out} =$  \_\_\_\_\_

**Problem 2 (15 points)**

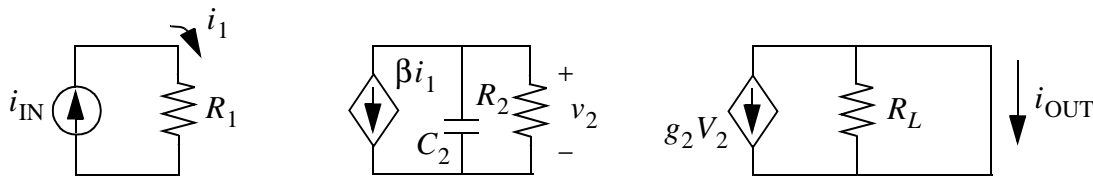a. Find the phasor representing the ratio of short-circuit output current to input current for the following circuit:



$A_1 \equiv \frac{I_{out}}{I_{in}} =$  \_\_\_\_\_

b. What is the general shape of the frequency response? Sketch magnitude vs frequency on dB scale provided on pg. 2.



**Problem 3 (20 points)**

---

Sketch the Bode plot on the graphs provided for the following function. Please show your work. (Neatness and clarity are important.) Only straight-line approximations are wanted.


$$\mathbf{F} = \frac{200j\omega \times \left(1 + \frac{j\omega}{200}\right)}{(2 + j\omega)(1 + 100j\omega)(1 + 0.0002j\omega)}$$

**Problem 3 Worksheet**

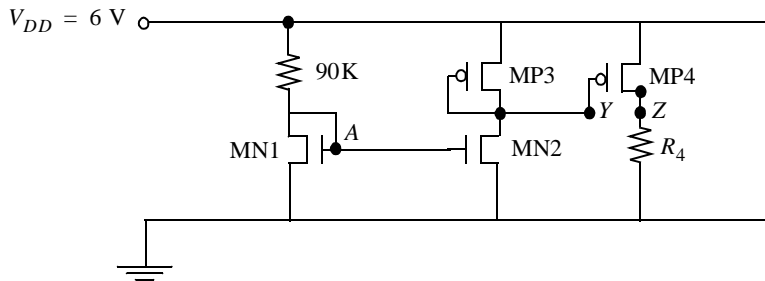**Problem 4 (25 points)**

In the circuit below, the reference node  $A$  is at a potential of 1.5 V. The  $W/L$  ratios for the n-channel devices are chosen as:  $(W/L)_2 = 2(W/L)_1$ . For the p-channel devices  $(W/L)_4 = 10(W/L)_3$ . Also,  $\left(\frac{W}{L}\right)_3 = 4\left(\frac{W}{L}\right)_1$ .

- Find  $W/L$  for n-channel device MN1 (to produce the required 1.5 V at node  $A$ ).
- Find the drain current of MN2 and the node voltage  $V_Y$ .
- Find the value of  $R_4$  needed to produce a voltage of 3 V at node  $Z$ .



$$(W/L)_1 = \underline{\hspace{2cm}}$$

$$I_{D2} = \underline{\hspace{2cm}}$$


$$V_Y = \underline{\hspace{2cm}}$$

$$R_4 = \underline{\hspace{2cm}}$$

**Problem 4 Worksheet**

**Problem 5 (25 points)**

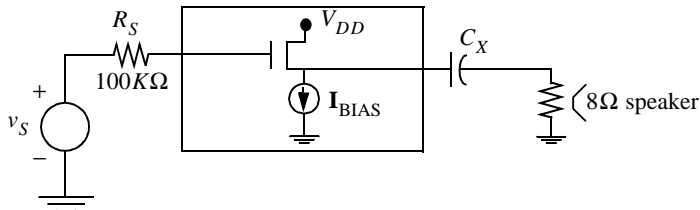- a) You are given one “power nMOS” transistor and need to construct a transistor circuit to drive an 8 ohm speaker through a coupling capacitor  $C_X$ . (The “power nMOS” transistor has a 1V threshold, a  $W/L$  of  $10^4$ , and  $\mu C_{ox} = 50\mu\text{A}/\text{V}^2$ . The source is connected to the body internally.) Your circuit should have a voltage gain of about 0.5 at higher frequencies (that is, at frequencies high enough that the impedance of  $C_X$  is negligible). (Note that  $C_X$  must be quite large to have a good low frequency response.) The bias current source you have available is essentially ideal (i.e., infinite parallel resistance). You choose the circuit below.



- a) Draw the small-signal model for this amplifier in the box opposite, ignoring all internal device capacitances and parasitic resistances.

- b) Solve for the “mid-band” gain  $A_M$  (formula in terms of circuit and device parameters). The mid-band gain is a real quantity. It is the gain at frequencies high enough that coupling capacitors act as shorts, yet the frequency is low enough that capacitors to ground are negligible.

$$A_M = \underline{\hspace{2cm}}$$


- c) Find the mid-band gain of the circuit  $A_M$  at a bias current of  $I_{BIAS} = 10 \text{ mA}$ .

$$A_M = \underline{\hspace{2cm}}$$



**Problem 5 Answer and Worksheet**

**a.**

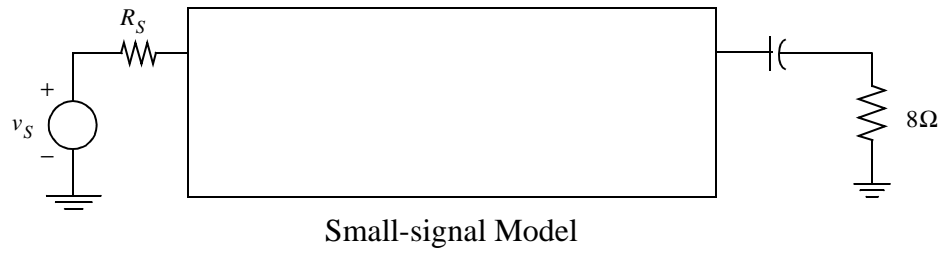

**b.**

**c.**

## Appendix A:

## Appendix B:

## Appendix C: Formulas

$$(EQ 2.7) \quad n_o \cdot p_o = n_i^2(T)$$

$$(EQ 2.34) \quad v_{dn} = -\mu_n E$$

$$(EQ 2.55) \quad J_n = J_n^{dr} + J_n^{diff} = qn\mu_n E + qD_n \frac{dn}{dx}$$

$$(EQ 2.56) \quad J_p = J_p^{dr} + J_p^{diff} = qp\mu_p E - qD_p \frac{dp}{dx}$$

$$(EQ 2.67) \quad R = \left( \frac{1}{qN_d\mu_{nt}} \right) \left( \frac{L}{W} \right) = R_{\square} \left( \frac{L}{W} \right) = R_{\square} N_{\square}$$

$$(EQ 3.1) \quad \frac{dE}{dx} = \frac{\rho}{\epsilon}$$

$$(EQ 3.4) \quad E(x) = -\frac{d\phi(x)}{dx}$$

$$(EQ 3.56) \quad X_{do} = x_{no} + x_{po} = \sqrt{\left( \frac{2\epsilon_s\phi_B}{q} \right) \left( \frac{1}{N_a} + \frac{1}{N_d} \right)}$$

$$(EQ 3.88) \quad V_{FB} = -(\phi_{n+} - \phi_p)$$

$$(EQ 3.89) \quad Q_G(V_{GB} = V_{FB}) = 0$$

$$(EQ 3.95) \quad V_{Tn} = V_{FB} - 2\phi_p + \frac{1}{C_{ox}} \sqrt{2q\epsilon_s N_a (-2\phi_p)}$$

$$(EQ 4.18) \quad V_{DS_{SAT}} = V_{GS} - V_{Tn}$$

$$(EQ 4.19) \quad I_{D_{SAT}} = \left( \frac{W}{2L} \right) \mu_n C_{ox} (V_{GS} - V_{Tn})^2 = \left( \frac{W}{2L} \right) \mu_n C_{ox} V_{DS_{SAT}}^2$$

$$I_D = 0 \text{ A} \quad (V_{GS} \leq V_{Tn})$$

$$(EQ 4.59) \quad I_D = (W/L) \mu_n C_{ox} [V_{GS} - V_{Tn} - (V_{DS}/2)] (1 + \lambda_n V_{DS}) V_{DS} \quad (V_{GS} \geq V_{Tn}, V_{DS} \leq V_{GS} - V_{Tn})$$

$$I_{D_{SAT}} = (W/2L) \mu_n C_{ox} (V_{GS} - V_{Tn})^2 (1 + \lambda_n V_{DS}) \quad (V_{GS} \geq V_{Tn}, V_{DS} \geq V_{GS} - V_{Tn})$$

$$(EQ 4.60) \quad V_{Tn} = V_{TO_n} + \gamma_n (\sqrt{-V_{BS} - 2\phi_p} - \sqrt{-2\phi_p})$$

$$(EQ 4.67) \quad g_m \equiv \left( \frac{W}{L} \right) \mu_n C_{ox} (V_{GS} - V_{Tn}) = \sqrt{2 \left( \frac{W}{L} \right) \mu_n C_{ox} I_D}$$

$$\text{(EQ 6.10)} \quad \phi_B = V_{th} \ln\left(\frac{p_{po}}{p_{no}}\right) \text{ and } \phi_B = V_{th} \ln\left(\frac{n_{no}}{n_{po}}\right)$$

$$\text{(EQ 6.22)} \quad p_n(x_n) = p_{no} \cdot e^{V_D/V_{th}} \text{ and } n_p(-x_p) = n_{po} e^{V_D/V_{th}}$$

$$\text{(EQ 6.30)} \quad J = qn_i^2 \left( \frac{D_p}{N_d W_n} + \frac{D_n}{N_a W_p} \right) (e^{V_D/V_{th}} - 1)$$

$$\text{(EQ 6.31)} \quad I_D = qn_i^2 A \left( \frac{D_p}{N_d W_n} + \frac{D_n}{N_a W_p} \right) (e^{V_D/V_{th}} - 1) = I_o (e^{V_D/V_{th}} - 1)$$

$$\text{(EQ 6.48)} \quad C_j = \frac{C_{jo}}{\sqrt{1 - V_D/\phi_B}}$$

### Appendix D: Values

$$q = 1.6 \times 10^{-19} \text{ C}$$

$$V_t = kT/q = 0.026 \text{ V}$$

$$\epsilon_0 = 8.85 \times 10^{-14} \text{ F/cm}$$

$$\epsilon_{\text{oxide}} = 3.9\epsilon_0$$

$$\epsilon_{Si} = 11.7\epsilon_0$$

### Appendix E: SIA unit multipliers:

$$M = 10^6$$

$$K = 10^3$$

$$m = 10^{-3}$$

$$\mu = 10^{-6}$$

$$n = 10^{-9}$$

$$p = 10^{-12}$$

$$f = 10^{-15}$$