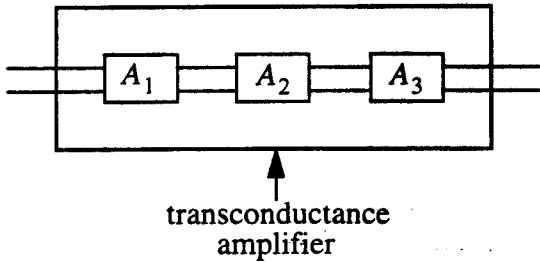


Problem 1 (15 pts., NO Partial Credit)

You buy three voltage amplifiers with the following specifications: $R_{in} = 10^5$, $R_{out} = 10^5$, $A = 10$. You hook them up in series (i.e., output 1 = input 2, etc.), and place them in a black box. You are going to sell this box as a transconductance amplifier. What are the specifications of the transconductance amplifier?



$$\frac{V_{out}}{V_1} = A_1 A_2 A_3 \times \frac{R_{o2}}{R_{i1} + R_{o2}} \times \frac{R_{o3}}{R_{o2} + R_{i3}}$$


$$G_m = \frac{2.5 \times 10^{-3} \text{ S}}{10^5 \text{ } \Omega}$$

$$R_{in} = 10^5 \text{ } \Omega$$

$$R_{out} = 10^5 \text{ } \Omega$$

Problem 2 (15 points)

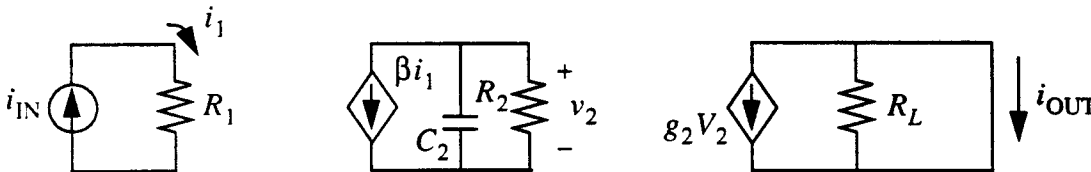a. Find the phasor representing the ratio of short-circuit output current to input current for the following circuit:




$$\tilde{I}_{out} = -g_2 \tilde{V}_2 = -g_2 \left(\frac{-\beta i_1 \times \frac{1}{j\omega C_2}}{\frac{1}{j\omega C_2} + R_2} \right) R_2$$


$$A_1 \equiv \frac{I_{out}}{I_{in}} = \frac{\beta g_2 R_2}{1 + j\omega R_2 C_2}$$

b. What is the general shape of the frequency response? Sketch magnitude vs frequency on dB scale provided on pg. 2.

SINGLE POLE LOW-PASS

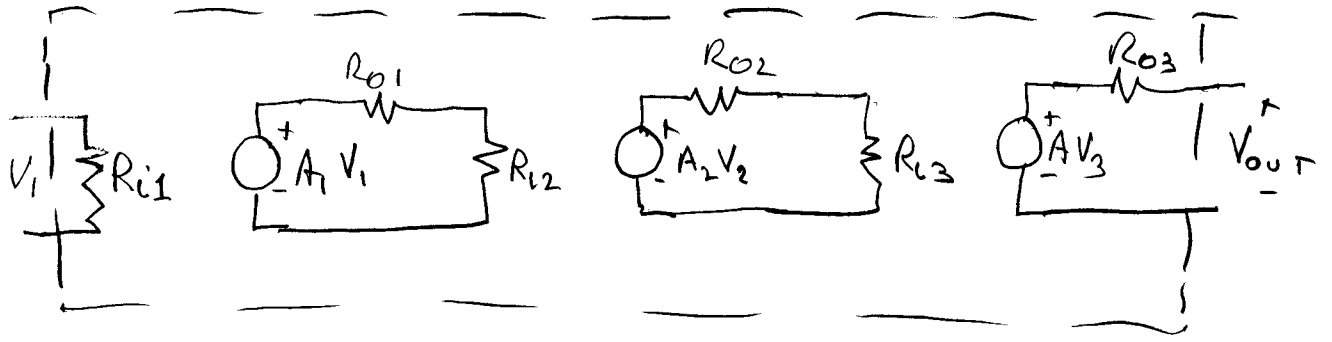


||

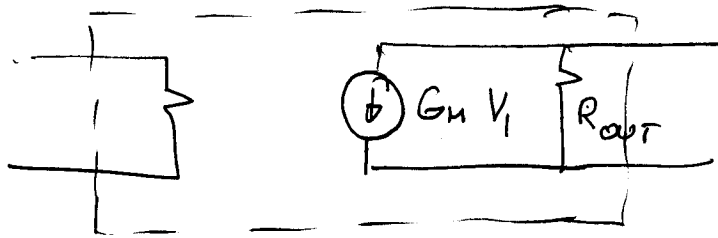

$$V_{out} = -G_N R_{out} V_1$$
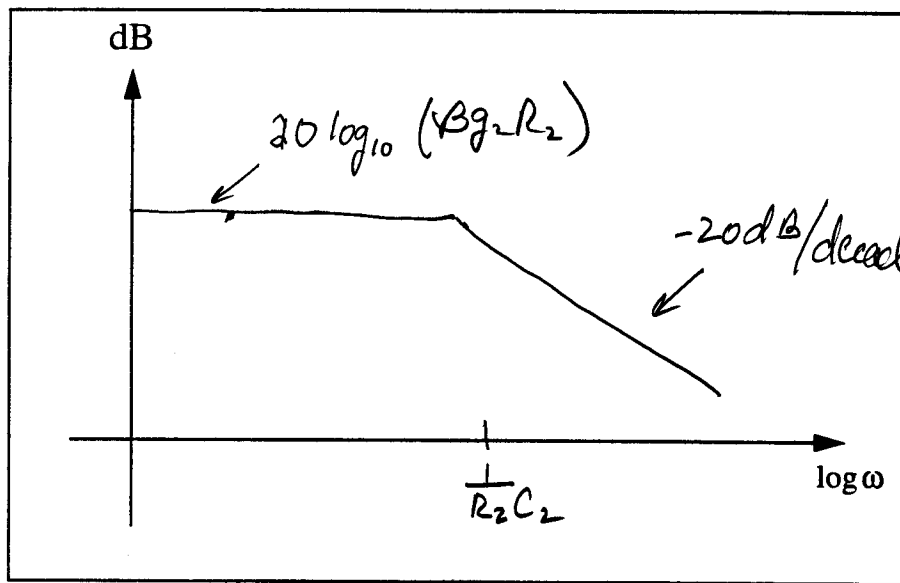
$$G_N = \underbrace{-A_1 A_2 A_3}_{-10^3} \times \underbrace{\frac{R_{i2}}{R_{o1} + R_{i2}} \times \frac{R_{i3}}{R_{o2} + R_{i3}}}_{\frac{1}{4}} \times \underbrace{\frac{1}{R_{o3}}}_{10^{-5}}$$



Problem 3 (20 points)

Sketch the Bode plot on the graphs provided for the following function. Please show your work. (Neatness and clarity are important.) Only straight-line approximations are wanted.


$$F = \frac{200j\omega \times \left(1 + \frac{j\omega}{200}\right)}{(2 + j\omega)(1 + 100j\omega)(1 + 0.0002j\omega)}$$
$$= \frac{\left(\frac{j\omega}{.01}\right) \left(1 + \frac{j\omega}{200}\right)}{\left(1 + \frac{j\omega}{2}\right) \left(1 + \frac{j\omega}{.01}\right) \left(1 + \frac{j\omega}{5 \times 10^3}\right)}$$

$$|F| = 0 \text{ dB @ } \omega = .01$$


$$\text{For } \omega \ll .01, \phi = 90^\circ, |F| = -20 \text{ dB/decade}$$

For $\omega > .01$ ADD PHASE & dB CONTRIBUTIONS:

Bode Plot

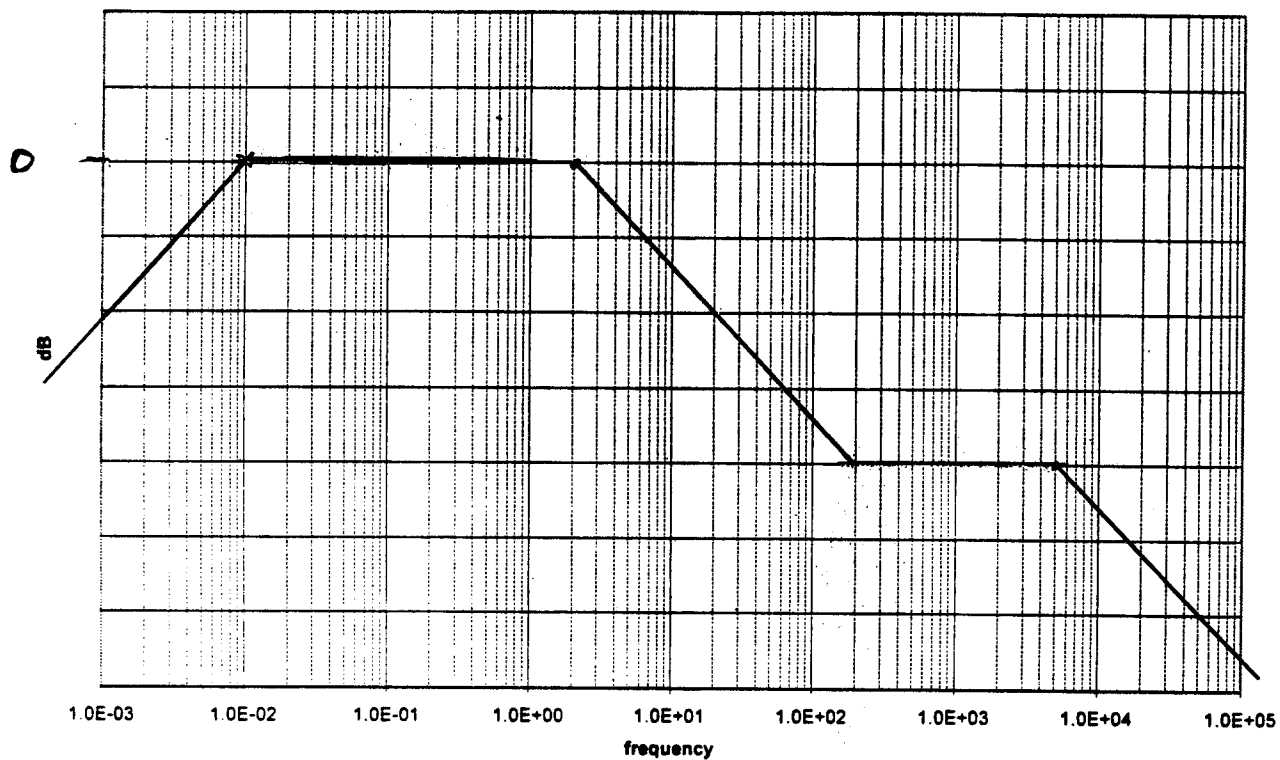


Bode Phase

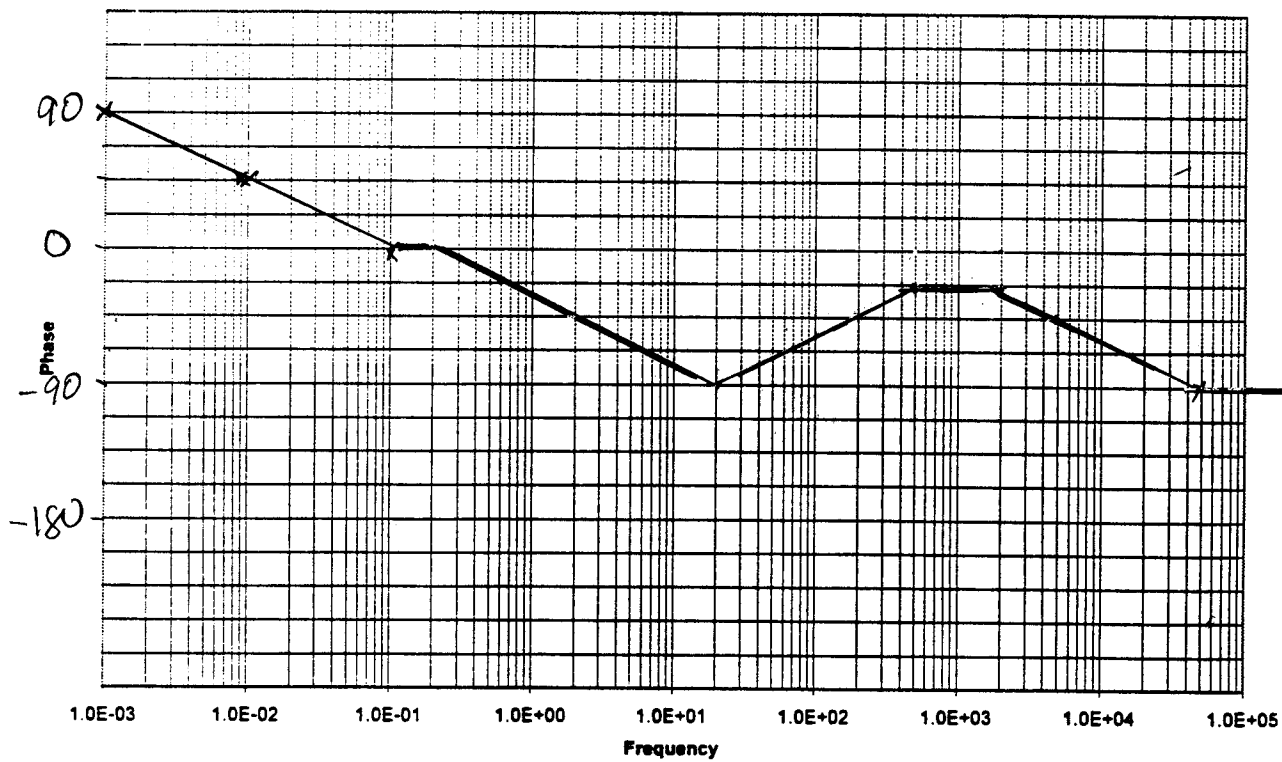

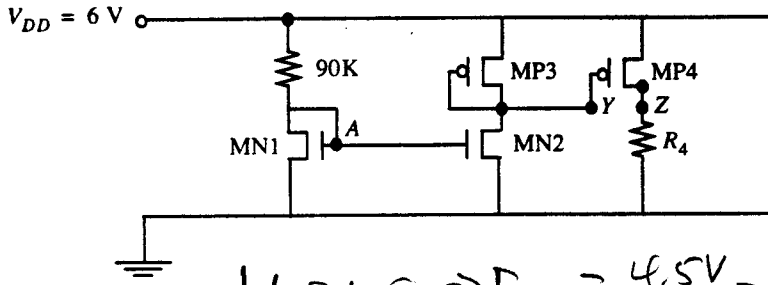Problem 4 (25 points)

In the circuit below, the reference node A is at a potential of 1.5 V. The W/L ratios for the n-channel devices are chosen as: $(W/L)_2 = 2(W/L)_1$. For the p-channel devices $(W/L)_4 = 10(W/L)_3$. Also, $\left(\frac{W}{L}\right)_3 = 4\left(\frac{W}{L}\right)_1$.

- Find W/L for n-channel device MN1 (to produce the required 1.5 V at node A).
- Find the drain current of MN2 and the node voltage V_Y .
- Find the value of R_4 needed to produce a voltage of 3 V at node Z.



$$V_A = 1.5 \Rightarrow I_{D1} = \frac{4.5V}{90K} = 50\mu A$$

$$(W/L)_1 = \underline{2}$$

$$50\mu A = \underbrace{\mu C_{ox}}_{50} \frac{W}{2L} \underbrace{(V_{GS} - V_T)}_1^2 \Rightarrow \frac{W}{L} = 2 \quad \textcircled{1}$$

$$\frac{W}{L}_2 = 2 \frac{W}{L}_1 \Rightarrow 100\mu A$$

$$I_{D2} = \underline{100\mu A}$$

$$100\mu A = \underbrace{\mu C_{ox}}_{25} \underbrace{\frac{W}{2L}}_4 \underbrace{\left(\frac{W}{L}\right)_3}_{3} \underbrace{(V_{GS} - V_T)}_1^2 \Rightarrow |V_{GS}| = 1.5V \quad \textcircled{3}$$


$$V_Y = \underline{4.5V}$$

$$I_{D4} = I_{D3} \times 10 = 1mA$$

$$R_4 = \underline{3K}$$

Problem 5 (25 points)

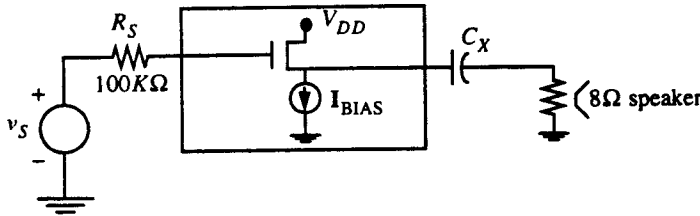- a) You are given one “power nMOS” transistor and need to construct a transistor circuit to drive an 8 ohm speaker through a coupling capacitor C_X . (The “power nMOS” transistor has a 1V threshold, a W/L of 10^4 , and $\mu C_{ox} = 50\mu A/V^2$. The source is connected to the body internally.) Your circuit should have a voltage gain of about 0.5 at higher frequencies (that is, at frequencies high enough that the impedance of C_X is negligible). (Note that C_X must be quite large to have a good low frequency response.) The bias current source you have available is essentially ideal (i.e., infinite parallel resistance). You choose the circuit below.



- a) Draw the small-signal model for this amplifier in the box opposite, ignoring all internal device capacitances and parasitic resistances.

ENTERED DEVICE S-S MODEL OK
ON CORRECT AMP MODEL OK

- b) Solve for the “mid-band” gain A_M (formula in terms of circuit and device parameters). The mid-band gain is a real quantity. It is the gain at frequencies high enough that coupling capacitors act as shorts, yet the frequency is low enough that capacitors to ground are negligible.

FOR S-S MODEL $V_{out} = g_m(V_g - V_0) r_{o||R_L}$
 ie $V_0 = V_g$ $\frac{g_m r_{o||R_L}}{1 + g_m r_{o||R_L}}$

$$A_M = \frac{g_m r_{o||R_L}}{1 + g_m r_{o||R_L}}$$

- c) Find the mid-band gain of the circuit A_M at a bias current of $I_{BIAS} = 10$ mA.

@ 10mA $r_o = \frac{1}{\lambda I} = 2k$

$V_{GS} - V_T = 0.2V$


$g_m = \frac{2I_D}{V_{GS} - V_T} = 0.1$

$r_{o||R_L} \approx R_L$

$A_M = \underline{0.44}$

Problem 5 Answer and Worksheet

a.

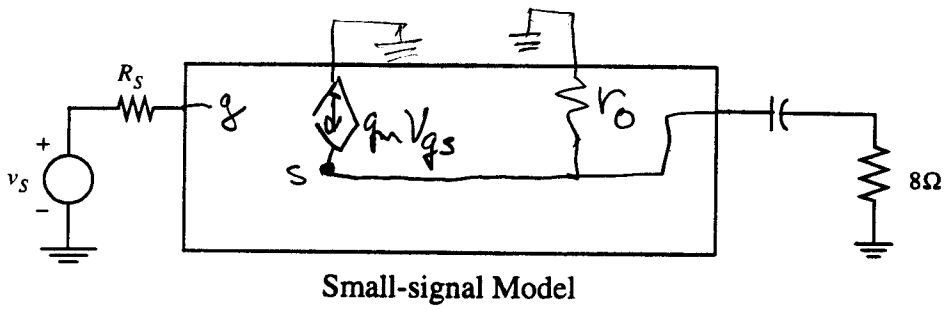

b.



c.
$$I_D = \mu C_{ox} \frac{W}{2L} (V_{GS} - V_T)^2 \Rightarrow V_{GS} - V_T = 0.2$$