

EECS 190

FALL 1996

NAME SOLUTIONS

MIDTERM #2

$$k_n' = k_p' = 10^{-4} \text{ A/V}^2$$

$$Y_n = Y_p = 0$$

$$\lambda_n = \lambda_p = .01$$

$$V_{Tn} = V_{Tp} = 1 \text{ V.}$$

$$C_{gd} = 1 \text{ fF}$$

$$C_{db} = 10 \text{ fF}$$

$$C_{gs} = 100 \text{ fF}$$

$$C_{gb} = 5 \text{ fF}$$

$$C_{sb} = 10 \text{ fF}$$


SHOW YOUR WORK!

- 1 a 2.1V.
 b 220 MΩ
 c .45 m²
 d 203 KRAD/sec.

X

- 2 a 3700
 b 400 RAD/SEC
 c 9.4 MRAD/SEC
4 a SHUNT - SERIES
 b .01
 c X
 d 25
 e 2.5 MΩ

Problem 1)

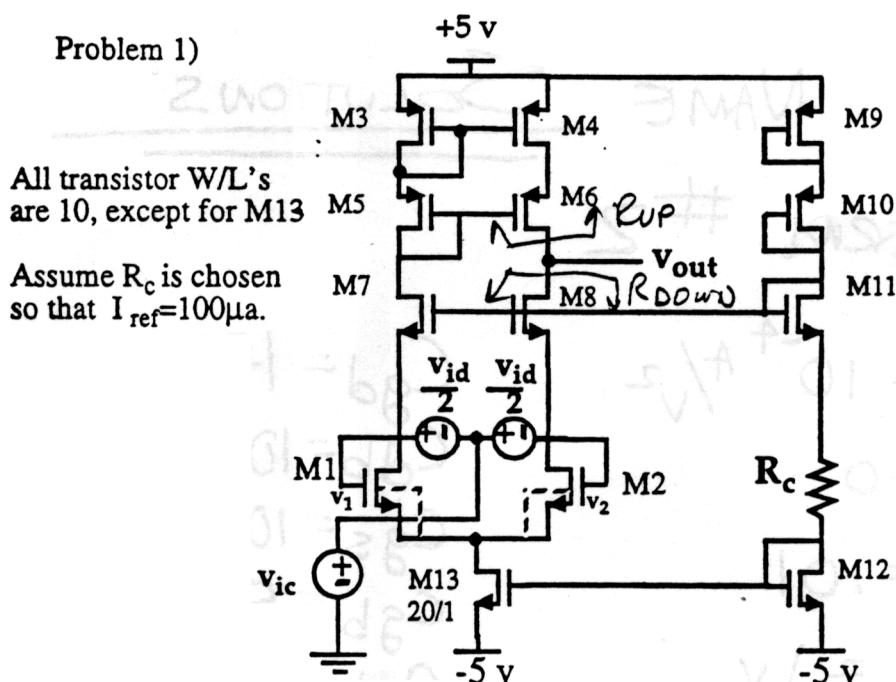

All transistor W/L's are 10, except for M13

Assume R_c is chosen so that $I_{ref} = 100\mu A$.

$$I_{ref}$$

$$\begin{aligned} V_{dsat} &= \left(\frac{2 I_{DS}}{2' W/L} \right)^{1/2} \\ &= \left(\frac{2 \cdot 10^{-4}}{10^{-4} \cdot 10} \right)^{1/2} \\ &= 45 V. \end{aligned}$$

a) What is the DC voltage at v_{out} ? $2.1 V$

$$2V_+ - 2V_{DSAT} = 2.9$$

$$5 - 2.9 = 2.1 V$$

b) What is R_{out} (seen at v_{out})? 2.25×10^6

$$R_{op} = R_o (1 + g_m R_o) = 10^6 \cdot 45 \times 10^{-3} \cdot 10^6 = 4.5 \times 10^9 \Omega$$

$$R_{DOWNS} = R_{op}$$

$$R_{out} = R_{op} || R_{DOWNS}$$

c) What is $G_m = i_{out}/v_{id}$ (i_{out} is the current out if v_{out} is grounded)? $45 mS$

$$G_m = g_m = 45 mS$$


c) What is the -3db freq of the gain, v_{out}/v_{id} ? $2.03 \times 10^5 \text{ rad/sec}$

AT THE V_{out} NODE

$$C_{out} = C_{db6} + C_{gd6} + C_{db8} + C_{gd8} = 22 fF$$


$$\begin{aligned} W_{3dB} &= \frac{1}{2\pi \cdot 2.03 \times 10^5 \cdot 2.2 \times 10^6} \\ &= 2.03 \times 10^5 \text{ rad/sec} \end{aligned}$$

Problem 2)

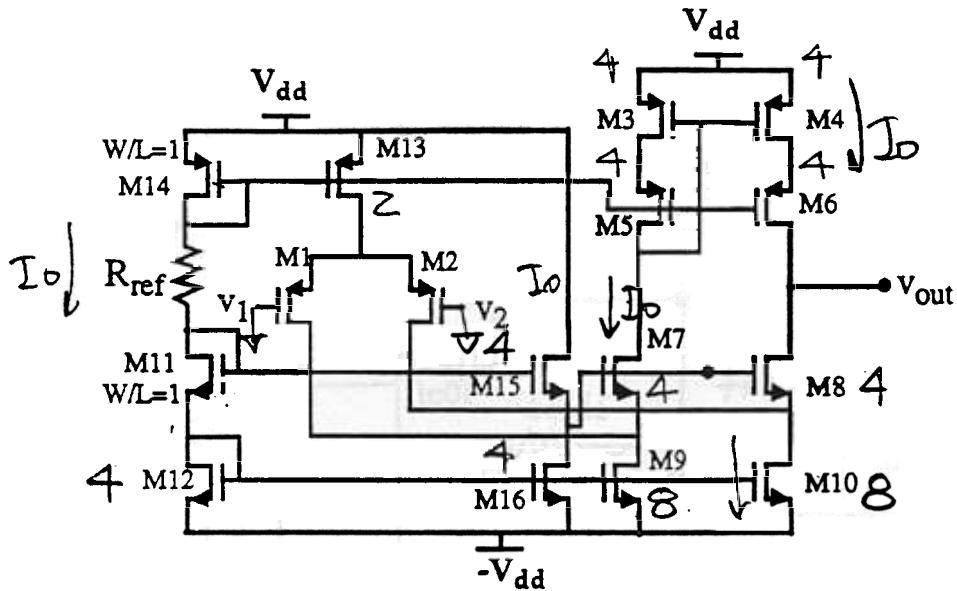

Choose the values of the W/L's for all the transistors (except for M11 and M14 which are 1), so that the currents in all transistors have the same value, I_o , except for M9, M10 and M13 which are twice that value or $2I_o$. Also, choose those sizes so that M3, M4, M9 and M10 are biased at the edge of saturation. $\lambda=0$ for this problem.

M1	<u>Any value</u>
M2	<u>Same as M1</u>
M3	<u>4</u>
M4	<u>4</u>
M5	<u>4</u>
M6	<u>4</u>
M7	<u>4</u>
M8	<u>4</u>
M9	<u>8</u>
M10	<u>8</u>
M12	<u>4</u>
M13	<u>2</u>
M15	<u>4</u>
M16	<u>4</u>

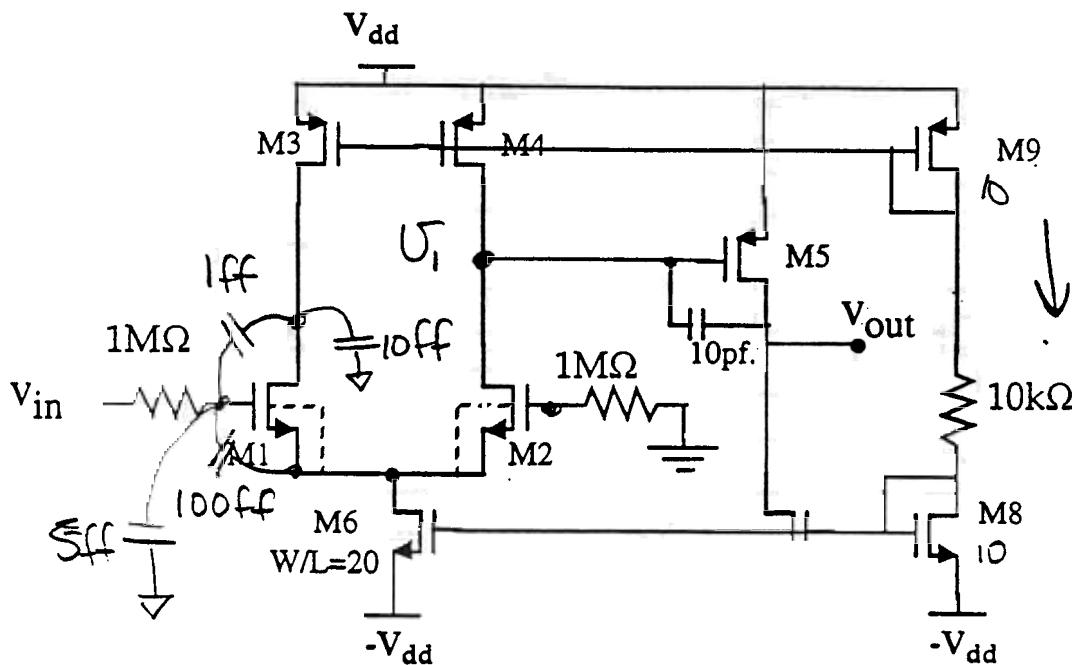

a) What is the DC gain $\frac{3.7 \times 10^3}{}$

$$\frac{U_{\text{out}}}{U_{\text{in}}} = \left(\underbrace{\frac{g_m}{2} \left(\frac{r_o}{2} \right)}_{\text{1ST STAGE}} \right) \left(\underbrace{\frac{g_m}{2} \frac{r_o}{2}}_{\text{2ND STAGE}} \right) = \frac{(g_m r_o)^2}{8}$$

For parts b) & c) USE $g_m = 10^{-3}$ & $r_o = 1 \text{ M}\Omega$ FOR

b) What is the lowest frequency pole $\frac{400 \text{ RAD/SEC}}{\text{ALL TRANSISTORS}}$
 $M5: C_{gs} = 10 \text{ pF}$


$$w_1 = \frac{1}{r_o/2 \cdot 10^{-11} \cdot \frac{g_m r_o}{2}} = 400 \text{ RAD/SEC}$$

CHECK MILLER ON M2 $\left(\frac{g_m r_o}{4} \right) \text{ff} = 172 \text{ ff} \quad \underline{\text{WITH SAME } r_o}$

c) What is next lowest frequency pole $\frac{9.4 \times 10^6 \text{ RAD/SEC}}{\text{}}$


SINCE M5 AND THE 10PF CAP LOOK LIKE $\frac{1}{j\omega}$
 at $W \gg w_1$, THE GAIN AT U_1 IS SMALL
 THIS NO MILLER MULT. THE EFFECTIVE
 CAPACITANCE AT THE GATE OF M2 IS
 $\approx C_{gs2} + C_{gd2} + C_{gb2} \approx 106 \text{ fF}$. $w_2 = \frac{1}{106 \cdot 1.06 \times 10^{-13}} \text{ RAD/SEC}$

Problem 4)

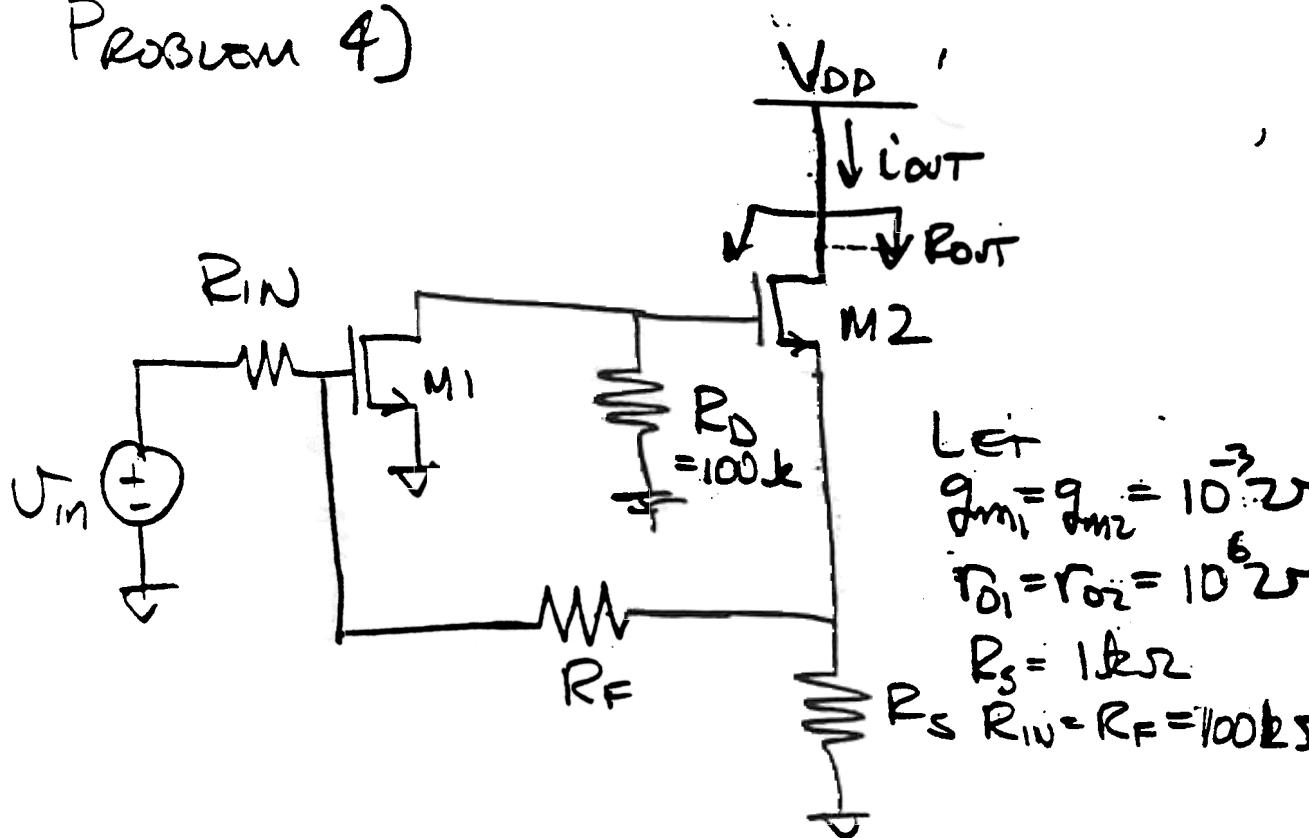

a) WHAT KIND OF FEEDBACK? SUBTRACTS


WHAT IS f ? $\frac{R_S}{R_F + R_S}$

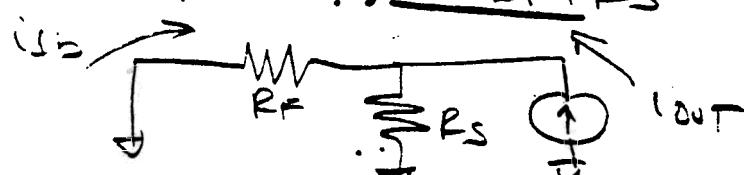

DRAW THE BASIC AMPLIFIER, WITH LOADING
OF THE FEEDBACK NETWORK, ON THE
NEXT PAGE.

d) CALCULATE THE GAIN OF THE BASIC
AMPLIFIER WITH LOADING.

WHAT IS R_{OUT} ?

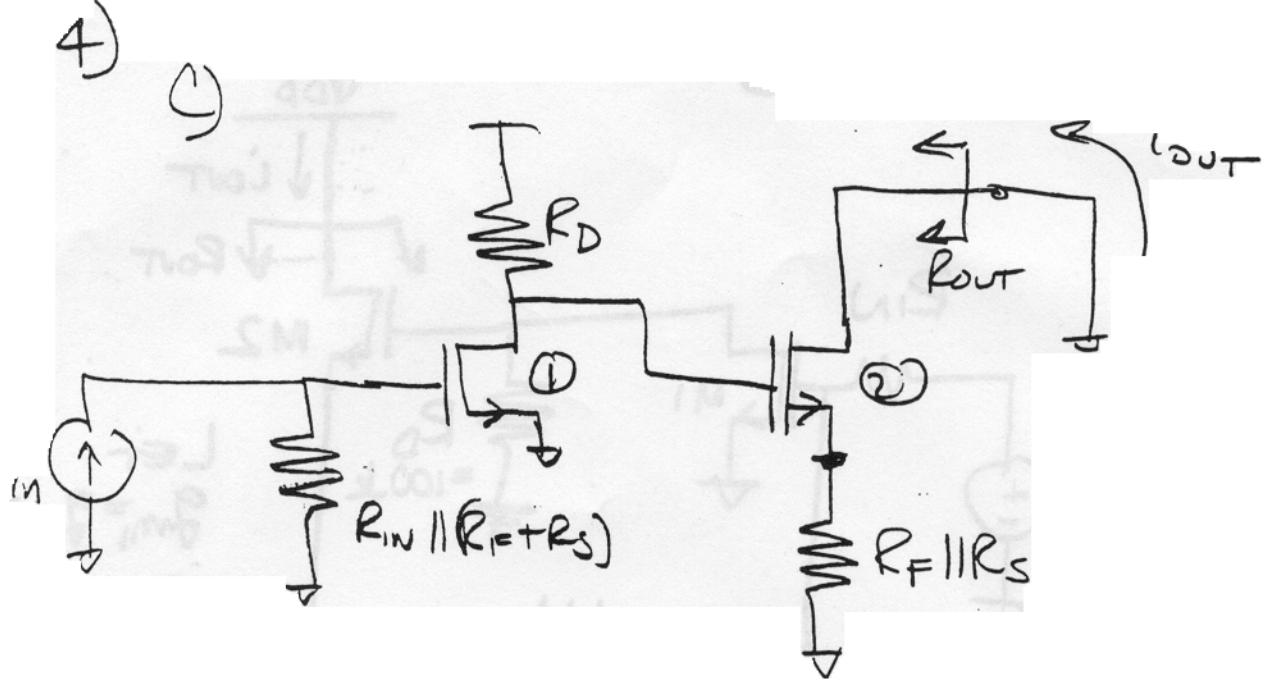

d)

$$A_v = g_m 1 \left[R_{in} / (R_F + R_S) \right] (R_D || r_e) \left[\frac{g_m 2}{1 + g_m 2 (R_F || R_S)} \right]$$

$$= \frac{10^{-3} (50\Omega) 91k}{10^{-3} (1\Omega)} = 2300$$

e)

r_{out}'

$$\frac{(R_F || R_S) + r_o 2 (1 + g_m 2 (R_F || R_S))}{2 \times 10^6 \Omega}$$

$$R_{out} = (1 + T') r_{out}' = (1 + 23) (2 \times 10^6) \Omega$$

$$= 48 \times 10^6 \Omega$$

$$T \text{ af} = 23$$