

NAME SOLUTIONS

MIDTERM #2

FALL, 1997

avg. 46
s.d. 10

EECS 140
R.W. BRODERSEN


SHOW YOUR WORK.
GIVE ANSWERS THAT ARE ACCURATE
TO WITHIN $\pm 10\%$.

PLEASE COPY YOUR ANSWERS ONTO
THIS PAGE.

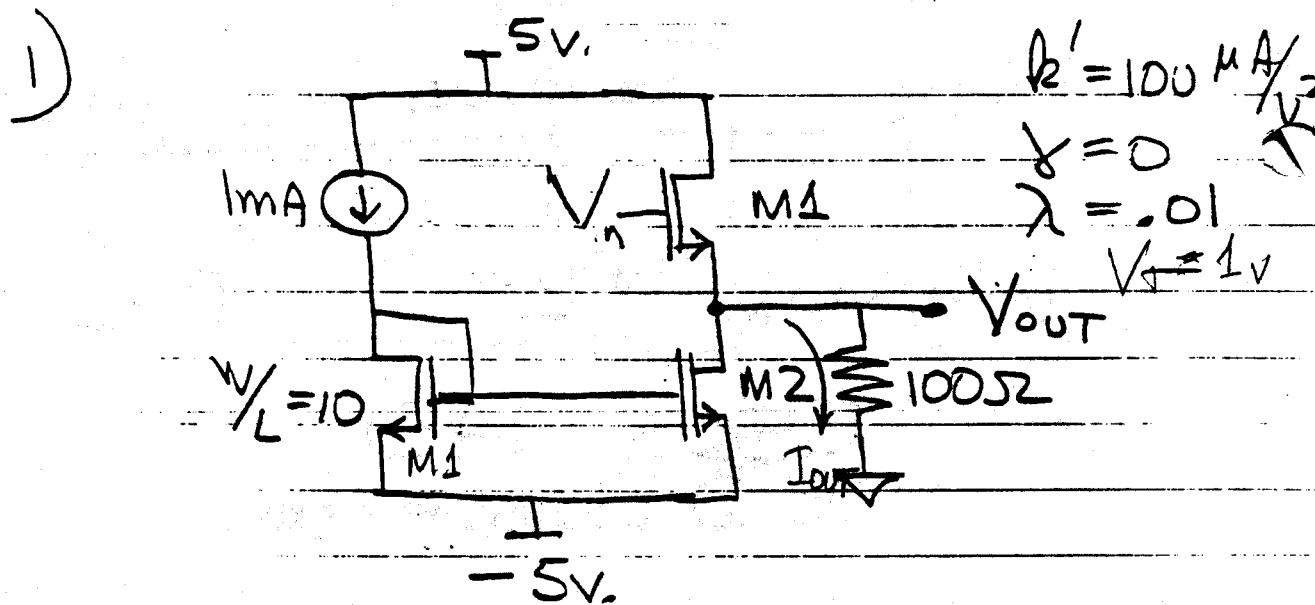- (5) a) $(W/L)_{M2} = 300$ (5) 3a) SHUNT-SERIES
(5) b) $(W/L)_{M1} = 1200$ (5) b) $f \frac{R_4}{R_2 + R_4}$
(5) c) 15% (5) c) $f = \frac{R_1}{R_1 + R_2 + R_4} \frac{g_m R_3}{1 + g_m R_3 R_4}$
T' $\frac{R_6}{R_1 + R_2 + R_4 + R_5}$
(5) 2a) $V_{OUT, MAX} = 4.55V$ (5) d) $V_{OUT} / V_{IN} = \frac{R_5}{R_1} \left(1 + \frac{R_2}{R_4}\right)$
(5) $V_{OUT, MIN} = 1.1V$ (5)
(5) b) GAIN 450
(10) c) $\omega_{P1} = 50 \text{ MRAD/SEC}$
(5) $\omega_{P2} = 286 \text{ MRAD/SEC}$

65 TOTAL

ALL PARTS COUNT 5 POINTS
EXCEPT 2C WHICH COUNTS 15 (FOR
BOTH PARTS)



$$-5V < V_{in} < +5V$$

a) WHAT IS THE W/L OF $M2$ SO THAT $V_{out, MIN} = -3V$.

$$I_{DS, M2} = -I_{OUT} = -\frac{-3V}{100\Omega} = 30mA$$

$$\left(\frac{W}{L}\right)_{M2} = \frac{30mA}{1mA} \left(\frac{W}{L}\right)_{M1} = 300$$

b) WHAT IS THE W/L OF $M1$ SO THAT $V_{out, MAX} = +3V$

$$I_{DS1} = 60mA = \frac{k'}{2} \left(\frac{W}{L}\right)_1 (5 - 1 - 3)^2$$

$$= \frac{10^{-4}}{2} \left(\frac{W}{L}\right)_1 \left(\frac{W}{L}\right)_1 = 1200$$

c) WHAT IS THE EFFICIENCY OF THIS CIRCUIT WITH YOUR VALUES FOR $M1$ & $M2$

CLASS A


$$Power_{SUPPLY} = 1mA \cdot 10V + 30mA \cdot 10V = 310mW$$

$$Power_{LOAD} = \frac{V_{P,PK}^2}{2R} = \frac{9}{2 \cdot 100} = 45mW$$

$$EFFICIENCY = \frac{45}{310} = 15\%$$

2)

T

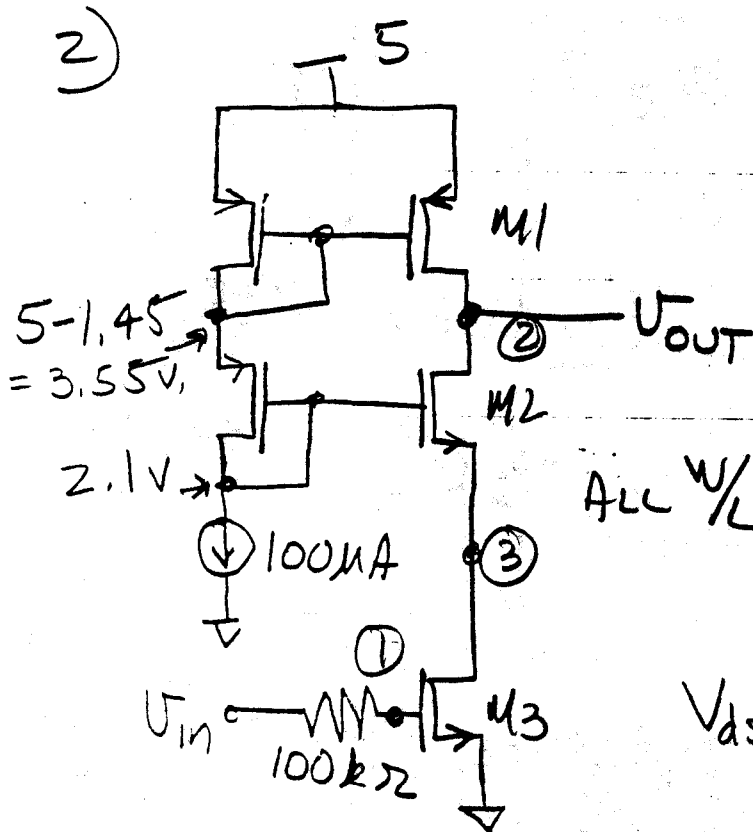

$\lambda = .01$
 $k' = 100 \mu A/V^2$
 $\gamma = 0$
 $V_{TP} = -1V$
 $V_{TN} = +1V$
 $C_{GS} = 20 fF$
 $C_{GB} = C_{GD} = C_{DB} = C_{SB} = 5$

ALL W/L 'S = 10

$$V_{dsat} = \left(\frac{2I_{D5}}{\mu W/L} \right)^{1/2} = \left(\frac{2 \times 10^{-4}}{10^{-4} \cdot 10} \right)^{1/2} = .45V$$

a) WHAT IS THE MAXIMUM & MINIMUM VOLTAGE OVER WHICH THE GAIN IS HIGH?

$V_{out, MAX} = \underline{4.55V}$ $V_{out, MIN} = \underline{1.1V}$
 $3.55 + V_T = 4.55V$ $2.1 - V_T = 1.1V$

b) WHAT IS THE MAXIMUM GAIN? $\underline{450}$


$g_m = (2k' \frac{W}{L} I_{D5})^{1/2} = (2 \cdot 10^{-4} \cdot 10 \cdot 10^{-4})^{1/2} = .45 \times 10^{-3}$
 $A = -g_m R_{out}$
 $R_{out} = r_{o, m1} \parallel r_{o2} (1 + g_{m2} r_{o3}) \approx r_{o, m1} = \frac{1}{\lambda I_{D5}} = \frac{1}{.01 \times 10^{-4}} = 1M\Omega$

c) WHAT ARE THE 2 LOWEST POLES? $\omega_{p1} \underline{50MRAD/sec}$

① $R = 100k\Omega$
 $C = C_{GS3} + C_{GB3} + 2C_{GD} = 35 \times 10^{-15}$
 $\omega_{p1} = \frac{1}{RC} = \frac{1}{35 \times 10^{-10}} = \underline{MRAD}$
 GAIN OF -1 TO NODE 3
 $R_{m2} \approx \frac{1}{g_m}$


② $R = R_{out} = 1M\Omega$
 $C = C_{GD1} + C_{DB1} + C_{GD2} + C_{DB2} = 20 fF$
 $\omega_{p2} = \frac{1}{RC} = \frac{1}{1M\Omega \cdot 20 \times 10^{-15}} = \underline{50MRAD}$

3)

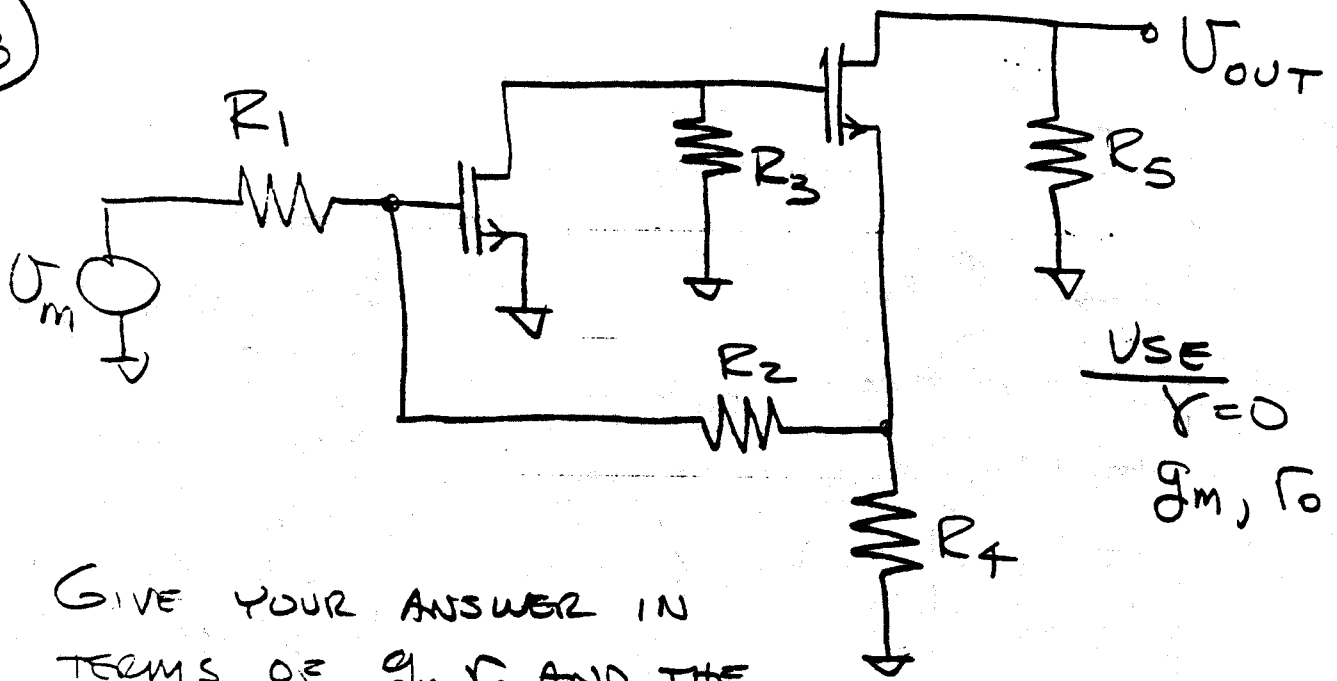


GIVE YOUR ANSWER IN TERMS OF g_m, r_o AND THE RESISTORS.

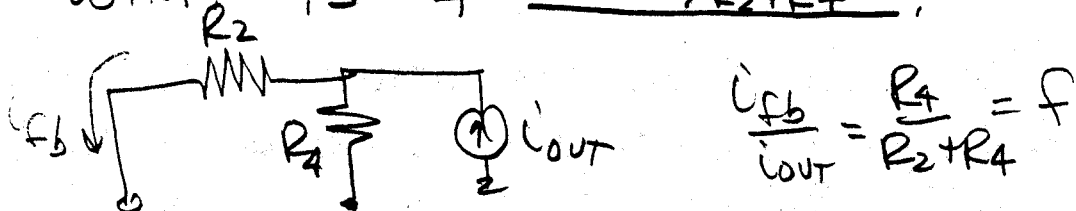- a) WHAT KIND OF FEEDBACK? SHUNT-SERIES
 b) WHAT IS $f = \frac{R_4}{R_2 + R_4}$?



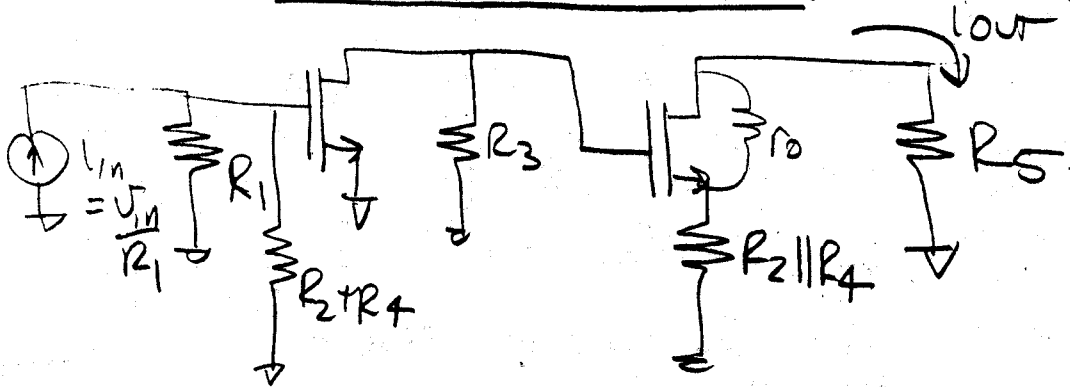- c) WHAT IS THE LOOP GAIN WITH LOADING, T'

$$T' = R_1 \parallel (R_2 + R_4) g_m (r_o) \left(\frac{g_m}{1 + g_m (R_2 \parallel R_4)} \right) \left(\frac{r_o}{r_o + R_2 \parallel R_4 + R_5} \right) \cdot f$$



- d) WHAT IS THE GAIN, $\frac{U_{OUT}}{U_{IN}}$ IF T' IS ASSUMED LARGE $\frac{R_5}{R_1} (1 + R_2/R_4)$

$$\frac{I_{OUT}}{I_{in}} = \frac{1}{f} = 1 + \frac{R_2}{R_4}$$

$$U_{OUT} = I_{OUT} R_5$$

$$U_{IN} = I_{in} R_1$$

$$\frac{U_{OUT}}{U_{IN}} = \frac{R_5}{R_1} \left(\frac{I_{OUT}}{I_{in}} \right)$$