

EECS 140
MIDTERM 2
FALL 1998

Name: SOLUTIONS

Assume the $W/L = 10$ for all transistors unless otherwise indicated.

$$V_{TN} = V_{TP} = 0.5V$$

$$k_n' = k_p' = 100\mu A/V^2$$

$$\gamma_n = \gamma_p = 0$$

$$\lambda_n = \lambda_p = 0.01$$

$$C_{GS} = 100\text{ff}$$

$$C_{GD} = C_{GB} = C_{DB} = C_{SB} = 10\text{ff}$$

$$(4) \text{ 1a. } V_{\max} = \underline{3.08}$$

$$(4) \text{ b. } V_{\min} = \underline{3.65}$$

$$(4) \text{ c. } \underline{47\%}$$

$$(10) \text{ 6. } \omega_c = \underline{450} \text{ RAD/SEC}$$

$$(4) \text{ 7. } A_{dm} = \underline{21}$$

$$(4) \text{ } A_{cm} = \underline{.5}$$

$$(4) \text{ } v_{out}/v_{in} = \underline{-10, 2}$$

$$(10) \text{ 2. } W/L = \underline{.43}$$

$$(5) \text{ 3. } R_{out} = \underline{37M\Omega}$$

$$(5) \text{ } v_{out}/v_{in} = \underline{3.4 \times 10^3}$$

$$(5) \text{ 4. } \omega_{p1} = \underline{1.9k} \text{ RAD/SEC}$$


$$(5) \text{ } \omega_{p2} = \underline{110k} \text{ RAD/SEC}$$

SHOW YOUR WORK!!

$$(4) \text{ 5a. } \underline{\text{SHUNT-SHUNT}}$$

$$(4) \text{ b. } f = \underline{-1 \times 10^{-4}}$$

$$(4) \text{ c. } T = \underline{210}$$

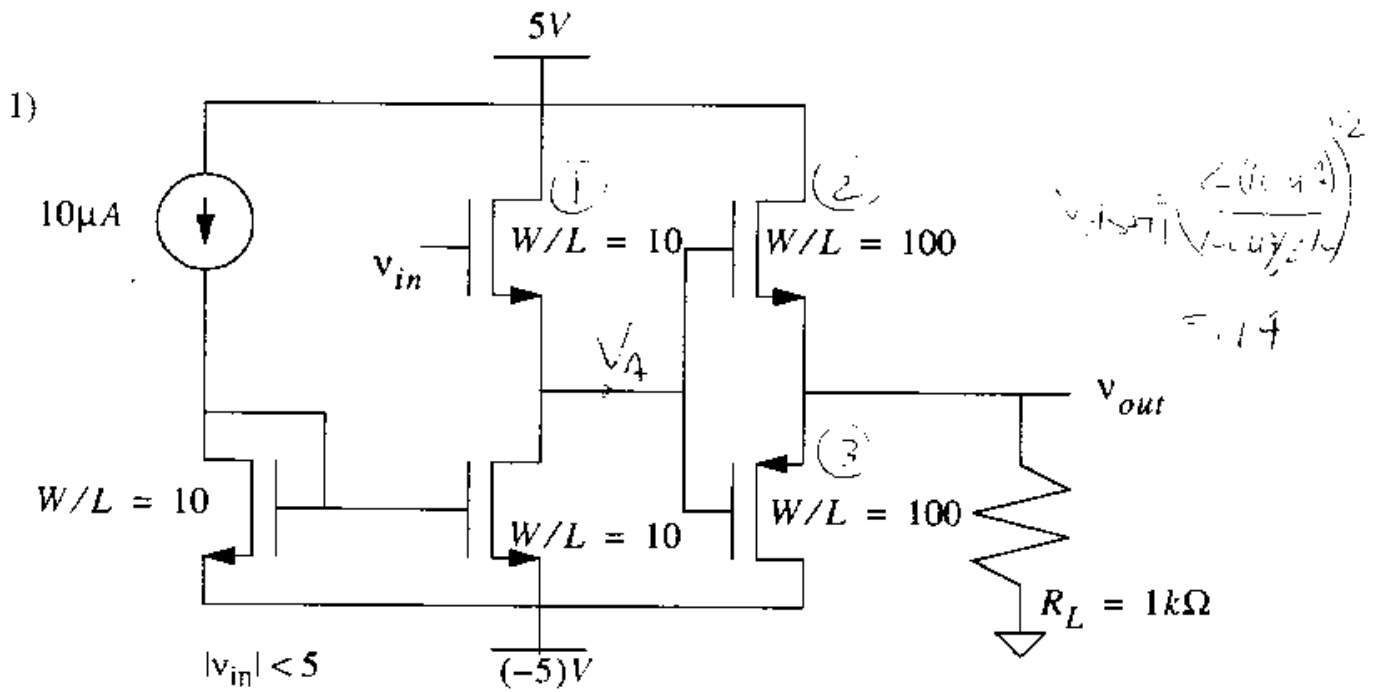

1. What is the maximum voltage at V_{out} ? 3.08V

$$V_{out,max} = V_{in,max} - (V_T + V_{DSAT1}) - (V_{DSAT2})$$

$$= 5 - 0.5 - 0.14 - 0.5$$

$$= 3.86 - \left(\frac{2V_{out}/k_L}{\mu_n \cdot 100}\right)^{1/2}$$

$$V_{out}^2 - 7.9V_{out} + 14.9 = 0 \quad V_{out} = 4.04, 3.08$$

2. What is the minimum voltage? -3.65

Assume MOS IN LINEAR, $V_A = -5$

$$V_{out} = -5 + V_T + V_{DSAT3} = -4.5 + \left(\frac{2V_{out}/k_L}{\mu_n \cdot 100}\right)^{1/2}$$

$$V_{out}^2 + 9.2V_{out} + 20.7 = 0$$

$$V_{out} = -3.65, -5.55$$

3. What is the efficiency of this circuit? 47%


max $S_{in} = 3.08V$

$$P_{supply} = 2(10V \cdot 10\mu A) + (2)5 \frac{1}{\pi} \frac{V_o}{R_L}$$

$$= 4 \times 10^{-4} + 10 \frac{3.08}{\pi} = 10mW$$

$$P_L = \frac{V_o^2}{2R_L} = \frac{1}{2} \frac{(3.08)^2}{1k} = 4.7mW \quad \eta = \frac{P_L}{P_{supply}} = 47\%$$

2)

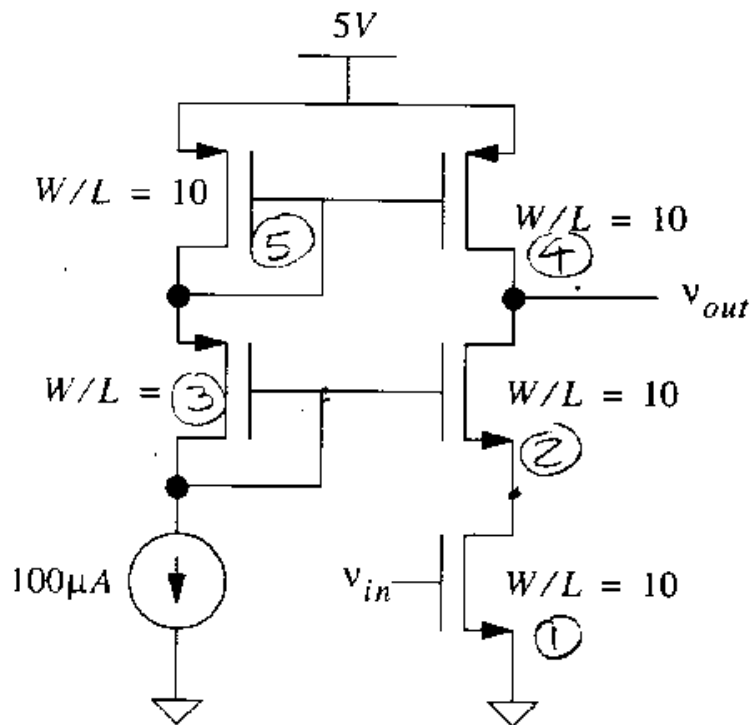

What is the value of the missing W/L so that the output swing is maximum? $W/L = \underline{.43}$

$$V_{i_{SAT}}(100\mu A) = \left(\frac{2(100)\mu A}{100 \mu A / V^2 \cdot 10} \right)^{1/2} = .45V$$


$$5 = V_{dsat1} + (V_{dsat2} + V_{T2}) + (V_{dsat3} + V_{T3}) + (V_{dsat5} + V_{T5})$$

$$V_{dsat3} = 5 - (1.5) - 3(.45) = 2.15$$

$$= \left(\frac{2(100)}{100 W/L} \right)^{1/2}$$

$$\underline{\underline{\left(\frac{W}{L} \right)_3 = .43}}$$

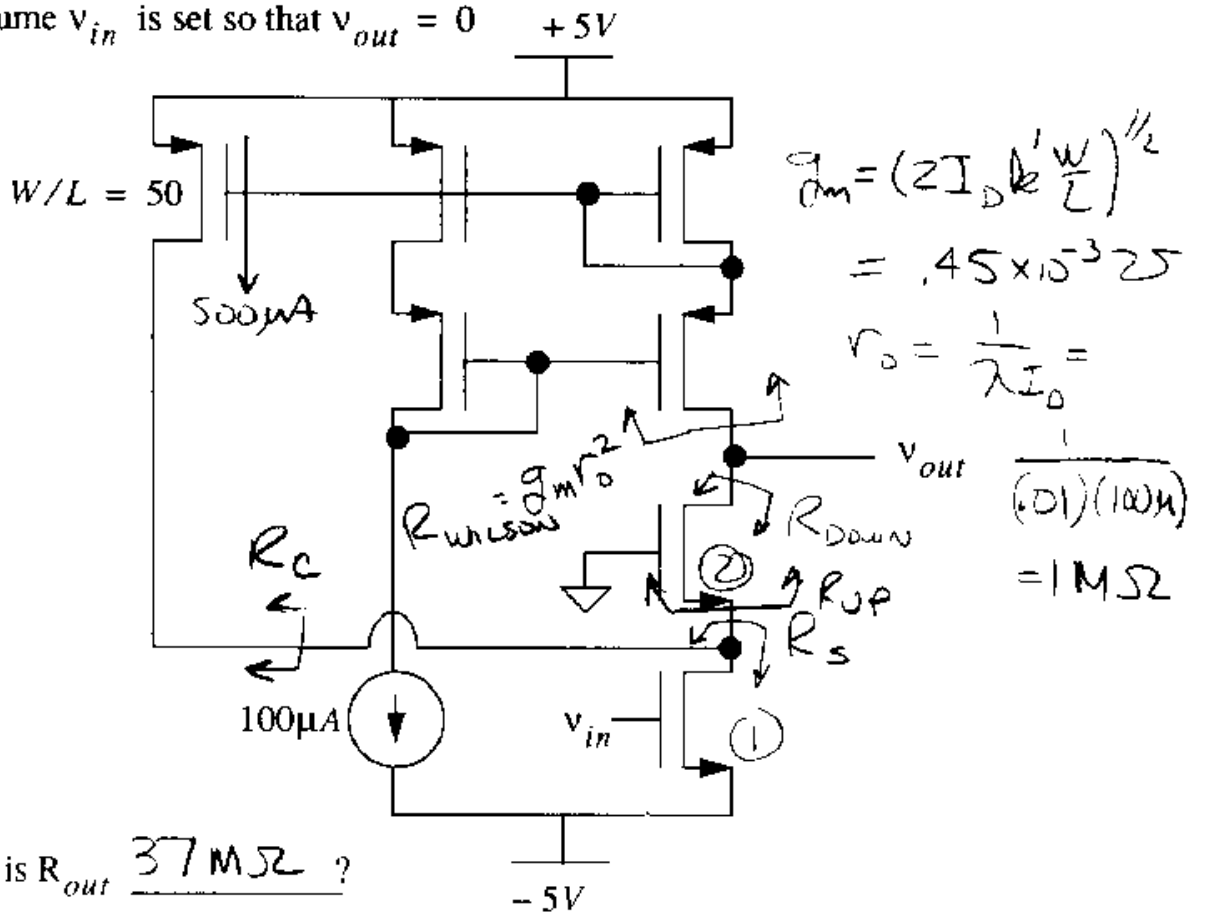3) Assume v_{in} is set so that $v_{out} = 0$



a) What is R_{out} 37 MΩ ?

$$R_{WILSON} = .45 \times 10^{-3} \times 10^{12} = 450 \text{ M}\Omega$$


$$R_s = \frac{1}{\lambda_5 (100\mu\text{A})} \parallel \frac{1}{\lambda_6 (100\mu\text{A})} = 91 \text{ k}\Omega$$

$$R_{DOWN} = (g_{m2} R_s) r_{o2} = .45 \times 10^{-3} \times 91 \times 10^3 \times 10^6 = 41 \text{ M}\Omega$$

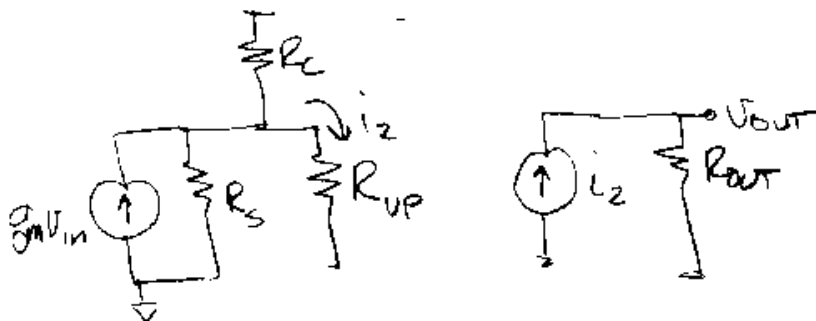
b) What is $\frac{v_{out}}{v_{in}}$ 3400 ?

$$R_{out} = R_{WILSON} \parallel R_{DOWN} = 450 \text{ M}\Omega \parallel 41 \text{ M}\Omega$$

$$\frac{v_{out}}{v_{in}} = g_m \frac{R_s \parallel R_c}{R_{UP} \parallel R_s \parallel R_c} R_{out} = (2 \times 600\mu\text{A} \times 100\mu\text{A} / 2 \cdot 10)^{1/2} \left(\frac{1}{\frac{1}{11} + 1} \right) 37 \text{ M}\Omega = 3.4 \times 10^3$$



4)

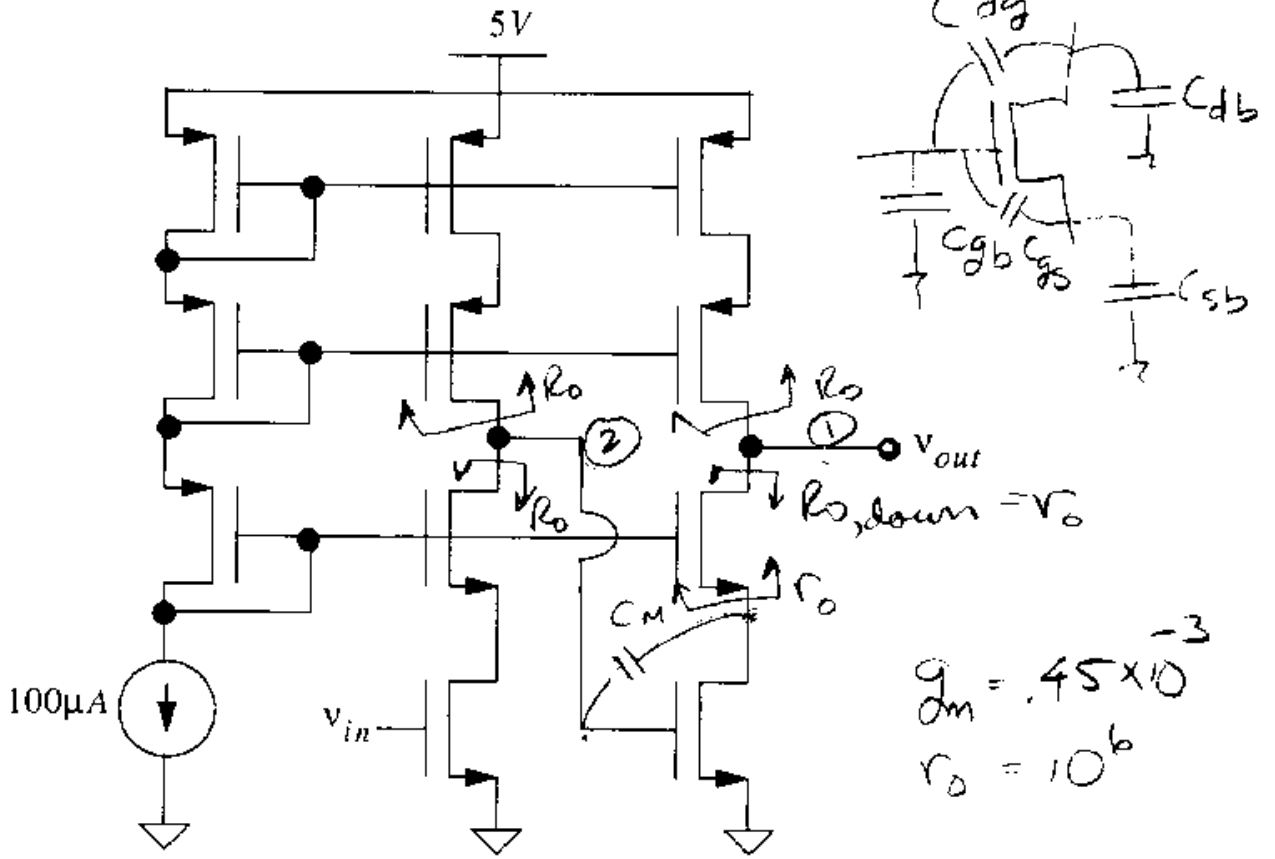

What are the 2 lowest poles of this circuit?

$$\omega_{p1} = 110 \text{ RAD/SEC}$$

$$\omega_{p2} = 1.9 \text{ RAD/SEC}$$

$$C_1 = 2(C_{db} + C_{gd}) = 40 \text{ fF}$$

$$R_o = g_m r_o^2 = .45 \times 10^{-3} \cdot 10^{12}$$

$$= 450 \text{ MS}$$

ASSUMING ALL
IN SATURATION

$$\omega_{p1} = \frac{1}{(R_o/2) C_1} = \frac{1}{225 \times 10^6 \cdot 40 \times 10^{-15}}$$

$$= 110 \text{ RAD/SEC}$$

$$\omega_{p2} = \frac{1}{(225 \times 10^6 \times (40 \text{ fF} + 2250 \text{ fF} + 10 \text{ fF} + 100 \text{ fF}))}$$

$$= \frac{1}{2400 \text{ fF}}$$

$$= 1.9 \text{ RAD/SEC}$$

$$\omega_{p2} = \frac{1}{R_o/2 (C_1 + C_m + C_{gb} + C_{gs})}$$

$$C_m = g_m (r_o || r_o) C_{gd} =$$

$$= .45 \times 10^{-3} \times 10^6 / 2 \times 10^{-15}$$

$$= 2250 \text{ fF}$$

