

EECS 140
MIDTERM 2
FALL 1998

Name : SOLUTIONS

Assume the W/L = 10 for all transistors unless otherwise indicated.

$$V_{TN} = V_{TP} = 0.5V$$

$$k_n' = k_p' = 100 \mu A/V^2$$

$$\gamma_n = \gamma_p = 0$$

$$\lambda_n = \lambda_p = 0.01$$

$$C_{GS} = 100fF$$

$$C_{GD} = C_{GB} = C_{DB} = C_{SB} = 10fF$$

$$(4) 1a. V_{max} = \underline{3.08}$$

$$(10) 6. w_c = \underline{450} \text{ rad/sec}$$

$$(4) b. V_{min} = \underline{3.65}$$

$$(4) c. \underline{47\%}$$

$$(4) 7. A_{dm} = \underline{21}$$

$$(4) A_{cm} = \underline{.5}$$

$$(10) 2. W/L = \underline{.43}$$

$$(4) v_{out}/v_{in} = \underline{-10, 2}$$

$$(5) 3. R_{out} = \underline{37M\Omega}$$

$$(5) v_{out}/v_{in} = \underline{3.4 \times 10^3}$$

$$(5) 4. \omega_{p1} = \underline{1.9} \text{ rad/sec}$$


$$(5) \omega_{p2} = \underline{110} \text{ rad/sec}$$

SHOW YOUR WORK!!

$$(4) 5a. SHUNT-SHUNT$$

$$(4) b. f = \underline{-1 \times 10^{-4}}$$

$$(4) c. T' = \underline{210}$$

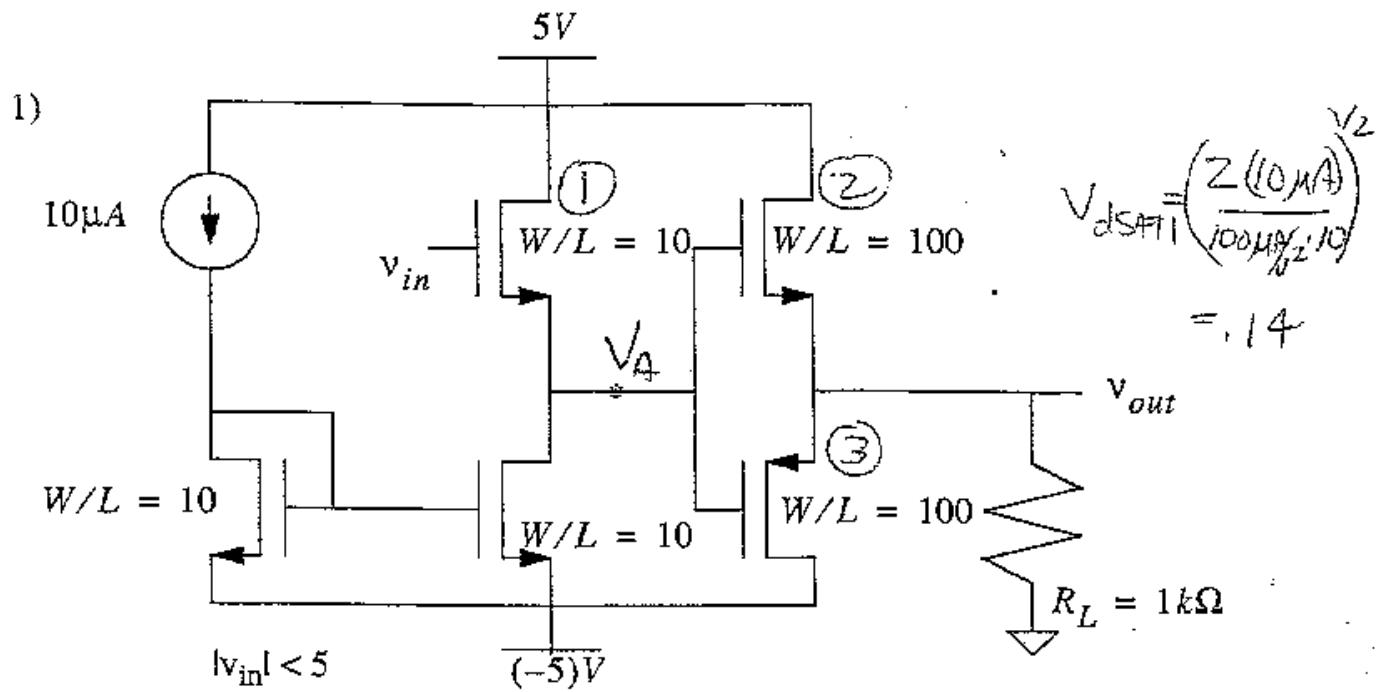

1. What is the maximum voltage at V_{out} ? 3.08V.

$$\begin{aligned} V_{out, max} &= V_{in, max} - (V_T + V_{dsAT1}) - (V_T + V_{dsAT2}) \\ &= 5 - .5 - .14 - .5 - V_{dsAT2} \\ &= 3.86 - \left(\frac{2 V_{out}/R_L}{k \cdot 100} \right)^{1/2} \end{aligned}$$

$$V_{out}^2 - 7.9 V_{out} + 14.9 = 0 \quad V_{out} = 4.84, 3.08$$

2. What is the minimum voltage? -3.65

Assume M3 in linear, $V_A = -5$

$$V_{out} = -5 + V_T + V_{dsAT3} = -4.5 + \left(\frac{2 V_{out}/R_L}{k \cdot 100} \right)^{1/2}$$

$$V_{out}^2 + 9.2 V_{out} + 20.7 = 0$$

$$V_{out} = -3.65, -5.55$$

3. What is the efficiency of this circuit? 47% Push Pull

~~MAX SWING~~ $\pm 3.08V$.


$\overbrace{V_o}^{V_o}$

$$(2) 5 \frac{1}{\pi} \frac{V_o}{R_L}$$

$$= 4 \times 10^{-4} + 10^{-2} \frac{3.08}{\pi} = 10 \text{ mW}$$

$$P_L = \frac{V_o^2}{2R_L} = \frac{1}{2} \frac{(3.08)^2}{10^3} = 4.7 \text{ mW} \quad \eta = \frac{P_L}{P_{SUPPLY}} = 47\%$$

2)

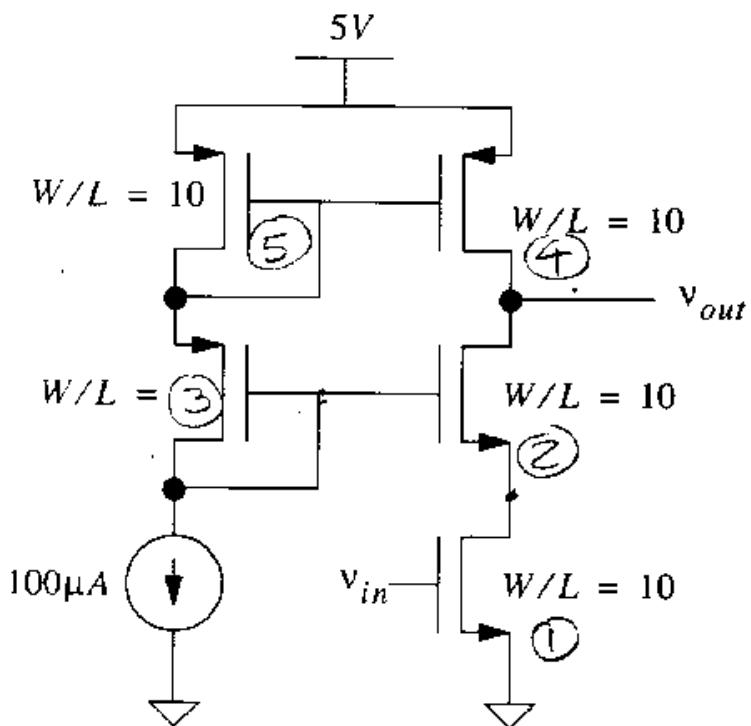

What is the value of the missing W/L so that the output swing is maximum? $W/L = \underline{\underline{,43}}$

$$\sqrt{V_{dsat}(100\mu A)} = \left(\frac{2(100)\mu A}{100\mu A/\sqrt{2} + 10} \right)^{1/2} = .45V.$$


$$S = V_{dsat1} + (V_{dsat2} + V_{T2}) + (V_{dsat3} + V_{T3}) + (V_{dsat4} + V_{T4})$$

$$V_{dsat3} = S - (1.5) - 3(.45) = 2.15$$

$$= \left(\frac{2(00)}{100(W/L)} \right)^{1/2}$$

$$(W/L)_3 = ,43$$

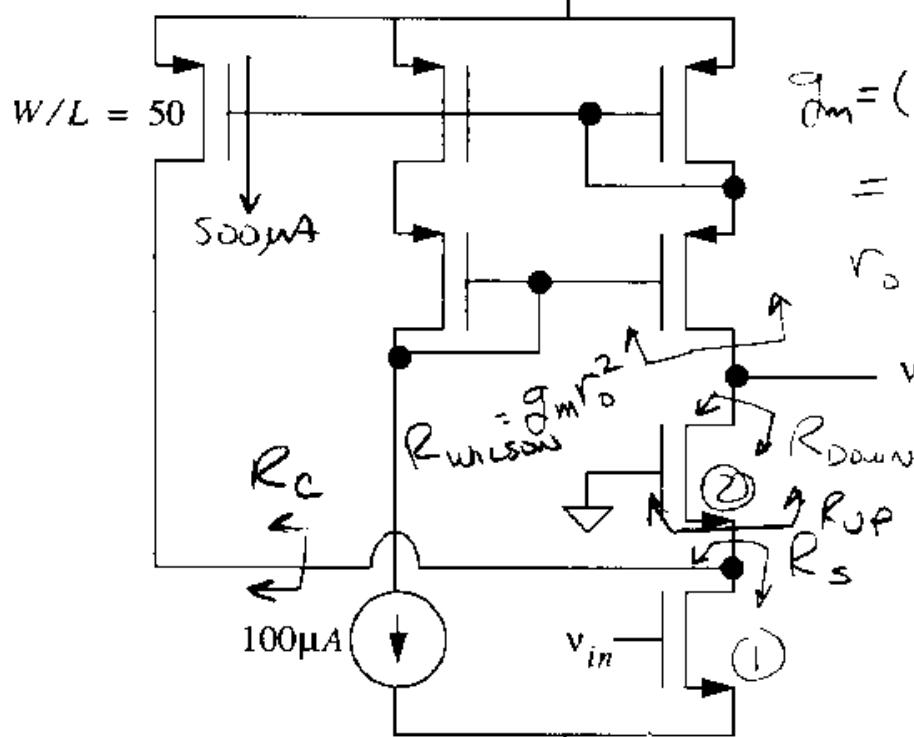3) Assume v_{in} is set so that $v_{out} = 0$



$$g_m = (2I_D k' \frac{W}{L})^{1/2}$$

$$= 4.5 \times 10^{-3} \text{ A}$$

$$r_o = \frac{1}{2I_D} = \frac{1}{(0.1)(100\mu\text{A})} = 1 \text{ M}\Omega$$

a) What is R_{out} ?

$$R_{Wilson} = 4.5 \times 10^{-3} \times 10^{12} = 450 \text{ M}\Omega$$

$$R_s = \frac{1}{2I_5(100\mu\text{A})} \parallel \frac{1}{2I_6(100\mu\text{A})} = 91 \text{ k}\Omega$$

$$R_{down} = (g_m R_s) r_o = 4.5 \times 10^{-3} \times 91 \times 10^3 \times 10^6 = 41 \text{ M}\Omega$$


b) What is $\frac{v_{out}}{v_{in}}$?

$$R_{out} = R_{Wilson} \parallel R_{down}$$


$$= 450 \text{ M}\Omega \parallel 41 \text{ M}\Omega$$

$$\frac{v_{out}}{v_{in}} = g_m \frac{R_s \parallel R_c}{R_{up} \parallel R_s \parallel R_c} R_{out} = \left(2 \times 600\mu\text{A} \times 100\mu\text{A} / 2 \cdot 10\right)^{1/2} \left(\frac{1}{1+1}\right) 37 \text{ M}\Omega$$

$$= 3.4 \times 10^3$$

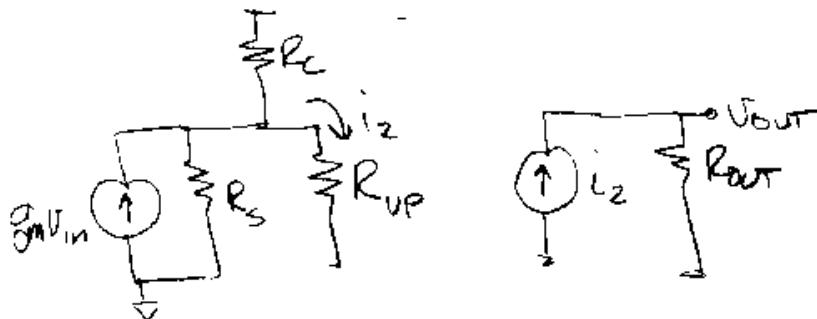

4)

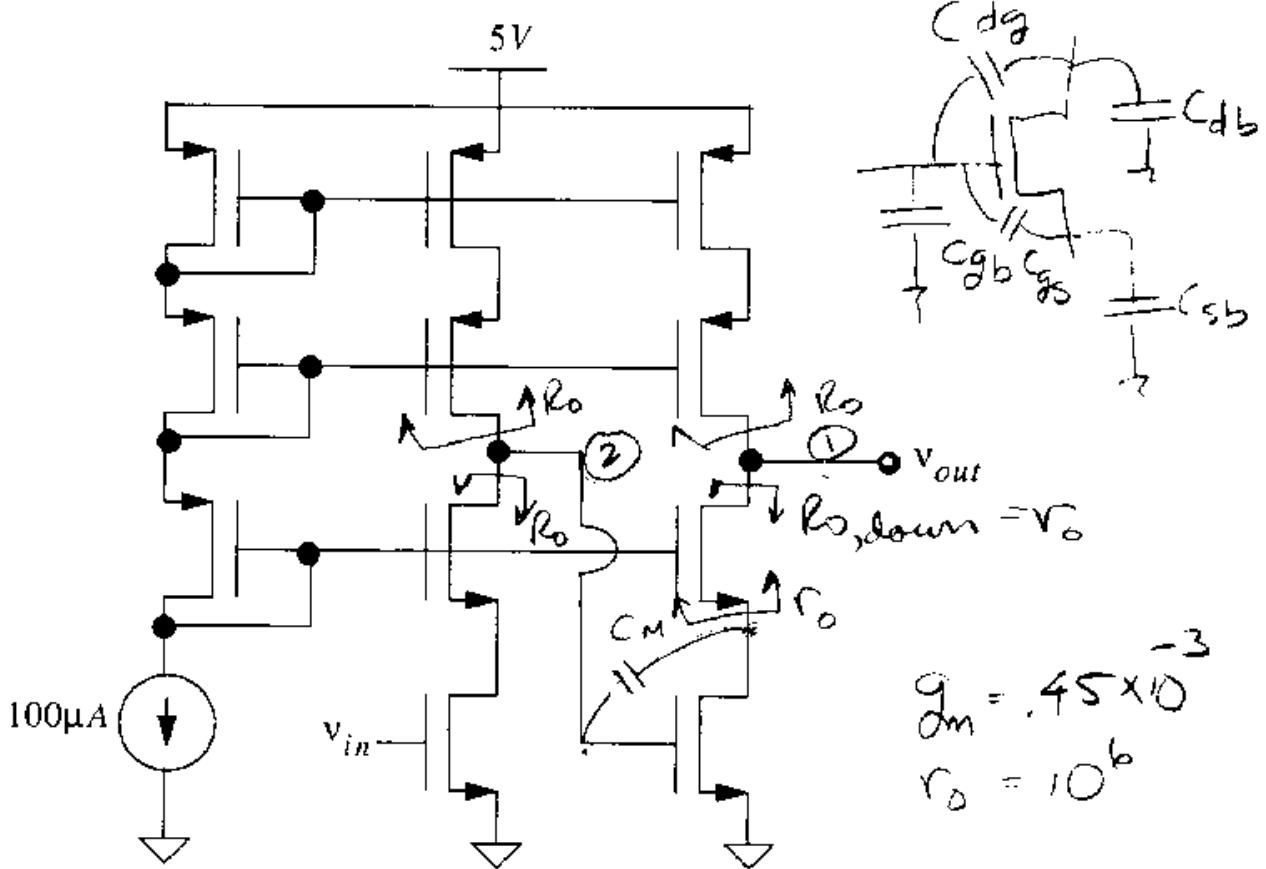

$$g_m = .45 \times 10^{-3}$$

$$r_o = 10^6$$

What are the 2 lowest poles of this circuit?

$$\omega_{p1} = \frac{110}{2250 \text{ rad/sec}}$$

$$\omega_{p2} = \frac{1.9}{2250 \text{ rad/sec}}$$

$$C_1 = 2(C_{db} + C_{gd}) = 40 \text{ fF}$$

$$R_o = g_m r_o^2 = .45 \times 10^{-3} \cdot 10^6 = 450 \text{ M}\Omega$$

$$\omega_{p1} = \frac{1}{(R_o/2) C_1} = \frac{1}{225 \times 10^6 \cdot 40 \times 10^{-15}} = 110 \text{ rad/sec}$$


$$\omega_{p2} = \frac{1}{(225 \times 10^6 \times (40 \text{ fF} + 2250 \text{ fF} + 10 \text{ fF} + 100 \text{ fF}))}$$

$$= 1.9 \text{ rad/sec}$$

$$\omega_{p2} = \frac{1}{R_o/2 (C_1 + C_M + C_{gb} + C_{gs})}$$


$$C_M = g_m (r_o || r_s) C_{gd} = .45 \times 10^{-3} \times 10^6 / 2 \times 10^{-15} = 2250 \text{ fF}$$

5)

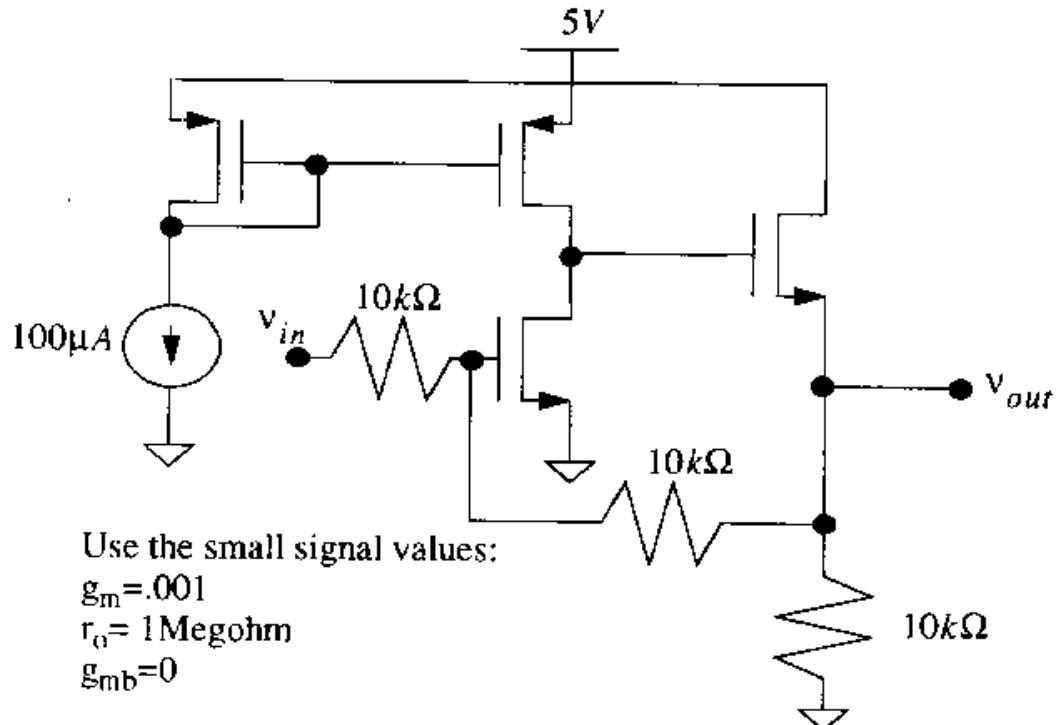


a) What kind of feedback is this? SHUNT - SHUNT

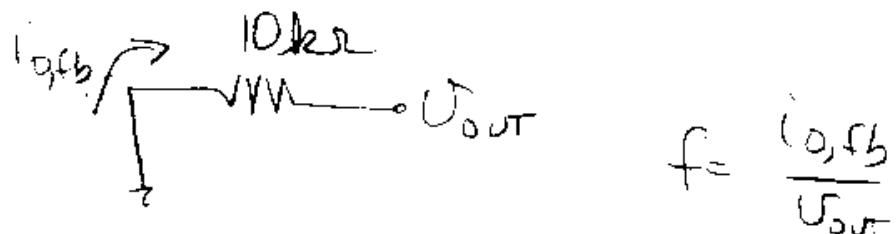b) What is the value of f ? $f = 1 \times 10^{-3}$ Hz



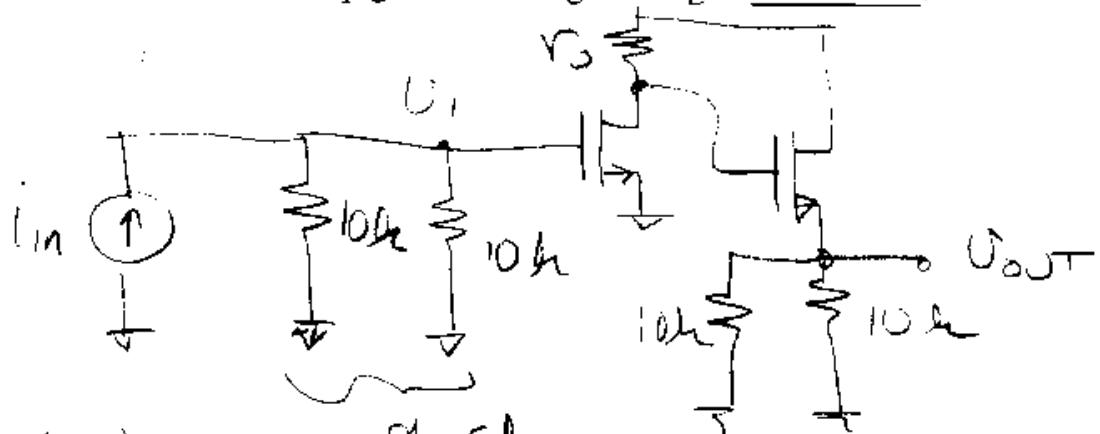
c) What is the loop gain including loading $T \cdot 210$?



$$\alpha' = -(5k) g_m \left(\frac{5}{2}\right) \frac{g_m 5k}{1 + g_m 5k} = 5 \times 5 \times 10^5 \left(\frac{5}{6}\right) = -2.1 \times 10^6$$

$$+ I' = +2.1 \times 10^2$$

6)

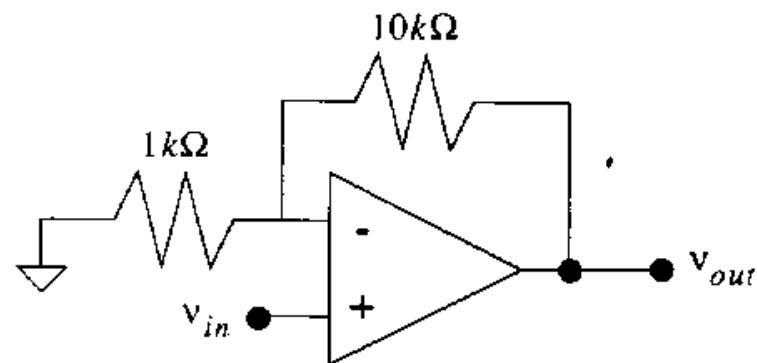

The above basic amplifier has the following characteristics:

$$R_{in} = \infty$$

$$R_{out} = 0\Omega$$

The transfer function is :


$$H(\omega) = \frac{10^4 \cdot \left(1 - \frac{j\omega}{10^6}\right)}{\left(1 + \frac{j\omega}{10^6}\right) \cdot \left(1 + \frac{j\omega}{10^8}\right) \cdot \left(1 + \frac{j\omega}{\omega_c}\right)}$$

the zero


$$f = \frac{1/2}{10^6 + 1/2} \\ = \frac{1}{11}$$

What is the location of ω_c so that the phase margin is 45° ?

$$\omega_c = 450 \text{ RAD/sec}$$

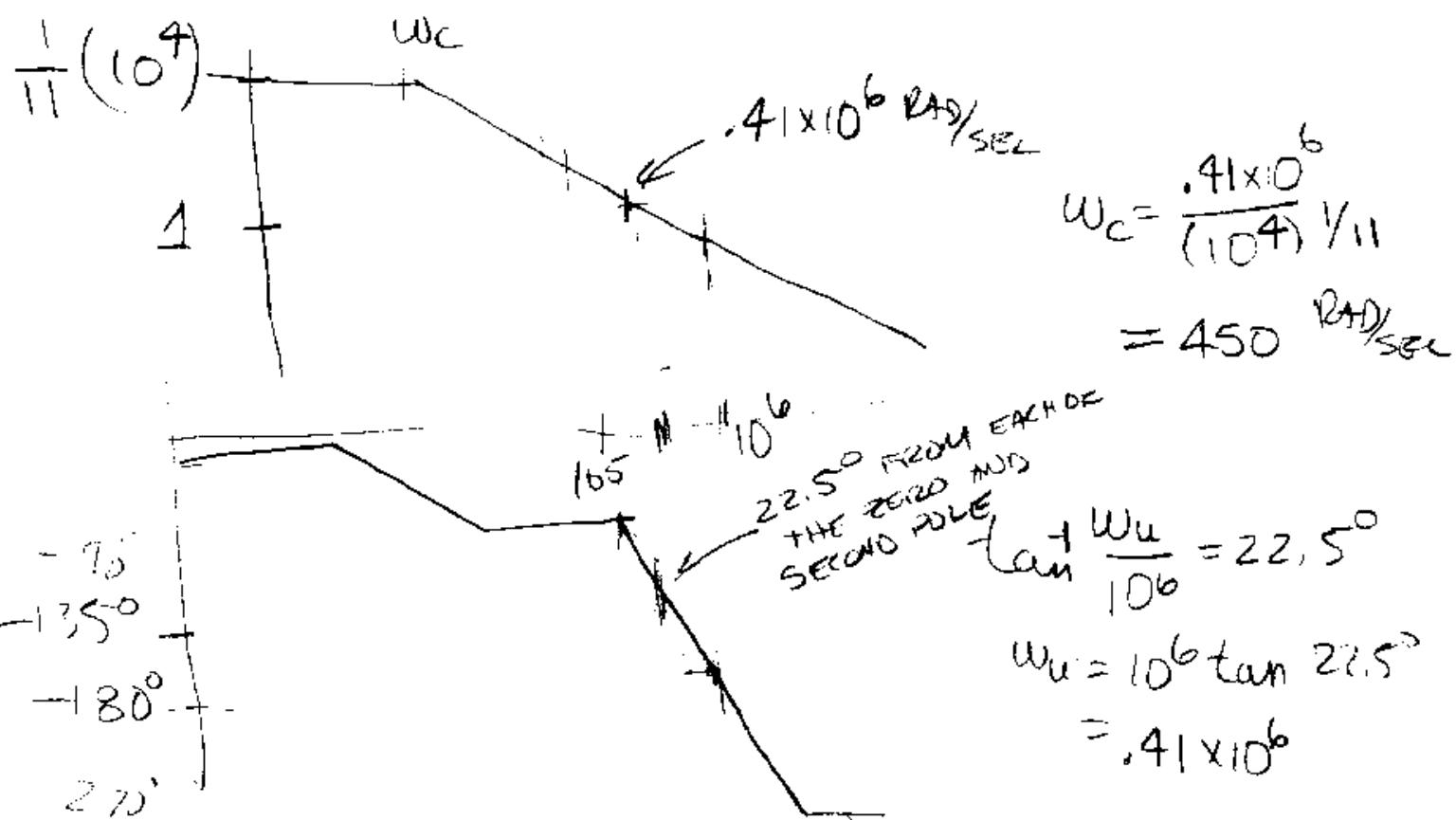

7)

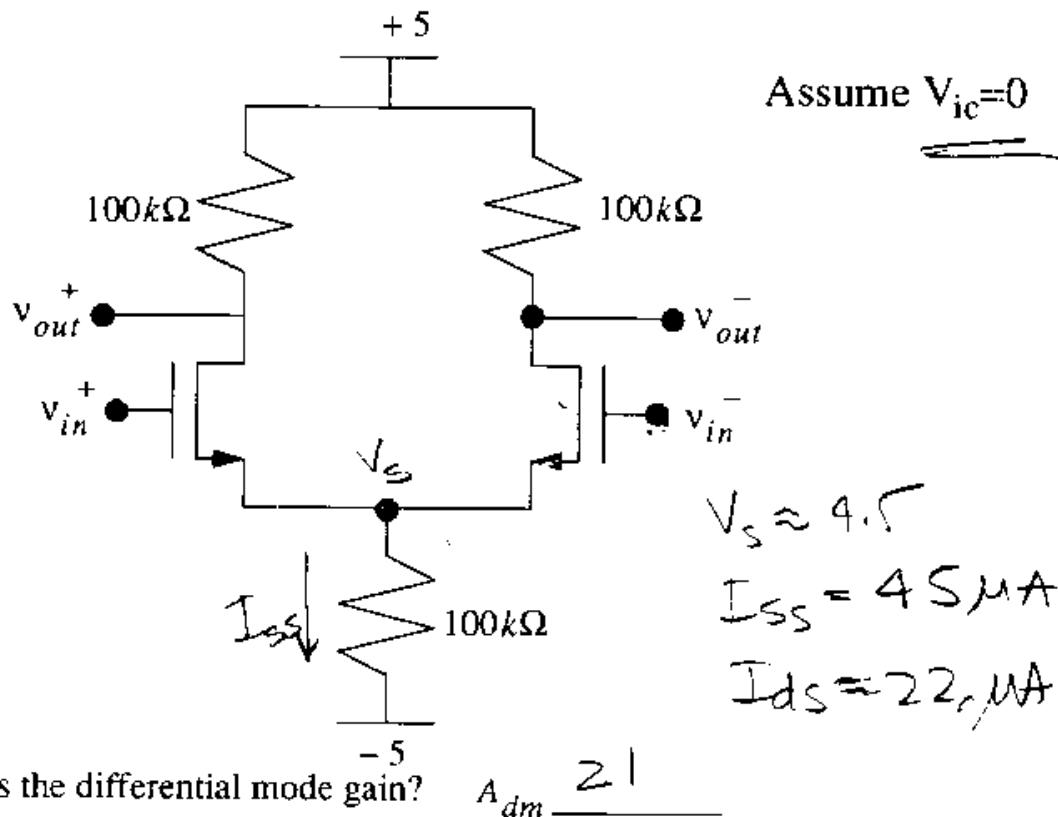

a) What is the differential mode gain? $A_{dm} = \frac{21}{1 + 2g_m 100k\Omega}$

$$g_m = (2I_{ds}/V_L)^{1/2} = .21 \times 10^{-3} \quad | \quad r_o = \frac{1}{(0.1 \cdot 22 \times 5 \cdot 10^3)} = 4.5 \times 10^6 \Omega$$

$$R_{on} = r_o || 100k\Omega \approx 100k\Omega$$

b) What is the common mode gain? $A_{cm} = 0.5$

$$\frac{g_m 100k}{1 + 2g_m 100k} \approx \frac{100k}{200k} = 0.5$$

c) If $v_{in+} = v_{in}$, $v_{in-} = 0$, what is $\frac{(v_{out-} - (v_{in}))}{(v_{in})} = -10.25$?

$$\begin{aligned} \underline{v_{out}} &= A_{cm} \underline{V_{ic}} - A_{dm} \underline{V_{id}} & V_{ic} &= \frac{\underline{v_{in}}}{2} \\ &= 0.5 \left(\frac{\underline{v_{in}}}{2} \right) - \frac{21}{2} \left(\underline{v_{in}} \right) & V_{id} &= \underline{v_{in}} \\ &= (-25 - 10.5) \underline{v_{in}} & &= -10.25 \underline{v_{in}} \end{aligned}$$