

University of California
College of Engineering
Department of Electrical Engineering
and Computer sciences

EE140

Midterm Exam

Mar. 13, 2003

Name: Solution

SID#: _____

grad undergrad

- Closed book except for 1 - 8.5" x 11" sheet of your notes.
- There are two problems. Be sure to show all your work to receive full or partial credit.

1	
2	
Total	

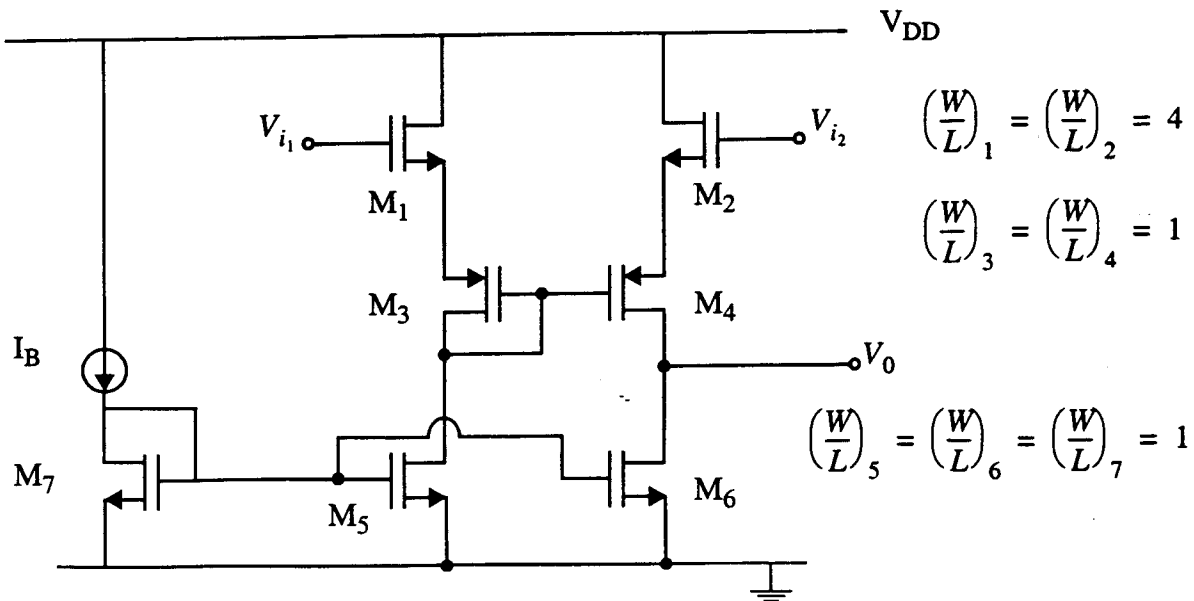


Fig. 1.

1) In the amplifier of Fig. 1, assume all NMOS devices have $V_T = V_{T_n}$, and all PMOS devices have $V_T = V_{T_p}$. You may neglect body effect. Further, assume all devices are minimum length, and are characterized by k'_n, λ_n and k'_p, λ_p for NMOS and PMOS devices respectively.

a) (10 pts.)

For the nominal input $V_{i_1} = V_{i_2} = V_{DD}$, determine the circuit operating point. Fill in the data below in terms of symbolic parameters. $V_{T_n}, V_{T_p}, k'_n, k'_p, \lambda_n, \lambda_p, I_B, \left(\frac{W}{L}\right)$'s, etc.

I_{D_1}	I_B
I_{D_2}	I_B
V_{S_1}	$V_{DD} - V_{T_n} - \Delta V_{1,2}$
V_{S_2}	$V_{DD} - V_{T_n} - \Delta V_{1,2}$
V_{D_3}	$V_{DD} - V_{T_n} - \Delta V_{1,2} - V_{T_p} - \Delta V_{3,4} $
V_0	$= V_{D_3}$ (Symmetry!)

$$\Delta V_{1,2} = \sqrt{\frac{2 I_B}{k'_n \left(\frac{W}{L}\right)_{1,2}}}$$

$$|\Delta V_{3,4}| = \sqrt{\frac{2 I_B}{k'_p \left(\frac{W}{L}\right)_{3,4}}}$$

b) (10 pts.)

Determine the common mode input range, consistent with keeping all devices active.

$$\Delta V_{5,6} + |V_{T_P}| + |\Delta V_{3,4}| + V_{T_n} + \Delta V_{1,2} \leq V_{in,cm} \leq V_{DD} + V_{T_n}$$

c) (10 pts.)

If $V_{i_2} = V_{DD}$, determine the output range, consistent with keeping all devices active.

$$\Delta V_6 \leq V_o \leq V_{DD} - V_{T_n} - \Delta V_2 - |\Delta V_4|$$

d) (10 pts.)

For the operating point with $V_{I_1} = V_{I_2} = V_{DD}$, determine the differential mode circuit

$$G_m, \text{ i.e. } G_{m_{diff}} = \frac{i_{out}}{(v_{i_1} - v_{i_2})}$$

$$\frac{g_{m_2}}{1 + g_{m_2} \frac{1}{g_{m_4}}} = \frac{g_{m_2} g_{m_4}}{g_{m_2} + g_{m_4}}$$

e) (10 pts.)

For the operating point with $V_{i_1} = V_{i_2} = V_{DD}$, determine R_{out} .

$$r_{o_6} // r_{o_4} \left(1 + \frac{g_{m_4}}{g_{m_2}} \right)$$

f) (10 pts.)

Determine the common mode gain, i.e. $A_{v-cm} = \frac{v_o}{v_{in}} \Big|_{v_{i_1} = v_{i_2} = v_{in}}$

$$\approx 1$$

$$\frac{r_{o_{5,6}}}{\frac{1}{g_{m_1}} + \frac{1}{g_{m_3}} + r_{o_{5,6}}}$$

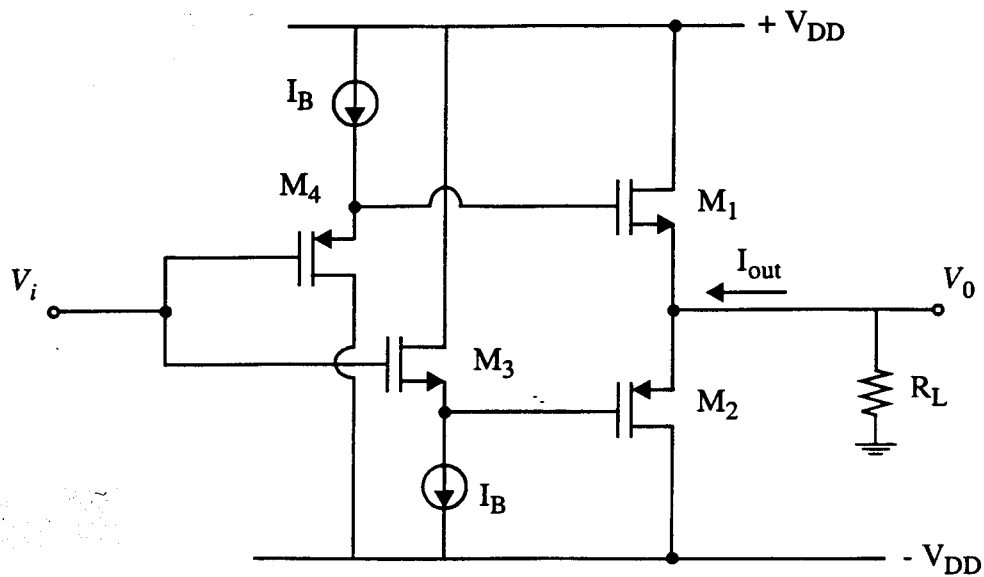


Fig. 2

2) For the circuit of Fig. 2, take the following: $\left(\frac{W}{L}\right)_1 = N\left(\frac{W}{L}\right)_3$; $\left(\frac{W}{L}\right)_2 = N\left(\frac{W}{L}\right)_4$;

$k'_n\left(\frac{W}{L}\right)_3 = k'_p\left(\frac{W}{L}\right)_4$. Neglect body effect and channel length modulation.

Assume $V_{T_n} = V_{T_p}$.

a) (10 pts.)

For $V_i = 0$ and $R_L = \infty$, determine V_0 , I_{D_1} and I_{D_2} .

V_0	$V_0 \approx 0$
I_{D_1}	$N I_B$
I_{D_2}	$N I_B$

b) (10 pts.)

For the bias condition determined in part (a), determine the circuit G_m .

$$g_{m1} + g_{m2}$$

$$g_{m1} = \frac{2NI_B}{\Delta V_1}$$

$$\Delta V_1 = \sqrt{\frac{2NI_B}{k'_n \left(\frac{W}{L}\right)_1}}$$

$$g_{m2} = g_{m1}$$

$$\Delta V_2 = \Delta V_1$$


c) (10 pts.)

For the bias condition determined in part (a), determine R_{out} .

$$\frac{1}{g_{m1}} \parallel \frac{1}{g_{m2}} = \frac{1}{g_{m1} + g_{m2}}$$

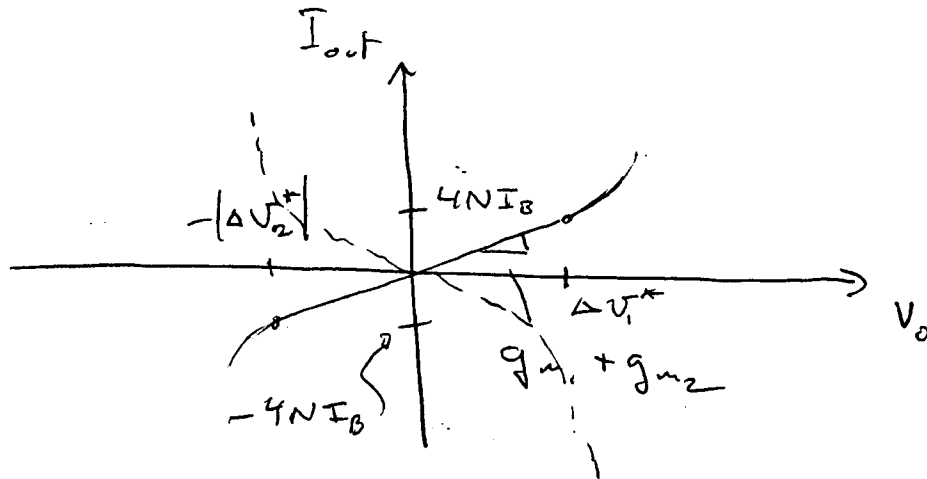d) (10 pts.)

Take $V_i = 0$ and $R_L = \infty$. Determine the large signal $I_{out} - V_0$ curve obtained by applying an appropriate test source at the circuit output.



$$g_{m1}(V_0) = k'_n\left(\frac{w}{L}\right)_1 \Delta V_1(V_0) = k'_n\left(\frac{w}{L}\right)_1 (\Delta V_1^* - V_0) \quad V_0 \leq \Delta V_1^*$$

$$g_{m2}(V_0) = k'_p\left(\frac{w}{L}\right)_2 \Delta V_2(V_0) = k'_p\left(\frac{w}{L}\right)_2 (\Delta V_2^* + V_0)$$

$$-|\Delta V_2^*| \leq V_0$$

$$V_0 > \Delta V_1^* \Rightarrow g_{m1} = 0 \quad (\text{cut-off})$$

$$g_{m2}$$