



University of California  
College of Engineering  
Department of Electrical Engineering  
and Computer Sciences

E. Alon

Tuesday, October 7, 2008  
6:30-8:00pm

## EECS 141: FALL 2008—MIDTERM 1

For all problems, you can assume that all transistors have a channel length of 100nm and the following parameters (unless otherwise mentioned):

**NMOS:**

$$V_{Tn} = 0.2V, \mu_n = 400 \text{ cm}^2/(V \cdot s), C_{ox} = 1.125 \text{ } \mu\text{F}/\text{cm}^2, v_{sat} = 1e7 \text{ cm/s}, \lambda = 0$$

**PMOS:**

$$|V_{Tp}| = 0.2V, \mu_p = 200 \text{ cm}^2/(V \cdot s), C_{ox} = 1.125 \text{ } \mu\text{F}/\text{cm}^2, v_{sat} = 1e7 \text{ cm/s}, \lambda = 0$$

<b>NAME</b>	Last	First
-------------	------	-------

<b>GRAD/UNDERGRAD</b>	
-----------------------	--

**Problem 1:** \_\_\_\_ / 18

**Problem 2:** \_\_\_\_ / 20


**Problem 3:** \_\_\_\_ / 26

**Total:** \_\_\_\_ / 64


**PROBLEM 1. (18 pts) Complex Gates and Elmore Delay.**

- a) (6 pts) Implement the function  $F = \overline{(A \cdot B + C)} \cdot (D + E)$  with a complex static CMOS gate. Assuming  $R_{sqp} = 3R_{sqn}$ , you should size your gate so that the worst-case pull up resistance is equal to the worst-case pull-down resistance.

 - b) (6 pts) Using the switch model for the transistors, draw the RC network you would use to calculate the delay of the gate shown below when  $B = V_{DD}$ ,  $C = 0V$ , and A transitions from  $0V$  to  $V_{DD}$ . You can assume that  $C_G = C_D = 2\text{fF}/\mu\text{m}$ ,  $R_{sqn} = 10\text{k}\Omega/\square$ , and  $R_{sqp} = 30\text{k}\Omega/\square$ .




- c) (6 pts) Using the same model and component values you drew in part b), what is the delay of the gate under the same situation (i.e., when  $B = V_{DD}$ ,  $C = 0V$ , and A transitions from  $0V$  to  $V_{DD}$ )? You should provide your answer for the delay in both absolute ps and in units of  $t_{inv}$ . For your convenience the gate has been repeated below.

 


**PROBLEM 2. (20 pts) IV Characteristics, VTCs, and Energy**

- a) **(2 pts)** For a long-channel (quadratic) NMOS transistor with  $V_{GS} = V_{DS} = 1.2V$ , how does the drain current change if the mobility of the device  $\mu_n$  is doubled? How about if  $C_{ox}$  is doubled?
- b) **(6 pts)** Now let's look at a short-channel (velocity-saturated) NMOS transistor with  $V_{GS} = V_{DS} = 1.2V$ . Using the velocity saturated model for this transistor, how much drain current would you get from a  $1\mu m$  wide transistor if you doubled  $\mu_n$  to  $800 \text{ cm}^2/(V\cdot s)$ ? How about if you doubled  $C_{ox}$  to  $2.25 \mu F/cm^2$ ?


- c) (6 pts) For parts c) and d), you should use the simple switch model of the transistors with  $R_{sqn} = 10\text{k}\Omega/\square$ ,  $R_{sqp} = 20\text{k}\Omega/\square$ ,  $V_{DD} = 1.2\text{V}$ , and  $V_{TN} = |V_{TP}| = 0.2\text{V}$ . Draw the VTC of the circuit shown below and provide the values of  $V_{OH}$ ,  $V_{OL}$ ,  $V_{IH}$ , and  $V_{IL}$ .

 

- d) (6 points) For this same circuit (repeated below), how much energy is supplied by  $V_{DD}$  to charge  $C_L$  when  $In$  steps from  $V_{DD}$  to  $0V$ ?

 

 **PROBLEM 3. Logical Effort and Gate Sizing (26 points)**



a) (6 pts) What is the path effort from In to Out?

b) (2 pts) What EF/stage minimizes the delay of this chain of gates?

c) (8 pts) Size the gates to minimize the delay from In to Out.


Size	Value (fF)
a	
b	
c	
d	



- d) **(4 pts)** By changing only the order (but not the types) of the gates, can you reduce the total capacitance of the gates in this chain? If so, draw the re-ordered chain (you do not need to recalculate the sizes) and explain why the capacitance is reduced; if not, explain why this isn't possible.

- e) (6 points) While maintaining the same logical functionality and without changing  $C_{in}$ , can you improve the delay of this chain of gates (repeated below) by changing the number and/or types of gates? Please draw an improved schematic for the new chain of gates; you don't need to provide gate sizes.

Original chain:

 

Improved chain: