



University of California
 College of Engineering
 Department of Electrical Engineering
 and Computer Science

J. M. Rabaey

511 Cory Hall

TuTh3:30-5pm

e141@eecs

EECS 141: SPRING 98 —MIDTERM 1

For all problems, you can assume the following transistor parameters:

NMOS:

$$V_{Tn} = 0.75V, k'_n = 20 \mu A/V^2, \lambda = 0, \gamma = 0.5 V^{1/2}, 2\Phi_F = -0.6V$$

PMOS:

$$V_{Tp} = -0.75V, k'_p = 7 \mu A/V^2, \lambda = 0, \gamma = 0.5 V^{1/2}, 2\Phi_F = -0.6V$$

NAME	<div style="display: flex; justify-content: space-between;"> Last First </div>
-------------	--

GRAD/UNDERGRAD	
-----------------------	--

Problem 1:

Problem 2:

Problem 3:

Total	
--------------	--

Problem 1: Device Operation and DC characteristics

Consider the following simple logic gate:


 


FIG. 1 : Simple Gate

 The PMOS is implemented in a 0.35 μm CMOS process, and its I-V characteristics are plotted on the chart below.



Calculate answers to the following questions based only upon data points read from this plot. That is, do NOT attempt to solve by fitting analytical equations in V_{gs} and V_{ds} to this data.

a. Determine approximate values of V_{OH} , V_{OL} , and V_M of the gate.

V_{OH} :
V_{OL} :
V_M :

b. Determine t_{pLH} and t_{pHL} . Assume an ideal step at the input.

t_{pLH} :
t_{pHL} :

c. Determine the static power dissipation of the gate in both the high and low output states.

$P_{stat} (Out = high)$:
$P_{stat} (Out = low)$:

d. Suppose that the bulk voltage of the PMOS is raised above VDD. Determine the impact on the following parameters and explain your answer in a couple of words:

Why?

VOH: Increase Decrease Unchanged


VOL: Increase Decrease Unchanged

tpLH: Increase Decrease Unchanged

tpHL: Increase Decrease Unchanged

Pstat: Increase Decrease Unchanged

PROBLEM 2: MOS Devices

 

Consider the following simple circuit (implemented in the 1.2 μm CMOS technology). Assume $V_{DD} = 3\text{ V}$. Assume that V_{out} is initially set at 0 V.

a. Determine the final value of V_{out} after the transients have subsided.

V_{out} (end of transient) =

b. Determine the energy taken from the supply during the transient. How much energy is dissipated in the two transistors?

$E(\text{supply}) =$

$E(\text{transistors}) =$

c Assume that the NMOS devices represent real deep-submicron transistors. Discuss the voltage that the output will reach after we wait **for an infinite amount of time** after the initiation of the transient. Explain your answer.

$V_{out}(t = \infty)$

c. Determine an ordering of the input signals, such that the PMOS network can be laid out a contiguous diffusion strip.

d. Size the PMOS transistors such that the resistance of the PMOS network is always equal or smaller than a single minimum-size PMOS device, yet is minimal in area.