

Midterm #1 Solutions – EECS 145L Fall 2001

1	Op Amp	Inverting op-amp circuit amplifier	Non-inverting op-amp circuit amplifier	Differential op-amp circuit amplifier	Instrumentation amplifier
High Z_{in}	YES	NO	YES	NO	YES
Differential input	YES	NO	NO	YES	YES
Defined gain over a frequency band	NO	YES	YES	YES	YES

[1 point off for each wrong answer]

2a

Op-amp equation $V_0 = -AV_3$

Kirchhoff's current law at node V_2 : $\frac{V_1 - V_2}{100 \text{ k}\Omega} + \frac{V_3 - V_2}{1 \text{ k}\Omega} + \frac{0 - V_2}{1 \text{ k}\Omega} = 0$

$$V_1 = V_2 + 100V_2 - 100V_3 + 100V_2 = 201V_2 - 100V_3$$

Kirchhoff's current law at node V_3 : $\frac{V_2 - V_3}{1 \text{ k}\Omega} + \frac{V_0 - V_3}{100 \text{ k}\Omega} = 0$

$$100V_2 = 100V_3 + V_3 - V_0 = (101 + A)V_3$$

$$V_1 = \left[\frac{201(101 + A)}{100} - 100 \right] V_3 = \left[\frac{1030 + 201A}{100} \right] V_3$$

$$V_1 = \left[201 - \frac{100(100)}{101 + A} \right] V_2 = \left[\frac{1030 + 201A}{101 + A} \right] V_2$$

$$V_2 = \frac{(101 + A)V_1}{1030 + 201A} \approx \frac{1 + A/100}{100 + 2A} V_1$$

$$V_3 = \frac{100V_1}{1030 + 210A} \approx \frac{V_1}{100 + 2A}$$

$$V_0 = \frac{-100AV_1}{1030 + 201A} \approx \frac{-AV_1}{100 + 2A}$$

[7 points off for setting up the first three equations but not solving them]

[10 points off for following through with the erroneous starting equation $V_2 = V_1/101$]

2b

f = 10 Hz, $A = 10^5$

$$V_2 \approx V_1/201 \approx 5 \times 10^{-3} V_1 \quad V_3 \approx 100V_1/(201 \times 10^5) \approx 5 \times 10^{-6} V_1 \quad V_0 \approx -0.5 V_1$$

f = 1 MHz, $A = 1$

$$V_2 \approx 100V_1/10000 \approx 10^{-2} V_1 \quad V_3 \approx 100V_1/10000 \approx 10^{-2} V_1 \quad V_0 \approx -10^{-2} V_1$$

[15 points off for determining A s only]

[2 points off if some answers off by 2x]

To solve 2b without using 2a:

At 10 Hz, $A = 10^5$ is larger than the closed loop gain of 100 and the virtual short rule gives

$$V_2 = V_1 \cdot 500 \Omega / 100 \text{ k}\Omega = 5 \times 10^{-3} V_1 \quad V_0 = -100 V_2 = -0.5 V_1 \quad V_3 \approx -V_0/10^5 \approx 5 \times 10^{-6} V_1$$

At 1 MHz, $A = 1$, negative feedback fails, and the circuit gain is limited by the op-amp gain of -1

$$V_0 = -V_3$$

$V_2 \approx V_3$ (voltage drop across 1 k Ω resistor is 1% of the 2V₃ voltage drop across 100 k Ω resistor)

$$V_2 = V_1 \cdot 1 \text{ k}\Omega / 100 \text{ k}\Omega \approx 10^{-2} V_1 \quad V_3 \approx 10^{-2} V_1 \quad V_0 = -10^{-2} V_1$$

Midterm #1 Solutions – EECS 145L Fall 2001

3a The lower corner frequency is given by the RC time constant of the high-pass filter


$$f_c = 1/(2 \pi RC) = 1/(2 \pi 0.16 \times 10^{-3}) \approx 1 \text{ kHz}$$

[1 point off for 6.25 kHz]

3b The frequency where the gain of the buffer amplifier falls to 0.5 is the frequency where A falls to 1 which is 1 MHz. [2 MHz was also allowed].

[4 points off if LPF formula used to get 500 to 2000 Hz]


3c

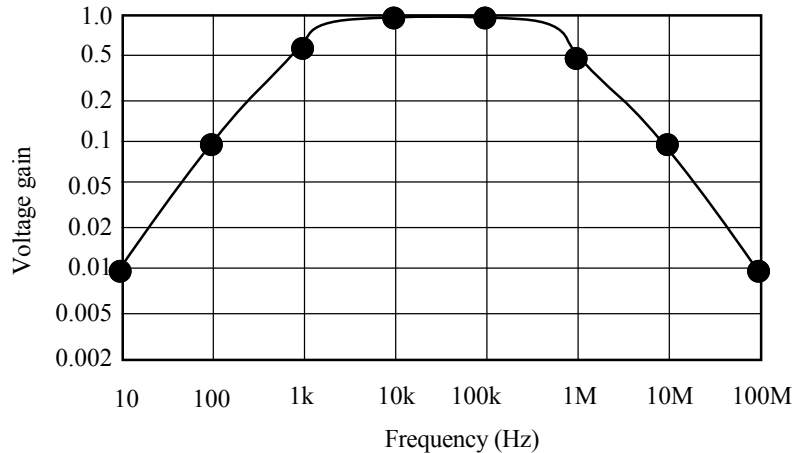

[5 points off if gain does not decrease as 1/f above 1 MHz]

[5 points off if gain does not increase as f below the f_c value answer in 3a]

4

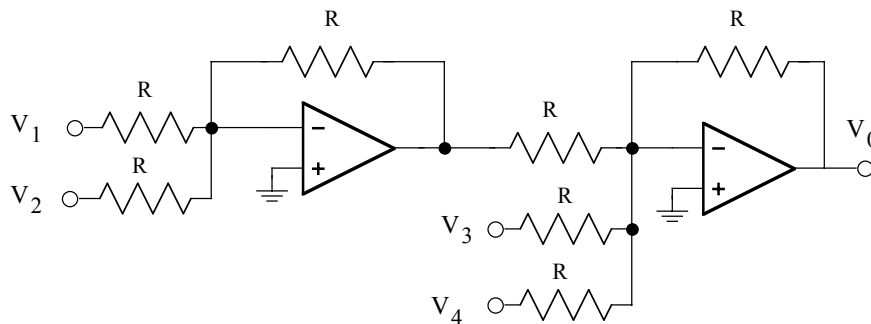

[2 points off for overall sign error, e.g. $V_0 = -V_1 -V_2 + V_3 + V_4$]

[2 points off for a working circuit that uses three op amps]


[5 points off for using two differential amps to take $V_1 - V_3$ and $V_2 - V_4$ and then connecting the output directly together]

[5 points off for one summing amp plus two resistors connected to the + input of a buffer amp; this input is not a summing point]

[2 points off for the following circuit with resistor values shown because of the overall sign error, e.g. $V_0 = -V_1 -V_2 + V_3 + V_4$]

[4 points off for the following circuit with no resistor values shown]

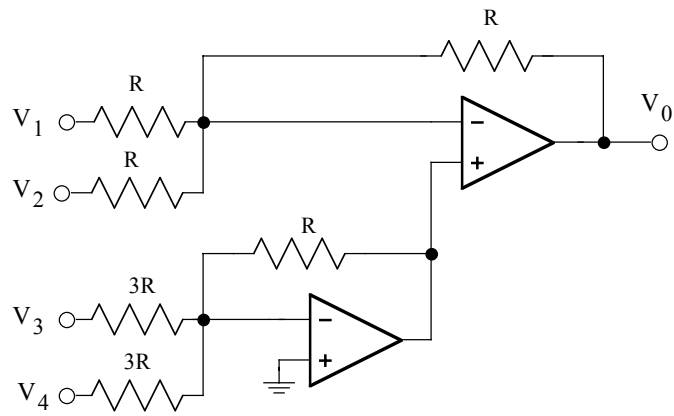Midterm #1 Solutions – EECS 145L Fall 2001



145L midterm #1 grade distribution:

Problem

1	13.4 (15 max)
2	22.5 (40 max)
3	17.7 (25 max)
4	17.3 (20 max)

maximum score = 100

average score = 70.9

31-40	1	F
41-50	0	D
51-60	4	C
61-70	8	C-B
71-80	6	B
81-90	5	B-A
91-95	2	A
96-100	0	