


UNIVERSITY OF CALIFORNIA, BERKELEY  
 Electrical Engineering and Computer Sciences Department

EECS 145L Electronic Transducer Lab  
 MIDTERM #1 (100 points maximum)  
 October 5, 2005

(closed book, calculators OK, equation sheet provided)  
 (You will not receive full credit if you do not show your work)

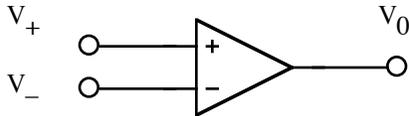**PROBLEM 1 (15 points)**

An amplifier has two inputs  $V_+$  and  $V_-$ , and one output,  $V_0$ .



If  $V_0 = aV_+ + bV_-$ , derive the common mode and differential mode gains as a function of a and b.

**PROBLEM 2 (15 points)**


In the table below, fill in YES or NO in each of the 15 boxes

	Op Amp	Inverting op-amp circuit amplifier	Non-inverting op-amp circuit amplifier	Differential op-amp circuit amplifier	Instrumentation amplifier
High $Z_{in}$					
Differential input					
Defined gain over a frequency band					

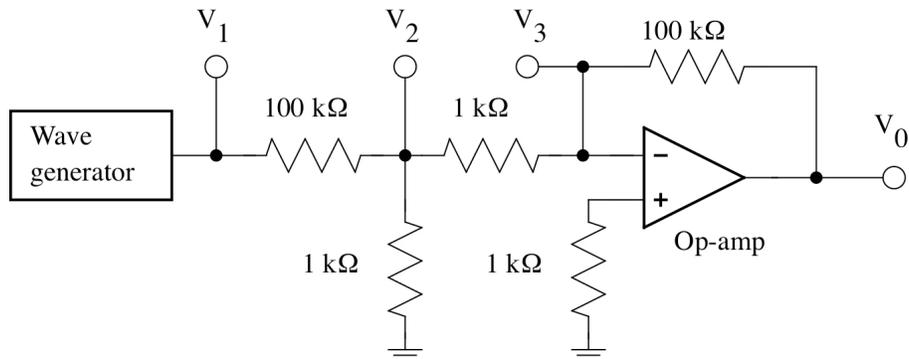**PROBLEM 3 (35 points)**

In the op-amp amplifier circuit shown below, assume the following:

- The op-amp open-loop gain  $A = 10^6 \text{ Hz}/f$ .
- Op-amp input currents are zero
- Output offset can be neglected
- The wave generator produces a pure sinewave of frequency  $f$  and has zero output impedance



- 3a** (15 points) Derive expressions for  $V_2$ ,  $V_3$ , and  $V_0$  as a function of input  $V_1$  at the frequency  $f = 10 \text{ Hz}$ . You may neglect small terms that contribute less than a few percent.


**3b** (20 points) Derive expressions for  $V_2$ ,  $V_3$ , and  $V_0$  as a function of input  $V_1$  at the frequency  $f = 10^6$  Hz. You may neglect small terms that contribute less than a few percent.

**PROBLEM 4 (35 points)**

Design an analog filter circuit that has the following properties

- Gain between 0.9 and 1.0 for frequencies between 100 Hz and 20 kHz
- Gain less than 0.001 for frequencies above 55 kHz
- Gain less than 0.01 at 60 Hz
- Gain less than 0.001 for frequencies below 2 Hz

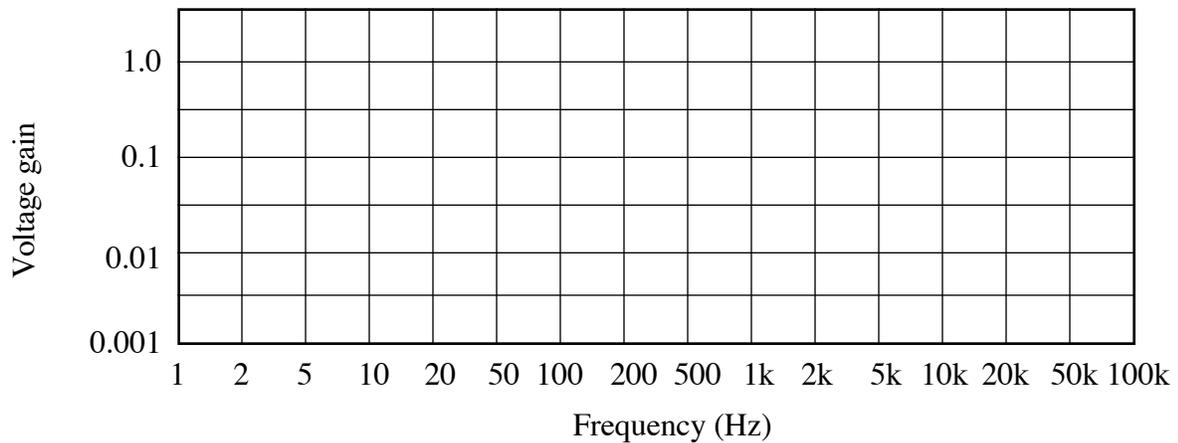**4a** (10 points) Sketch the required gain vs. frequency below



NAME (please print) \_\_\_\_\_ SID \_\_\_\_\_

- 4b** (25 points) Design a filtering circuit that meets the requirements above with the minimum complexity and cost. **For each filtering element, give type, corner frequency, and order number.** (Hint: see equation sheet for a table of  $f/f_c$  vs. gain and order.) Do not give resistor and capacitor values.