

NAME (please print) _____ SID _____

UNIVERSITY OF CALIFORNIA, BERKELEY
Electrical Engineering and Computer Sciences Department
EECS 145L Electronic Transducer Lab
MIDTERM #1 (100 points maximum)
October 8, 2008

(closed book, calculators OK, equation sheet provided)
(You will not receive full credit if you do not show your work)

PROBLEM 1 (36 points)

Briefly define the following terms:

1.1 Electronic sensor

1.2 Sensitivity of an electronic sensor

1.3 Instrumentation amplifier

NAME (please print) _____ SID _____


1.4 Differential gain (of an amplifier with two inputs)

1.5 Common mode gain (of an amplifier with two inputs)

1.6 Johnson noise (of a resistor)

PROBLEM 2 (30 points)

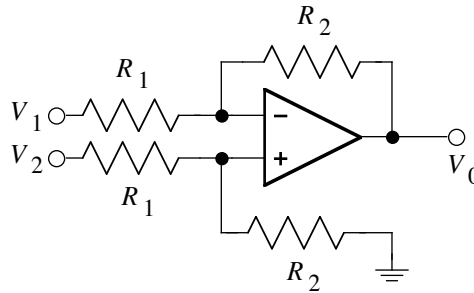2.1 (15 points) Derive an equation for the output V_0 of the op-amp circuit shown below as a function of the input voltages V_1 and V_2 and the resistors R_1 and R_2 . Assume that the op-amp has infinite open loop gain and infinite input impedances.




2.2 (15 points) Using the equation derived in part 2.1, write an equation for the differential and common-mode gains as functions of the resistors R_1 and R_2 .

PROBLEM 3 (34 points)

Design an analog filter circuit that has the following properties

- Gain between 0.9 and 1.0 for frequencies between 100 Hz and 20 kHz
- Gain less than 0.001 for frequencies above 52 kHz
- Gain less than 0.01 at 60 Hz
- Gain less than 0.001 for frequencies below 2 Hz

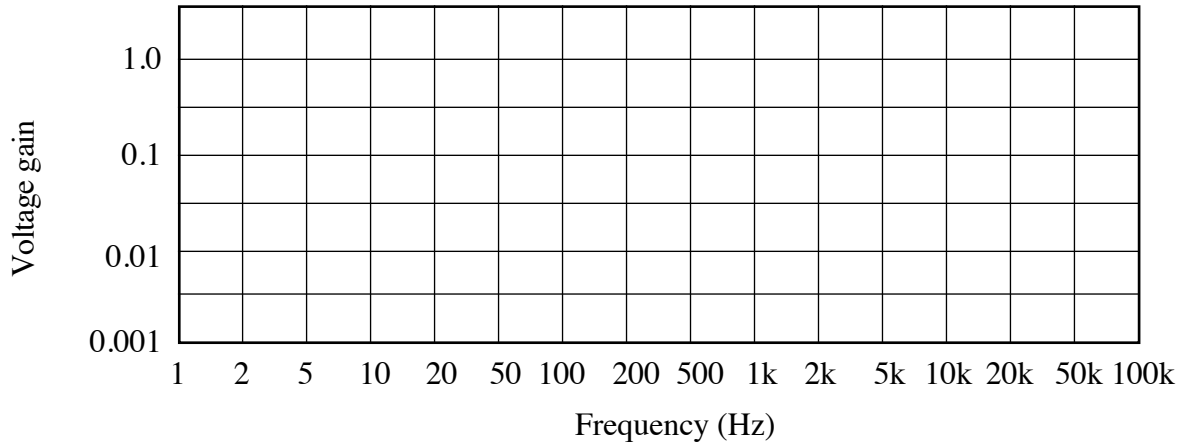3.1 (10 points) Sketch the required gain vs. frequency below



3.2 (24 points) Design a filtering circuit that meets the requirements above with the minimum complexity and cost. **For each filtering element, give type, corner frequency, and order number.** (Hint: see equation sheet for a table of f/f_c vs. gain and order.) Do not give resistor and capacitor values.