

NAME (please print) \_\_\_\_\_ SID \_\_\_\_\_

UNIVERSITY OF CALIFORNIA, BERKELEY  
Electrical Engineering and Computer Sciences Department  
EECS 145L Electronic Transducer Lab  
MIDTERM #2 (100 points maximum)  
November 22, 2010

(closed book, calculators OK, equation sheet provided)  
(You will not receive full credit if you do not show your work)

**PROBLEM 1 (10 points)**

Draw an electronic circuit that drives a light emitting diode to produce a light intensity that is proportional to the circuit input voltage.

**PROBLEM 2 (10 points)**

Describe how you would use a Peltier thermoelectric heat pump to cool an electronic circuit.

NAME (please print) \_\_\_\_\_ SID \_\_\_\_\_

**PROBLEM 3 (10 points)**

Describe how you would use a metal film strain gauge (gauge factor  $G_s = 2$ ) to convert a strain  $\Delta L/L = 0.1\%$  into a output voltage of 1 V.

**PROBLEM 4 (10 points)**

Describe the hazardous condition that the ground fault interrupter is designed to detect, how it senses the condition, and what action it takes when the condition occurs.

NAME (please print) \_\_\_\_\_ SID \_\_\_\_\_

**PROBLEM 5 (10 points)**

Describe how you would calibrate a sensor so that you could use its electronic output to determine any physical input within its range.

**PROBLEM 6 (50 points)**

Design a thermocouple-based system for measuring the temperature of a furnace over the temperature range from 100 °C to 500 °C and that uses a thermistor to measure the temperature of the air near the reference junction.

Assume the following:

- The thermistor has a resistance of 11,053 ohms at 10 °C, 10,000 ohms at 20 °C, and 9,048 ohms at 30 °C.
- To reduce the effects of thermistor self heating, you use a 2 V bias for the thermistor bridge
- The thermocouple has a voltage output of 50  $\mu$ V per °C

NAME (please print) \_\_\_\_\_ SID \_\_\_\_\_

**6.1** (13 points) Draw a circuit that uses a thermistor to produce an output of  $-1V$  at an air temperature of  $10^{\circ}C$ ,  $0 V$  at an air temperature of  $20^{\circ}C$ , and  $+1V$  at an air temperature of  $30^{\circ}C$ .

**6.2** (13 points) Draw a circuit that uses a thermocouple to produce an output of  $1V$  at a differential temperature of  $100^{\circ}C$  and  $5V$  at a differential temperature of  $500^{\circ}C$ . Show the location of the thermistor.

NAME (please print) \_\_\_\_\_ SID \_\_\_\_\_

**6.3** (13 points) Draw a summing circuit that combines the thermistor and thermocouple circuit outputs (**6.1** and **6.2**) to produce 1.0 V at 100 °C and 5.0 V at 500 °C furnace temperatures, independent of room temperature over the 10 °C to 30°C range.

**6.4** (6 points) If the thermistor has a thermal dissipation coefficient of 1 mW/°C in **6.1** what is the temperature of the thermistor at an air temperature of 20 °C?

**6.5** (5 points) If the bridge bias voltage in **6.1** were increased from 2 V to 10 V, what would be the temperature of the thermistor at an air temperature of 20 °C?