


Solutions for Midterm #1 - EECS 145M Spring 1999

1

Name	Interfacing component number
Transparent latch	3
Tri-state driver	4
Edge-triggered flip-flop	1
Sample-and-hold amplifier	2

[4 points off for each incorrect entry]

2a

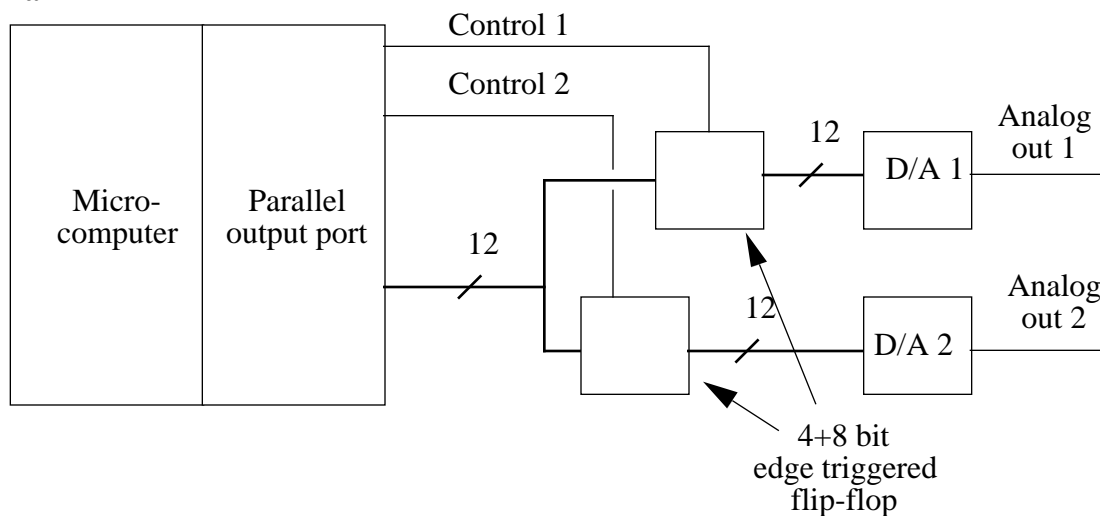

[4 points off for 8 bits to each D/A (12 were required), leaving none for control]

[4 points off for sending the same number to both D/As]

[2 points off for an 8-bit data bus (12 bits required)]

[2 point off for connecting tri-state buffers to the D/As, since the former have no latching capability]

2b (if using edge-triggered flip-flops)

- 1 output n1 C1 and C2 low (this asserts n1 on the lines)
- 2 output n1 with C1 high and C2 low (here n1 appears at the output of flip-flops #1)
- 3 D/A #1 converts n1 to an analog voltage
- 4 output n2 with C1 and C2 low (this asserts n2 on the lines)
- 5 output n2 with C1 low and C2 high
- 6 D/A #2 converts n2 into an analog voltage
- 7 output C1 and C2 low


2b (if using transparent latches)

- 1 output n1 with C1 high and C2 low (n1 appears at the output of latch #1)
- 2 D/A #1 converts n1 into an analog voltage

- 3 output n1 with C1 low and C2 low (latch #1 output is now frozen at n1)
- 4 output n2 with C1 low and C2 high (n2 appears at the output of latch #2)
- 5 D/A #2 converts n2 into an analog voltage
- 6 output n2 with C1 low and C2 low (latch #2 output is now frozen at n2)


[1 point off if the control bits and data bits are not written to the output port in the same operation]
 [1 point off if the control bits are written before the data- this will generally latch garbage and the D/As will start converting it before the good data arrive]

2c

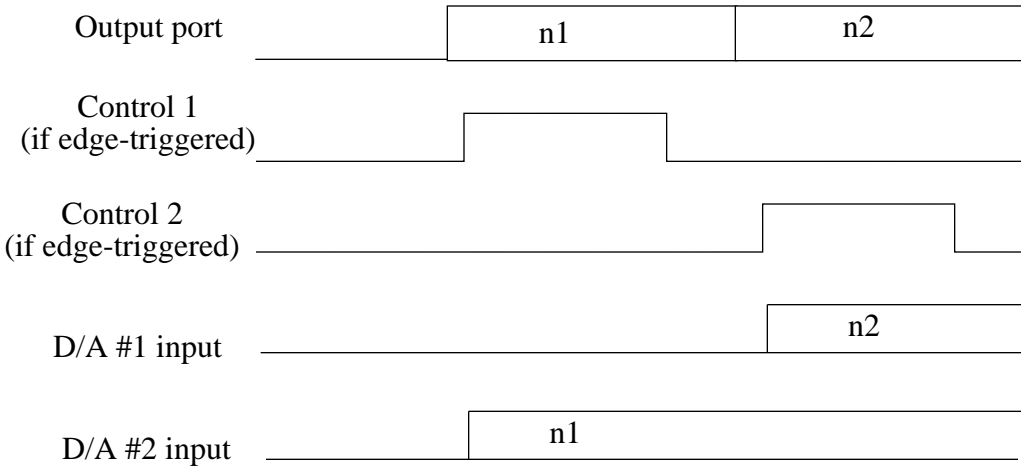

[1 point off if n1 and n2 are not shown as persisting at the D/A inputs until new values are written- when generating a waveform the D/A inputs must always be desired values]

3a

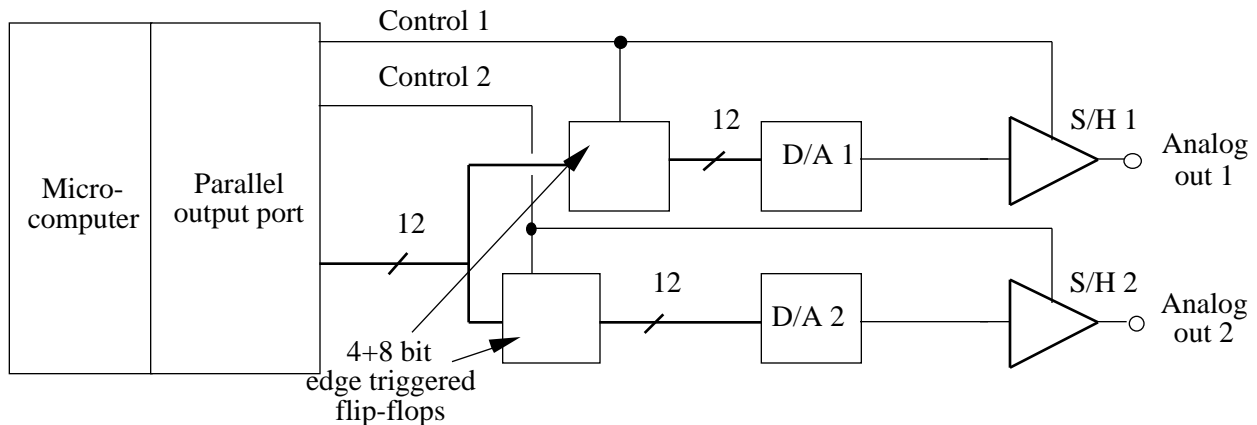

[6 points off if S/H not at D/A output]
 [4 points off if no control lines to S/Hs]
 [4 points off if same input always sent to both D/As]
 [1 point off for using an additional circuit to sense changes in the D/A input bits and put the S/H into hold mode during the glitch- this is an unnecessary complexity since this task can be done by the computer]

3b (if using edge-triggered flip-flops)

- 1 output n1 with C1 and C2 low (this asserts n1 on the lines)


- 2 output n1 with C1 high and C2 low (here n1 appears at the output of flip-flops #1 and S/H #1 goes into hold mode)
- 3 D/A #1 converts n1 to an analog voltage (here is where the glitch occurs)
- 4 output n2 with C1 and C2 low (this asserts n2 on the lines and puts S/H #1 back into sample mode)
- 5 analog output #1 (output of S/H #1) changes from the held value to the new stable value of the D/A #1 output
- 6 output n2 with C1 low and C2 high (here n2 appears at the output of flip-flops #2 and S/H #2 goes into hold mode)
- 7 D/A #2 converts n2 into an analog voltage (here is where the glitch occurs)
- 8 output C1 and C2 low (this puts S/H #2 back into sample mode)
- 9 analog output #2 (output of S/H #2) changes from the held value to the new stable value of the D/A #2 output

3b (if using transparent latches)

- 1 output n1 with C1 high and C2 low (n1 appears at the output of latch #1 and S/H #1 goes into hold mode)
- 2 D/A #1 converts n1 into an analog voltage (here is where the glitch occurs)
- 3 output n1 with C1 low and C2 low (latch #1 output is now frozen at n1 and S/H #1 goes into sample mode)
- 4 output n2 with C1 low and C2 high (n2 appears at the output of latch #2 and S/H #2 goes into hold mode)
- 5 D/A #2 converts n2 into an analog voltage (here is where the glitch occurs)
- 6 output n2 with C1 low and C2 low (latch #2 output is now frozen at n2 and S/H #2 goes into sample mode)


[3 points off if S/Hs not put into hold mode when the corresponding D/A input changes]

3c

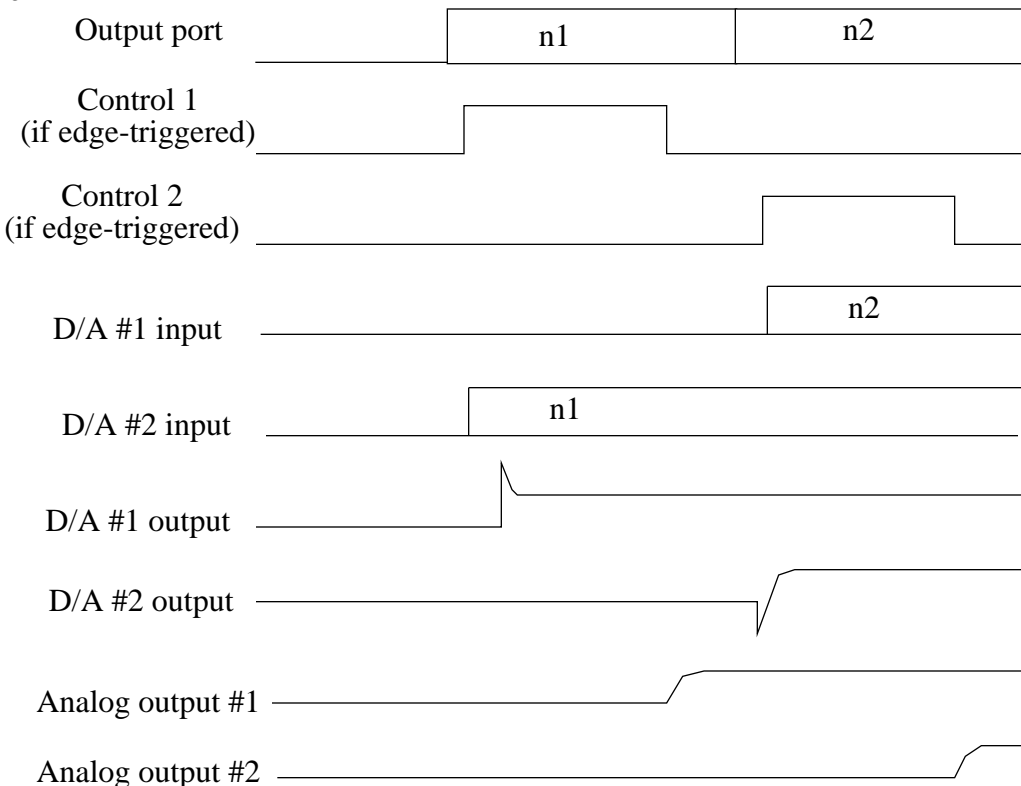

[2 points off if D/A analog outputs (with glitches) not shown]
 [2 points off if S/H control not shown]
 [2 points off if S/H analog outputs (with glitches gone) not shown]

4a

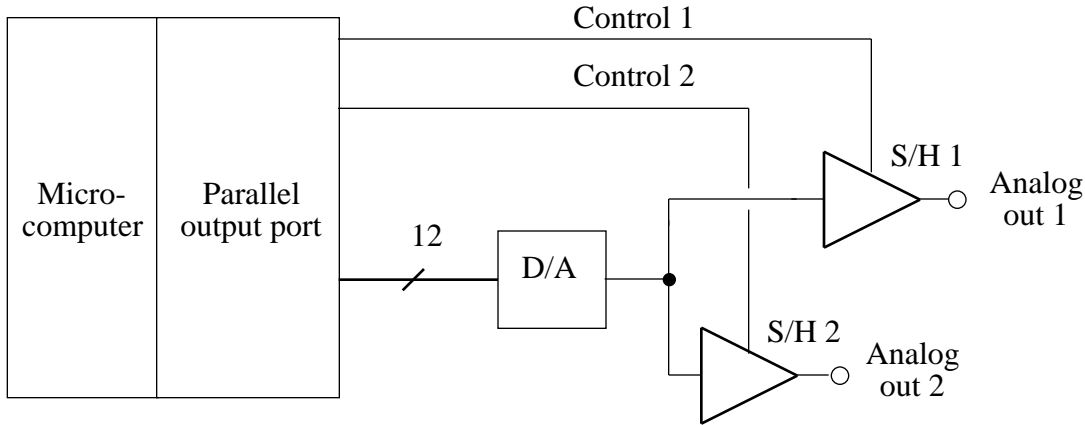


[5 points off if only one analog output line]
 [3 points off if S/H control lines not shown]
 [1 point off for unnecessary latches between output port and D/A]

4b

- 1 write n1 with C1 and C2 high (asserts n1 at D/A input and keeps S/Hs in hold mode)
- 2 after settling, write n1 with C1 low and C2 high (makes analog out 1 equal to stable D/A amplitude)
- 3 write n1 with C1 and C2 high (freeze n1 amplitude at output of S/H #1)
- 4 write n2 with C1 and C2 high (asserts n2 at D/A input and keeps S/Hs in hold mode)
- 5 after settling, write n2 with C1 high and C2 low (makes analog out 2 equal to stable D/A amplitude)
- 6 write n2 with C1 and C2 high (freeze n2 amplitude at output of S/H #1)

4c

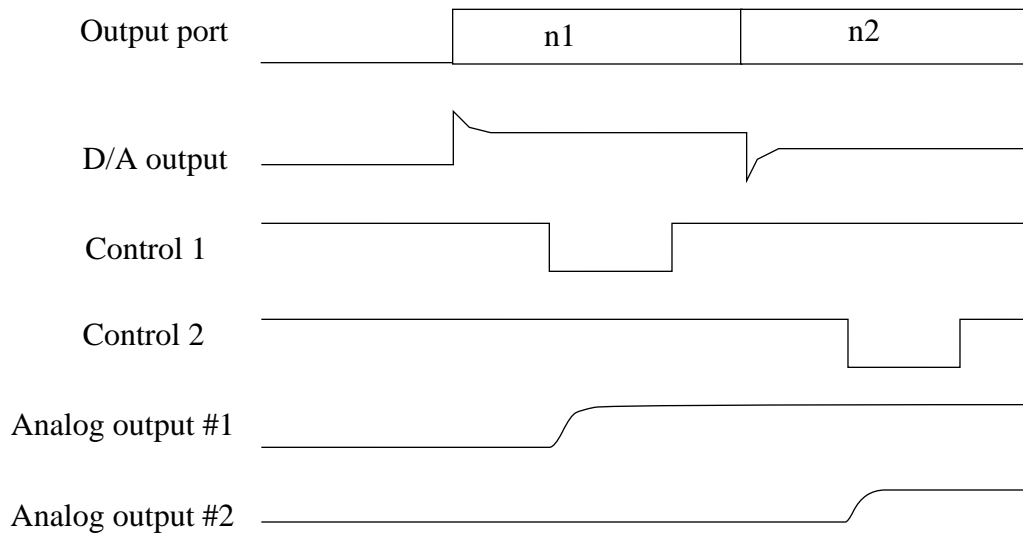

4d

For slow signals whose D/A input values change infrequently, the S/H outputs (which are normally in hold mode) may droop too much before new D/A input values are written. If this is the case, it is necessary to periodically refresh their S/H output amplitudes by performing the steps in 4b even though the D/A input values are the same.

[3 points off for an irrelevant answer]

[2 points off for creative guessing]

[1 point off for recognizing the S/H droop problem without providing a solution]

Midterm #1 class statistics:

Problem	max	average	rms
1	16	13.9	4.0
2	27	23.2	3.8
3	27	19.3	5.1
4	30	19.0	7.3
total	100	75.4	14.2

Grade distribution:

Range	number	<i>approximate</i> letter grade
31-40	1	F
41-50	0	F
51-60	2	D
61-70	6	C
71-80	6	B
81-90	6	A
91-100	4	A