

## EECS 40 Midterm Exam II

**Fall 2004**

Print Name (Last,First) \_\_\_\_\_

Sign Name \_\_\_\_\_

Do not begin exam until you are instructed to start.

Note that there are several versions of this exam in the room.

To get credit for a problem, make your method clear to the grader.

1	/24
2	/16
3	/15
4	/22
5	/23
Total	/100

**Problem 1 (24 points) General Questions**


- a. [1] Give a concise definition of the properties of an acceptor atom that could be used in a silicon wafer and explain what it does.
  
- b. [1] What is the power of 50 watts in decibels referred to a reference power of 1mW (this is often referred to as dBm)?
  
- c. [1] Identify clearly the meaning of the acronym *rms*.
  
- d. [1] What component can you use to couple a time-varying signal to an amplifier yet keep steady currents from flowing into the amplifier? \_\_\_\_\_
  
- e. [1] List two components that can form a circuit that acts as a frequency filter. \_\_\_\_\_ and \_\_\_\_\_ .
  
- f. [1] Draw a simple analog circuit that employs negative feedback (make clear where the feedback appears).
  
- g. [5] List in the table below different devices that are essentially just semiconductor diodes, and indicate their functions:

**Table 1: Diodes**

<b>Name of diode Device</b>	<b>Function of diode device (give distinguishing functions, being as specific as you can)</b>
1.	
2.	
3.	
4.	
5.	

**Problem 1 (continued)**

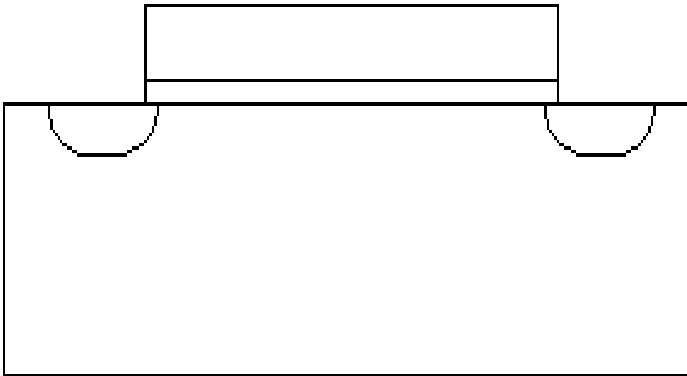h. [6] FET structure. On the cross-sectional transistor view of a silicon n-channel transistor shown below, mark the p-type regions with a **1**, the n-type regions with a **2**, metallic or heavily conducting regions with a **3**, insulating regions with a **4**, regions containing dopants predominantly from Group III of the periodic table with a **III**, and dopants predominantly from Group V of the periodic table with a **V**. (If more than one label applies to a particular region use each one that applies.) Also please indicate and name on the diagram the four terminals of the device.




i. [7] Small-signal resistance of a pn diode

One can apply the small-signal approach to pn diodes to represent how they will behave in response to a small variation of their bias current. To see this, first

- a. [3] Write the “exponential diode equation” (called the Shockley equation by your text) for the diode current,  $i_D$ , as a function of the diode voltage,  $v_D$ : (Note:  $q_e = 1.6 \times 10^{-19}$  C,  $k = 1.38 \times 10^{-23}$  JK<sup>-1</sup>.)
  
- b. [4] Find the small-signal resistance of this diode at room temperature when the diode current is 1 mA. (Assume that the diode ideality factor or “emission factor”  $n = 1$ .) The small-signal resistance  $r$  is defined as  $r = 1/(di_D/dv_D)$ . (Hint: Since the saturation current is much smaller than 1 mA, you can approximate  $i_D$  with just  $I_S$  times the exponential term.)

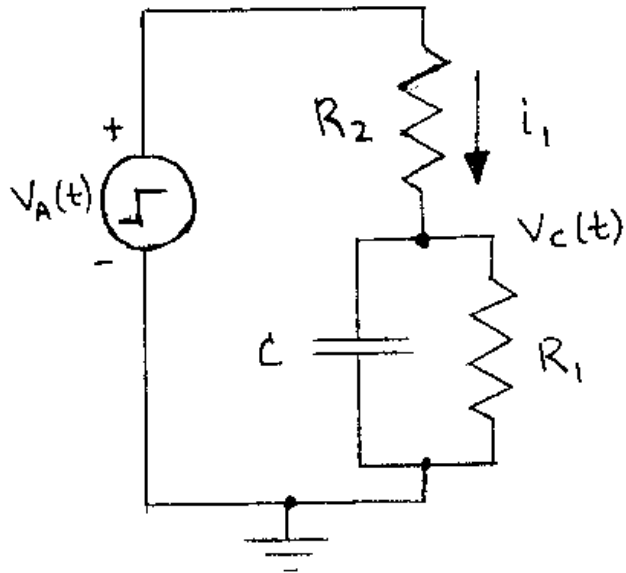**Problem 2 (16 points) First-Order Transient**

In the circuit below, let  $v_A(t) = -1$  V for  $t < 0$  and  $v_A(t) = 1$  V for  $t > 0$ .  $R_1 = 2000 \Omega$ ,  $R_2 = 3000 \Omega$ , and  $C = 10 \mu\text{F}$ .




- [2] Find  $v_C(t = 0^-)$ .
- [2] Find  $v_C(t = 0^+)$ .
- [2] Find the current  $i_1$  at  $t = 0^-$ .
- [2] Find  $i_1(t = 0^+)$ .

(continued on next page)


e. [4] Find the time constant for this circuit.

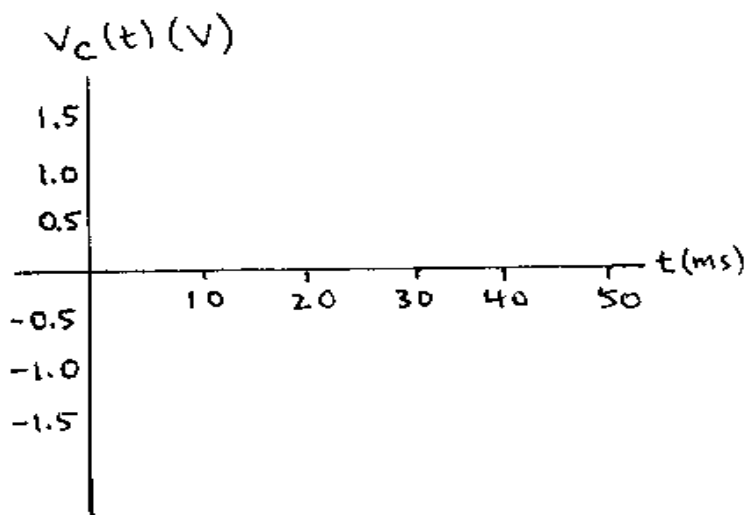d. [4] Find an expression for  $v_C(t)$  for  $t > 0$ , and sketch it below




**Problem 3 (15 points) Op-Amps**

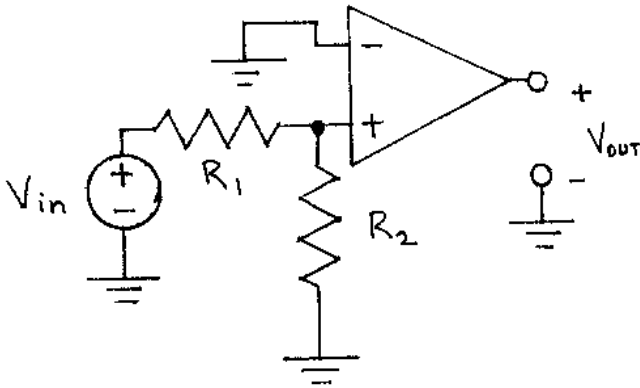- a. [7] The op-amp in the circuit below is ideal except that it has a finite gain  $A$ . If the measured voltages indicated are found to be  $v_{in} = 4.000$  V and  $v_{out} = 5.000$  V, with  $R_1 = 1$  M $\Omega$  and  $R_2 = 3$  k $\Omega$ , what is the value of  $A$ ?



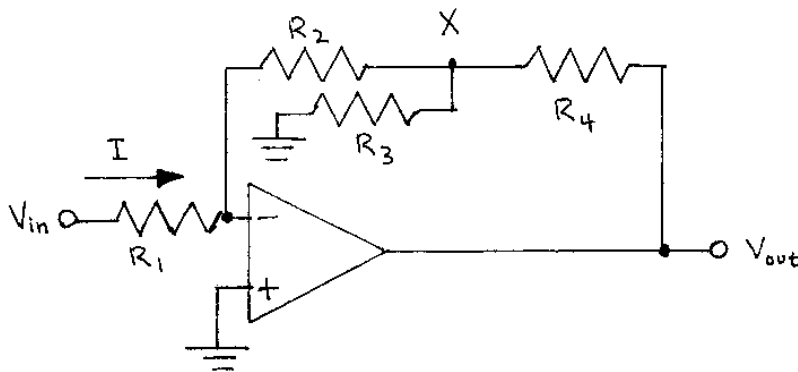
- b. [8] For the (ideal) op-amp circuit below find  $I$ ,  $v_x/v_{in}$  and  $v_{out}/v_{in}$ .  $R_1 = 6$  k $\Omega$ ,  $R_2 = 6$  k $\Omega$ ,  $R_3 = 5$  k $\Omega$ ,  $R_4 = 3$  k $\Omega$ . Assume that  $v_{in} = 6$  mV.




**Problem 4 (22 points) Diodes**

Each of the diodes in the following circuits is ideal.


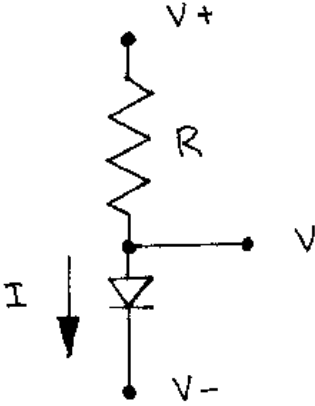
- a. [6] Find  $I$  and  $V$  for this circuit ( $R = 8\text{ k}\Omega$ ,  $V_+ = +4\text{ V}$ ,  $V_- = -3\text{ V}$ )



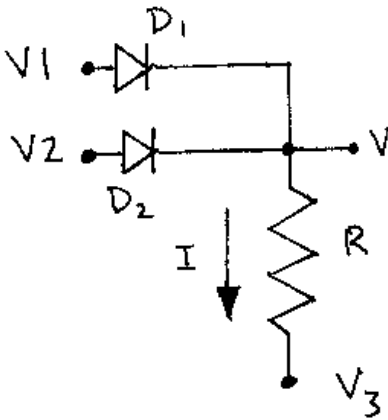- b. [8] Find  $I$  and  $V$  for this circuit ( $R = 3\text{ k}\Omega$ ,  $V_1 = +1\text{ V}$ ,  $V_2 = +3\text{ V}$ ,  $V_3 = -3\text{ V}$ ) and indicate which diodes are conducting and which are not conducting.



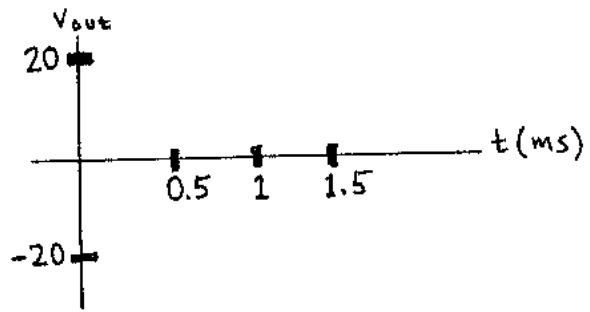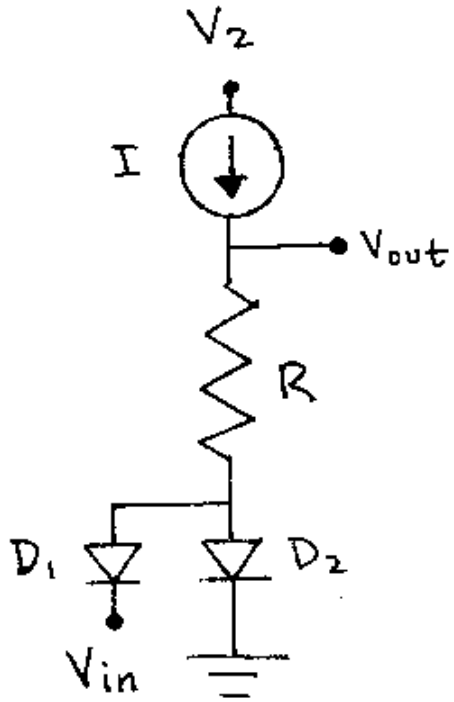
- c. [8] The voltage  $v_{in}$  in the circuit below is a 1 kHz, 10 V peak-to-peak sine wave.  $I = 2\text{ mA}$ ,  $V_2 = +10\text{ V}$ ,  $R = 1\text{ k}\Omega$ . Sketch the waveform resulting at  $v_{out}$  and indicate the values of the positive and negative peaks.





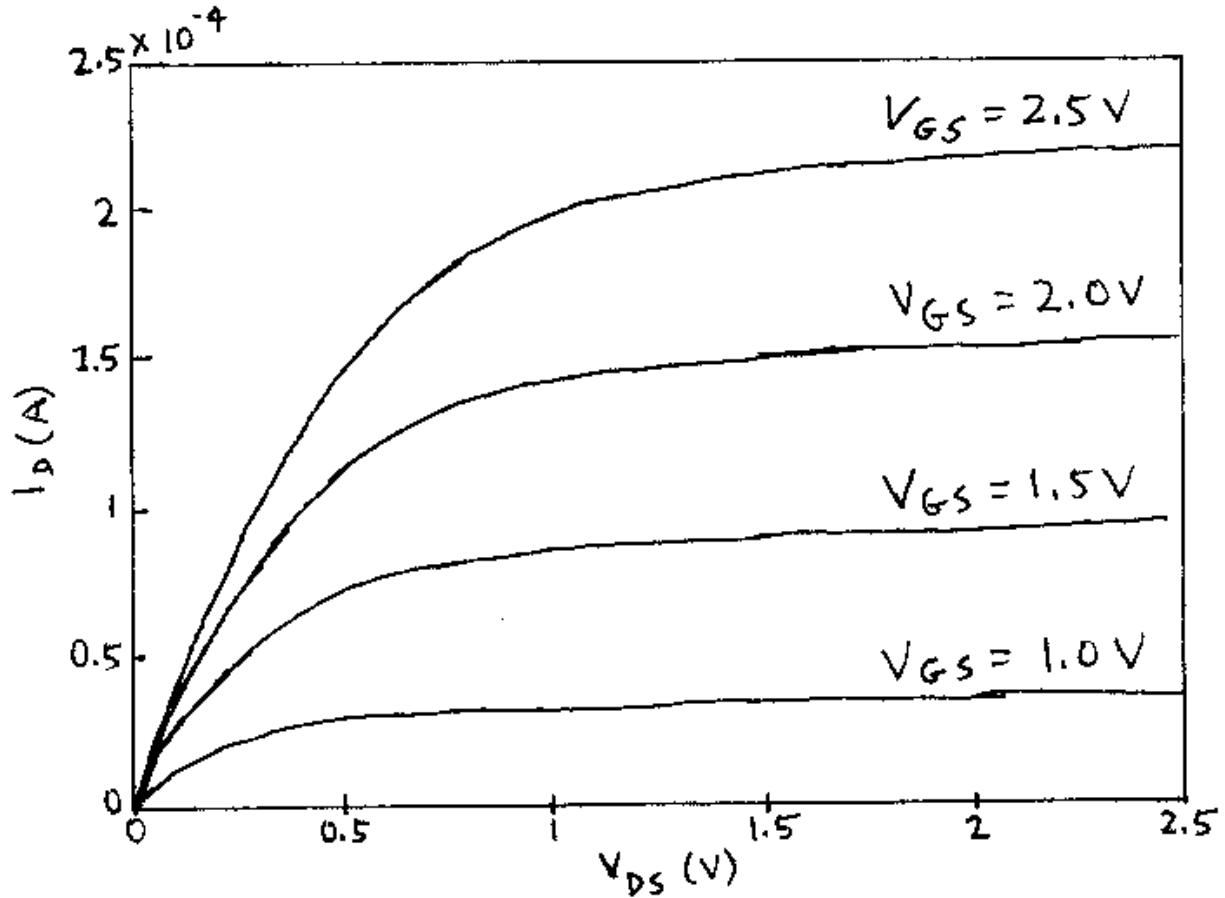**Problem 5 (23 points) MOSFET**

A set of MOSFET characteristics is shown below. Assume that  $V_T = 0.5 \text{ V}$ .




- a. [3] Indicate and label the three regions of MOSFET operation:
- b. [6] Write equations for  $I_D(V_{DS}, V_{GS})$  for each of the three regions and the conditions under which they apply. (Express your equations in unambiguous variables:  $\mu$ ,  $C_{ox}$ ,  $W$ ,  $L$ , ...).

Region: \_\_\_\_\_ Equation:

Region: \_\_\_\_\_ Equation:

Region: \_\_\_\_\_ Equation:

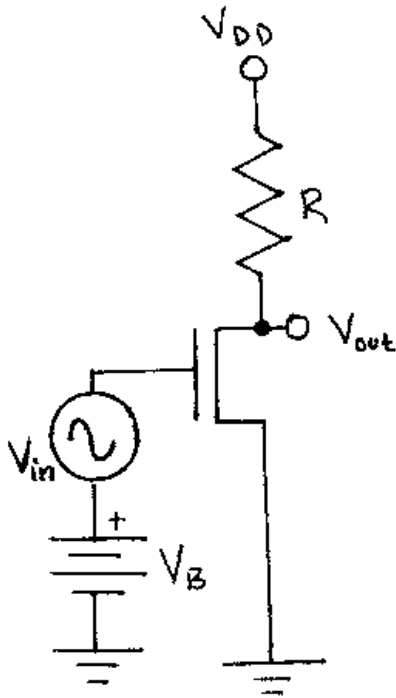The MOSFET is put in the circuit shown below ( $V_B = 1.5 \text{ V}$ ,  $R = 12.5 \text{ k}\Omega$ ,  $V_{DD} = 2.5 \text{ V}$ )



- c. [2] Identify the terminals of the MOSFET.
- d. [4] Draw the load line on the plot and find the Q point ( $I_{DQ}$ ,  $V_{DSQ}$ ).  
 $I_{DQ} = \underline{\hspace{2cm}}$  A       $V_{DSQ} = \underline{\hspace{2cm}}$  V
- e. [4] Assume that you are considering using this circuit as an analog amplifier and are worried about distortion of the signals. For a positive excursion of  $v_{in}$  of 0.5 V how much does  $v_{out}$  change (positive or negative)? For a negative excursion of  $v_{in}$  of -0.5 V how much does  $v_{out}$  change (positive or negative)?

$v_{out}$  for positive excursion of  $v_{in}$ :  $\underline{\hspace{2cm}}$  V  
 $v_{out}$  for negative excursion of  $v_{in}$ :  $\underline{\hspace{2cm}}$  V

(continued on next page)

g. [4] Draw a simple two-component circuit that represents this MOSFET under the following two extreme conditions:

$$V_{GS} - V_T > 0, V_{DS} < V_{GS} - V_T:$$



$$V_{GS} - V_T < 0:$$

