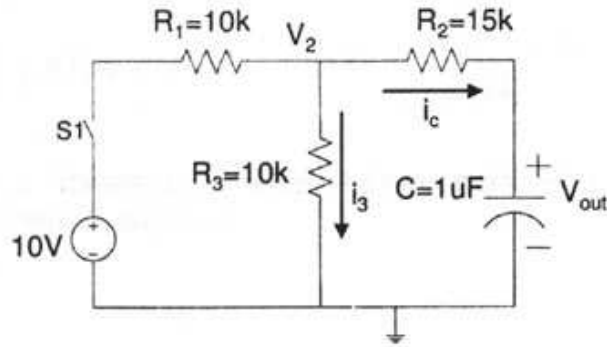



2. For  $t < 0$ , the switch was open and  $V_{out} = 0$ . At  $t = 0$  s, S1 closes. NOTE:  $\mu = 10^{-6}$ ;  $k = 10^3$ ;  $e^{-1} = 0.37$ ;  $e^{-2} = 0.14$ . Remember to put down units.



(a) (12 pts) Construct the differential equation of  $V_{out}$  in terms of all the given quantities.  
*Hint: you may solve this use Mesh or Nodal analysis, or even simpler, Thevenin equivalent circuit. Write all your steps.*

(b) (5pts) Write a closed-form expression for  $V_{out}(t)$  for  $t > 0$

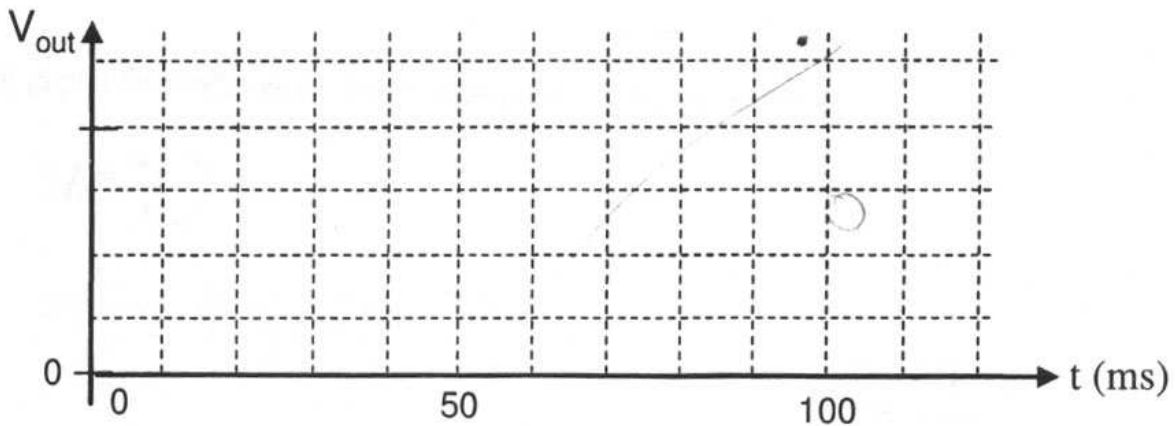(c) (8 pts) Plot  $V_{out}$  as a function of time  $t = 0$  to  $t = 100$ ms. **Label the y-axis and all key points:** starting value, 1 time constant value, value at infinity




(d) (5pts) As  $t$  approaches infinity, what value will  $i_3$  approach?

(e) (5 pts) Now, suppose someone disturbed the circuit and S1 is re-opened at 40 ms again!  
Construct the new differential equation.


(f) (6pts) What is the new time constant? What is the new expression for  $V_{out}(t)$  for  $t > 40$  ms.

(g) (5pts) in this case, as  $t$  approached infinity, what value will  $i_3$  approach?

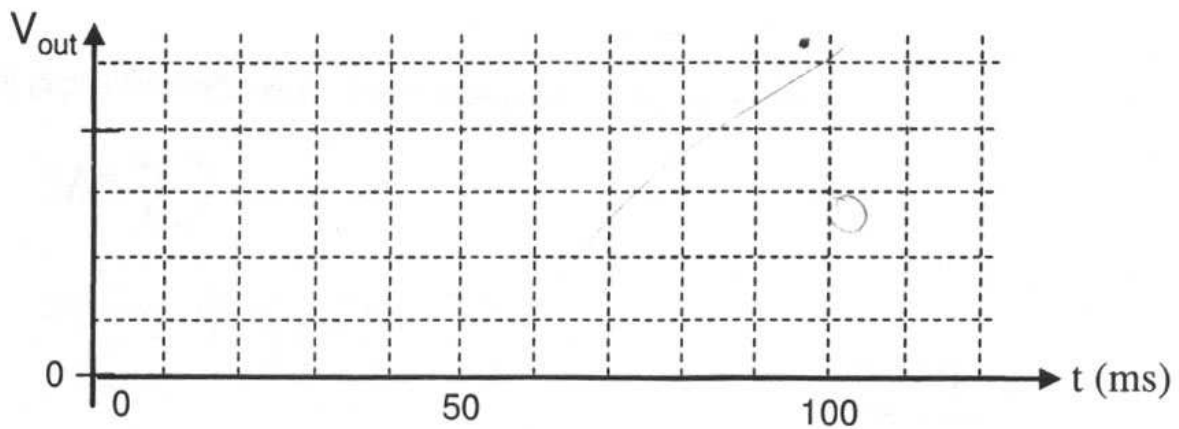(h) (5pts) plot the new  $V_{out}$  from  $t = 0$ ms to 100 ms to include the re-opening of the switch at 40 ms. **Label the y-axis and all key points:** starting value, value at switching point, 1 time constant values, value at infinity.



1. (50 pts) Equivalent Circuit.

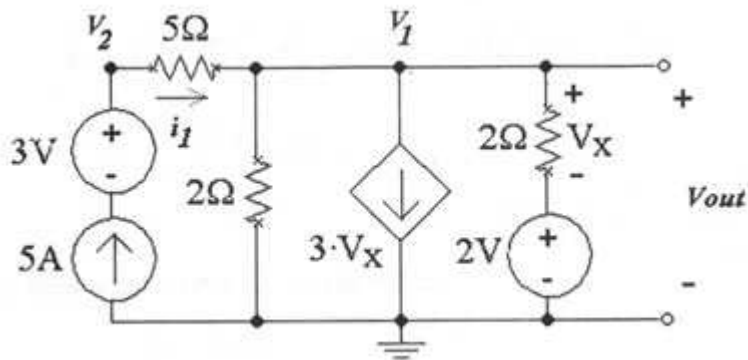


(b) (5 pts) Use KVL, write down the equation of  $V_x$  in terms of  $V_1$  and/or  $V_2$

(c) (5 pts) Use KCL, write down the equation for  $V_1$  and solve for  $V_1$ .

(d) (5 pts) Use KCL write down the equation for  $V_2$  and solve for  $V_2$ .

(e) (5 pts) Solve for  $V_{out}$  (this is simply the Thevenin Voltage)

(f) Now we short the two end terminals

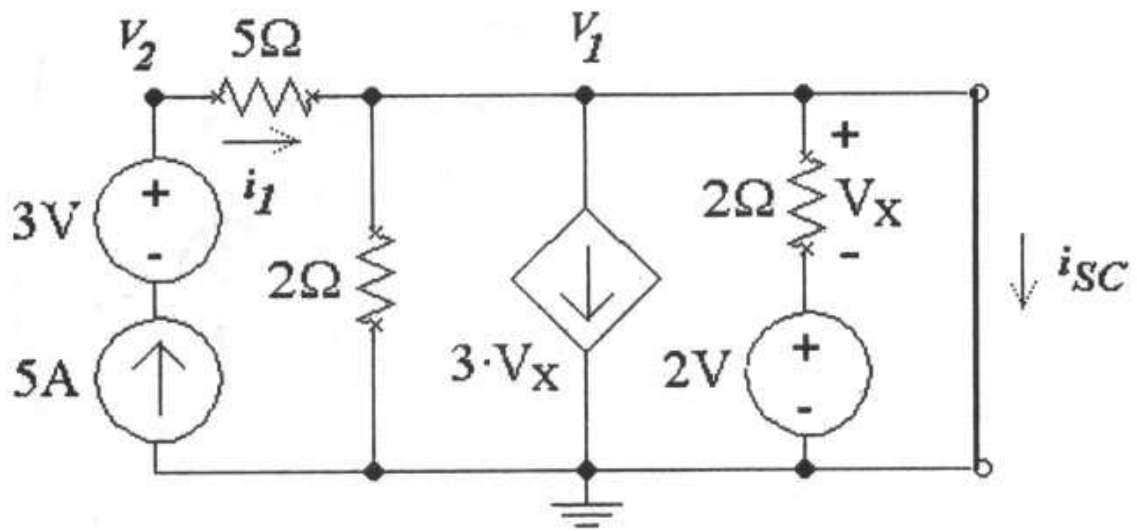

(5 pts) What is  $V_1$  ?

(g) (5 pts) What is  $V_x$ ?

(h) (5 pts) what is  $I_{sc}$ ?

(i) (5 pts) what is the Thevenin Resistance?

(j) (5 pts) draw the Thevenin Equivalent Circuit.