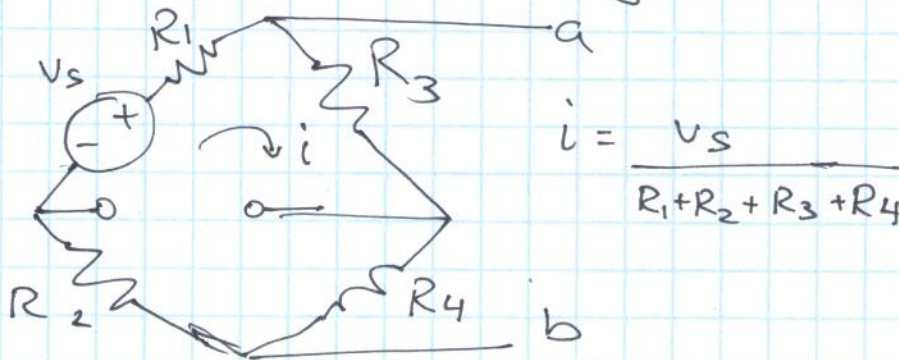


EE40 MT2.

①. $R_{th} = (R_1 + R_2) \parallel (R_3 + R_4) = \frac{(R_1 + R_2)(R_3 + R_4)}{R_1 + R_2 + R_3 + R_4}$ — 10 pts.

V_{th} : Need to use superposition thm. to make it easier to solve.
 though Mesh and Nodal Analysis received credit if solved properly. (10 pts).

Examine effect of V_s only:



$$V_{ab}|_{V_s} = i(R_3 + R_4)$$

$$= \frac{V_s(R_3 + R_4)}{R_1 + R_2 + R_3 + R_4}$$

$$V_{ab} = V_{ab}|_{V_s} + \underbrace{V_{ab}|_{I_s}}_{i}$$

↳ cont'd on next page.


points break up:

R_{th} :

- method: upto 5 pts
- execution: upto 3 pts.
- correct expression: 2 pts

V_{th} :

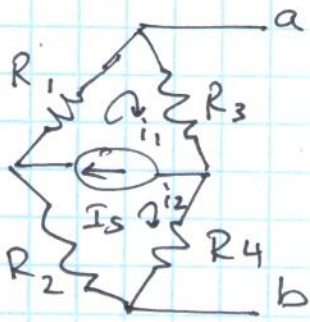- method: upto 6 pts
- execution: upto 3 pts.
- correct expr: 1 pts.




$$I_s = i_1 - i_2 \quad \text{--- ①}$$

$$V_{ab}|_{I_s} = i_1 R_3 + i_2 R_4 \quad \text{--- ②}$$

Apply KVL:
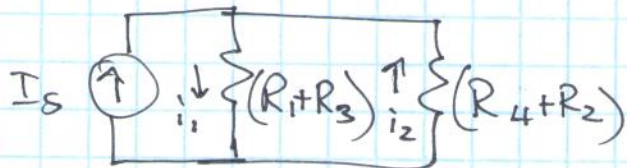
$$-i_2 R_2 - i_1 R_1 - i_1 R_3 - i_2 R_4 = 0$$



$$i_1 (R_1 + R_3) = -i_2 (R_2 + R_4)$$

$$I_s (R_1 + R_3) = (R_1 + R_3) i_1 - (R_1 + R_3) i_2$$

$$- \left(\begin{array}{l} 0 \\ 0 \end{array} = (R_1 + R_3) i_2 + (R_2 + R_4) i_2 \right)$$

$$I_s (R_1 + R_3) = - (R_1 + R_2 + R_3 + R_4) i_2$$

$$i_2 = \frac{-I_s (R_1 + R_3)}{R_1 + R_2 + R_3 + R_4}$$

$$i_1 = i_2 + I_s = \frac{-I_s (R_1 + R_3) + (R_1 + R_2 + R_3 + R_4) I_s}{R_1 + R_2 + R_3 + R_4}$$


$$\Rightarrow i_1 = \frac{(R_2 + R_4) I_s}{R_1 + R_2 + R_3 + R_4}$$

$$\Rightarrow V_{ab}|_{I_s} = \frac{R_3 (R_2 + R_4) I_s}{\Sigma R} - \frac{I_s (R_1 + R_3) R_4}{\Sigma R}$$

$$= \frac{I_s}{\Sigma R} (R_2 R_3 + \cancel{R_3 R_4} - R_1 R_4 - \cancel{R_3 R_4})$$

$$V_{ab}|_{I_s} = \frac{I_s (R_2 R_3 - R_1 R_4)}{R_1 + R_2 + R_3 + R_4}$$

Solution # 2

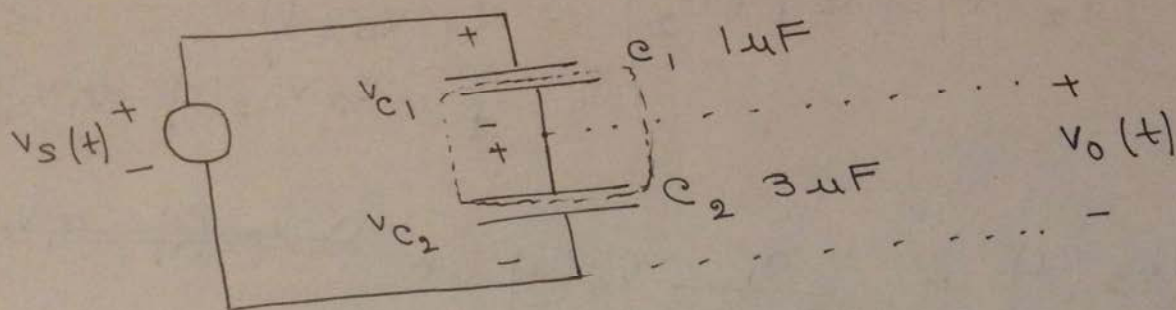

$$v_{C_1}(t) + v_{C_2}(t) = v_s(t)$$

At $t = 0$, $v_{C_1}(0) = -1 \text{ V}$ and so $v_{C_2}(0) = 1 \text{ V}$ because $v_s(0) = 0$

$$v_{C_1}(t) + v_{C_2}(t) = v_s(t)$$

~~$$C_1 v_{C_1}(t) = C_2 v_{C_2}(t)$$~~

Charge inside the dotted area is fixed

$\frac{C_2}{C_1}$

$$-C_1 v_{C_1}(t) + C_2 v_{C_2}(t) = -C_1 v_{C_1}(0) + C_2 v_{C_2}(0)$$



$$\Rightarrow -C_1 (v_s(t) - v_{C_2}(t)) + C_2 v_{C_2}(t) = C_2 v_{C_2}(0) - C_1 v_{C_1}(0)$$

$$\Rightarrow v_{c_2}(t) (c_1 + c_2) = c_1 v_s(t) + c_2 v_{c_2}(0) - c_1 v_{c_1}(0)$$

$$\therefore \Rightarrow v_{c_2}(t) = \frac{c_1}{c_1 + c_2} v_s(t) + \frac{c_2 v_{c_2}(0) - c_1 v_{c_1}(0)}{c_1 + c_2} = v_{out}(t)$$

$$\therefore v_{out}(t) = v_{c_2}(t) = \frac{c_1}{c_1 + c_2} v_s(t) + \frac{c_2 + c_1}{c_1 + c_2}$$

$$= 1 + \frac{1}{4} v_s(t)$$

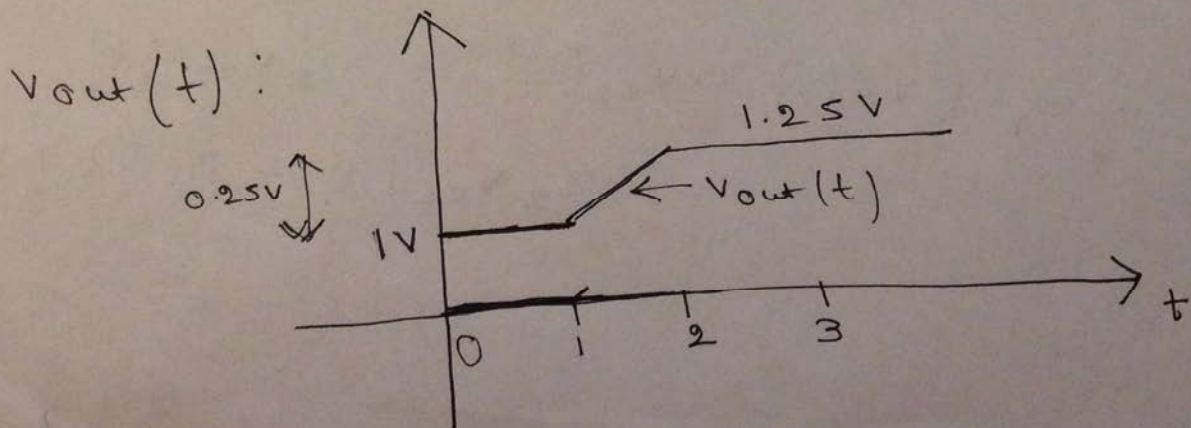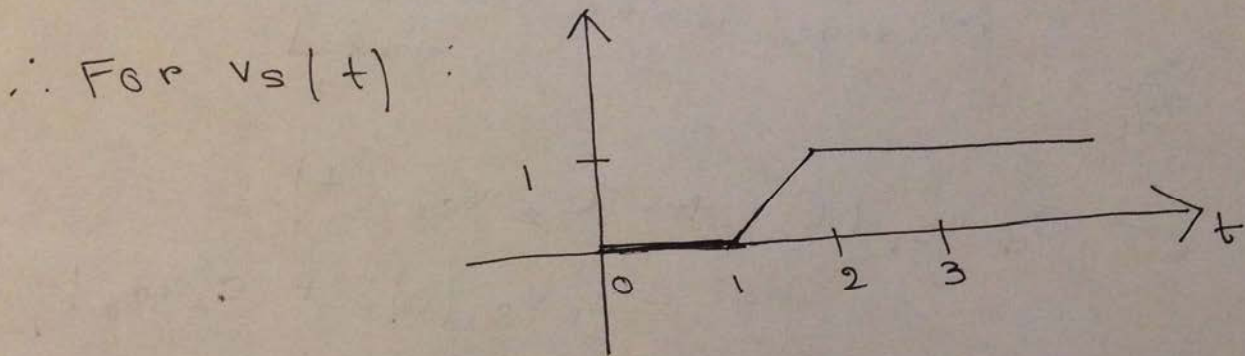

Rubric


+5 for initial value ($V_o(0) = 1V$)
and it stays flat till
 $t = 1s$)

+5 for ~~the~~ V_{out} going up
from $t = 1$ to $t = 2s$ as a
straight line

+5 for ~~the~~ final value ($V_o(t=2)$)
 $= 1.25V$
 ~~$V_o(0)$~~
and it stays flat after that)

+5 for working

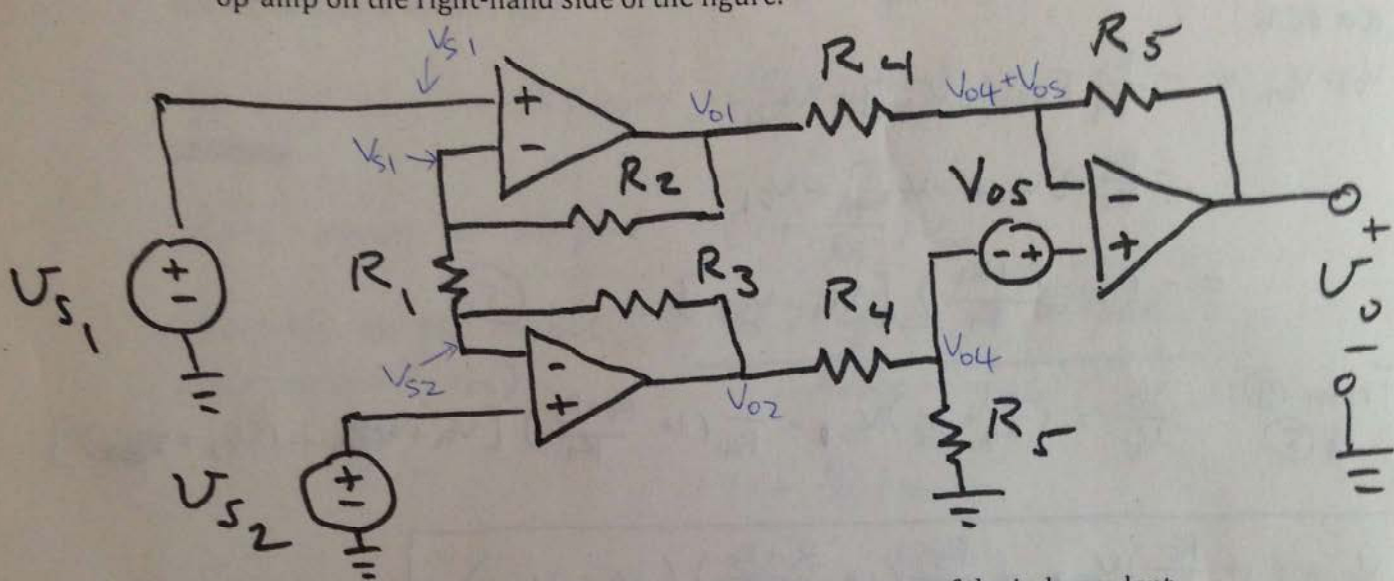3) [30 points total] In the circuit below, each of the op-amps is ideal. Voltage source V_{os} is a constant voltage used to model a non-ideality associated with the op-amp on the right-hand side of the figure.



a) [20 points] Determine an expression for v_o in terms of the independent sources and indicated circuits parameters.

$$\textcircled{1} \quad \frac{V_{o1} - V_{s1}}{R_2} = \frac{V_{s1} - V_{s2}}{R_1} = \frac{V_{s2} - V_{o2}}{R_3}$$

$$\Rightarrow V_{o1} = \frac{R_2}{R_1} [V_{s1} - V_{s2}] + V_{s1} \quad \text{--- --- } \textcircled{1a}$$

$$V_{o2} = -\frac{R_3}{R_1} [V_{s1} - V_{s2}] + V_{s2} \quad \text{--- --- } \textcircled{1b}$$

$$\textcircled{2} \quad \frac{v_o - (V_{o4} + V_{os})}{R_5} = \frac{V_{o4} + V_{os} - V_{o1}}{R_4}$$

$$\textcircled{3} \quad \frac{V_{o4} - V_{o2}}{R_4} + \frac{V_{o4}}{R_5} = 0$$

$$\textcircled{3} \Rightarrow V_{o4} \left(\frac{1}{R_4} + \frac{1}{R_5} \right) = \frac{V_{o2}}{R_4}$$

$$V_{o4} = \frac{1}{\frac{1}{R_4} + \frac{1}{R_5}} \frac{V_{o2}}{R_4} \quad \text{--- --- } \textcircled{3}'$$

$$\textcircled{2} \Rightarrow \frac{v_o}{R_5} = (V_{o4} + V_{os}) \left(\frac{1}{R_4} + \frac{1}{R_5} \right) - \frac{V_{o1}}{R_4}$$

$$\textcircled{3}' \Rightarrow \left(\frac{1}{\frac{1}{R_4} + \frac{1}{R_5}} \frac{V_{o2}}{R_4} + V_{os} \right) \left(\frac{1}{R_4} + \frac{1}{R_5} \right) - \frac{V_{o1}}{R_4}$$

$$\frac{V_o}{R_5} = \frac{V_{o2}}{R_4} + V_{os} \left(\frac{1}{R_4} + \frac{1}{R_5} \right) - \frac{V_{o1}}{R_4}$$

$$= \left(\frac{1}{R_4} + \frac{1}{R_5} \right) V_{os} + \frac{1}{R_4} (V_{o2} - V_{o1}) \quad \dots \quad (4)$$

From Qa & Qb

$$V_{o2} - V_{o1} = -\frac{R_3}{R_1} [V_{s1} - V_{s2}] + V_{s2}$$

$$- \frac{R_2}{R_1} [V_{s1} - V_{s2}] - V_{s1}$$

$$= - \left(1 + \frac{R_2 + R_3}{R_1} \right) [V_{s1} - V_{s2}] \quad \dots \quad (5)$$

From (4) & (5): $\frac{V_o}{R_5} = \left(\frac{1}{R_4} + \frac{1}{R_5} \right) V_{os} - \frac{1}{R_4} \left(1 + \frac{R_2 + R_3}{R_1} \right) [V_{s1} - V_{s2}]$

$$V_o = \left(1 + \frac{R_5}{R_4} \right) V_{os} - \frac{R_5}{R_4} \left(1 + \frac{R_2 + R_3}{R_1} \right) (V_{s1} - V_{s2})$$

output DC
shift due to
 V_{os}

Amp's gain

differential input

b) [10 points] For this circuit, if you have some freedom in choosing resistor values, what choice(s) should you make to minimize the effect of non-zero V_{os} relative to the signal inputs v_{s1} and v_{s2} ?

gain of the amplifier: $\frac{R_5}{R_4} \left(1 + \frac{R_2 + R_3}{R_1}\right)$

V_{os} 's effect at output: $\left(1 + \frac{R_5}{R_4}\right) V_{os}$

refer V_{os} to the input = V_{os} 's effect at output
(input referred V_{os}) $\frac{\text{Amp gain}}{\text{Amp gain}}$

$$= \frac{\left(1 + \frac{R_5}{R_4}\right) V_{os}}{\frac{R_5}{R_4} \left(1 + \frac{R_2 + R_3}{R_1}\right)}$$

$$= \frac{\left(1 + \frac{R_4}{R_5}\right) V_{os}}{1 + \frac{R_2 + R_3}{R_1}}$$

want to minimize this input referred V_{os} , so we want to increase the gain of the amplifier, meaning increasing $\frac{R_5}{R_4} \left(1 + \frac{R_2 + R_3}{R_1}\right)$


so increasing $\frac{R_2 + R_3}{R_1}$ and/or decreasing $\frac{R_4}{R_5}$

↑ effective

↑ not that effective.

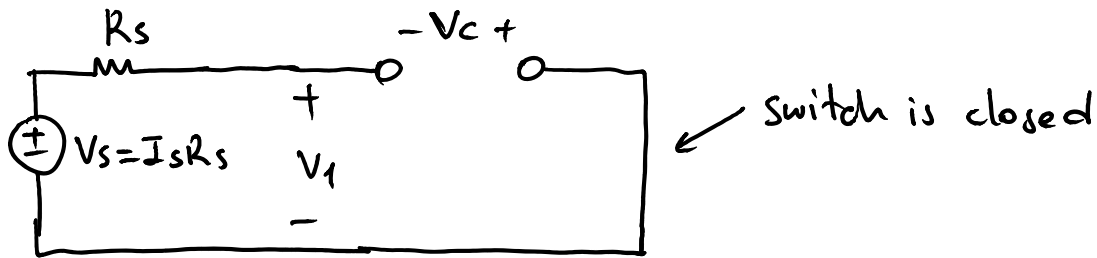
Q4

at $t=0^-$ capacitor is at steady state \rightarrow open circuit



KVL: $V_c + I_s R_s = 0 \rightarrow V_c(0^-) = -I_s R_s = V_i$

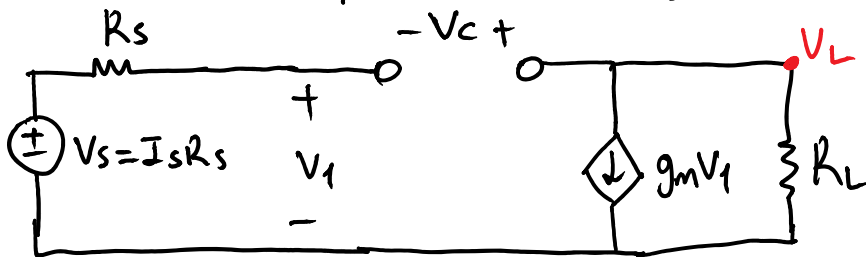at $t=0^+$ switch opens. At steady state ($t \rightarrow \infty$), capacitor becomes an open circuit again.




$V_L = -g_m V_1 R_L$, $V_1 = I_s R_s$ since there is no current through R_s

$V_L = -g_m R_L I_s R_s$

KVL: $V_c + I_s R_s - V_L = 0 \rightarrow V_c = -I_s R_s - g_m R_L I_s R_s$


$V_c(\infty) = -I_s R_s (g_m R_L + 1) = V_f$

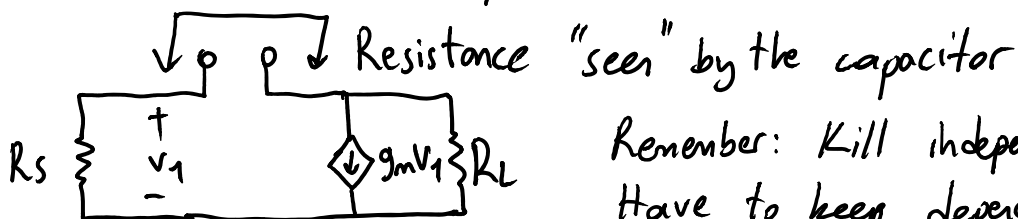Time constant: Need to find resistance "seen" by the capacitor. Then $Z = R_{eq} C$



Remember: Kill independent sources. Have to keep dependent sources.

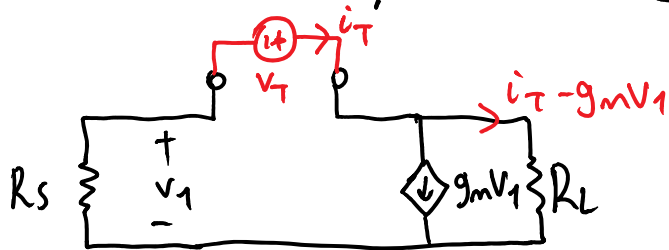Method: apply a test voltage, look at how much current is drawn by the circuit. Resistance looking into that terminal is equal to $\frac{\text{test voltage}}{\text{current drawn}} = \frac{V_T}{i_T}$



$$V_1 = -i_T R_s$$

KVL: $(i_T - g_m V_1) R_L - V_1 - V_T = 0$, $i_T R_L + g_m i_T R_s R_L + i_T R_s = V_T$


$$\rightarrow i_T (R_L + R_s + g_m R_L R_s) = V_T$$

$$\rightarrow R_{eq} = R_L + R_s + g_m R_L R_s$$

$$Z = (R_L + R_s + g_m R_L R_s) C$$

Capacitor equation: $V_C(t) = V_f + (V_i - V_f) e^{-t/Z}$
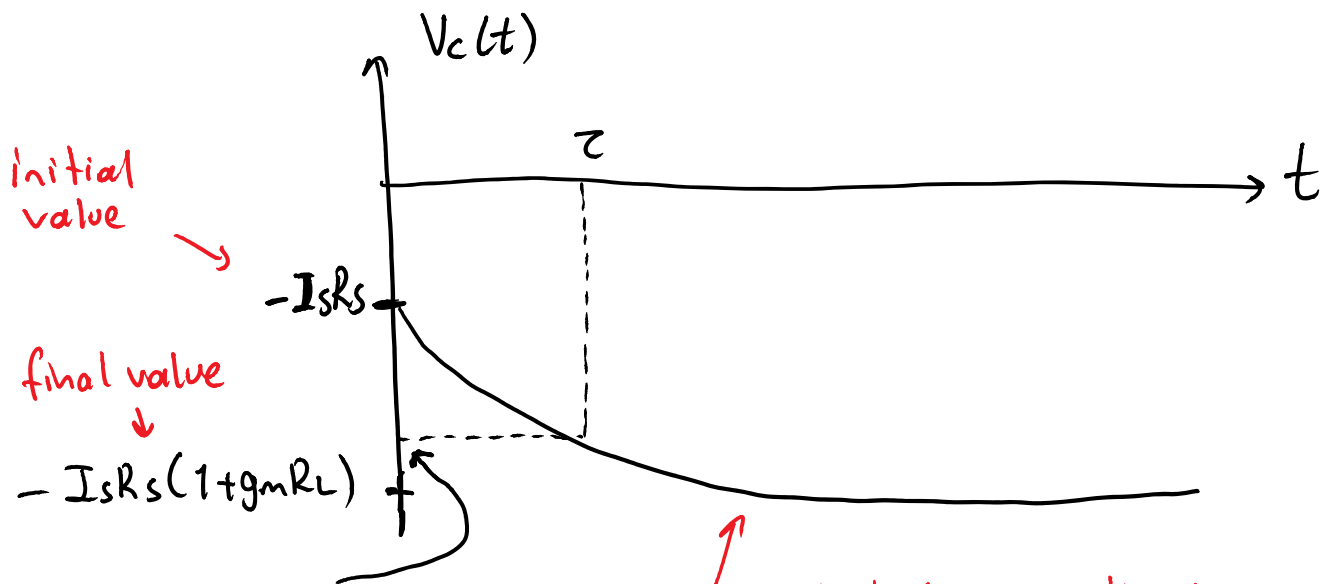
$$V_C(t) = -I_s R_s (1 + g_m R_L) + (I_s R_s g_m R_L) e^{-t/Z}$$



$$I_s R_s g_m R_L \left(\frac{1}{e} - 1 \right) - I_s R_s$$

$$\approx -I_s R_s g_m R_L \times 0.632 \quad (\text{assuming } g_m R_L \gg 1)$$

exponential decay with time constant Z