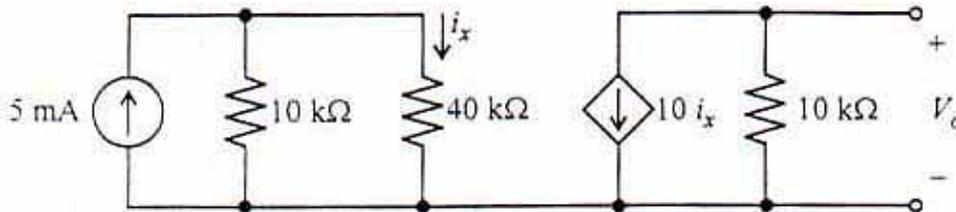


**EE40 Midterm 2 Solutions  
Spring 2000**

**Problem #1: Circuits with Dependent Sources [20 points]**


a) Find  $V_0$ . [4 pts]



Current divider formula:  $i_x = (10 \text{ kohm}/(10 \text{ kohm} + 40 \text{ kohm})) * 5 \text{ mA} = 1 \text{ mA}$   
 $V_0 = (-10i_x)(10 \text{ kohm}) = (-10 * 1 \text{ mA})(10 \text{ kohm}) = -100 \text{ V}$

b) In the circuit below, the independent source values and resistance are known. Use the **nodal analysis technique** to write **3 equations sufficient to solve for  $V_a$ ,  $V_b$ , and  $V_c$** . To receive credit, you must write your answer in the box below.

[6 pts] DO NOT SOLVE THE EQUATIONS!

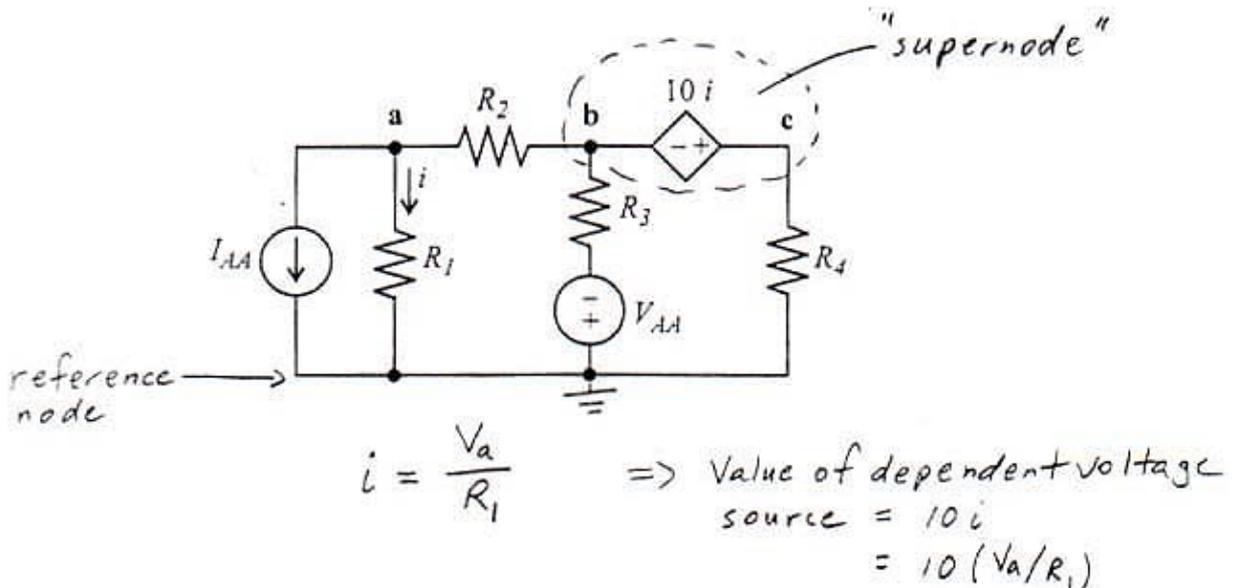


Write the nodal equations here: Note that the only unknowns in these equations are  $V_a$ ,  $V_b$ ,  $V_c$

node a:  $I_{AA} + V_a/R_1 + (V_a - V_b)/R_2 = 0$

supernode:  $(V_b - V_a)/R_2 + (V_b + V_{AA})/R_3 + V_c/R_4 = 0$

relationship due to dependent source:  $V_c - V_b = 10V_a/R_1$

c) Consider the following circuit:

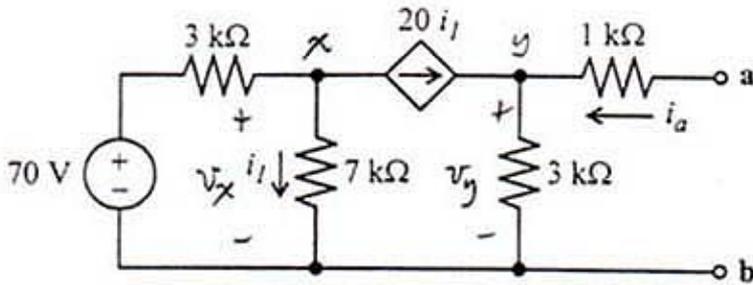

i) Find the voltage  $V_{ab}$  [5 pts]


$$i_1 = V_x / 7 \text{ kohm}$$

$$\text{Applying KCL to node x: } 70 - V_x / 3 \text{ kohm} = i_1 + 20i_1 = 21i_1 = 21V_x / 7 \text{ kohm}$$

$$70 - V_x = 9V_x \Rightarrow V_x = 7$$

$$i_1 = 7 \text{ V} / 7 \text{ kohm} = 1 \text{ mA}; i_a = 0 \Rightarrow V_{ab} = V_y = 20i_1(3 \text{ kohm}) = 60 \text{ V}$$

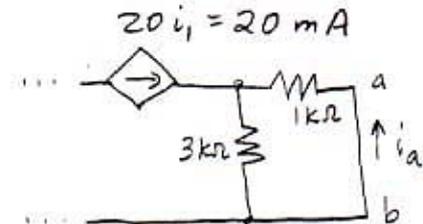
ii) What is the current  $i_a$  when the terminals **a** and **b** are shorted together? [3 pts]



Current divider formula:

$$i_a = (3 \text{ kohm} / (3 \text{ kohm} + 1 \text{ kohm}))(-20 \text{ mA}) = -15 \text{ mA}$$

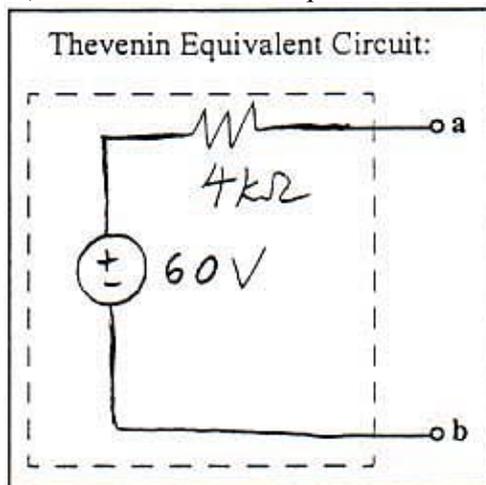iii) Draw the Thevenin Equivalent Circuit. [2 pts]




$$V_{th} = V_{oc} = V_{ab} \text{ from part (i)}$$

$$R_{th} = -V_{oc} / I_{sc} = V_{ab} \text{ from part (i)} / i_a \text{ from part (ii)} = 60 \text{ V} / -15 \text{ mA} = 4 \text{ kohm}$$

**Problem #2: Transient Response [30 points]**

Problem #1: Circuits with Dependent Sources [20 points]

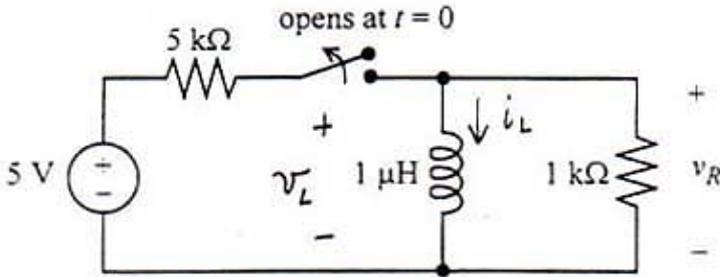a) In the circuit below, the switch has been in the closed position for a long time.



i) Find the value of  $V_R$  just after the switch opens ( $t = 0^+$ ). [3 pts]


Before the switch is opened, the voltage across the inductor is zero ( $V_L = L di/dt = 0$ ), i.e. the 1 kohm resistor is shorted out by the inductor. The current flowing through the inductor  $i_L(0^-) = 5 \text{ V}/5 \text{ kohm} = 1 \text{ mA}$ .  
 $i_L(0^+) = i_L(0^-) = 1 \text{ mA}$ , since inductor current cannot change instantaneously.  
 $V_R(0^+) = -i_L(0^+)(1 \text{ kohm}) = (-1 \text{ mA})(1 \text{ kohm}) = -1 \text{ V}$

ii) How much energy is dissipated in the 1 kohm resistor after the switch is opened? [2 pts]

All of the energy which was stored in the inductor at  $t = 0$  is dissipated in the 1 kohm resistor after the switch is closed.

$$E = 0.5L[i(0)]^2 = 0.5(10^{-6} \text{ H})(10^{-3} \text{ A})^2 = 0.5 \cdot 10^{-12} \text{ J} = 0.5 \text{ pJ}$$

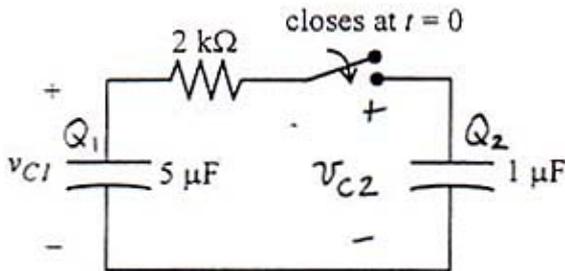b) In the circuit below, the 5 microF capacitor is initially charged to 5 V ( $V_{C1}(0^-) = 5 \text{ V}$ ). (The 1 microF capacitor is initially uncharged.) The switch is then closed at time  $t = 0$ . What is the final value of  $V_{C1}$ ? [5 pts]



Conservation of charge:

$$Q_{1\text{final}} + Q_{2\text{final}} = Q_{1\text{initial}}$$

$$(5 \text{ microF})(V_{C1\text{final}}) + (1 \text{ microF})(V_{C2\text{final}}) = (5 \text{ microF})(V_{C1\text{initial}})$$


In the final state ( $t = 0$ ), the voltages across the capacitors are equal, i.e.  $V_{C1\text{final}} = V_{C2\text{final}}$

$$(6 \text{ microF})(V_{C1\text{final}}) = (5 \text{ microF})(5 \text{ V})$$


$$V_{C1\text{final}} = (5/6)(5 \text{ V}) = 4.17 \text{ V} \sim 4.2 \text{ V}$$

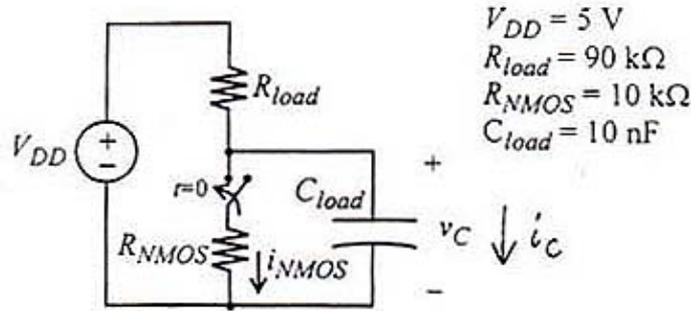c) The following is a circuit model for an NMOS inverter, in which the transistor is turned on at time  $t = 0$ :

NMOS is off  
for  $t < 0$   
 $\Rightarrow i_{NMOS} = 0$   
for  $t \leq 0^-$



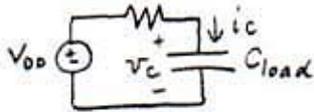i) What is the value of  $V_C$  at  $t = 0^-$ ? [3 pts]



In steady state (before the switch closes),  $i_C = 0$ ;  $V_C = V_{DD} = 5V$

ii) What is the value of  $i_{NMOS}$  at  $t = 0^+$  [3 pts]

$V_C(0^+) = V_C(0^-)$ , since capacitor voltage cannot change instantaneously.

$i_{NMOS}(0^+) = V_C(0^+)/R_{NMOS} = 5 V/10 \text{ kohm} = 0.5 \text{ mA}$


iii) What is the final value of  $V_C$ ? [3 pts]

In steady state,  $i_C = 0$ . Therefore, we have a simple voltage divider:

$$V_C(\infty) = [R_{NMOS}/(R_{NMOS} + R_{load})] * V_{DD}$$

$$= (10/(10+90))(5 V) = 0.5 V$$

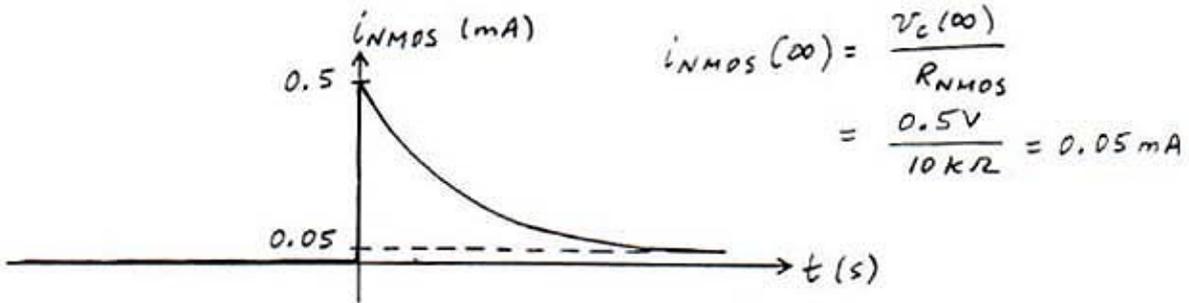iv) Neatly sketch the graph of  $i_{NMOS}$  for all  $t$ , labeling the axes. [5 pts]



v) Write an equation for  $i_{NMOS}$  as a function of time, for  $t > 0$ . [6 pts]

$$i_{NMOS} = i_{NMOS\text{final}} + [i_{NMOS}(0^+) - i_{NMOS\text{final}}]e^{-(t/Req)C}$$

$R_{eq}$  is equivalent resistance seen by the capacitor:  $R_{eq} = R_{load} \parallel R_{NMOS}$

$R_{eq} = (90)(10)/(90+10) = 9 \text{ kohm}$ ;  $R_{eq}C = (9 \text{ kohm})(10 \text{ nF}) = 9 \cdot 10^{-5} \text{ s}$

Equation:  $0.05 + 0.45e^{-(t/9 \cdot 10^{-5})} \text{ mA}$


**Problem #3: Op-Amp Circuits [25 points]**

Assume the op-amps in this problem are ideal.

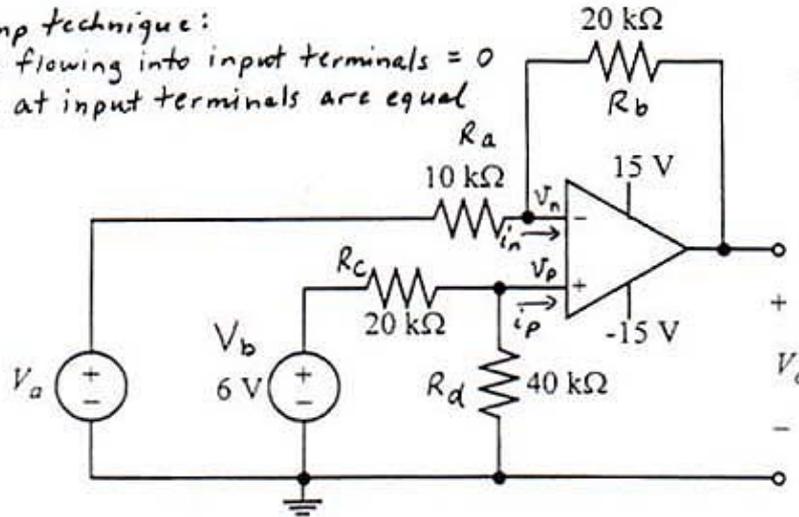a) Consider the following circuit:

ideal op-amp technique:

- currents flowing into input terminals = 0
- voltages at input terminals are equal



Apply KCL at (-) node:

$$\frac{V_a - V_n}{R_a} + \frac{V_o - V_n}{R_b} = 0$$

$$\Rightarrow V_o = -\frac{R_b}{R_a} (V_a - V_n) + V_n$$

Since  $i_p = 0$ , we can use the voltage divider formula:

$$V_p = \frac{R_d}{R_c + R_d} V_b$$

$$\Rightarrow V_o = -\frac{R_b}{R_a} \left[ V_a - \frac{R_d}{R_c + R_d} V_b \right] + \frac{R_d}{R_c + R_d} V_b$$

i) Find an expression for  $V_o$  as a function of  $V_a$ . [6 pts]

This is a difference amplifier circuit (which you've studied in the lab) with  $R_a/R_b = R_c/R_d = 1/2$

$$V_o = (R_b/R_a)(6 - V_a) = 2(6 - V_a) = 12 - 2V_a$$

ii) Find  $V_o$  for  $V_a = 2$  V. [3 pts]

$$V_o = 12 - 2(2) = 8 \text{ V}$$

iii) For what values of  $V_a$  will the op-amp be saturated? [6 pts]


$$V_o = 12 - 2V_a \Rightarrow V_a = (12 - V_o)/2$$

$$V_o \text{ saturates at } 15 \text{ V: } V_a \leq (12 - 15)/2 = -3/2 \text{ V}$$

$$V_o \text{ saturates at } -15 \text{ V: } V_a \geq (12 - (-15))/2 = 27/2 \text{ V}$$

Values of  $V_a$  for which the op-amp will be saturated:  $V_a \leq -1.5 \text{ V}$ ;  $V_a \geq 13.5 \text{ V}$

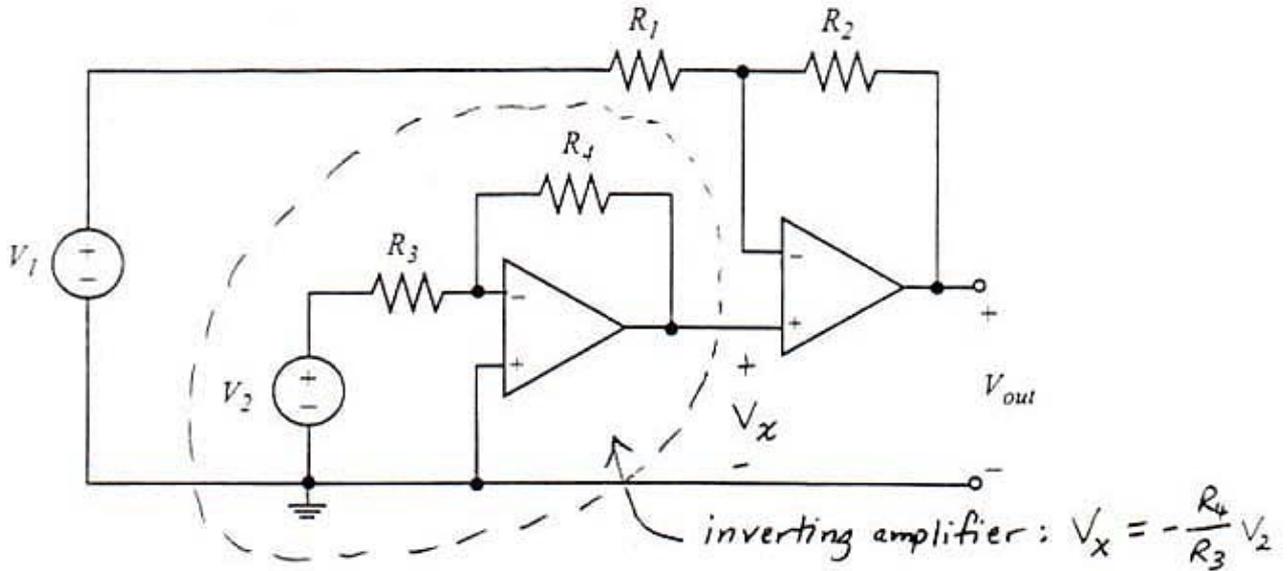
b) In the following circuit, the op=amps are operating linearly.




Find  $V_{out}$  in terms of  $V_1$ ,  $V_2$ ,  $R_1$ ,  $R_2$ ,  $R_3$ ,  $R_4$  [10 pts] (Hint: The superposition method might be helpful here.)

Find the individual contributions of each voltage source:

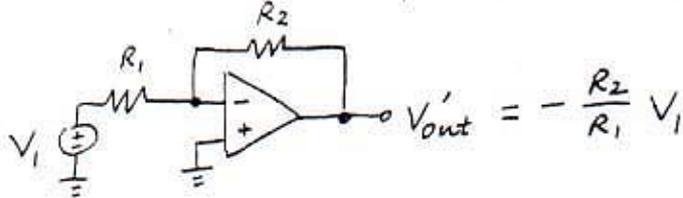i) Set  $V_2$  to 0 V:  $V_x = 0$ , so the circuit simplifies to a simple inverting amplifier



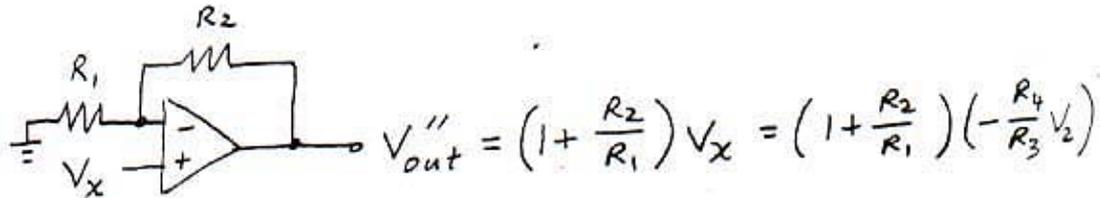ii) Set  $V_1$  to 0 V: circuit simplifies to simple non-inverting amplifier




Add the contributions of each source together:

$$V_{out} = V_{out}' + V_{out}'' = -\left(\frac{R_2}{R_1}\right)(V_1) - \left(\frac{R_4}{R_3}\right)\left(1 + \frac{R_2}{R_1}\right)(V_2)$$

**Problem #4: Semiconductor properties; p-n diodes [25 points]**

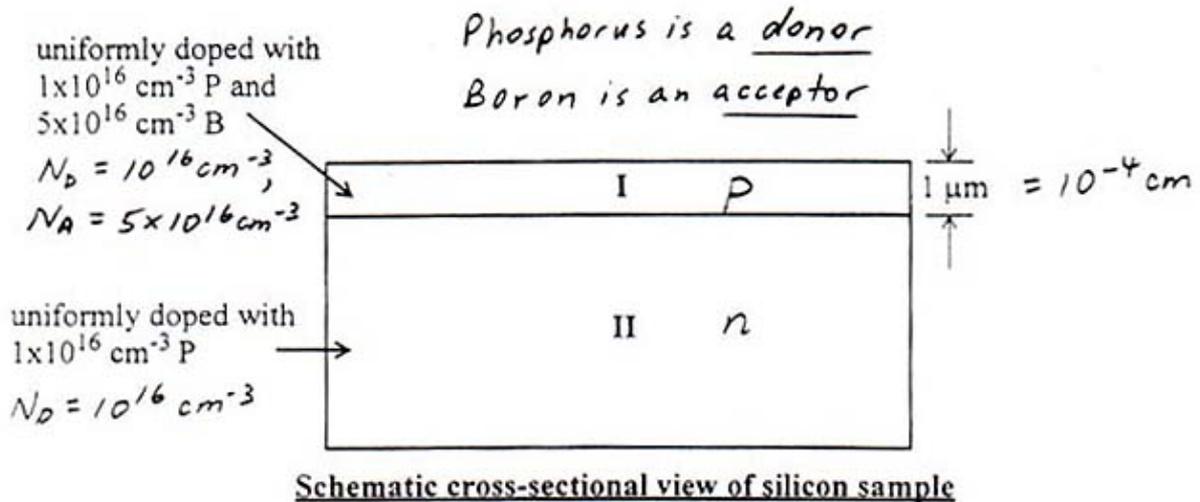a) Consider a silicon sample maintained at 300K under equilibrium conditions, uniformly doped with  $1 \cdot 10^{16} \text{ cm}^{-3}$  phosphorus atoms. The surface region of the sample is additionally doped uniformly with  $5 \cdot 10^{16} \text{ cm}^{-3}$  boron atoms, to a depth of 1 microm, as shown in the figure below.



i) In the figure above, indicate the type of regions (I and II) by labelling them as "n" or "p" type. [2 pts]

ii) What are the electron and hole concentrations in Region I? [5 pts]

$N_A > N_D$ , and  $N_A \gg n_i$  so  $p = N_A - N_D = 5 \times 10^{16} - 1 \times 10^{16} = 4 \times 10^{16}$   
 $pn = n_i^2 \Rightarrow n = n_i^2/p = (1.45 \times 10^{16})^2 / 4 \times 10^{16} = 5256$   
 $n = 5256 \text{ cm}^{-3}$ ;  $p = 4 \times 10^{16} \text{ cm}^{-3}$

iii) What is the sheet resistance of Region I? [5 pts]

$\rho = 1/(q\mu_n n + q\mu_p p) \sim 1/q\mu_p p$   
 >From plot on Page 2,  $\mu_p \sim 350 \text{ cm}^2/\text{Vs}$  for  $N_A + N_D = 6 \times 10^{16} \text{ cm}^{-3}$   
 $R_s = \rho/t = 1/q\mu_p p = [(1.602 \times 10^{-19})(350)(4 \times 10^{16})(10^{-4})]^{-1} = 4458 \text{ ohm/square}$

iv) Suppose any voltage between 0 V and 5 V can be applied to Region I. What fixed voltage ("bias") would you apply to Region II, to guarantee that no current would ever flow between Region I and Region II? Briefly explain your answer. [3 pts]


To prevent current from flowing, we need to ensure that the p-n junction will never be forward biased. Thus, the n-type region must be biased at 5 V or higher.

b) If a diode is operated only within a small range of forward-bias voltages, its behavior can be accurately modeled by a resistor, whose value is dependent on the bias voltage. Derive an expression for the diode "small-signal" resistance:

$R_{\text{diode}} = (dI/dV)^{-1}$  in terms of the saturation current  $I_s$ , the bias voltage  $V$ , and the absolute temperature  $T$ . [5 pts]

$I = I_s(e^{qV/kT} - 1)$   
 $dI/dV = I_s(q/kT)e^{qV/kT}$   
 $R_{\text{diode}} = (kT/qI_s)e^{-qV/kT}$

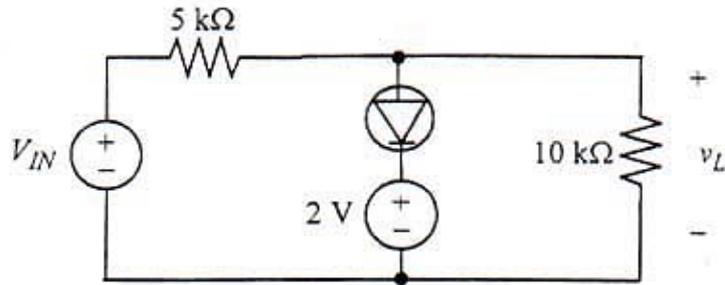
c) Plot  $V_L$  vs.  $V_{IN}$  for  $-10 \text{ V} < V_{IN} < 10 \text{ V}$  on the axes provided, for the circuit below. Note that the diode is a perfect rectifier. Label the axes. [5 pts]



When the diode is off, we have a simple voltage-divider circuit

$$v_L = \frac{10}{5+10} V_{IN} = \frac{2}{3} V_{IN}$$

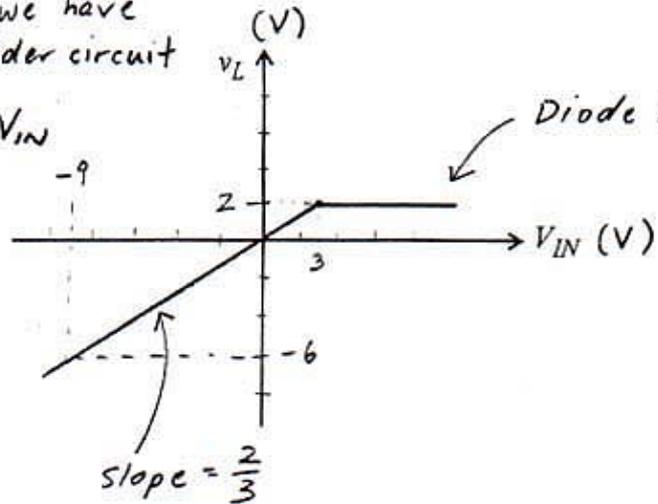Diode turns on when  $v_L$  reaches 2V, i.e. when  $\frac{2}{3} V_{IN} = 2V$ , or  $V_{IN} = 3V$



Posted by HKN (Electrical Engineering and Computer Science Honor Society)  
University of California at Berkeley

If you have any questions about these online exams  
please contact [examfile@hkn.eecs.berkeley.edu](mailto:examfile@hkn.eecs.berkeley.edu).