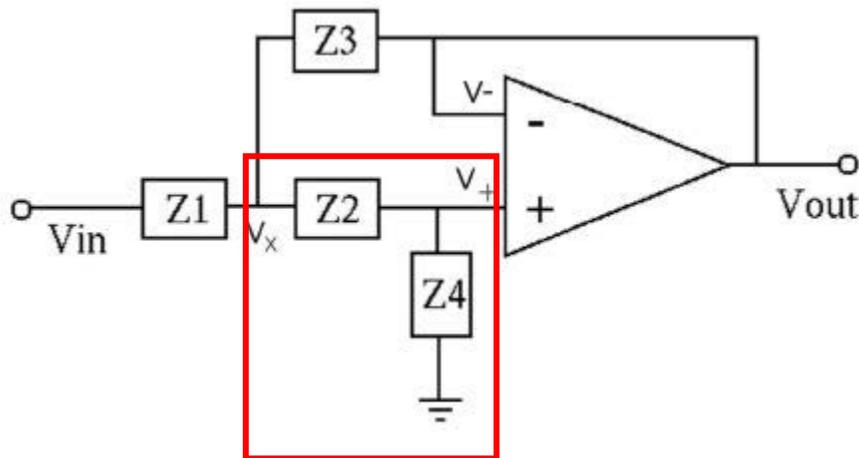


Grader: Terry Kim

Problem1

a) Consider the circuit below.



from the negative feedback, we know $V_+ = V_- = V_{out}$

KCL at V_x node

$$\frac{V_{in} - V_x}{Z_1} = \frac{V_x - V_{out}}{Z_3} + \frac{V_x - V_{out}}{Z_2} \quad (5pts)$$

Voltage divider in the red box above with Z_2 & Z_4


$$V_{out} = \left(\frac{Z_4}{Z_2 + Z_4} \right) V_x$$

$$V_x = \frac{Z_2 + Z_4}{Z_4} V_{out} \text{ or}$$

$$V_x = \left(1 + \frac{Z_2}{Z_4} \right) V_{out} \quad (5pts)$$

(b) Find ω such that $v_x = 0$ for this circuit at $t = \infty$.

(5 points)

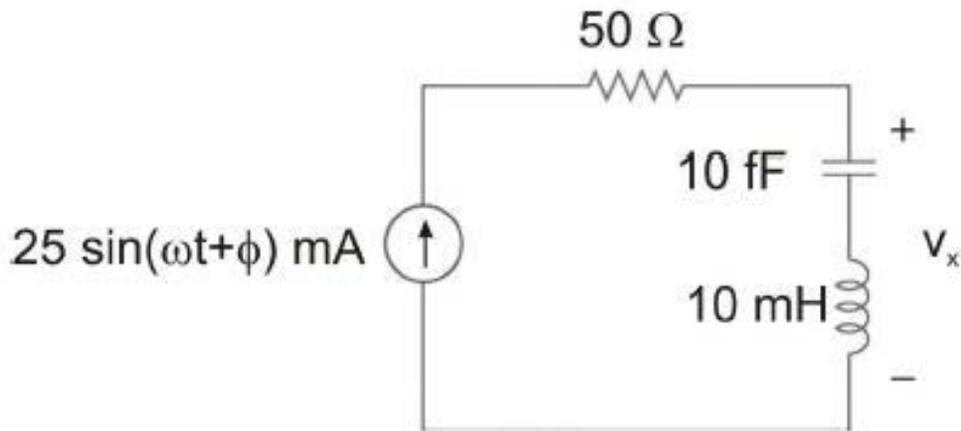

In order to have

$V_x = 0$, we need to have impedance across V_x should be zero.

$$Z_x(\omega) = Z_c(\omega) + Z_L(\omega) = 0$$

$$Z_x(\omega) = \frac{1}{j\omega C} + j\omega L = 0$$

$$Z_x(\omega) = \frac{-j}{\omega C} + j\omega L = 0$$

$$Z_x(\omega) = j\left(\frac{-1}{\omega C} + \omega L\right) = 0$$

$$Z_x(\omega) = 0 \text{ when } \left(\frac{-1}{\omega C} + \omega L\right) = 0$$

$$\omega = \frac{1}{\sqrt{LC}} = \frac{1}{\sqrt{10 \times 10^{-15} \times 10 \times 10^{-3}}} = \frac{1}{\sqrt{1 \times 10^{-16}}}$$

$$\omega = 1 \times 10^8 \frac{\text{rad}}{\text{s}}$$

(5pts)

a) What is the value of V_c at $t = 0^+$? Write It in the **BOX BELOW**. (5 points)


$$V_c(0^-) = \frac{R_2}{R_1 + R_2} V_S = V_c(0^+)$$

Since V_c cannot change instantaneously.

b) Using whatever method you like, provide a symbolic expression for the voltage $V_c(t)$ for $t > 0$ in the **BOX BELOW**. (15 points)

Open, no
current
can flow

Equivalent circuit is:

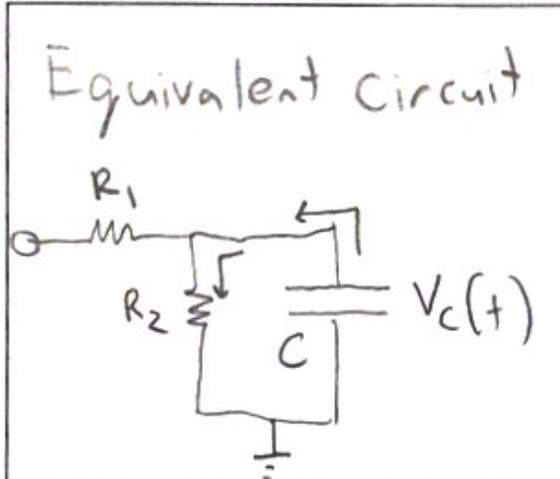

$\tau = R_2 C$


$$V_c(t) = V_c(\infty) + [V_c(0^+) - V_c(\infty)] \cdot e^{-t/\tau}$$

$V_c(\infty) = 0 \Rightarrow$


$$V_c(t) = \frac{R_2}{R_1 + R_2} \cdot V_s \cdot e^{-t/R_2 C}$$

MT#2 Problem 3

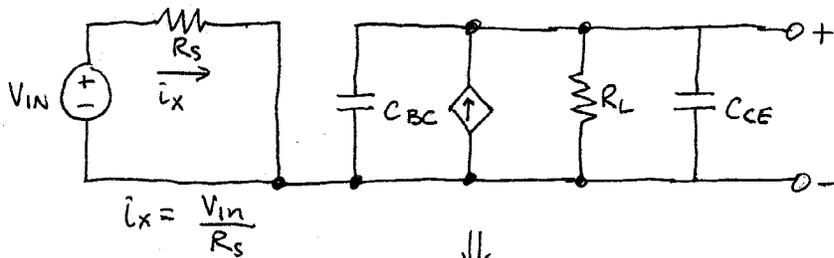
(a) assuming V_{BE} is a DC voltage: \rightarrow it becomes a short circuit



$$i_x = \frac{V_{in}}{R_S}$$

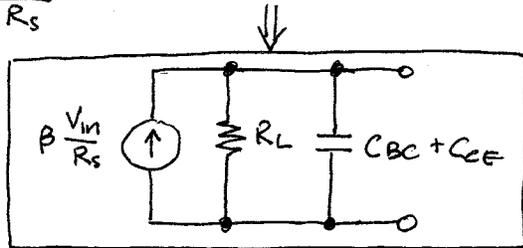


assuming V_{BE} is an AC voltage:

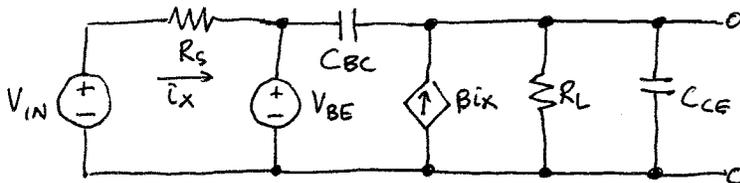


$$i_x = \frac{V_{IN} - V_{BE}}{R_S}$$

Thevenin to Norton:

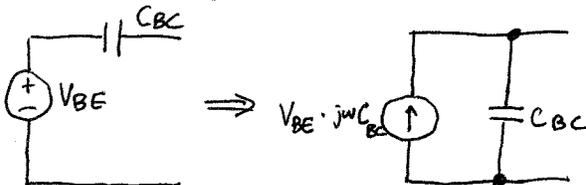

Substitute into above ckt:

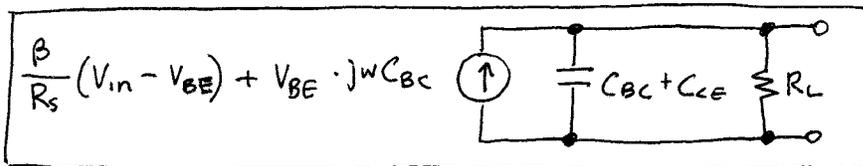

(b) V_{BE} is DC

$$V_{out} = \frac{\beta}{R_S} \cdot V_{in} \cdot \left(R_L \parallel \frac{1}{j\omega(C_{BC} + C_{CE})} \right) \Rightarrow \boxed{\frac{V_{out}}{V_{in}} = \frac{\beta}{R_S} \left[\frac{R_L}{1 + j\omega(C_{BC} + C_{CE})R_L} \right]}$$

V_{BE} is AC

$$V_{out} = \left[\frac{\beta}{R_S} \cdot V_{in} - \frac{\beta}{R_S} \cdot V_{BE} + V_{BE} \cdot j\omega C_{BC} \right] \cdot \left[\frac{R_L}{1 + j\omega(C_{BC} + C_{CE})R_L} \right]$$

In this case, the output voltage is a function of both V_{in} and V_{BE} .

By superposition, the total output is:

$$V_{out} = H_1(\omega) \cdot V_{in} + H_2(\omega) \cdot V_{BE} \quad \text{where} \quad \begin{cases} H_1(\omega) \triangleq \frac{V_{out}}{V_{in}} \Big|_{V_{BE}=0} \\ H_2(\omega) \triangleq \frac{V_{out}}{V_{BE}} \Big|_{V_{in}=0} \end{cases} \rightarrow$$

MT#2 Problem 3

(b) continued...


The question asked for $\frac{V_{out}}{V_{in}}$, which is $H_1(\omega)$. So, we only need to write that transfer function:

$$V_{out}|_{V_{BE}=0} = \left[\frac{\beta}{R_s} \cdot V_{in} \right] \cdot \left[\frac{R_L}{1 + j\omega(C_{bc} + C_{ce})R_L} \right]$$

$$H_1(\omega) = \frac{V_{out}}{V_{in}}|_{V_{BE}=0} = \left[\frac{\beta}{R_s} \right] \left[\frac{R_L}{1 + j\omega(C_{bc} + C_{ce})R_L} \right]$$

(this is the same as the answer in the DC case above)

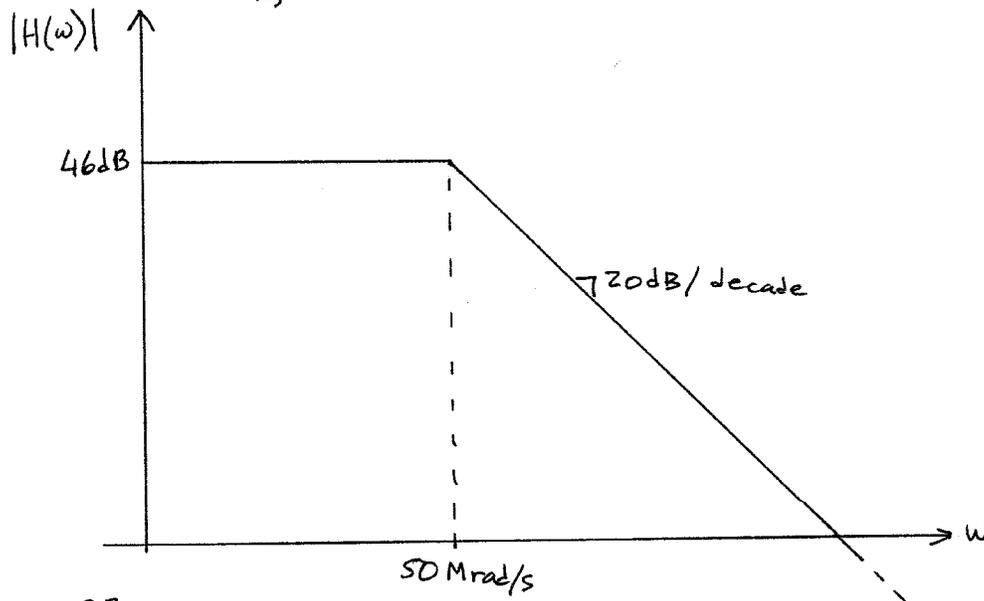(c) The transfer function is a single-pole lowpass with DC gain equal to $\frac{\beta R_L}{R_s}$ and the pole located at $\omega = \frac{1}{(C_{bc} + C_{ce})R_L}$





$$\frac{\beta R_L}{R_s} = 200$$

$$20 \log(200) = 46 \text{ dB}$$

$$\frac{1}{(C_{bc} + C_{ce})R_L} = 50 \text{ Mrad/s} = 8 \text{ MHz}$$

MT # 2 Problem 4

a)

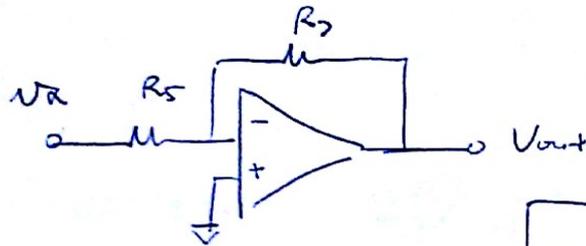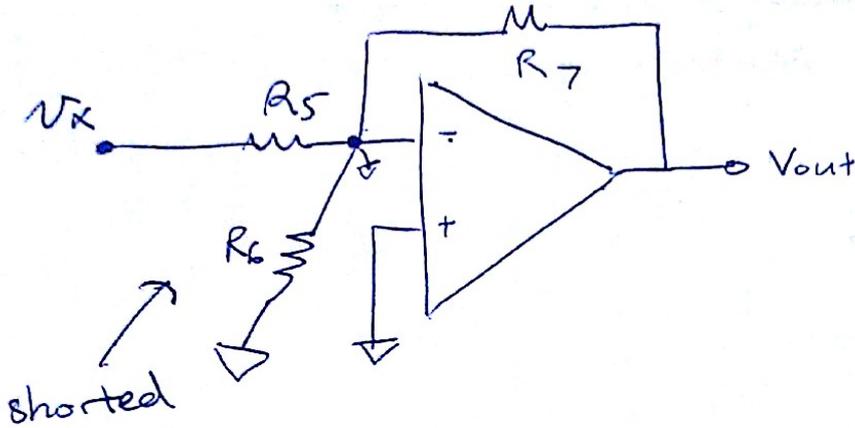


⇒ Inverting amp ⇒

$$\frac{V_{out}}{V_x} = -\frac{R_7}{R_5}$$

b)
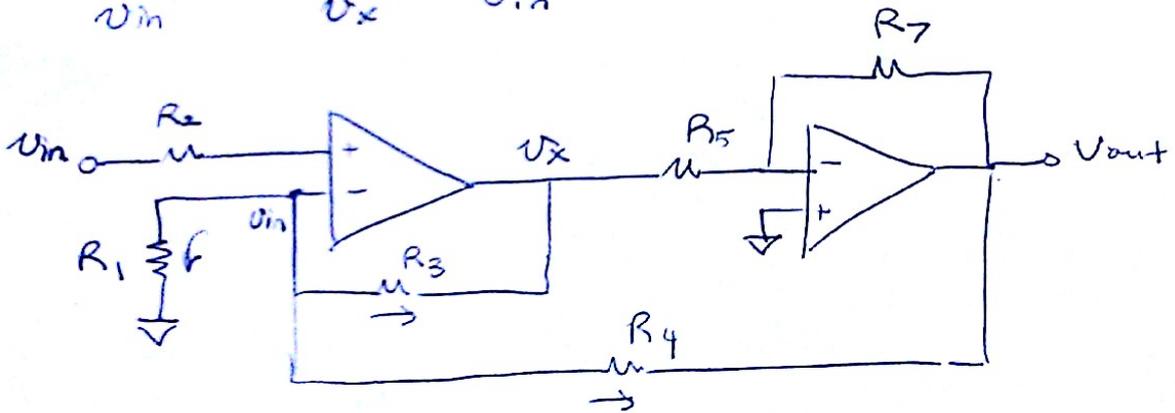
$$\frac{V_{out}}{V_{in}} = \frac{V_{out}}{V_x} \cdot \frac{V_x}{V_{in}}$$



$$\frac{V_{in}}{R_1} + \frac{V_{in} - V_x}{R_3} + \frac{V_{in} - V_{out}}{R_4} = 0$$

$$\frac{V_{in}}{R_1} + \frac{V_{in}}{R_3} + \frac{V_{in}}{R_4} = \frac{V_{out}}{R_4} + \frac{V_x}{R_3} = \frac{V_{out}}{R_4} - \frac{R_5}{R_7 R_3} V_{out}$$

$$\frac{V_{out}}{V_{in}} = \frac{1/R_1 + 1/R_3 + 1/R_4}{1/R_4 - \frac{R_5}{R_3 R_7}} = \frac{R_3 R_4 R_7 + R_1 R_4 R_7 + R_1 R_3 R_7}{R_1 R_3 R_7 - R_1 R_4 R_5}$$

Rubric for # 3:

- a) +2 Correct definition of i_x
 - +1 For trying something
 - +5 for correct V_{th} or I_N
 - +5 for correct R_{eq}
 - +2 for drawing the 2-element equivalent circuit
- b) +3 Nodal/Mesh equations
 - +4 Correct Answer (+2 if very close but wrong)
 - +1 If answer is in proper form
 - +2 If answer does not contain V_{BE}
- c) +10 for Low Pass Filter shape and proof (+5 for shape without proof)
 - +2 for $|H(\omega)|$
 - +3 for ω_c
 - 2 for missing labels on axis

Rubric for #4:

- a) +5 for recognizing equivalent ckt or for solving one nodal equation at V_+ (right amp)
 - +2.5 for shorting R_6 or equations do not contain R_6
 - +5 For correct answer
 - 1 for missing sign
 - Full credit given for correct answer.
- b) +2.5 for utilizing result from part a.
 - +5 for proper setup for KCL at V_- (left amp)
 - +5 for correct answer
 - 2.5 for algebraic error or answer is close but wrong
 - 1 for wrong sign