

**EE40 Spring 1996
Midterm #2
A.M. Flynn, R.T. Howe, R.M. White**

Problem #1

(a) What is the phasor current corresponding to the actual current

$$i(t) = 2 \cos(10^4 t - 60^\circ) \text{ mA}$$

(write answer in both polar and rectangular forms)


(b) What is the actual voltage $v(t)$ corresponding to the phasor voltage

$$V = (-5 - j5) \text{ volts?}$$

The angular frequency is equal to ω .

(c) A single circuit element (R, L, or C) is found to have the impedance $-j333$ ohms when measured at 1.0 MHz (10^6 Hz). What type of circuit element is it and what is its value?

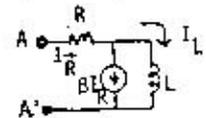
(d) Determine the impedance Z_{in} , at angular frequency ω , looking into terminals AA' of the circuit shown



below. Your answer should depend only on R, L, ω , and B. Show your work.

(e) The ratio V_{out} / V_{in} for a circuit is found to be $\frac{A / j\omega C1}{R2 + 1 / j\omega C1}$, where $A = 100$, $R = 2 \times 10^3$ ohms, $C = 4 \times 10^{-9}$ F. Draw the Bode plot for this circuit; label all significant values on the plot.

Problem #2 Transients

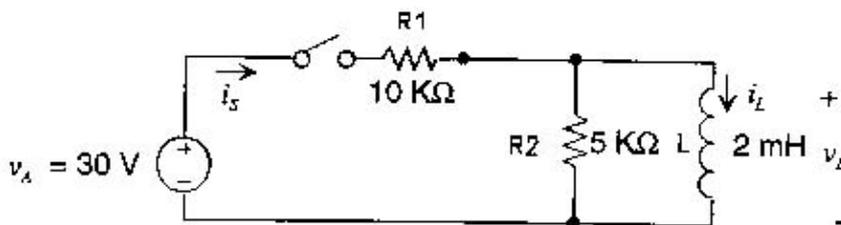


The switch has been closed for a long time, and at $t = 0$, the switch is opened.

(a) What is i_S at $t = 0^-$ (just before the switch is opened)?


- (b) What is the value of i_L at $t = 0^+$ (just after the switch is opened)?
- (c) What is the value of v_L at $t = 0^+$?
- (d) Find an expression for i_L for $t > 0$
- (e) Sketch i_L for $t > 0$.
- (f) Find an expression for v_L for $t > 0$.
- (g) Sketch v_L for $t > 0$.

Problem #3 Frequency Response

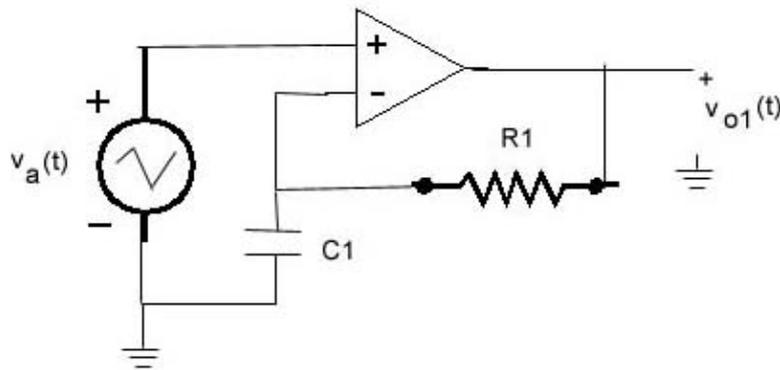- (a) Find the transfer function V_{o1} / V_a for the op-amp circuit below. You can assume that the op-amp is ideal.




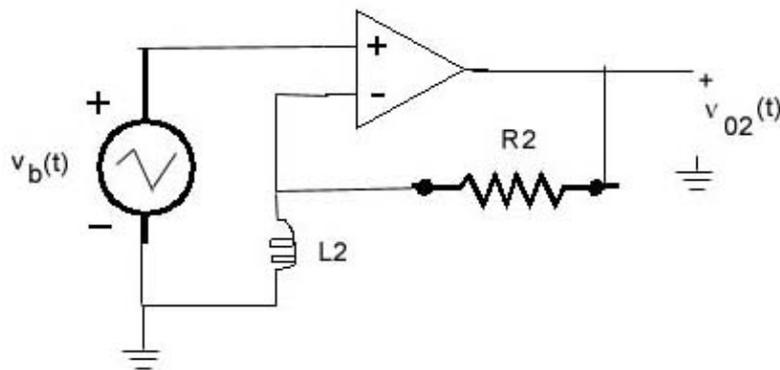- (b) Sketch the phase of V_{o1} / V_a on the graph below, for the case where $R_1 = 5 \text{ k ohms}$ and $C_1 = 200\text{nF}$.
- (c) Find the transfer function V_{o2} / V_b for the op-amp circuit below. You can assume that the op-amp is ideal.




- (d) Sketch the phase of V_{o2} / V_b in degrees on the graph below, for the case where $R_2 = 100 \text{ ohms}$ and $L_2 = 100 \text{ microH}$
- (e) Sketch the magnitude $|V_{o2} / V_b|$ in dB for the op-amp circuit below. The same values are used as in parts (b) and (d):

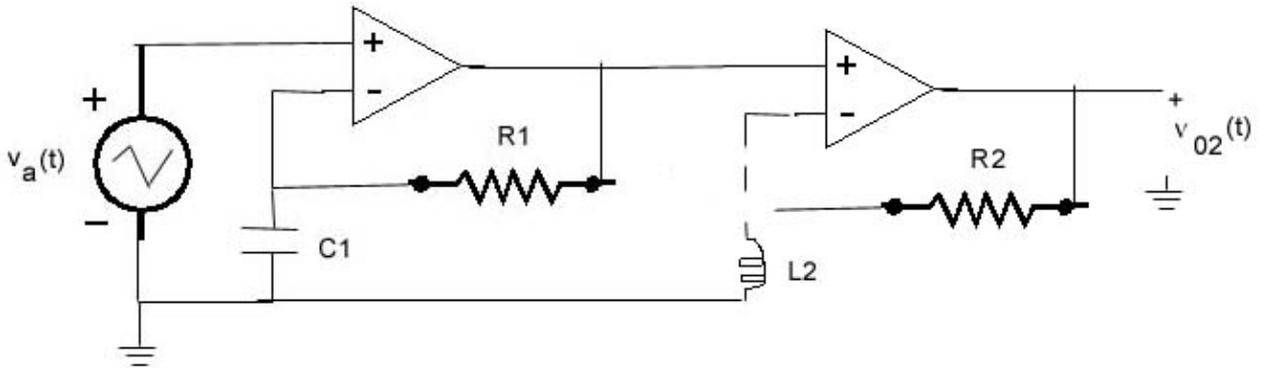$R_1 = 5 \text{ k ohms}$, $C_1 = 200\text{nF}$, $R_2 = 100 \text{ ohms}$, $L_2 = 100 \text{ microH}$.



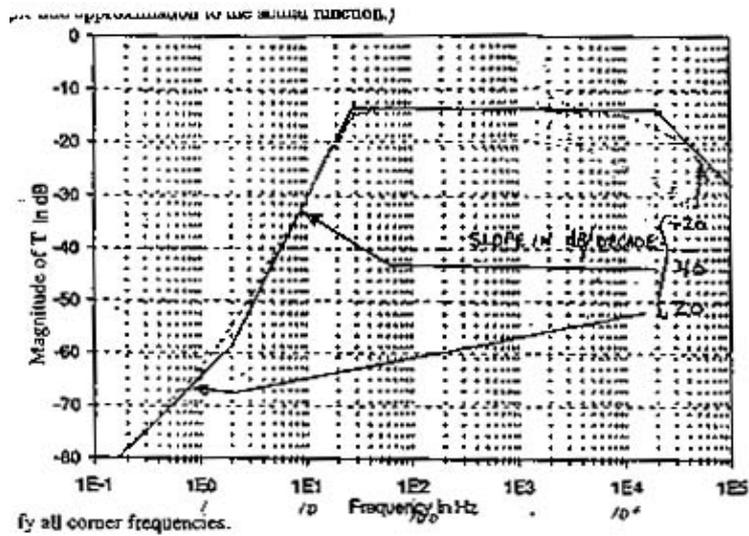Problem #4 Bode Plot [20 Points]

You have a graphic equalizer on your stereo which acts to filter the frequencies reaching your amplifier and speakers. You find that when it is set as shown in the graph below, it sounds great. (The solid lines give the straight-line approximation to the actual function.)



- (a) Identify all corner frequencies.
- (b) How many poles and how many zeroes are in the transfer function? [Hint: the sum must be equal to the answer in part (a).]
- (c) Write an expression for the transfer function T , assuming that the phase is 90° at 0.1Hz .
- (d) What is the phase of T , at $f \gg 10^5\text{Hz}$?

EE40, Midterm #2, Spring 1996

**Posted by HKN (Electrical Engineering and Computer Science Honor Society)
University of California at Berkeley
If you have any questions about these online exams
please contact examfile@hkn.eecs.berkeley.edu.**