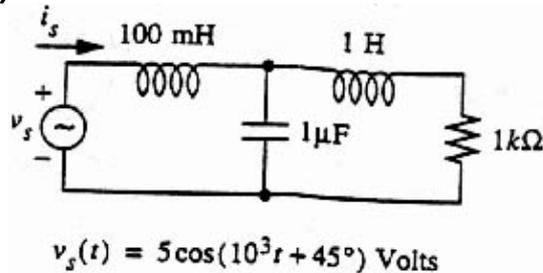



**EE 40, Spring/1997
Midterm #2
Professors T.-J. King and R.M White**

Problem #1 (18 points)




- What is the phasor corresponding to $v_s(t)$? Express your answer in exponential and rectangular forms. [4 pts.]
- What is the impedance seen by the voltage source? Express your answer in exponential and rectangular forms. [5 pts.]
- What is the instantaneous current delivered by the voltage source? [4 pts.]
- What is the time-averaged power supplied by the voltage source? [5 pts.]

Problem #2 (20 points)

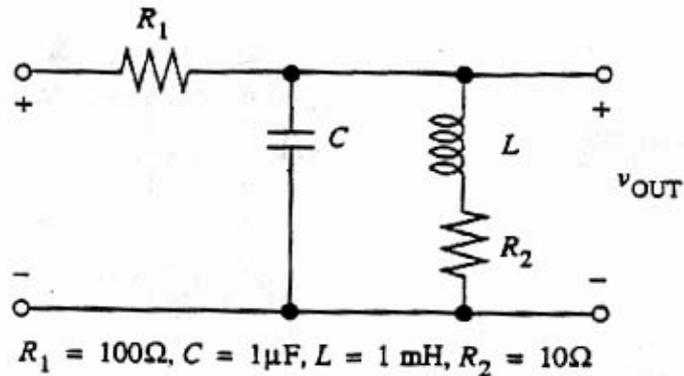

- What is the transfer function $\mathbf{G} = v_{\text{OUT}}/v_{\text{IN}}$ at very low frequency, ω approaching 0? [2 pts.]
- What is the transfer function $\mathbf{G} = v_{\text{OUT}}/v_{\text{IN}}$ at very high frequency, ω approaching infinity? [2 pts.]
- For what intermediate frequency ω_0 is \mathbf{G} real? [6 pts.]
- What is $\mathbf{G}(\omega_0)$? [4 pts.]
- Sketch the general behavior of $|\mathbf{G}(\omega)|$ vs. ω on the axes provided. (y-axis from 0 to 1, x-axis from 0 to 10^9). Note: This is not a Bode plot. Indicate values of $|\mathbf{G}(0.5\omega_0)|$ and $|\mathbf{G}(2\omega_0)|$ on your plot. [6 pts.]

Problem #3 (25 points)

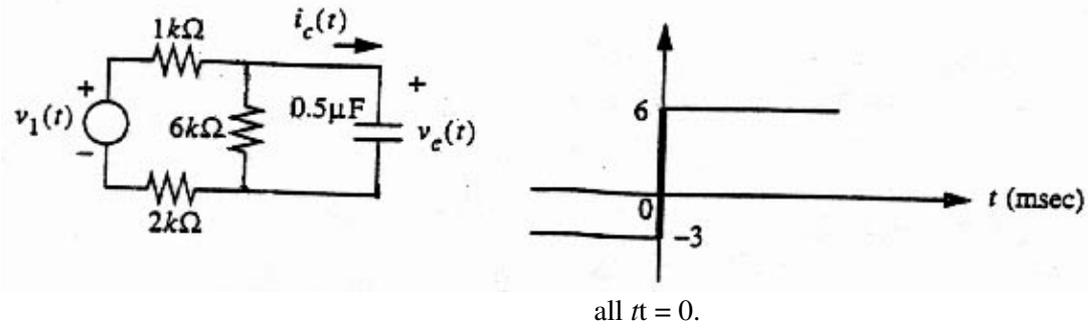


$v_c(t)$ is -3 V for

all $t > 0$.

- What is the value of i_c at $t = 0^-$? [2 pts.]
- What is the value of v_c at $t = 0^-$? [4 pts.]
- What is the value of i_c at $t = 0^+$? [4 pts.]
- Find an expression for v_c , for $t > 0$. [5 pts.]
- Sketch v_c for all t . (Label the axes on the plot.) [4 pts.]
- Find an expression for i_c , for $t > 0$. [3 pts.]
- Sketch i_c for all t . (Label the axes on the plot.) [3 pts.]


1

Problem #4 (20 points)

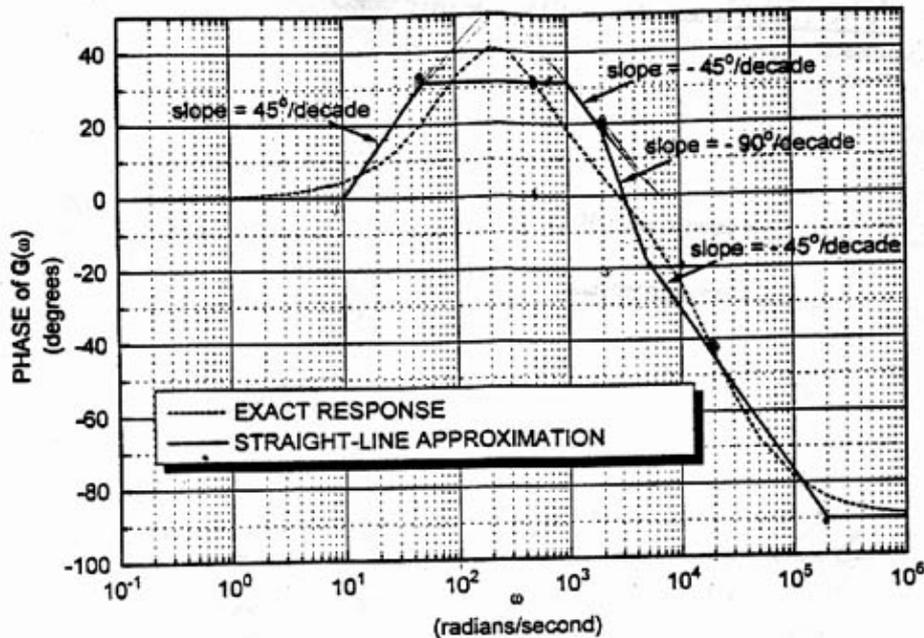


- Identify all corner frequencies. [6 pts.]
- How many poles and zeros are in the transfer function? [3 pts.]
- Write an expression for the transfer function $G(\omega)$, assuming that the magnitude is 20 dB at $\omega = 0.1$ rad/sec. [4 pts.]
- Neatly sketch the Bode magnitude plot (magnitude of $G(\omega)$ in decibels vs. frequency on a logarithmic scale). Straight-line approximations are adequate. [7 pts.]

Problem #5 (15 points)

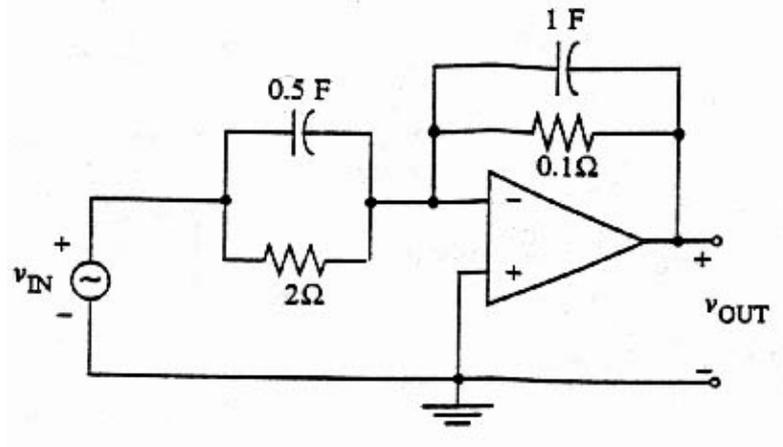

- Find the transfer function v_{OUT}/v_{IN} for the op-amp circuit. You can assume that the op-amp is ideal. [6 pts.]
- Sketch the Bode magnitude plot of v_{OUT}/v_{IN} . Straight-line approximations are adequate. [6 pts.]
- If the op-amp were slightly "unbalanced" with an input offset voltage of 10 mV, what would be the value of the spurious output voltage? (Hint: The superposition theorem might be helpful here.)

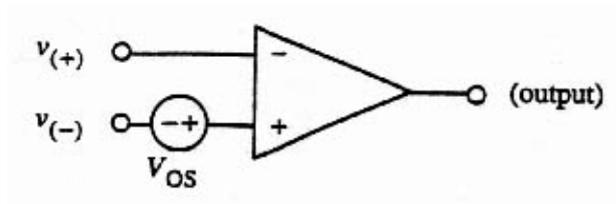Note: An op-amp with a voltage offset can be modelled as an offset-free op-amp plus an offset-voltage source: [3 pts.]



**Posted by HKN (Electrical Engineering and Computer Science Honor Society)
University of California at Berkeley**
If you have any questions about these online exams
please contact examfile@hkn.eecs.berkeley.edu.