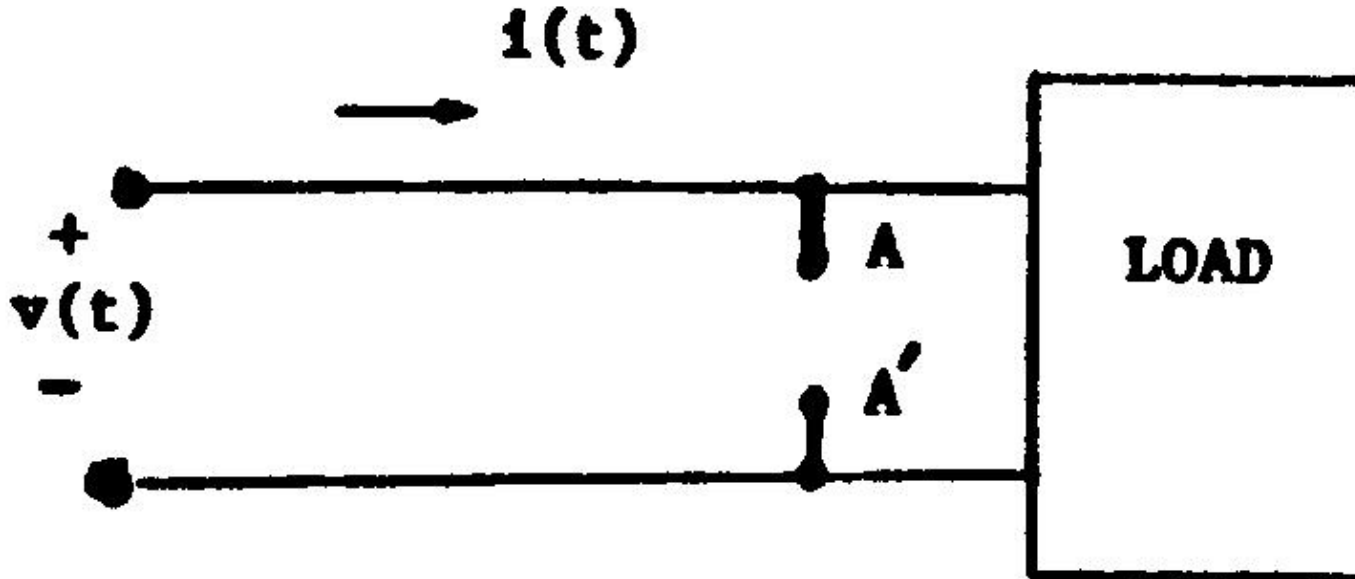


1



$$v(t) = 110\sqrt{2}\cos(\omega t + 10^\circ)$$

$$f = 60\text{Hz}$$


$$i(t) = 2\sqrt{2}\sin(\omega t + 30^\circ)$$

- a) Find the time average power supplied to the load.
- b) Find the impedance of the load.
- c) Find the inductance or capacitance which when connected between terminals A and A' will make the current  $i(t)$  in phase with the voltage  $v(t)$ .

2.

$|V_{out}/V_{in}|$

dB  
(Ref = 1)

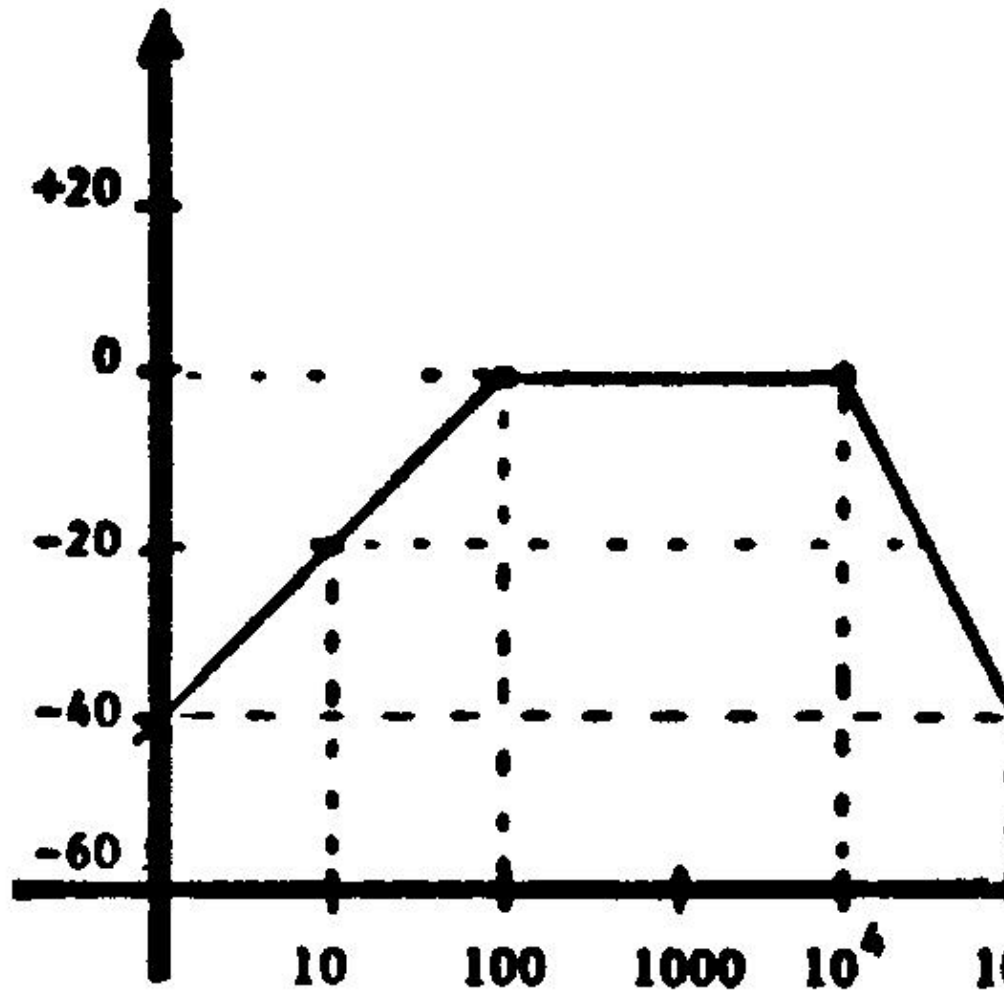


(a) (12 pts.) The ratio of output voltage amplitude to input voltage amplitude for a circuit as shown above. Find the mathematical expression for

$$|V_{out} / V_{in}|$$


(b) (13 pts)

**(b)(18 pts.)**

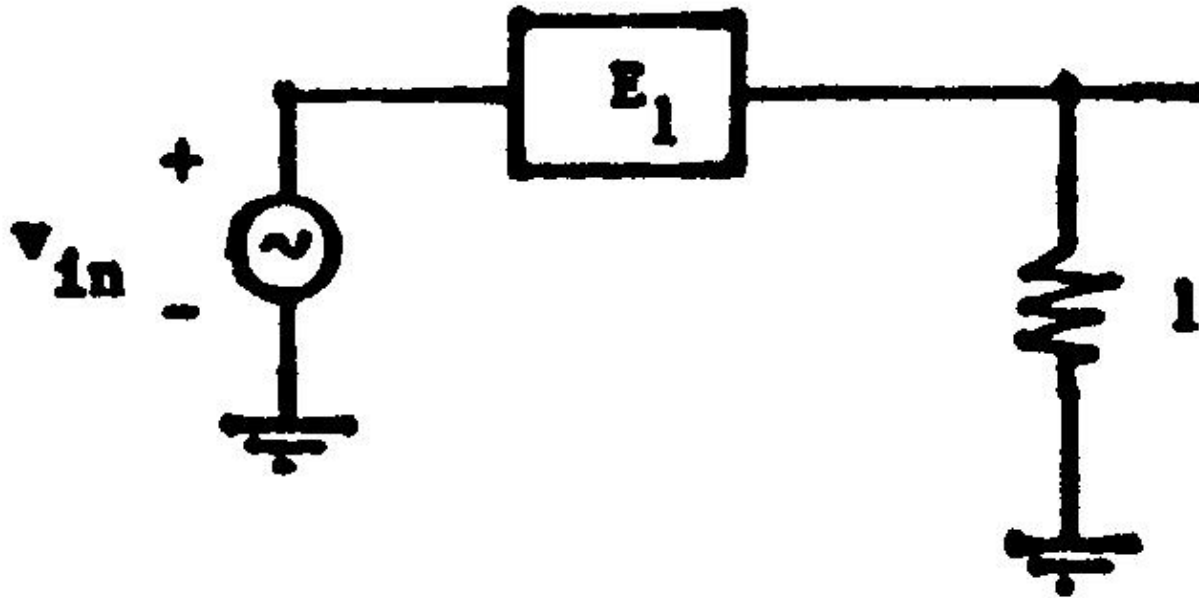

What circuit element, with what value, should be used for  $E_1$  to give the Bode plot of this figure?


3 (20 pts)

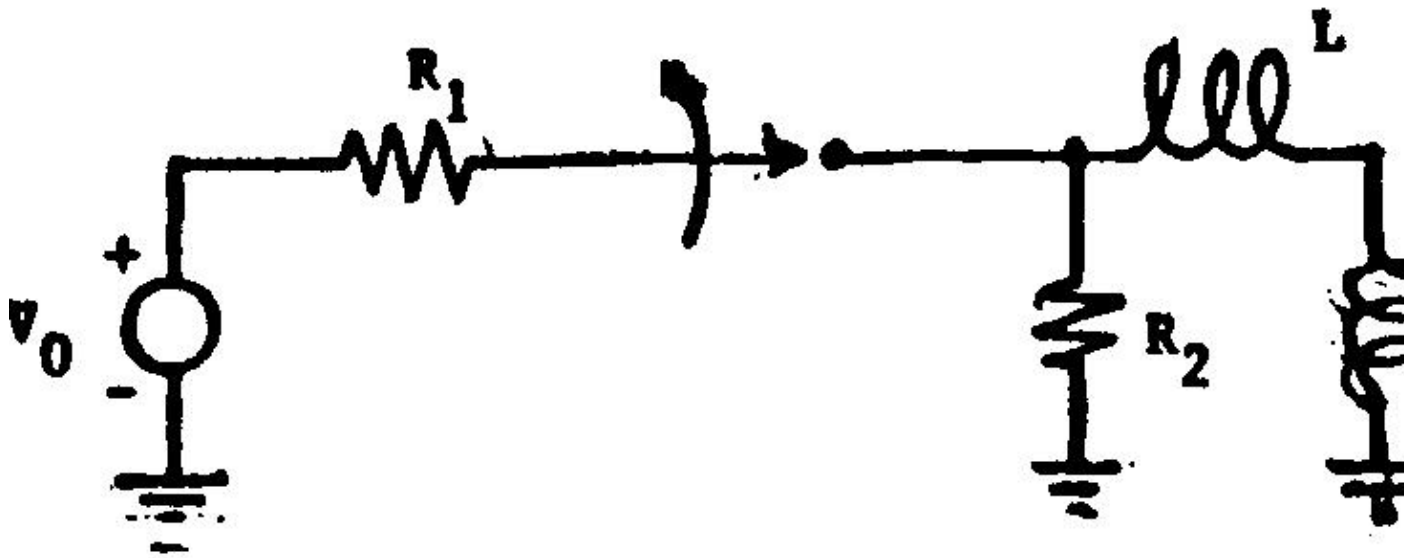



Let  $V_0=60\text{V}$ ,  $R_1=10,000\ \Omega$ ,  $R_2=2,000\ \Omega$ ,  $L=2\text{mH}$ . The switch is closed until time  $t=0$ , when it is opened. Make a reasonably accurate graph of

$v(t)$  versus time.

4. (20 pts) Op-Amp.

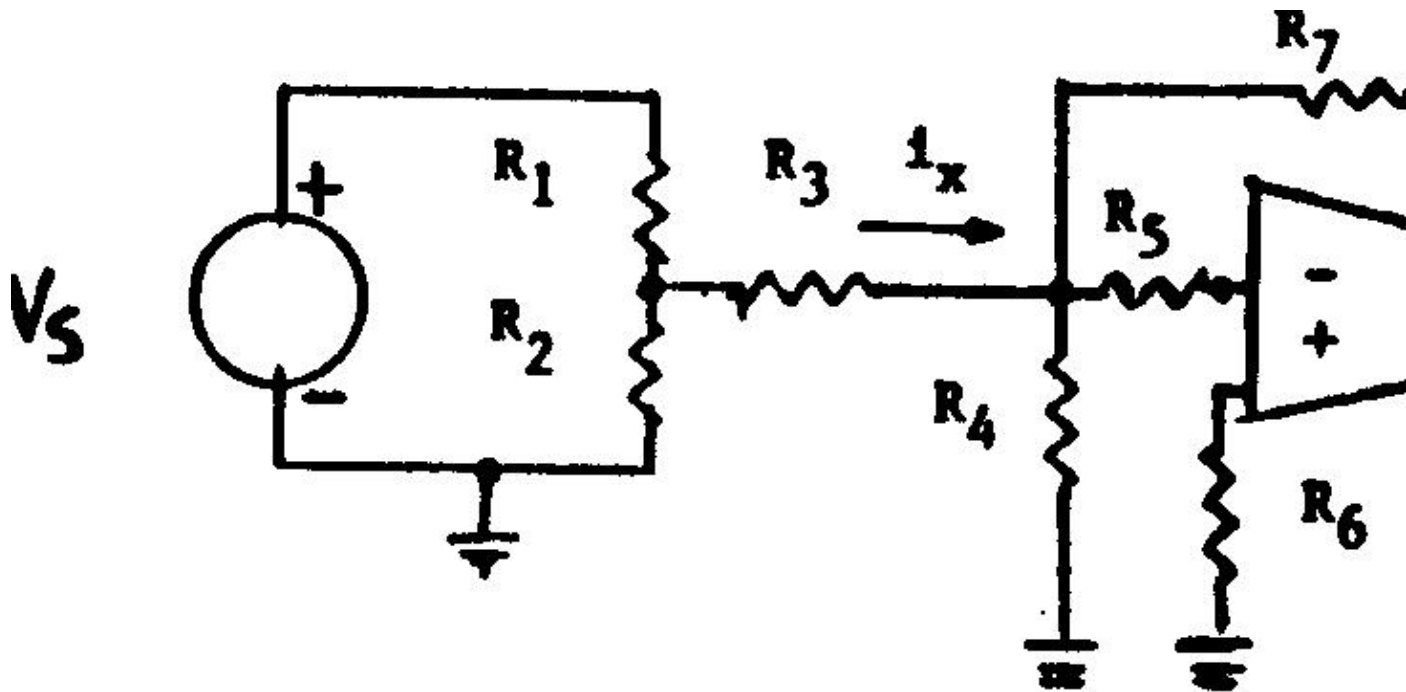


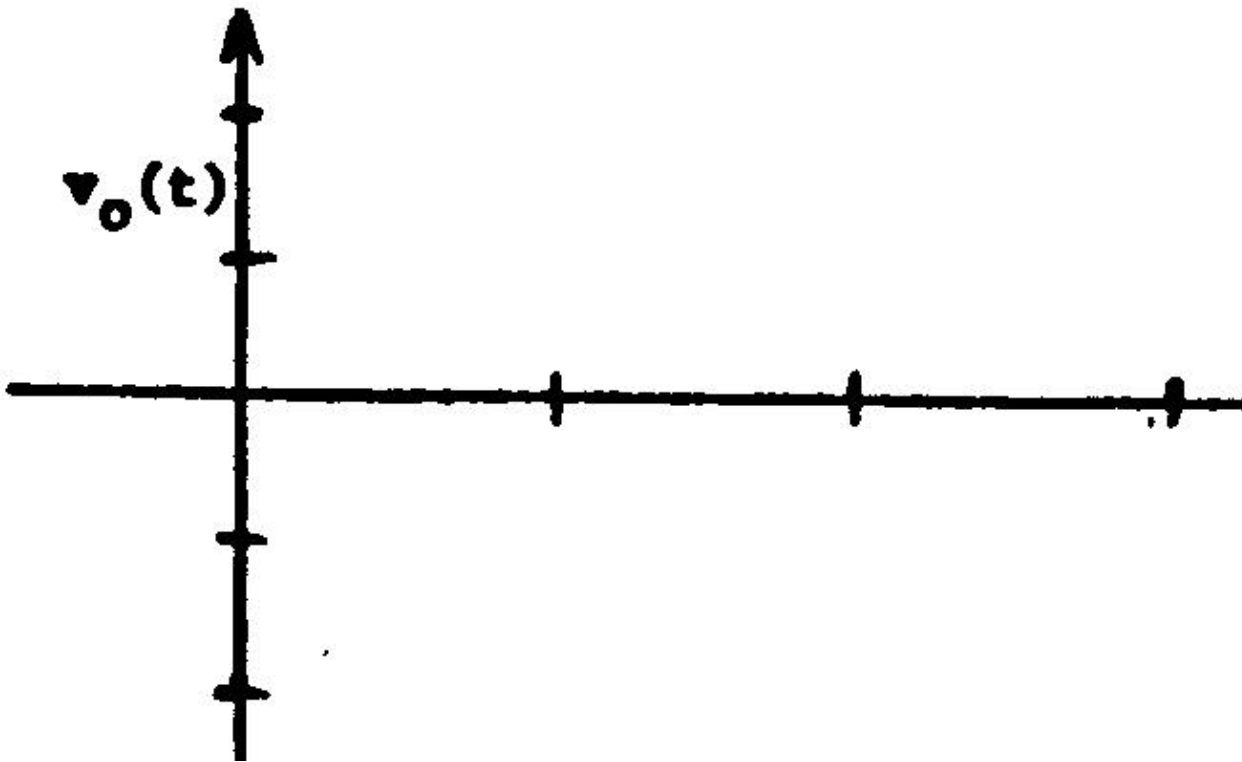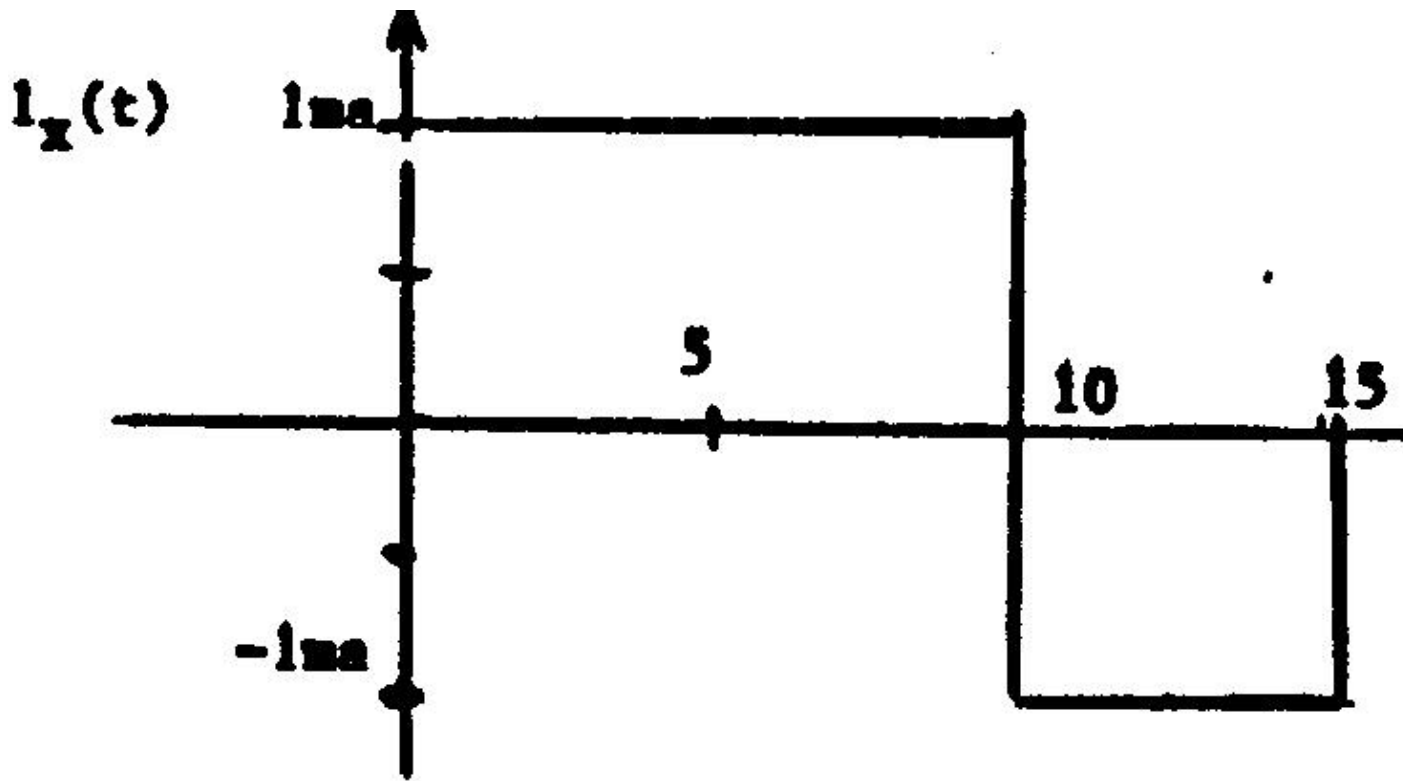- a) Find an algebraic expression for  $V_0/V_1$
- b) Sketch  $V_0(t)$  when  $i_x$  is the waveform given below and all resistors are  $10\text{k}\Omega$ .




5 (30 pts) Transistor Bias

## V. (30 points) Transistor Bias

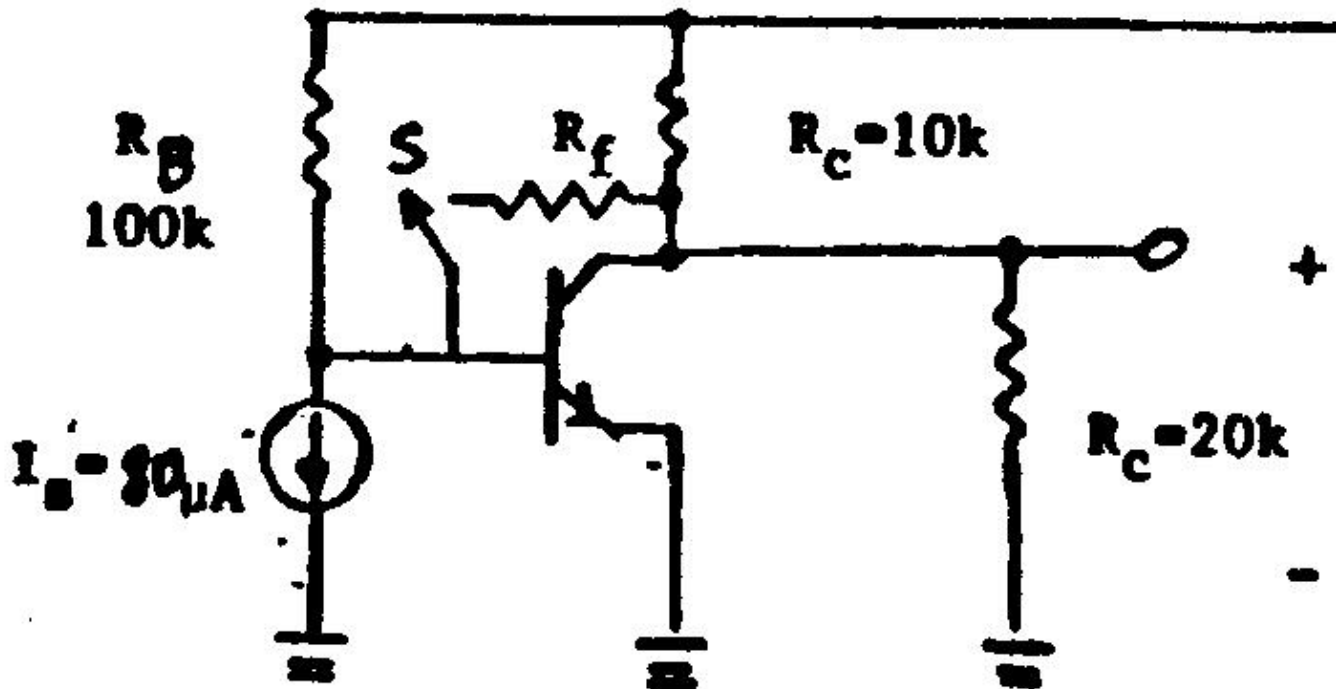

- Find  $V_{\text{set}}$  when the switch is open.
- What value of  $R_f$  will make  $V_{\text{set}} = 2\text{V}$  when the switch is closed?

6 (30 pts)

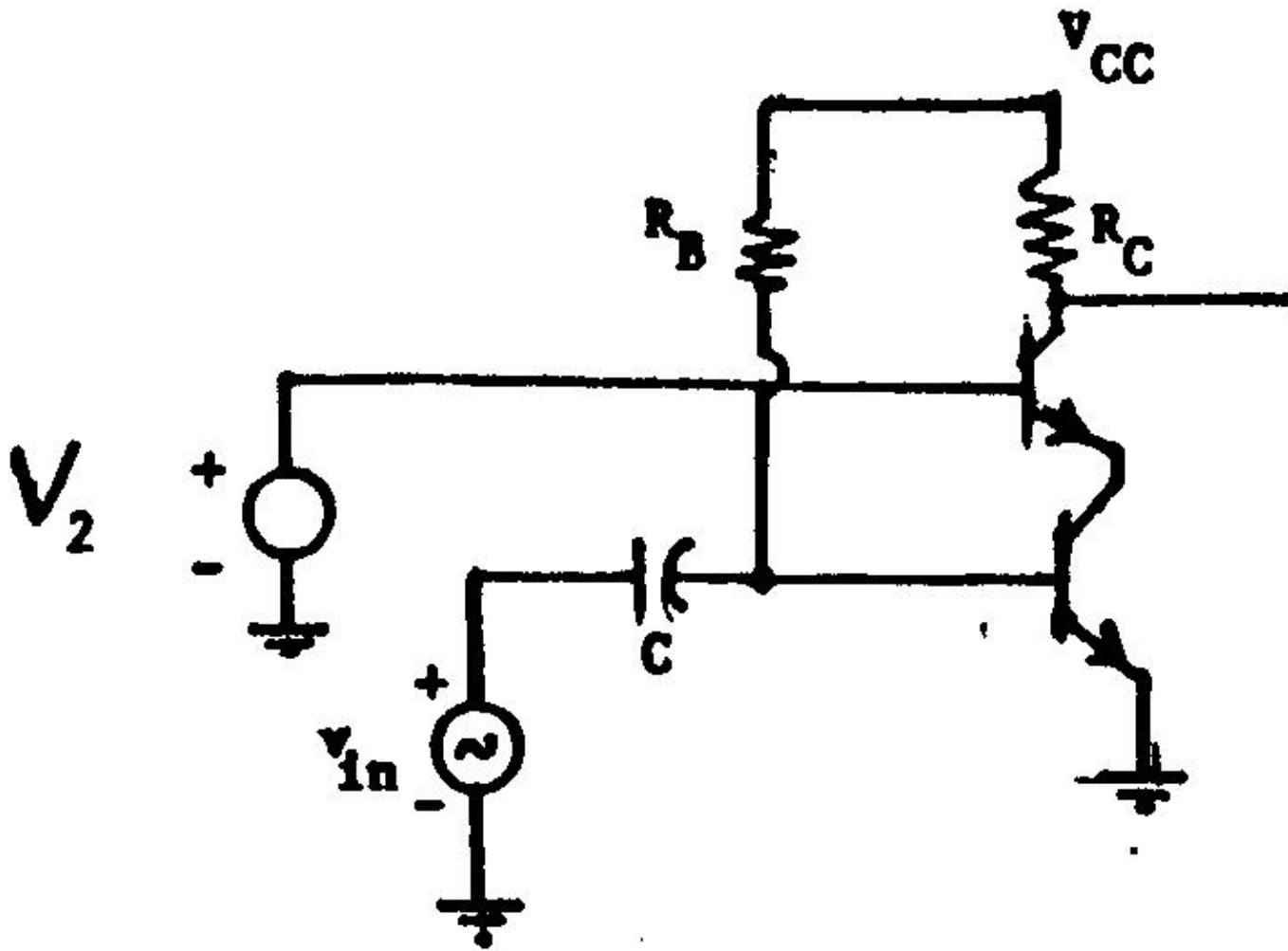

The above circuit is known as a "cascode" amplifier. Let  $R_B = 7 \cdot 10^5$ ,  $R_C = 5000$ ,  $V_{CC} = 10V$ ,  $\beta = 20$  (for both transistors),  $V_2 = 5V$ .

Assume that the impedance of  $C$  is nearly zero at the operating frequency.


(a) (15 pts) Construct a small-signal model.

(b) (15 pts) Find the small-signal voltage amplification  $|V_{out} / V_{in}|$ . (The answer should be a number)

7 (30 pts) Digital Gates.



**VII. (30 points) Digital Gates.**

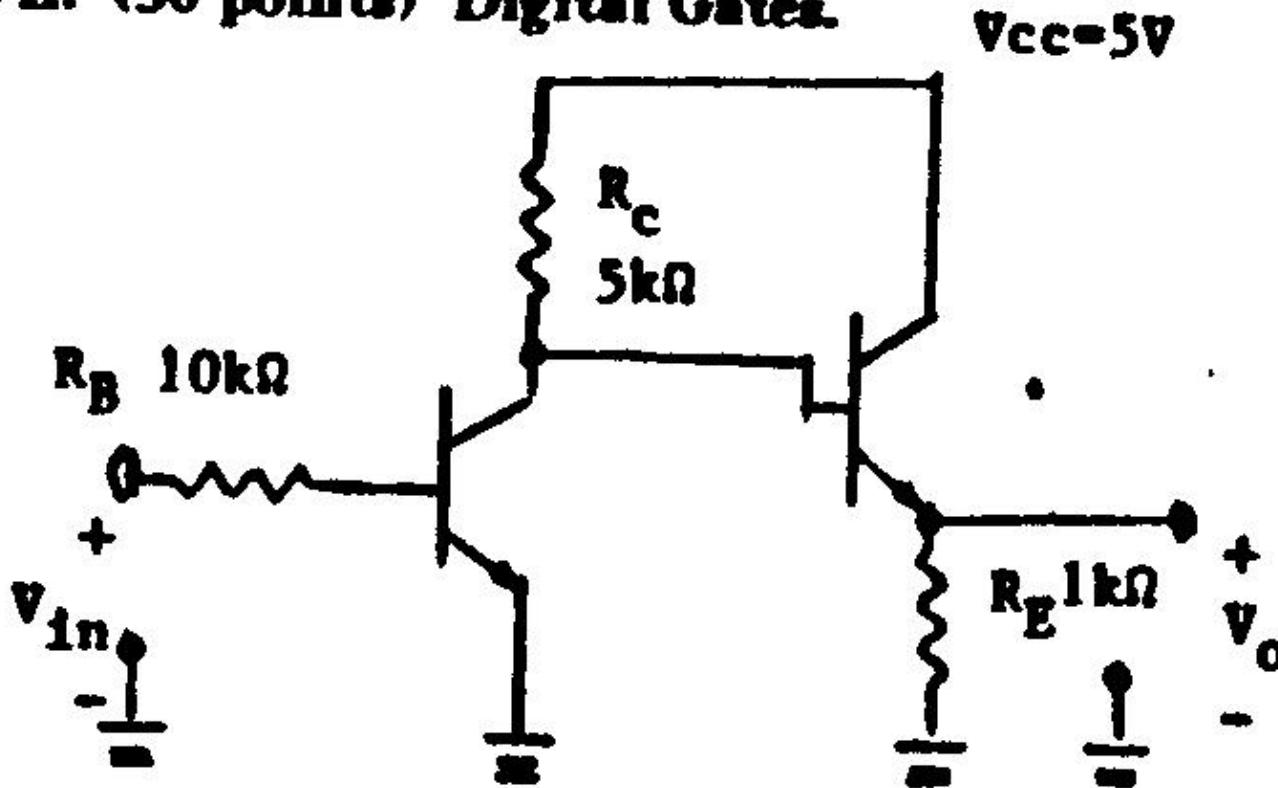

a) Sketch  $V_{out}$  vs  $V_{in}$  and label value.

b) Find the FANOUT (the maximum number of identical gates which could be attached to this gate and operated within the voltage specifications given above).


**VIII.(20 pts.)**

**$R = 50k\Omega$**

**$C = 10^{-10}F$**

**$V_T = 3V$**

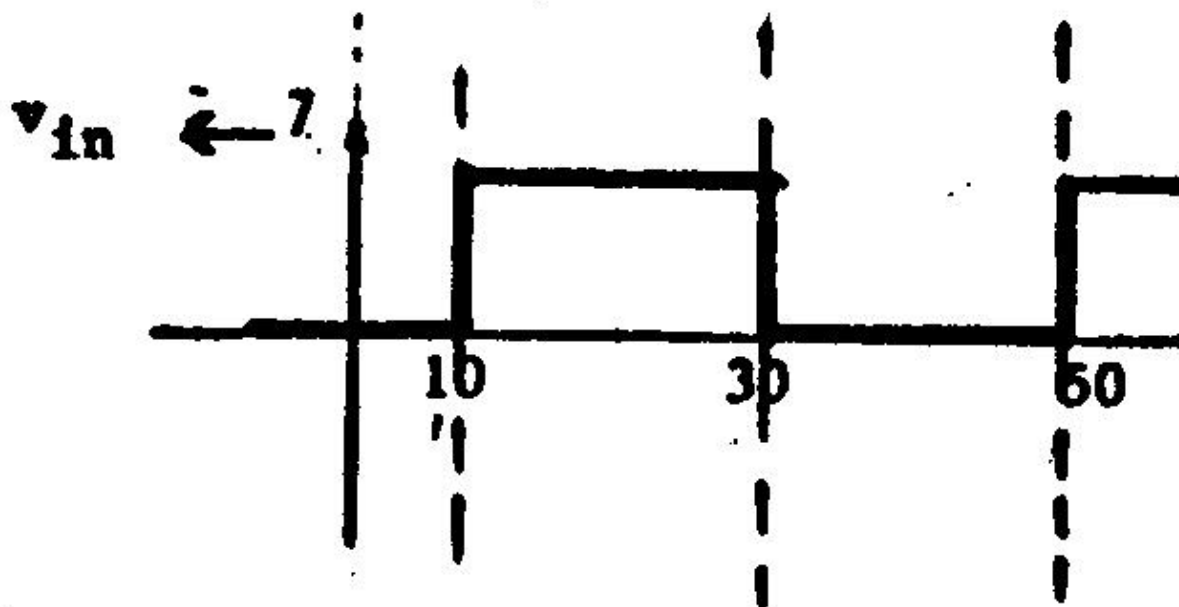**Assume  $K$  (in the two equations for  $i_D$ )**



**(a) Sketch  $i_{D1}(t)$  with switch  $S_1$  open. (Your shape.)**



