

EE 40, Spring 1998
Midterm 2
Professor S. Schwarz, Professor R. M. White

Problem #1 (25 Points)


The phasor representing the sinusoid $v(t)$ is $\mathbf{v} = (1+2j)/1-3j$. The angular frequency ω is 100 radians/sec.

[8 pts.] a) Find the amplitude of the sinusoid.

[8 pts.] b) Find the phase angle of the sinusoid.

[9 pts.] c) Find the first time after $t = 0$ at which v has its maximum value.

Problem #2 (25 Points)

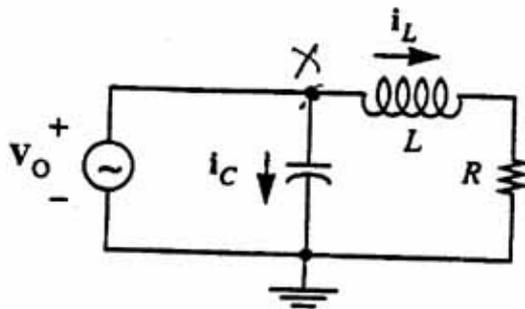

In the above circuit, $V_0 = 10$ V (real, $C = 10^{-8}$ F, $L = 2 \times 10^{-4}$ H, $R = 100$ ohms, $\omega = 10^6$ radians/sec.


[5 pts.] a) Find the numerical value of the phasor \mathbf{i}_C . Express answer in simplest rectangular form $A + jB$.

[10 pts.] b) Find the numerical value of the phasor \mathbf{i}_L . Express answer in simplest rectangular form $A + jB$.

[10 pts.] c) Find the time-averaged power produced by the voltage source. (That is, find the power that comes out of the voltage source and goes into the rest of the circuit.)

Problem #3 (25 Points)


For a certain circuit block, the ratio $|V_{out}|/|V_{in}|$ is represented by the following:

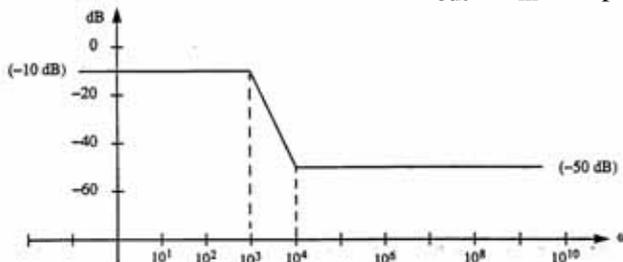

The general expression for this transfer function is

$$\frac{|V_{out}|}{|V_{in}|} = \frac{(1 + A \omega)^M}{(B + C \omega)^N}$$

Find A, B, C, M and N. Note: 0 dB corresponds to $|V_{out}|/|V_{in}| = 1$.

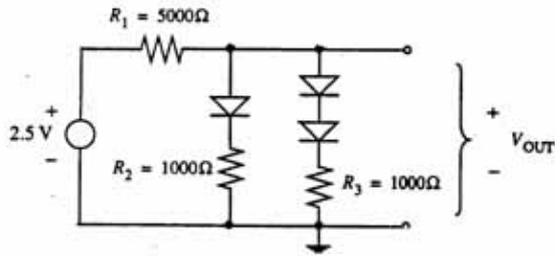Problem #4 (25 Points)

Find V_{out} in the above circuit. The diodes are to be represented by the large-signal diode model (including the 0.7 V drop across a forward-biased diode.) **Make sure your answer is reasonable and consistent.** Explain your reasoning.

**Posted by HKN (Electrical Engineering and Computer Science Honor Society)
University of California at Berkeley**
**If you have any questions about these online exams
please contact examfile@hkn.eecs.berkeley.edu.**